
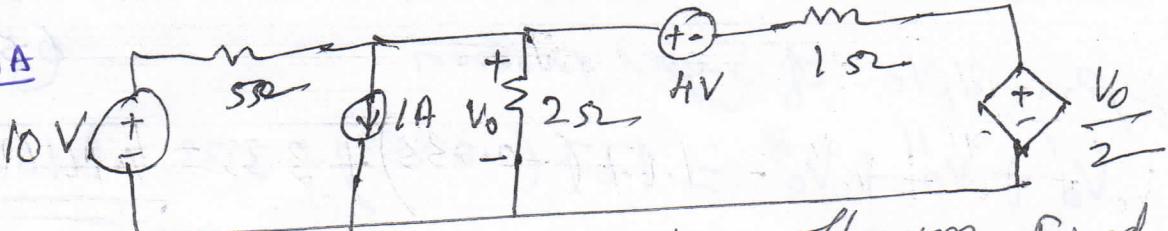


Q1A

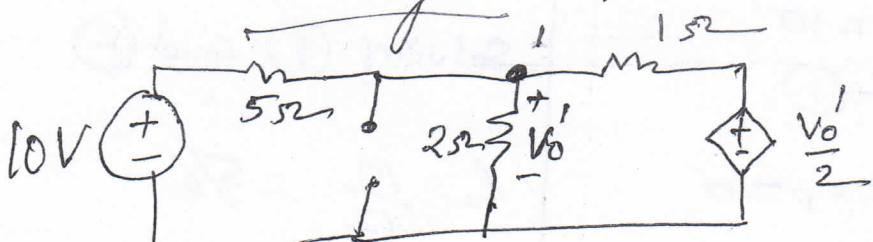

Superposition Theorem Find V_o

10V Source only acting.



at node 1


$$\frac{V_o'}{2} + \frac{V_o' - V_o}{2} + \frac{V_o' - 10}{5} = 0$$

$$\underline{V_o' = 1.67 \text{ V}}$$

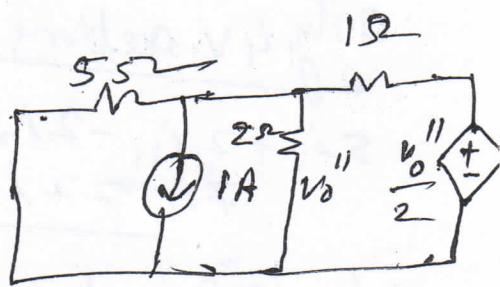(1.5 mark)

Apply 1A Current Source

$$\frac{V_o''}{2} + 1 + \frac{V_o''}{5} + \frac{V_o'' - V_o}{2} = 0$$



$$0.5V_o'' + 0.2V_o'' + V_o'' - 0.5V_o'' + 1 = 0$$


$$\underline{V_o'' = -0.833 \text{ V}}$$

(1.5 mark)

Only 4V Source is acting

$$i \times \frac{10}{7} + 4 + i \times i + \frac{V_o''}{2} = 0 \quad (1)$$
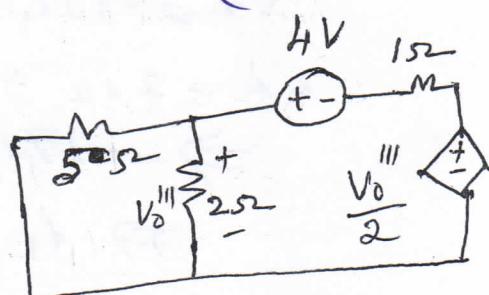
$$\text{from fig: } V_o''' = -i_{2\Omega} \times 2\Omega$$



$$\text{Sub: in above Eqn: } i_{2\Omega} = \cancel{i_{2\Omega}} \quad i \frac{5}{5+2} = \frac{5}{7} i \quad \frac{10}{7} i$$

$$\therefore V_o''' = -\frac{5}{7} i \times 2 = -\frac{10}{7} i \quad (2)$$

(1.5 mark)

$$(2) \text{ in } (1) \quad \frac{10}{7} i + 4 + i + \frac{1}{2} \left(-\frac{10}{7} i \right) = 0 \Rightarrow i = -2.33 \text{ A}$$

$$\therefore V_o''' = -\frac{10}{7} (-2.33) = 3.33 \text{ V}$$

By principle of Superposition

$$V_0' + V_0'' + V_0''' = 1.67(-0.833) + 3.33 = \underline{4.167}$$

6.5m

(OR)

using 10V

$$5i_1 + 2i_1 - 2i_2 = 10$$

$$\Rightarrow 7i_1 - 2i_2 = 10 \quad \textcircled{1}$$

$$2i_2 + i_2 + \frac{V_0}{2} - 2i_1 = 0$$

$$4i_1 - 6i_2 = V_0$$

$$2i_1 - 2i_2 = V_0$$

$$i_1 - i_2 = 2i_1 - 3i_2$$

$$i_1 = 2i_2 \quad \textcircled{2}$$

Solving \textcircled{1} and \textcircled{2}

$$i_2 = \frac{10}{12} = \underline{\underline{5/6}}$$

$$i_1 = \underline{\underline{5/3}}$$

$$\therefore V_0 = \underline{\underline{5/3}} \text{ V}$$

Only 4V acting

$$5i_1 + 2i_1 - 2i_2 = 0$$

$$7i_1 = 2i_2$$

$$4 = -2i_2 + 2i_1 - i_2 - \frac{V_0}{2}$$

$$8 + \frac{V_0}{2} = 2i_1 - 3\left(\frac{1}{2}\right)i_1 = \frac{-17}{2}i_1$$

$$V_0 = -17i_1 - 8$$

$$2i_1 - 2i_2 = V_0$$

$$\Rightarrow -17i_1 - 8 = 2i_1 - 2i_2$$

$$\Rightarrow i_1 = \frac{-8}{12} = -\frac{2}{3}$$

$$\therefore V_0 = \frac{34}{3} - 8 = \frac{10}{3}$$

only 1A acting

$$-5 = 5i_1 + 2i_1 - 2i_2$$

$$7i_1 - 2i_2 = -5$$

$$2i_2 + i_2 - 2i_1 + \frac{V_0}{2} = 0$$

\textcircled{1} \textcircled{2}

$$-2i_1 + 3i_2 = -V_0$$

$$-2i_1 - 2i_2 = V_0$$

$$2i_1 - 2i_2 = 4i_1$$

$$\Rightarrow 2i_1 - 4i_2$$

$$i_1 = 2i_2$$

$$\Rightarrow 14i_2 - 2i_2 = -$$

$$i_2 = -\frac{5}{12}$$


$$i_1 = -\frac{5}{6}$$

$$\therefore V_0 = -\frac{5}{6}$$

$$V_0 = \frac{5}{3} + \frac{10}{3} - \frac{5}{6}$$

$$= \frac{25}{6} \text{ V} = \underline{\underline{4.167}}$$

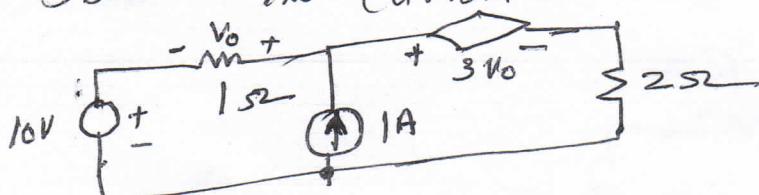Q18 Obtain the current in 2Ω resistor by Thevenin theorem.




Soln Remove 2Ω

$$\therefore V_{oc} = 10 + V_o - 3V_o$$

where V_o is the drop across 1Ω resistor $\therefore I \times 1 = 1V$

$$\therefore V_{oc} = 10 + 1 - 3 = \underline{\underline{8V}}$$

To find Short Circuit Current

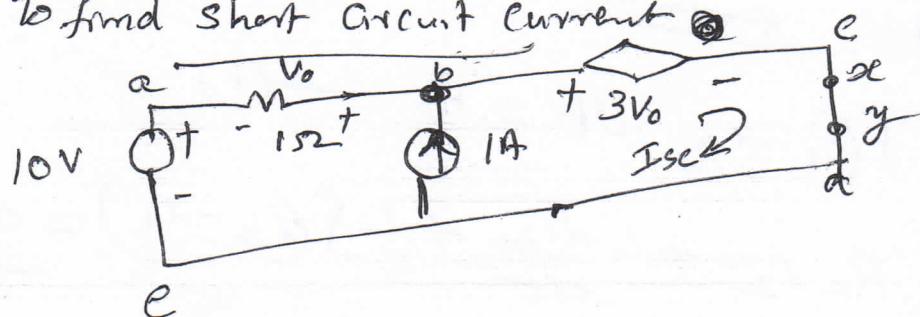

loop abcde, KVL

$$10 + V_o - 3V_o = 0 \quad \textcircled{1}$$

Applying KCL at node b

$$\frac{V_o}{1} = 1 - I_{sc}$$

from \textcircled{1}

$$10 + (1 - I_{sc}) - 3(1 - I_{sc}) = 0$$

$$\therefore I_{sc} = -4A$$

$$\therefore R_{th} = \frac{V_{th}}{I_{sc}} = \frac{8}{4} = 2\Omega$$

\therefore Current flowing through 2Ω resistor


$$\therefore I = \frac{V_{oc}}{R_{th} + R_L} = \frac{8}{2+2} = \underline{\underline{2A}} \text{ Ans}$$

$V_{th} = 1 \text{ mark}$

$I_{sc} = 1 \text{ mark}$

$R_{th} = 1/2 \text{ mark}$

$I = 1/2 \text{ mark}$

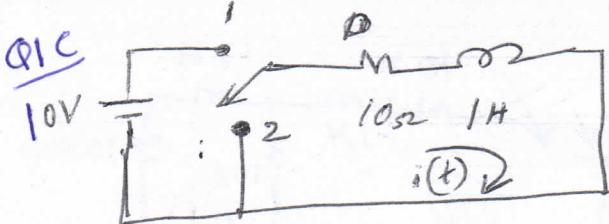

find $i(t)$

$$\text{at } t=0, i_0 = \frac{10}{10} = 1A$$

$$10i + L \frac{di}{dt} = 0$$

$$\text{at } t=0, i_0 = 1$$

$$-10 = \frac{di}{dt}; \text{ Integrating } i = -10t = -10 \times 5 \times 10^{-3} = -0.05A$$

(1 mark)

Ch: eq

$$s + 10 = 0$$

$$s = -10$$

$$i = K_1 e^{-10t}$$

$$i = K_1 \cancel{\underline{\underline{e^{-10t}}}}$$

$$t = \text{from see} \\ \text{Soln: } i = e^{-10t} = e^{-5 \times 10^3 t} = 0.9512 A$$

(1 mark)

(Ans 2-2)

Q.2A

Switch closed



Find $I_1(s)$, $I_2(s)$.

$$(s+20)I_1(s) - 10I_2(s) = \frac{100}{s}$$

$$-10I_1(s) + (s+20)I_2(s) = 0$$

$$\text{Det} = \begin{vmatrix} s+20 & -10 \\ -10 & s+20 \end{vmatrix}$$

$$= s^2 + 40s + 300 = (s+10)(s+30)$$

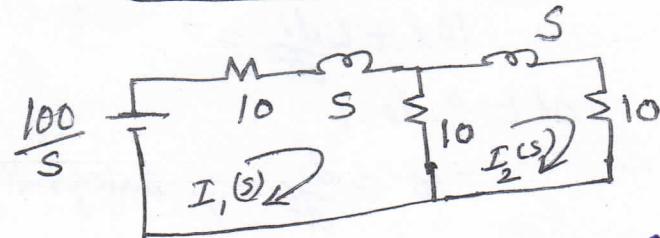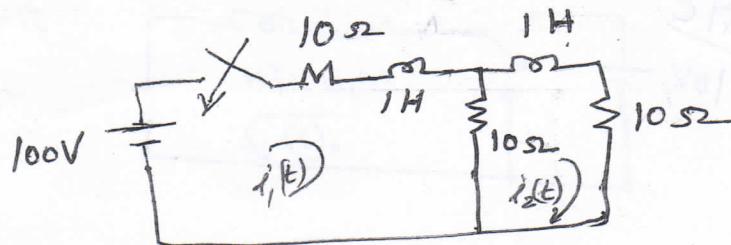

$$\therefore I_1(s) = \frac{\frac{100}{s}}{(s+10)(s+30)} = \frac{100s + 2000}{s(s+10)(s+30)}$$

Taking Laplace inverse

$$I_1(s) = \frac{6.66}{s} - \frac{5}{s+10} - \frac{1.67}{s+30}$$

Taking t^{-1}

$$I_1(t) = 6.66 - 5e^{-10t} - 1.67e^{-30t}$$

(2.5 mark)

Hence

$$I_2(s) = \frac{s+20}{(s+10)(s+30)} = \frac{1000}{s(s+10)(s+30)}$$

$$= \frac{3.33}{s} - \frac{5}{s+10} + \frac{1.67}{s+30}$$

$$I_2(t) = 3.33 - 5e^{-10t} + 1.67e^{-30t}$$

(2.5 mark)

Q 2 B

KCL

Final V(t)

$$C \frac{dV}{dt} + GV + \frac{1}{L} \int V dt = 0$$

diff

$$C \frac{d^2V}{dt^2} + G \frac{dV}{dt} + \frac{V}{L} = 0$$

Ch: eqn.

$$s^2 + 10s + 2 = 0$$

roots are $-9.7958, -0.2042$

$$s_1 = 4.3, s_2 = -5.3$$

$$\therefore V(t) = K_1 e^{-9.79t} + K_2 e^{-0.204t}$$

$$\text{at } t=0, V(0) = 10 \text{ V}$$

$$10 = K_1 + K_2 \quad \textcircled{3}$$

$$\text{diff: } \frac{dV}{dt} = -9.79K_1 e^{-9.79t} - 0.204K_2 e^{-0.204t} \quad \textcircled{4}$$

$$\text{from } \textcircled{1} \text{ at } t=0, V_0 = 10$$

$$C \frac{dV}{dt} = -10 \times 10 + 0$$

$$\frac{1}{L} \int V dt = \underline{\underline{\underline{I}}}_L = 0$$

inductor current = 0

$$\therefore \left. \frac{dV}{dt} \right|_{t=0} = -100$$

$$\textcircled{4} \text{ gives } -100 = -9.79K_1 - 0.204K_2 \quad \textcircled{5}$$

$K_1 = -0.02$

where $K_1 = -4.896, K_2 = 14.896$


$$\textcircled{2} \text{ gives } \therefore V(t) = -\underline{\underline{\underline{14.896}}}_L e^{-0.204t} + \underline{\underline{\underline{4.896}}}_L e^{-9.79t}$$

$K_2 = 14.896$

$I_L = 0.0209$

(1 mark)

Q2E

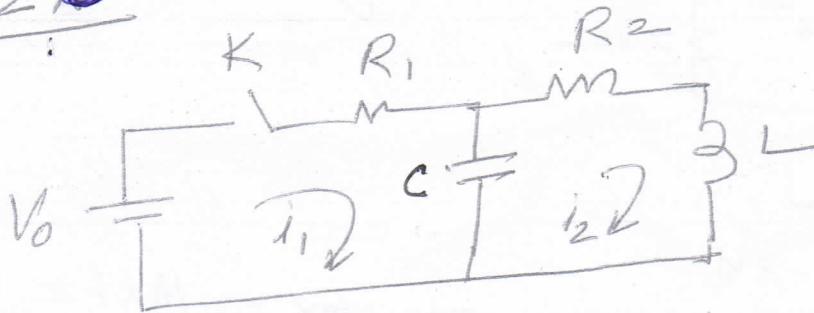

at $t=0$, switch closed

(1 mark)

$$i_1(0) = \frac{V}{R_1}, \quad i_2(0) = 0 \quad \text{Ans}$$

first loop

$$R_1 i_1 + \frac{1}{C} \int (i_1 - i_2) dt = V_0 \quad \text{--- (1)}$$

$$\text{Second loop} \quad R_2 i_2 + L \frac{di_2}{dt} + \frac{1}{C} \int (i_2 - i_1) dt = 0 \quad \text{--- (2)}$$

$$\text{at } t=0, \frac{1}{C} \int (i_2 - i_1) dt = 0 \quad \therefore \text{short circuit}$$

$$(2) \text{ gives } R_2 i_2 + L \frac{di_2}{dt} = 0 \quad \text{--- (3)}$$

$$\therefore \text{at } t=0, i_2(0) = 0 \quad \therefore \frac{di_2}{dt} = 0 \quad \text{Ans}$$

diff (1)

$$R_1 \frac{di_1}{dt} + \frac{i_1 - i_2}{C} = 0$$


$$\frac{di_1}{dt} = - \frac{(i_1 - i_2)}{R_1 C}$$

$$\text{at } t=0, i_1 = \frac{V}{R_1} \text{ and } i_2 = 0$$

$$\therefore \frac{di_1}{dt} = - \frac{V}{R_1^2 C} \quad \text{Ans}$$

(1 mark)

Q3A

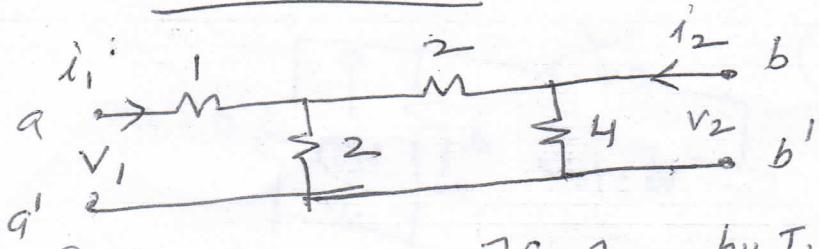
 h Parameters

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} h_{11} I_1 + h_{12} V_2 \\ h_{21} I_1 + h_{22} V_2 \end{bmatrix}$$

1 mark

bb' short circled $V_2 = 0$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = 2 \Omega$$

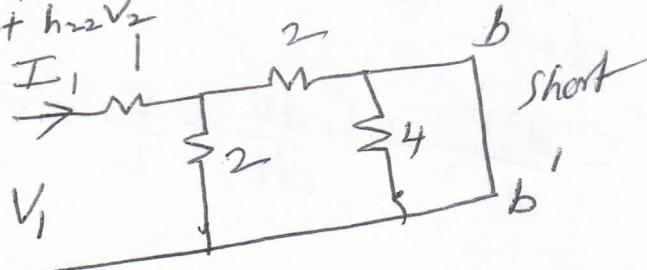

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = -\frac{1}{2}$$

If aa' open $\Rightarrow I_1 = 0$


$$V_1 = I_y \cdot 2$$

$$\therefore I_y = \frac{I_2}{2}$$

$$V_2 = I_x \cdot 4 \cdot 0$$

$$\therefore I_x = \frac{I_2}{4}$$

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{1}{2}$$

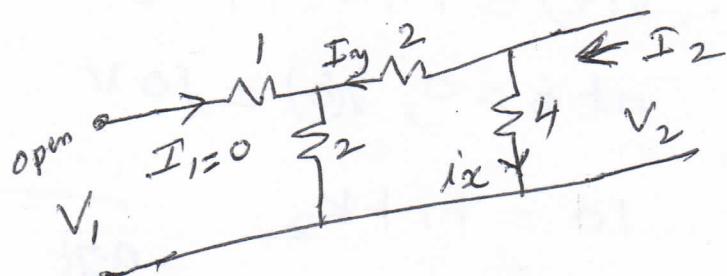

$$\begin{bmatrix} 2 & \frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix}$$

Each parameter
1 mark each

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{2} \Omega$$

(OR)

Δ star connection

$\frac{R_1 R_2}{R_1 + R_2 + R_3}$

Loop 1: $\frac{3}{2} I_1 + I_1 + I_2 = V_1 \quad \dots \quad (1)$
 $\sum I_1 + I_2 = V_1$

Loop 2: $I_2 + I_1 + I_2 = V_2 \quad \dots \quad (2)$
 $I_1 + 2I_2 = V_2$

$\therefore Z \text{ parameters} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} \frac{5}{2} & 1 \\ 1 & 2 \end{bmatrix}$

$\therefore h \text{ parameters} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} 2 & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} \end{bmatrix}$
 $\Delta = \frac{5}{2} \times 2 - 1 = \frac{4}{2}$

Q3B

$$y(n) = n x(n)$$

System is M, NC, L, TV, US, NIV
with illustration - 3m

3C

$$x(t) = e^{-2t} u(t)$$


$$E = \int_0^b (e^{-2t})^2 dt = \int_0^b e^{-4t} dt = \frac{1}{4} \quad 1.5m$$

P = 0 0.5m

4A


$$\begin{aligned} (i) \quad y(t) &= x(t) * h(t) \\ &= [\delta(t+1) - \delta(t-1)] * [\gamma(t+1) - 2\gamma(t) + \gamma(t-1)] \\ &= \gamma(t+2) - 2\gamma(t+1) + \gamma(t) \\ &\quad - \{\gamma(t) - 2\gamma(t-1) + \gamma(t-2)\} \\ &= \gamma(t+2) - 2\gamma(t+1) + 2\gamma(t-1) - \gamma(t-2) \end{aligned}$$

- 2m

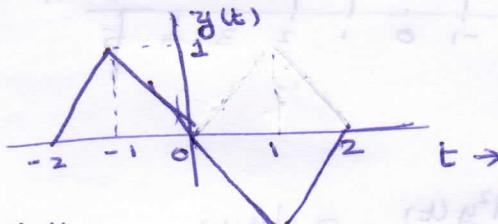

$$\begin{aligned} (ii) \quad y(t) &= x(t) * h(t) \\ &= x(t) + \{ x(t+2) - 2x(t) + x(t-2) \} \\ &= \gamma(t+2) - 2\gamma(t) + \gamma(t-2) \end{aligned}$$

- 2m

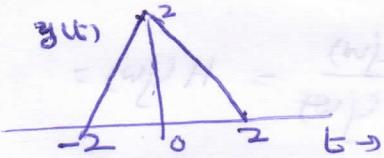

4B

$$e^{-2t} u(t) \xleftrightarrow{FT} \frac{1}{2+j\omega}$$

$$t e^{-2t} u(t) \xleftrightarrow{FT} \frac{1}{(2+j\omega)^2}$$

- 1m

$$t e^{-2t} \sin t u(t) = t e^{-2t} \left(\frac{e^{jt} - e^{-jt}}{2j} \right) \xleftrightarrow{FT} \frac{1}{2j} \left\{ \left(\frac{1}{2+j(\omega-1)} \right)^2 - \left(\frac{1}{2+j(\omega+1)} \right)^2 \right\}$$

- 1m

$$\therefore x(t) = \frac{d}{dt} \left\{ t e^{-2t} \sin t u(t) \right\} \xleftrightarrow{FT} j\omega \cdot \frac{1}{2j} \left\{ \right\}$$

$$= \frac{\omega}{2} \left\{ \left[\frac{1}{2+j(\omega-1)} \right]^2 - \left[\frac{1}{2+j(\omega+1)} \right]^2 \right\}$$

- 3m

$$4C \quad x(t) = \cos(\pi t) + \cos(4\pi t) + \sin(5\pi t)$$

$$= e^{j\pi t} + e^{-j\pi t} + \frac{e^{j4\pi t} + e^{-j4\pi t}}{2} + \frac{e^{j5\pi t} - e^{-j5\pi t}}{2j}$$

Comparing with $\sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}$, $\omega_0 = \pi$


$$x(t) = \sum_{k=-\infty}^{\infty} a_k e^{jk\omega_0 t}, \quad \omega_0 = \pi$$

$$a_1 = a_{-1} = y_2$$

$$a_2 = a_{-2} = y_2$$

$$a_3 = \frac{1}{2j}$$
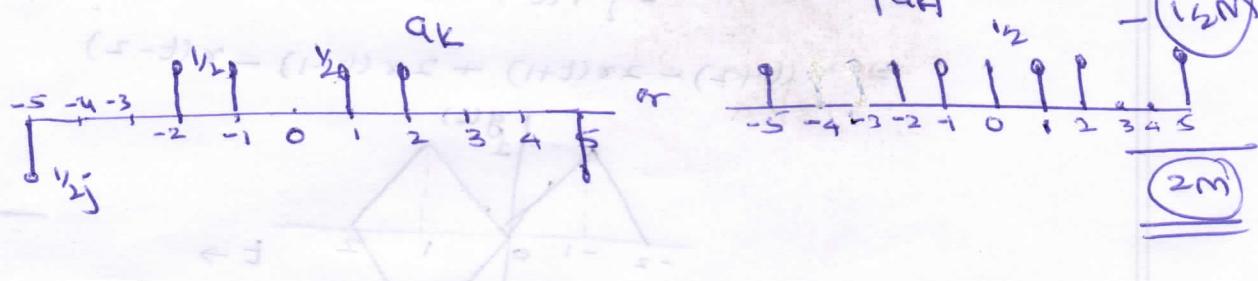
$$a_4 = -\frac{1}{2j} \quad a_k = 0 \text{ otherwise}$$



5A

$$\frac{d^2y(t)}{dt^2} + 3 \frac{dy(t)}{dt} + 2y(t) = \frac{dx(t)}{dt} + 3x(t)$$

$$(i) \text{ FT} \Rightarrow [(j\omega)^2 + 3j\omega + 2]Y(j\omega) = (j\omega + 3)X(j\omega)$$

$$\frac{Y(j\omega)}{X(j\omega)} = H(j\omega) = \frac{j\omega + 3}{(j\omega)^2 + 3j\omega + 2}$$

(ii) Take IFT

$$H(j\omega) = \frac{A}{(j\omega + 1)} + \frac{B}{(j\omega + 2)}$$

$$\Rightarrow A = 2, B = -1$$

$$\therefore h(t) = (2e^{-t} - e^{-2t})u(t)$$

$$(iii) \quad Y(j\omega) = X(j\omega) \cdot H(j\omega)$$

$$= \frac{1}{3+j\omega} \cdot \frac{j\omega + 3}{(j\omega + 1)(j\omega + 2)}$$

$$= \frac{1}{(j\omega + 1)(j\omega + 2)} = \frac{A}{j\omega + 1} + \frac{B}{j\omega + 2}$$

$$y(t) = (e^{-t} - e^{-2t})u(t)$$

$$\begin{aligned} A &= 1 \\ B &= -1 \end{aligned}$$

1.5M

5M

5B

$$X(j\omega) = \left[\frac{2}{\omega} \sin \omega \right] \left[\frac{1}{(j\omega + 1)} \right]$$

$$= x_1(j\omega) \cdot x_2(j\omega)$$

$$\therefore x(t) = x_1(t) * x_2(t)$$

$$= \text{rect}(t) * e^{-t} u(t)$$

$$t < -1, \quad x(t) = 0$$

$$-1 < t < 1, \quad x(t) = \int_{-1}^{t+1} e^{-\tau} d\tau$$


$$= 1 - e^{-(t+1)}$$

$$t > 1, \quad x(t) = \int_{t-1}^{t+1} e^{-\tau} d\tau$$

$$= \underline{\underline{e^{-t}(e^2 - e^{-2})}}$$

$$\frac{2}{\omega} \sin \omega \xrightarrow{\text{FT}} \text{rect}(t)$$

$$= \begin{cases} 1, & |t| \leq 1 \\ 0, & |t| > 1 \end{cases}$$

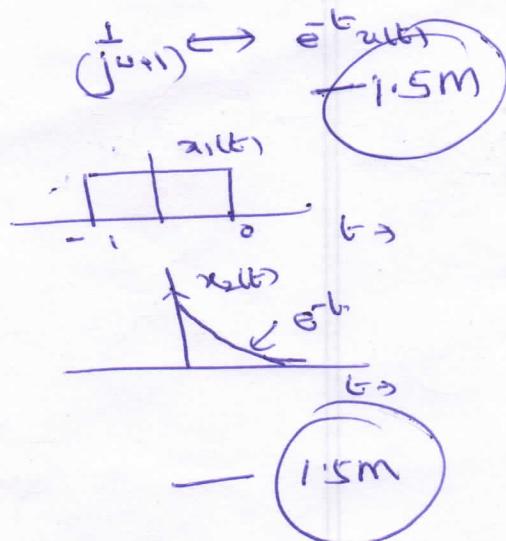

5C

$$X_2 = \int_{-\infty}^{\infty} \left(\frac{\sin \pi t}{\pi t} \right)^2 dt$$

using Parseval's theorem

$$\int_{-\infty}^{\infty} |x(t)|^2 dt = \frac{1}{2\pi} \int_{-\infty}^{\infty} |X(j\omega)|^2 d\omega$$

1/2 m

$$\therefore x(t) = \frac{\sin \pi t}{\pi t} \xrightarrow{\text{FT}} X(j\omega) = \begin{cases} 1, & |\omega| < \pi \\ 0, & |\omega| > \pi \end{cases}$$

$$\int_{-\infty}^{\infty} \left(\frac{\sin \pi t}{\pi t} \right)^2 dt = \frac{1}{2\pi} \int_{-\pi}^{\pi} 1 d\omega$$

$$= \underline{\underline{1}}$$

1

1m
2m