

FEEDBACK AMPLIFIERS

(1)

- * Depending on the polarity of the signal being fed back into a circuit, one may have negative or positive feedback.
- * Negative feedback results in decreased voltage gain, for which number of circuit features are improved.
- * Positive feedback drives a circuit into oscillation as in various types of oscillator circuits.
- * A typical feedback connection is shown in Fig (1):

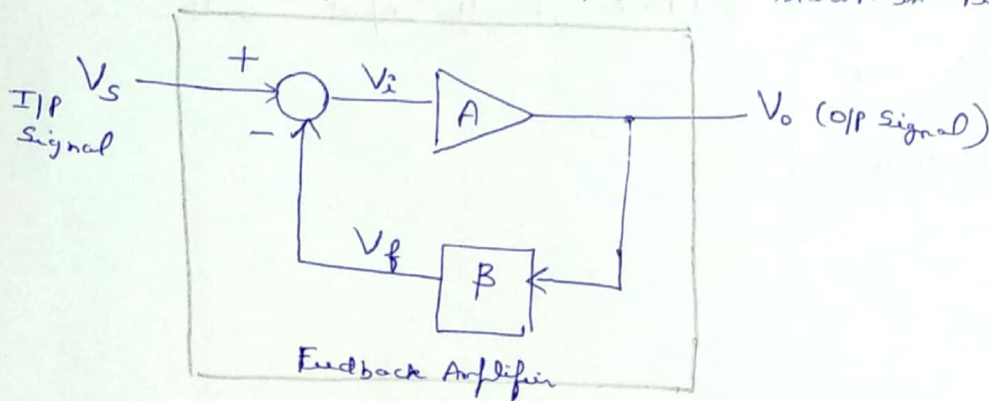


Fig (1): Simple block diagram of feedback amplifier

- * The i/p signal ' V_s ' is applied to a mixer network, where it is combined with a feedback signal ' V_f '.
- * The difference of these signals ' V_i ' is then the input voltage to the amplifier.
- * A portion of the op amplifier output ' V_o ' is connected to the feedback network (B), which provides a reduced portion of the output as feedback signal to the input mixer network.
- * If the feedback signal is of opposite polarity to the input signal, negative feedback results (Fig (1)).
- * Although negative feedback results in reduced overall voltage gain, a number of advantages are there. They are:

1. Higher input impedance
2. Better Stabilized Voltage gain
3. Improved frequency response
4. Lower o/p impedance
5. Reduced Noise
6. More linear operation

⇒ Feedback Connection Types

* There are 4 basic ways of connecting the feedback signal.

Both Voltage and Current be fed back to the input either in series or parallel. They are:

1. Voltage - series F.B (feedback)
2. Voltage - shunt FB
3. Current - series FB
4. Current - shunt FB

* In the list above, 'Voltage' refers to connecting the output voltage as input to the feedback network.

* 'Current' refers to tapping off some output current through the FB N/w.


* 'Series' refers to connecting the FB signal in series with the i/p signal voltage.

'Shunt' refers to connecting the FB signal in shunt (parallel) with an input current source.

* 'Series' FB connections tend to increase the input resistance, whereas shunt FB connections tend to decrease the input resistance.


* Voltage FB tends to decrease the o/p impedance, whereas current FB tends to increase the o/p impedance.

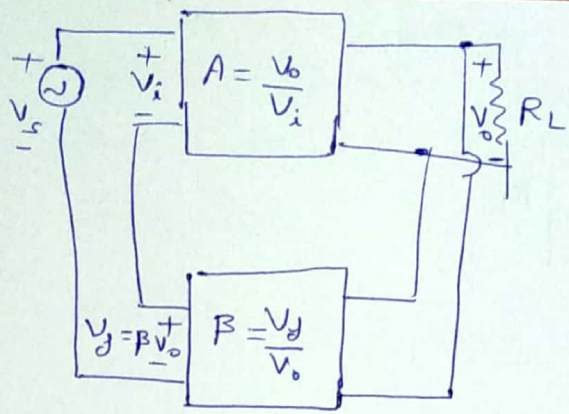* Typically, higher input and lower output impedances are desired for most cascade amplifiers. Both of these are provided using the voltage - series feedback connection.




(a)

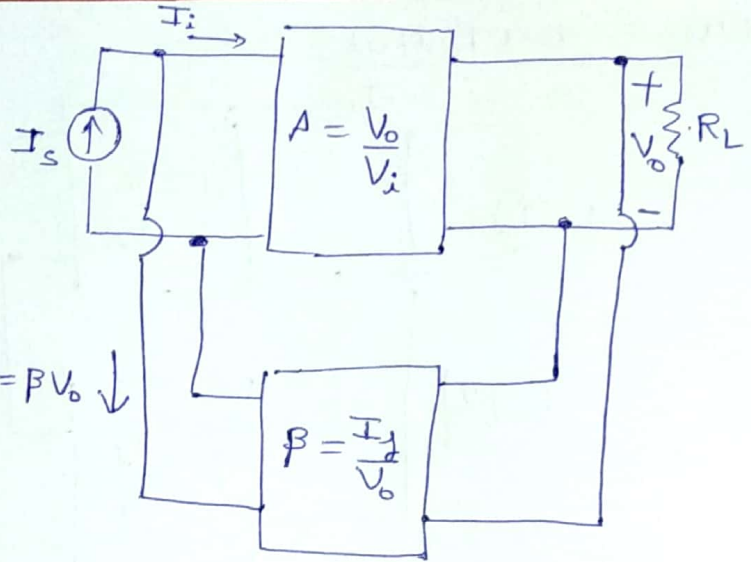Voltage Series Feedback, $A_f = \frac{V_o}{V_s}$




(b)

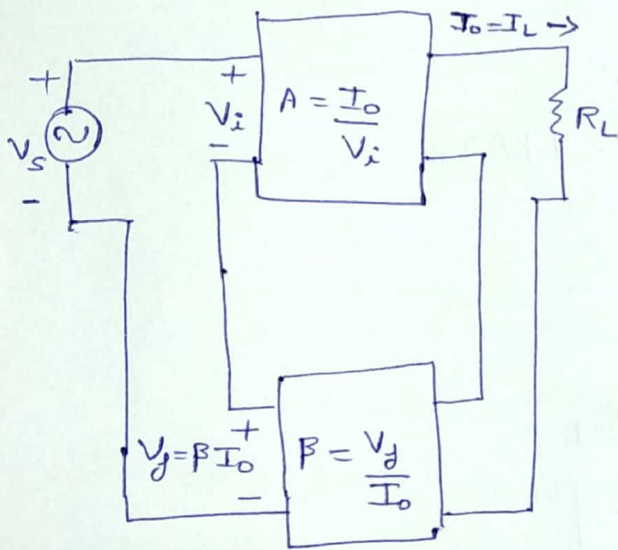Voltage-shunt feedback, $A_f = \frac{V_o}{I_s}$



(c)

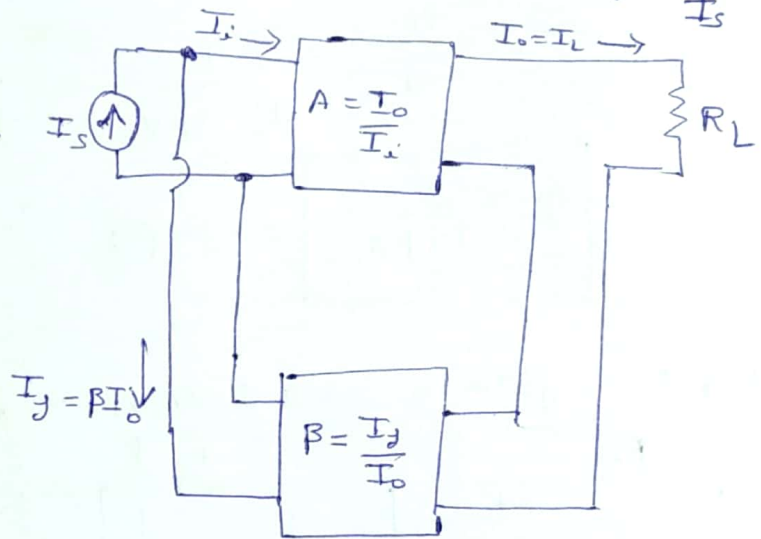Current-Series feedback $A_f = \frac{I_o}{V_s}$



(d)

Current-shunt feedback, $A_f = \frac{I_o}{I_s}$

⇒ Gain with Feedback

* The gain without feedback, A , is that of the amplifier stage.
 * With feedback ' β ', the overall gain of the circuit is reduced by a factor of $(1 + \beta A)$.

Voltage Series Feedback (Fig. a)

o/p V_o feedback in series with input signal.

If no feedback ($V_f = 0$), the gain of amplifier stage $A = \frac{V_o}{V_s} = \frac{V_o}{V_i}$ — (1)

If feedback ' V_f ' is connected in series with i/p signal, then

$$V_i = V_s - V_f$$

$$\text{Since } V_o = AV_i = A(V_s - V_f) = AV_s - AV_f$$


$$V_o = AV_s - A(\beta V_o)$$

$$\text{Then } (1 + \beta A)V_o = AV_s$$

So the overall voltage gain with FB,

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A} \text{ — (2)}$$

Voltage - Shunt Feedback

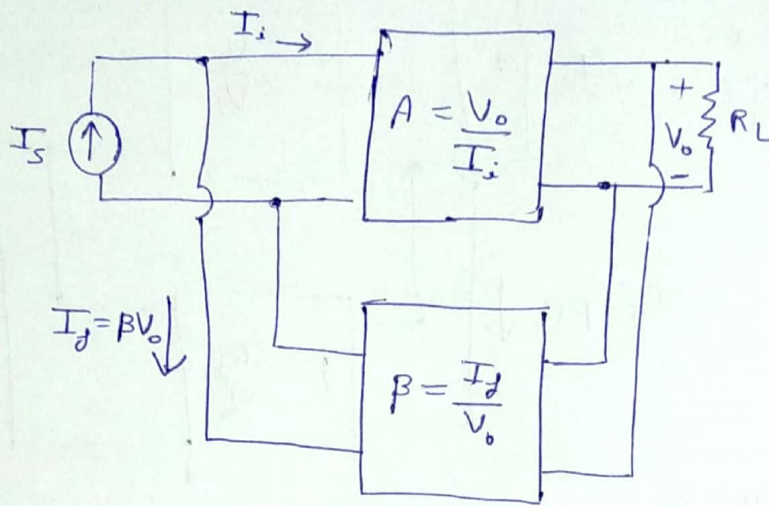

The gain with feedback for the circuit is,

$$A_f = \frac{V_o}{I_s} = \frac{A I_s}{I_s + \beta V_o} = \frac{A I_s}{I_s + \beta A I_s}$$

$$A_f = \frac{A}{1 + \beta A} \quad \text{--- (3)}$$

⇒ Input Impedance with Feedback

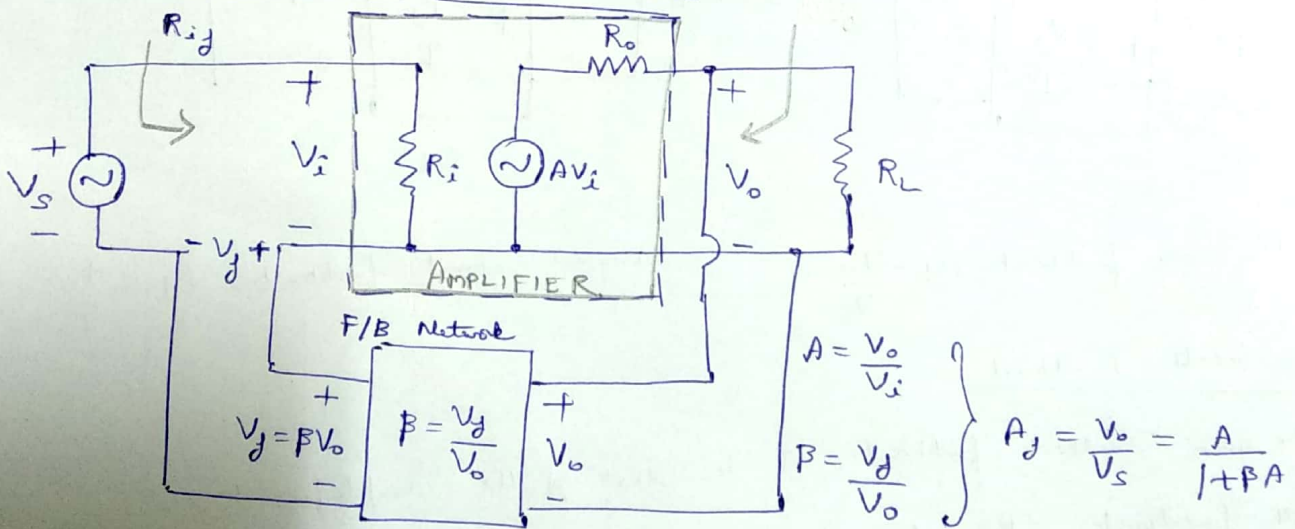


Fig: Voltage series feedback connection

The input impedance can be determined as follows:

$$I_i = \frac{V_i}{Z_i} = \frac{V_s - V_f}{Z_i} = \frac{V_s - \beta V_o}{Z_i} = \frac{V_s - \beta A V_i}{Z_i}$$

$$I_i Z_i = V_s - \beta A V_i$$

$$V_s = I_i Z_i + \beta A V_i = I_i Z_i + \beta A I_i Z_i$$

$$Z_{if} = \frac{V_s}{I_i} = Z_i + (\beta A) Z_i = Z_i (1 + \beta A) \quad \text{--- (4)}$$

The input impedance with series feedback is seen to be the value of (3) the input impedance without feedback multiplied by the factor $(1 + \beta A)$, and is applied to both Voltage-series (Fig @) and Current-series (Fig ©) Configurations.

Voltage Shunt Feedback

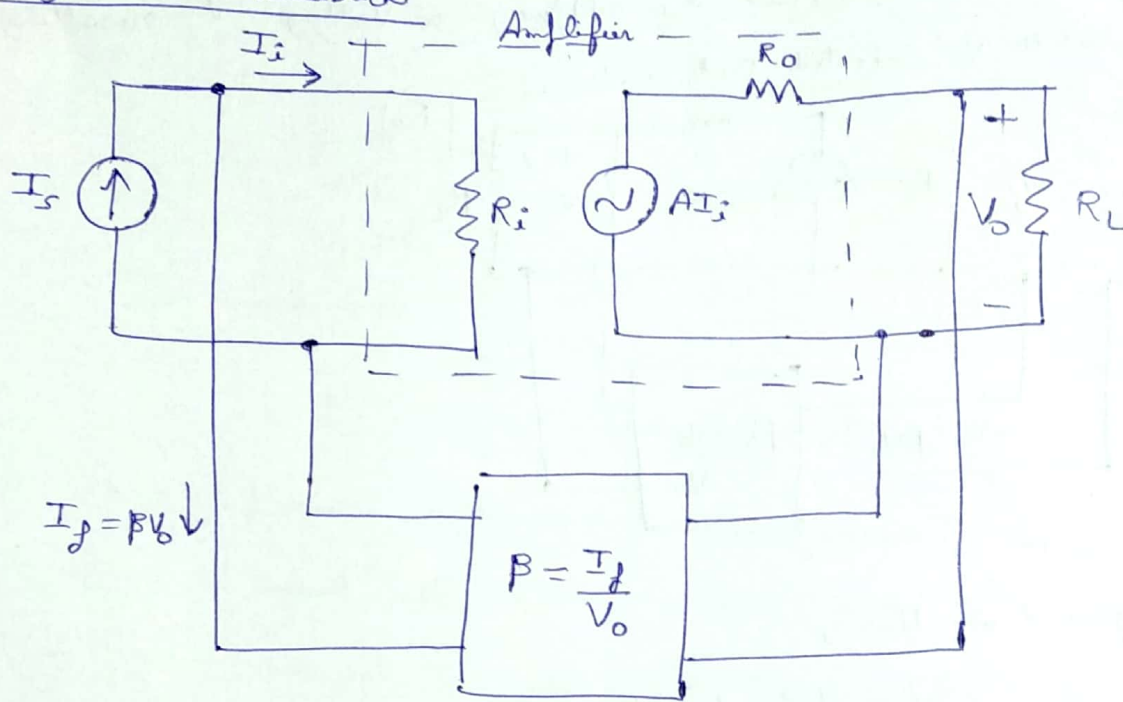


Fig: Voltage Shunt feedback Connection

The input impedance can be determined to be,

$$Z_{if} = \frac{V_i}{I_s} = \frac{V_i}{I_i + I_f} = \frac{V_i}{I_i + \beta V_o}$$

$$\div \text{ by } I_i$$

$$= \frac{V_i / I_i}{I_s / I_i + \beta V_o / I_i}$$

$$\boxed{Z_{if} = \frac{Z_i}{1 + \beta A}} \quad \text{--- (5)}$$


This reduced input impedance applies to the Voltage-series Connection (fig @) and the Voltage-shunt Connection of Fig ©.

Output Impedance with Feedback

For Voltage feedback, the output impedance is decreases, whereas Current feedback increases the output impedance.

Voltage-series Feedback : (Fig 14.3)

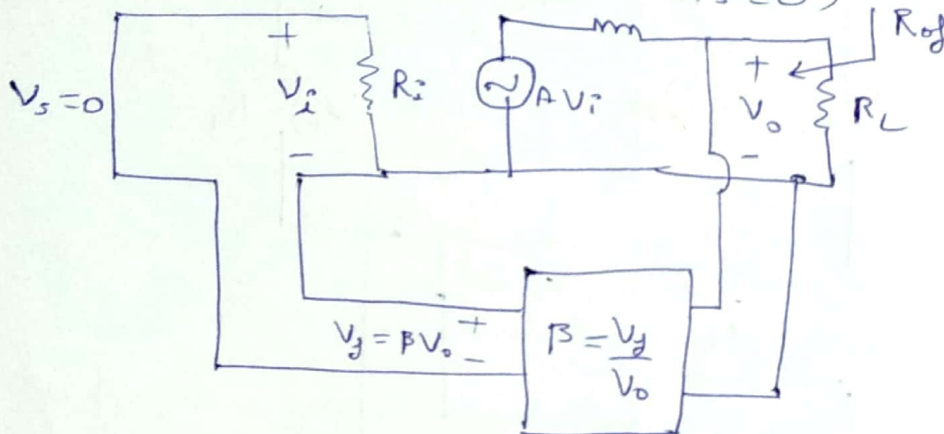The O/P impedance is determined by applying a Voltage 'V', resulting in a Current I, with V_s shorted out ($V_s = 0$)



The Voltage V is then,

$$V = IZ_o + AV_i$$

$$\text{For } V_s = 0, \quad V_i = -V_f$$

So that

$$V = IZ_o - AV_f = IZ_o - A(\beta V)$$

$$\Rightarrow V + \beta AV = IZ_o$$

allows Solving for the output resistance with feedback:

$$Z_{of} = \frac{V}{I} = \frac{Z_o}{1 + \beta A}$$

— (6)

Eqⁿ (6) shows that with Voltage-series feedback, the output impedance is reduced from that without feedback by the factor $(1 + \beta A)$.

Current-Series Feedback

(4)

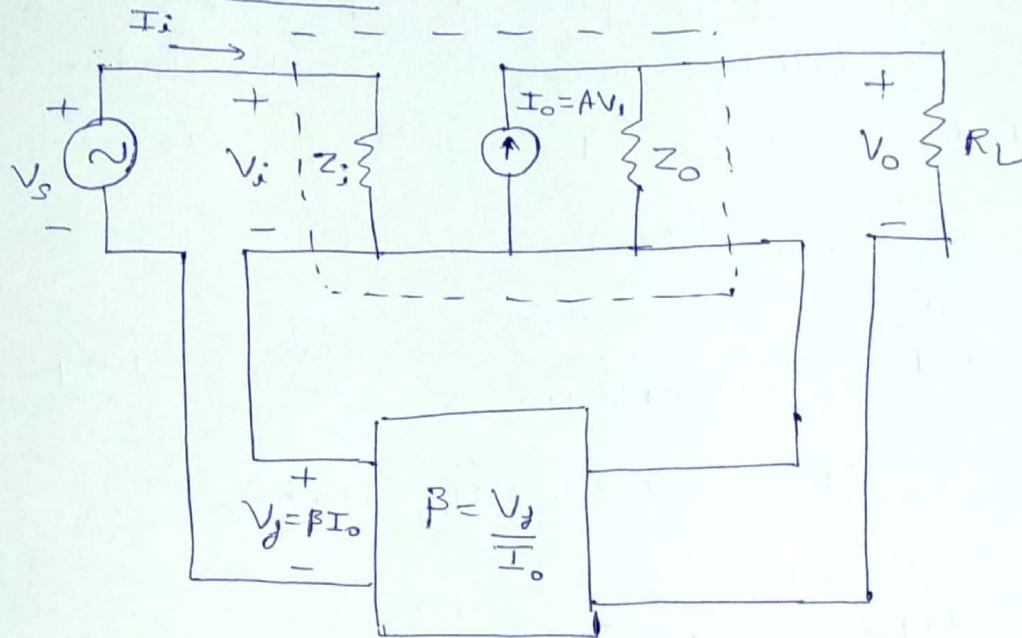


Fig: Current-Series Feedback Connection

The output impedance with current-series feedback can be determined by applying a signal 'V' to the output with V_s shorted out, resulting in a current 'I', the ratio of 'V' to 'I' being the output impedance.

With $V_s = 0$,

$$V_i = V_f$$

$$I = \frac{V}{Z_o} - A V_i = \frac{V}{Z_o} - A V_f = \frac{V}{Z_o} - A \beta I$$

$$Z_o (1 + \beta A) I = V$$

$$Z_{of} = \frac{V}{I} = Z_o (1 + \beta A) \quad \text{--- (7)}$$

Table 1: Effect of Feedback Connection on Input & Output Impedance

Voltage Series		Current-Series		Voltage Shunt		Current-Shunt	
Z_{if}	$Z_i (1 + \beta A)$ (increased)	$Z_i (1 + \beta A)$ (increased)		$\frac{Z_i}{1 + \beta A}$ (decreased)		$\frac{Z_i}{1 + \beta A}$ (decreased)	
Z_{of}	$\frac{Z_o}{1 + \beta A}$ (decreased)	$Z_o (1 + \beta A)$ (increased)		$\frac{Z_o}{1 + \beta A}$ (decreased)		$Z_o (1 + \beta A)$ (increased)	

Ex:1: Determine Voltage gain, input and output impedance with feedback for Voltage-series feedback having $A = -100$, $R_i = 10\text{ k}\Omega$ and $R_o = 20\text{ k}\Omega$ for feedback of (a) $\beta = -0.1$ and (b) $\beta = -0.5$.

Solⁿ Using eqⁿ (2), (4) and (6), we calculate

$$a. A_f = \frac{A}{1 + \beta A} = \frac{-100}{1 + (-0.1)(-100)} = \frac{-100}{11} = -9.09$$

$$Z_{if} = Z_i (1 + \beta A) = 10\text{ k}\Omega (11) = 110\text{ k}\Omega$$

$$Z_{of} = \frac{Z_o}{1 + \beta A} = \frac{20 \times 10^3}{11} = 1.82\text{ k}\Omega$$

$$b. A_f = \frac{A}{1 + \beta A} = \frac{-100}{1 + (-0.5)(-100)} = \frac{-100}{51} = -1.96$$

$$Z_{if} = Z_i (1 + \beta A) = 10\text{ k}\Omega (51) = 510\text{ k}\Omega$$

$$Z_{of} = \frac{Z_o}{1 + \beta A} = \frac{20 \times 10^3}{51} = 392.16\text{ }\Omega$$

This example (part-a) demonstrates the trade-off of gain for improved input and output resistance. Reducing the gain by a factor of 11 (from 100 to 9.09) is complemented by a reduced output resistance and increased input resistance by the same factor of 11.