



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

*(A constituent institution of MAHE, Manipal)*



# Basic Electrical Technology

## RL Transient

---

# Recap

## Network Reduction Techniques

- Y- $\Delta$  Transformation
- Source Transformation

## Circuit Analysis Techniques

- Mesh Current **Method**
- Node Voltage Method

## Theorems

- Thevenin's Theorem
- Superposition Theorem
- Max. Power Transfer Theorem

# Next What?

---

- So far studied about DC **resistive** network.
  - Currents & voltages were **independent** of time.
  - In other words, current (response) changed instantly as voltage (cause) changed.
  - Will the behaviour be same if inductor or capacitor was present in a circuit?
  - Answer is **NO**.
  - In inductor,  $v_L = L \, di/dt$
- (**Notice** that I have not considered the –ve sign because the direction of the voltage will be taken care of in the circuit diagram I'll draw)
- **Current** through an inductor **doesn't** change instantly but **voltage can**.


# What is Transient ?

Dictionary

English ▾

transient

Q



transient

*/ˈtranzɪənt/*

*adjective*

lasting only for a short time; impermanent.  
"a transient cold spell"

Similar:

transitory

temporary

short-lived

short-term

ephemeral

▾

*noun*

1. a person who is staying or working in a place for a short time only.

2. a momentary variation in current, voltage, or frequency.

Definitions from Oxford Languages

Feedback

▾

Translations and more definitions

# Growth of Current in an Inductive Circuit

Applying KVL,

$$V - R i - L \frac{di}{dt} = 0$$


Initial Conditions,

$$\text{At } t = 0 \text{ sec, } i = 0 \text{ A}$$

Final current & voltage equation,

$$i = \frac{V}{R} \left( 1 - e^{-\frac{Rt}{L}} \right)$$

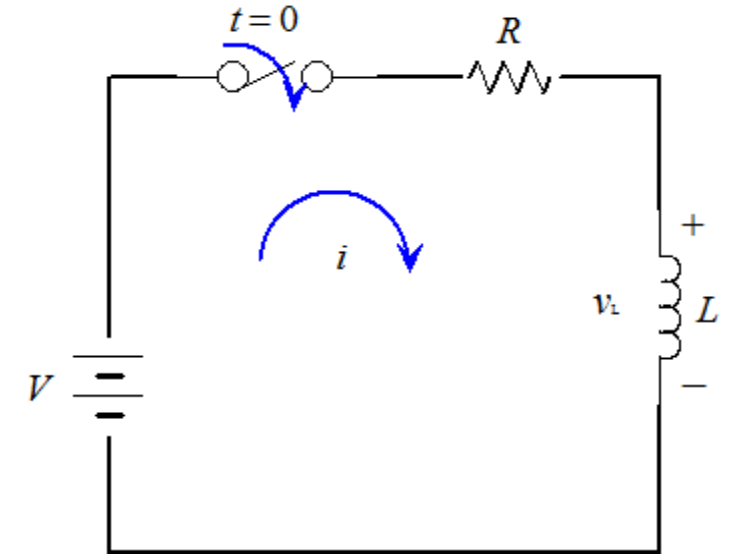
$$v_L = V e^{-\left(\frac{R}{L}\right)t}$$



# Growth of current in an inductive circuit

**Time Constant ( $\tau$ ):** Time taken by the current through the inductor to reach its final steady state value, had the initial rate of rise been maintained constant

$$\tau = \frac{L}{R}$$

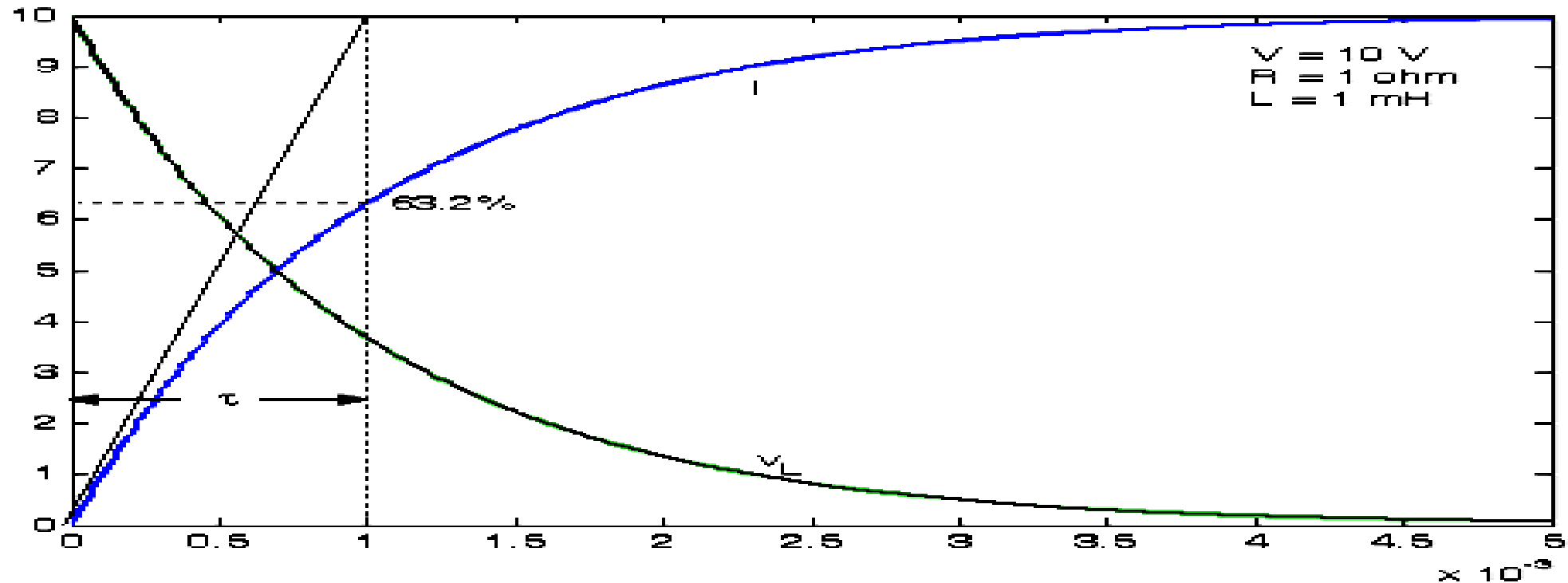


# Growth of current in an inductive circuit

The table shows how the current  $i(t)$  builds up in a R-L circuit.

Actual time (t) in sec	Growth of current in inductor (Eq.10.15)
$t = 0$	$i(0) = 0$
$t = \tau \left( = \frac{L}{R} \right)$	$i(\tau) = 0.632 \times \frac{V_s}{R}$
$t = 2\tau$	$i(2\tau) = 0.865 \times \frac{V_s}{R}$
$t = 3\tau$	$i(3\tau) = 0.950 \times \frac{V_s}{R}$
$t = 4\tau$	$i(4\tau) = 0.982 \times \frac{V_s}{R}$
$t = 5\tau$	$i(5\tau) = 0.993 \times \frac{V_s}{R}$

**Note:** Here  $V_s$  is the source voltage applied (which is same as  $V$  of previous slide)
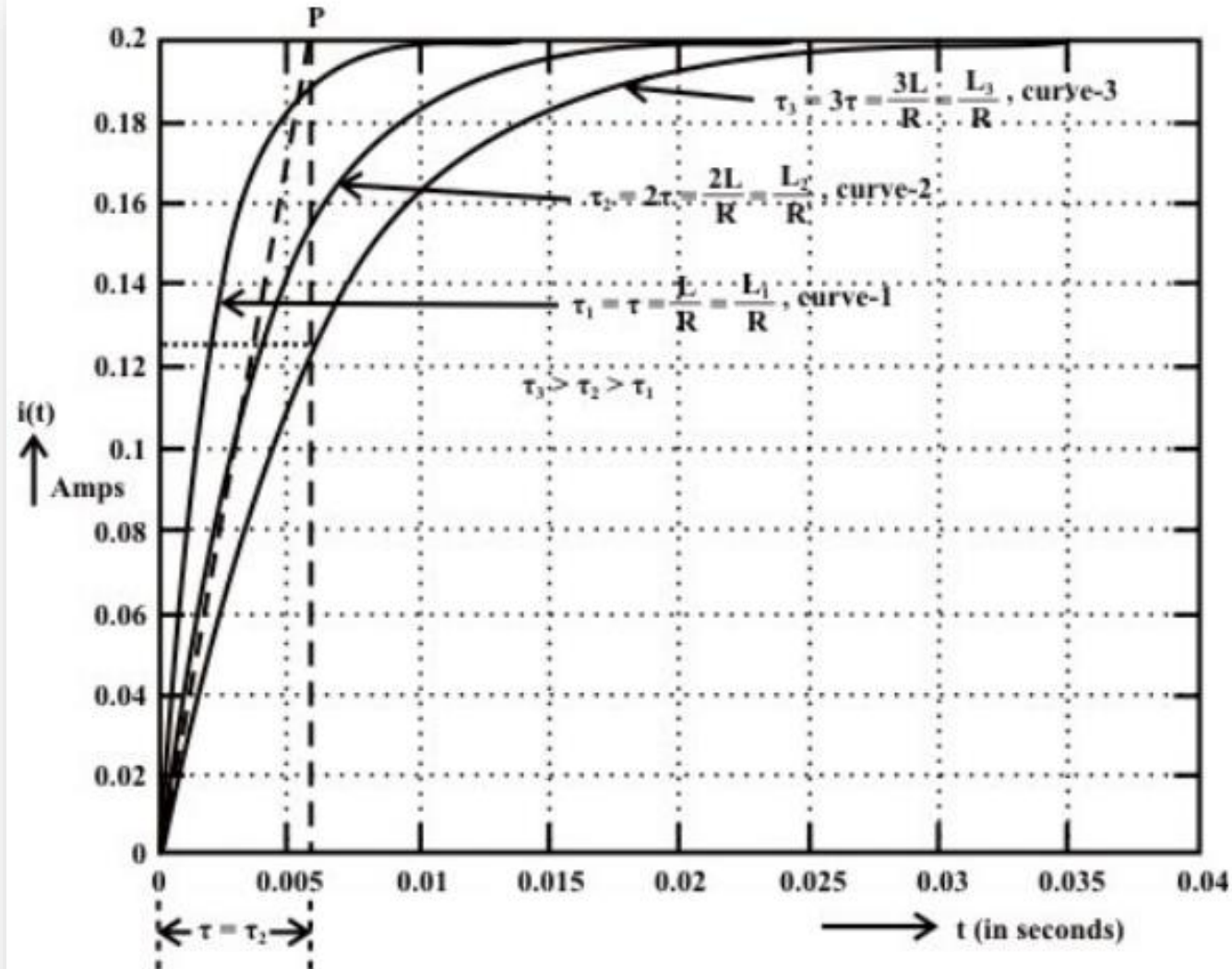
# Growth of current in an inductive circuit



**Time Constant** indicates how fast or slow the system response reaches its steady state from the instant of switching the circuit



# Illustration 1

---

A series R-L circuit having resistance  $10\ \Omega$  is connected to a 5 V dc voltage source through a switch. At  $t=0$  sec, the switch is turned on.

Find

- i. The maximum current that will flow in the circuit.
- ii. The inductance if 0.2 A current flows in the circuit at 1 ms after the voltage source is switched on.

Assume that initially no energy is stored in the inductor.

**Ans:**

- i.  $I_0 = 0.5\text{ A}$
- ii.  $L = 20\text{ mH (approx.)}$

# Decay of current in an Inductive Circuit

➤ Initial current is through inductor is

$$I_0 = V/R$$

➤ At  $t = 0$ , switch is moved from position  $a$  to  $b$


Applying KVL,

$$L \frac{di}{dt} + R i = 0$$


Using initial conditions and then solving

$$i = I_0 e^{\left(\frac{-Rt}{L}\right)}$$

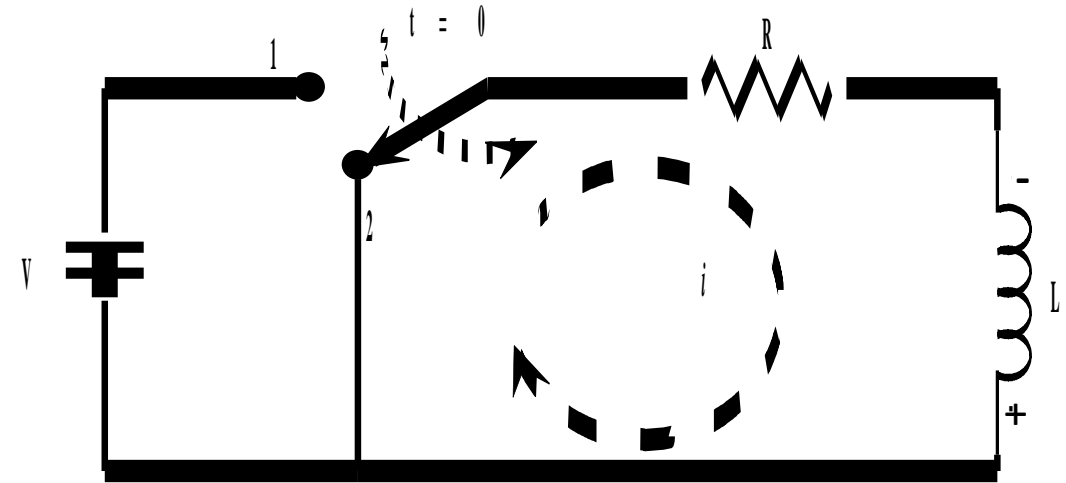
$$v_L = -V e^{-\left(\frac{Rt}{L}\right)}$$


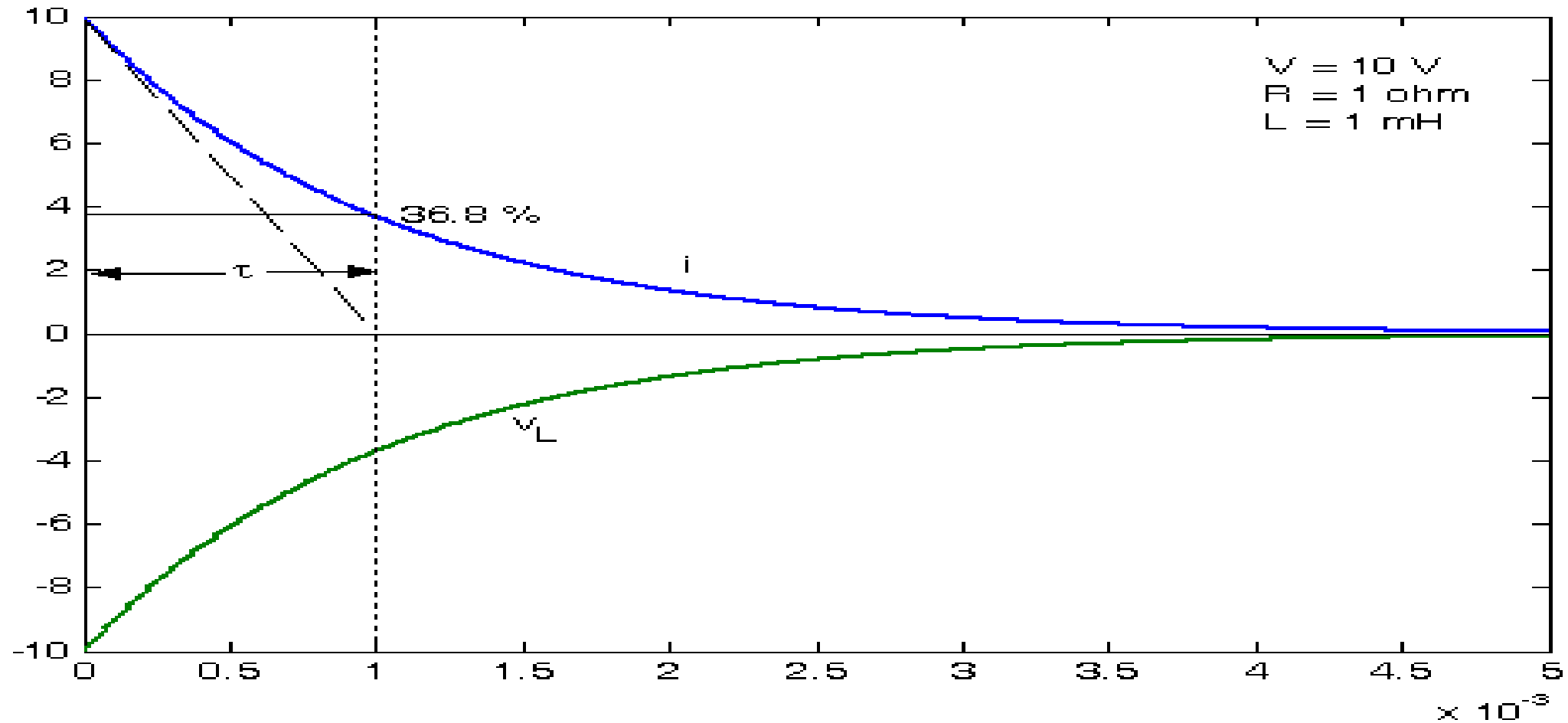
# Decay of current in an Inductive Circuit


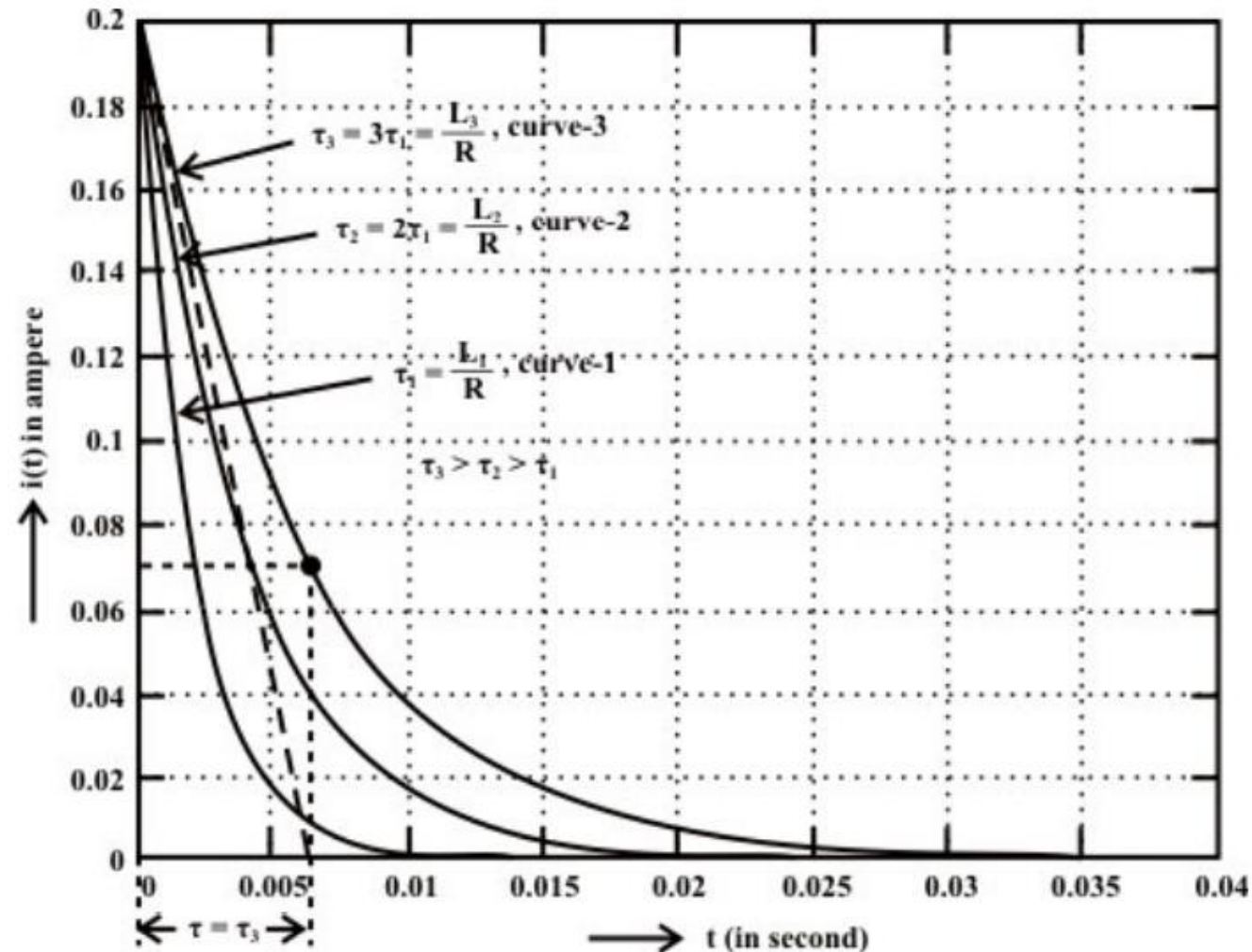
# Decay of current in an Inductive Circuit



**Time Constant** indicates how first or slow the system response decays after the source is removed.

# Some Remarks

---

- Current flowing through an inductor **cannot** change instantaneously (i.e.  $i(0^-) = i(0^+)$ ).
- Voltage across an inductor **can** change abruptly.
- Inductor acts as **short-circuit** when current flowing through it does not change.

# Illustration 2

---

A coil of resistance  $5\ \Omega$  and inductance of  $20\text{ mH}$  is connected to a battery of voltage  $12\text{ V}$  for a long time. At  $t = 0$ , the coil is short circuited. Find the time taken for the current to reach the value  $1.2\text{ A}$ .

**Ans: 2.77 ms**

# Illustration 3

In the circuit shown below, both the switches,  $S_1$  &  $S_2$ , are open initially. At  $t = 0$  sec,  $S_1$  is closed (&  $S_2$  remains open). At  $t = 4$  ms  $S_2$  is closed. Sketch the inductor current  $i(t)$  for  $0 \leq t \leq 25$  ms.

