

NAME: Sudipta Basak

Section A
Roll - 49

REG. NO: 200932194



Sudipta Basak
20.01.2022

NETWORK ANALYSIS & SIGNALS (ICE 2154)

BTECH III SEMESTER (EIE) END SEM EXAM

1.

A

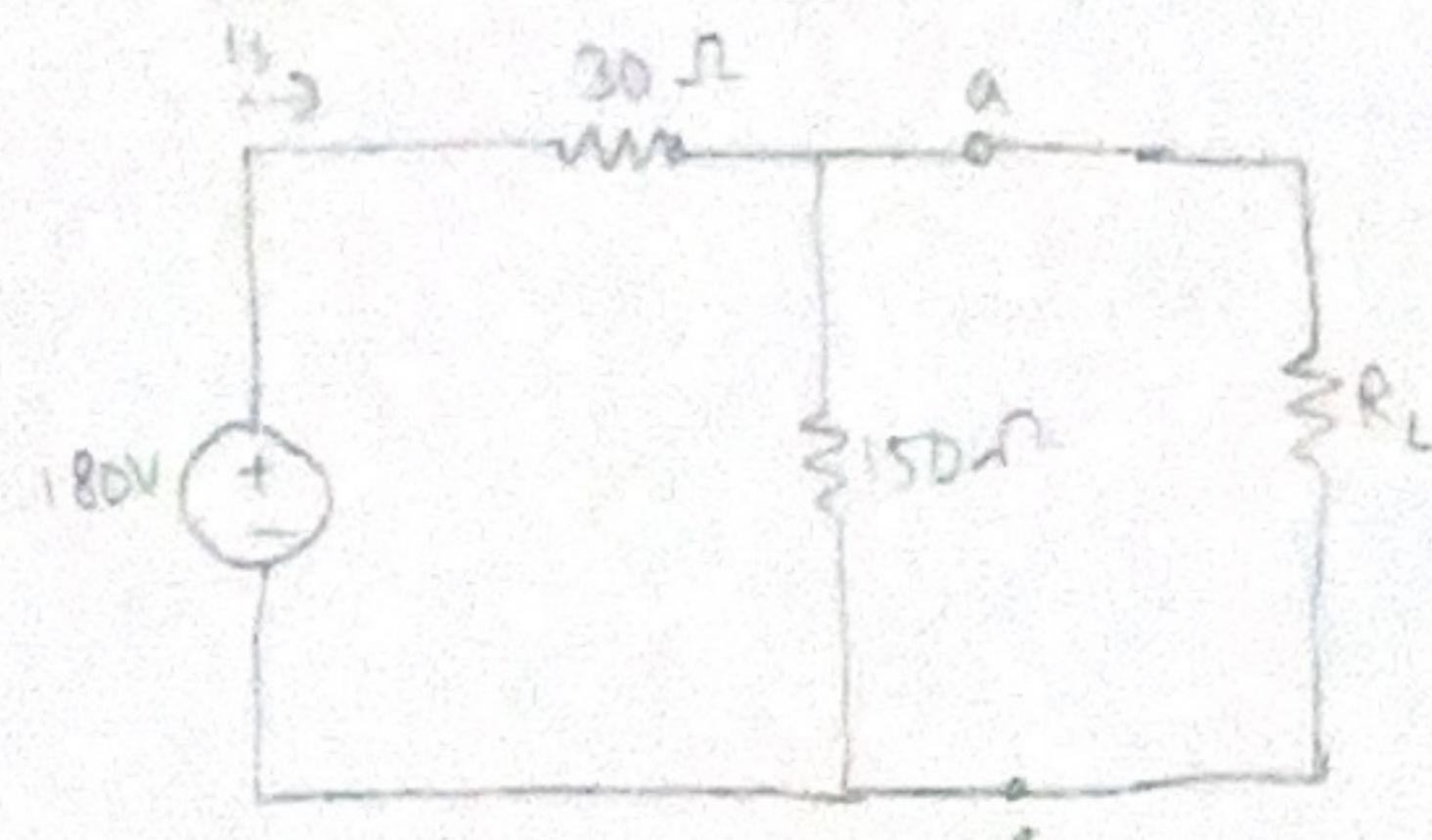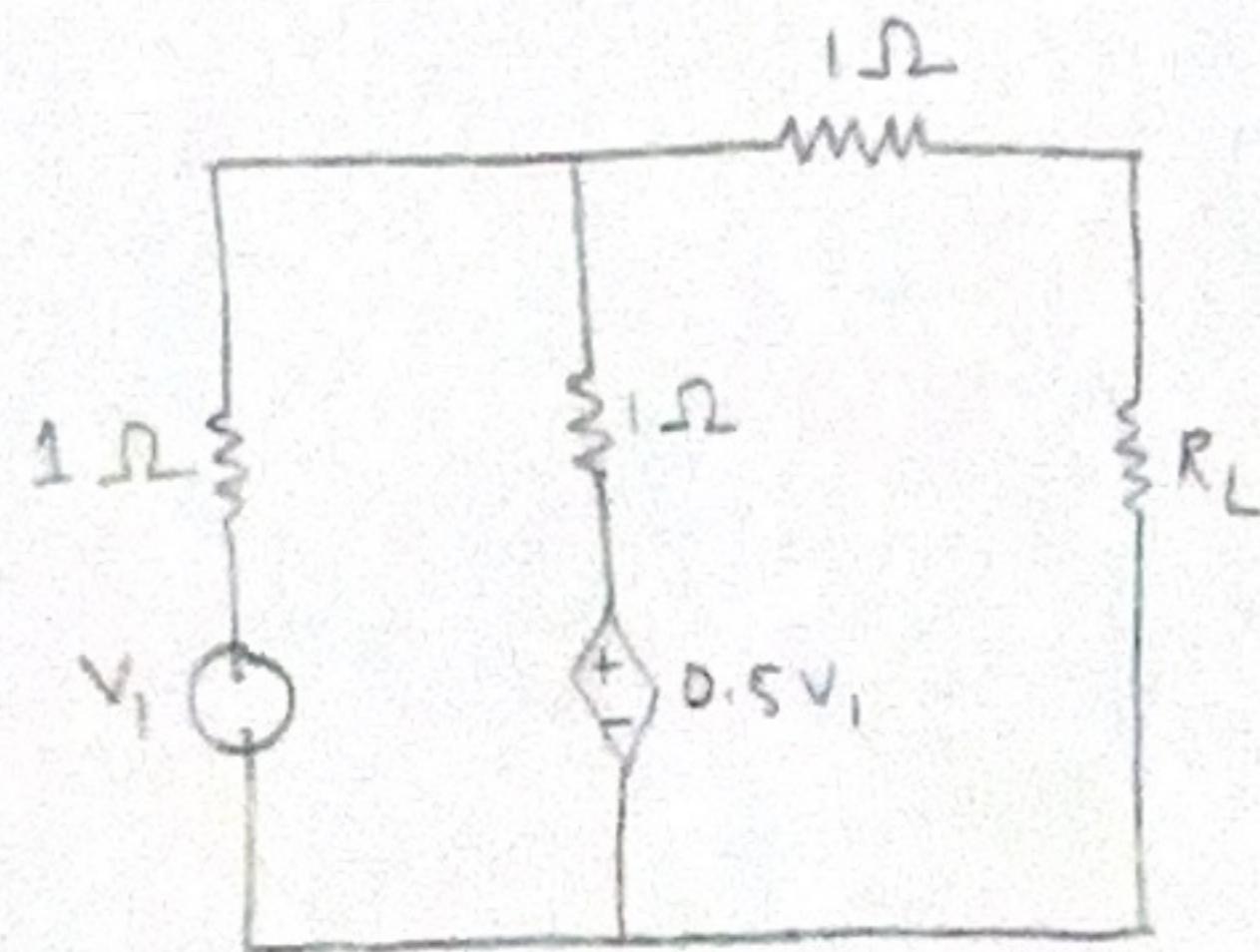

According to the MPT, the maximum power transfer to the load when the load resistance is equal to the source resistance of Thevenin resistance.


$$R_L = R_{Th}$$

R_L = load resistance

R_{Th} = Thevenin or source resistance

$$\text{The maximum power transfer (P}_{\max}\text{)} = \frac{V_{Th}^2}{4R_{Th}}$$


Calculation

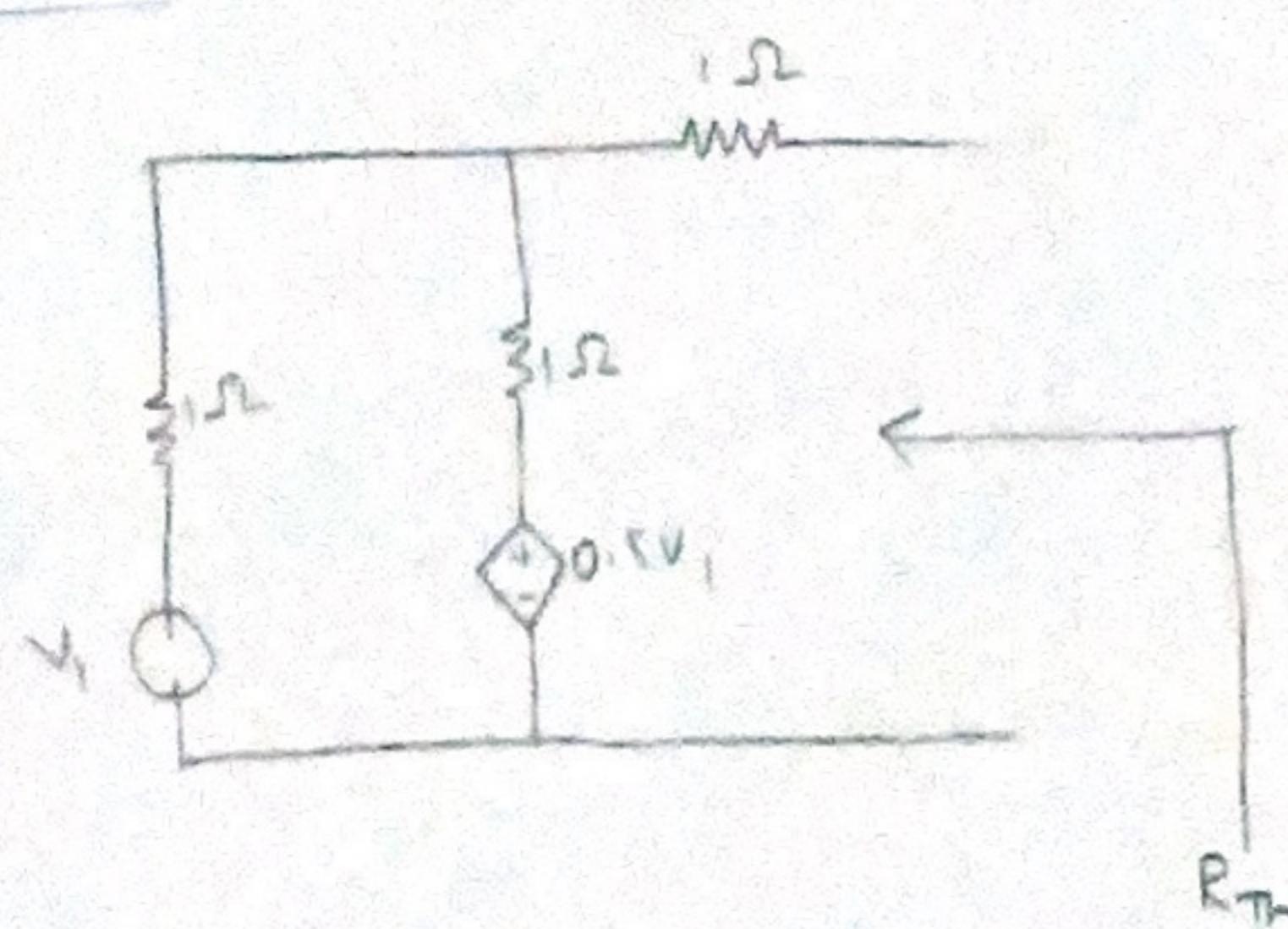

$$R_{Th} = R_L \\ = \frac{2 \times 1}{0.5 V_i} =$$

1.

(c)

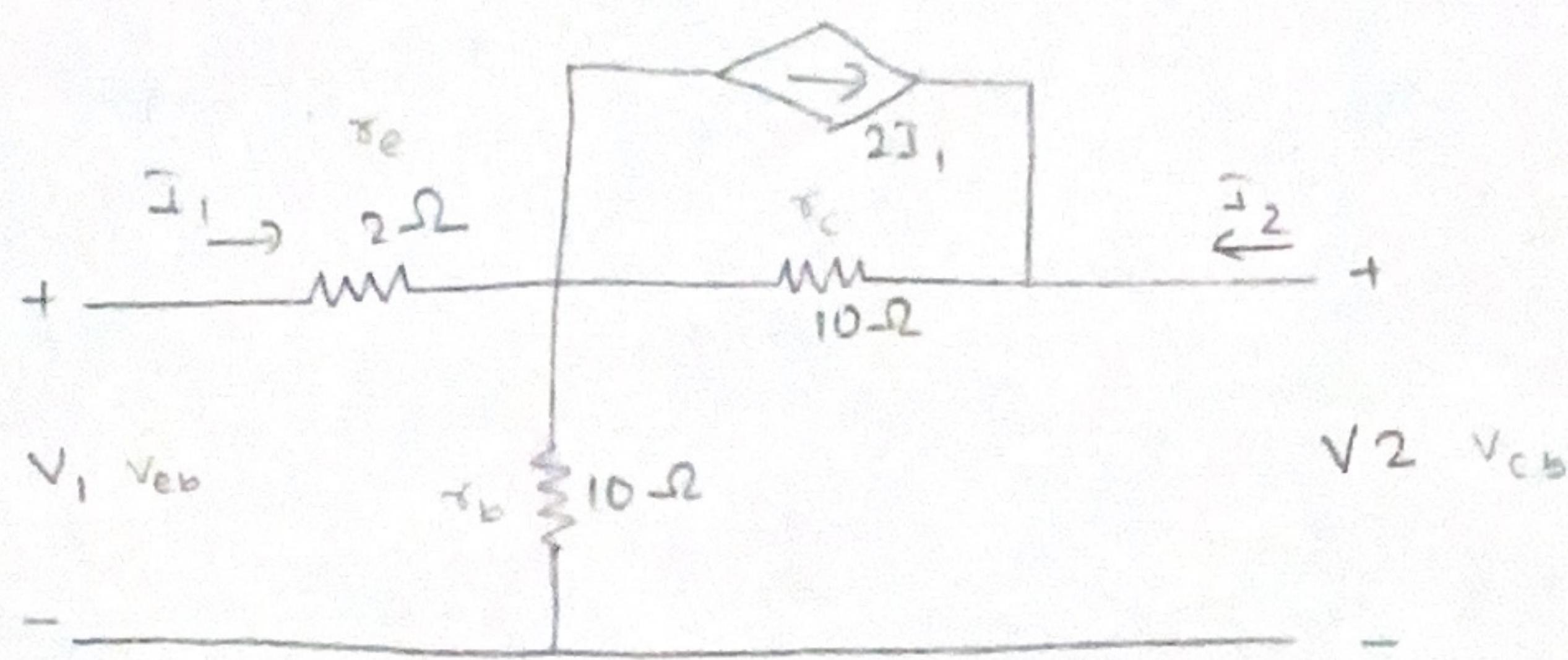

Applying KVL to the loops,

$$V_1 = I_1 r_e + 10(I_1 - I_2)$$

$$\text{or } V_1 = 2I_1 + 10I_1 - 10I_2$$

$$= 12I_1 - 10I_2$$

And,

$$-V_2 = (I_2 - I_1)10 + (I_2 - 2I_1)10$$

$$\text{or, } -V_2 = 10I_2 - 10I_1 + 10I_2 - 20I_1$$

$$\text{or, } -V_2 = 20I_2 - 30I_1$$

$$\text{or, } V_2 = 30I_1 - 20I_2$$

∴

$$\therefore V_1 = 12I_1 - 10I_2$$

$$V_2 = 30I_1 - 20I_2$$

i.e., $\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 12 & 10 \\ 30 & 20 \end{bmatrix} \begin{bmatrix} I_1 \\ -I_2 \end{bmatrix}$


$-I_2$ indicates the current at the output opposite to the assumed direction of I_2 of the original two port Z parameter representation.

Comparing with the original Z-parameter representan,

$$Z_{11} = 12 \quad ; \quad Z_{12} = 10$$

$$Z_{21} = 30 \quad ; \quad Z_{22} = 20$$

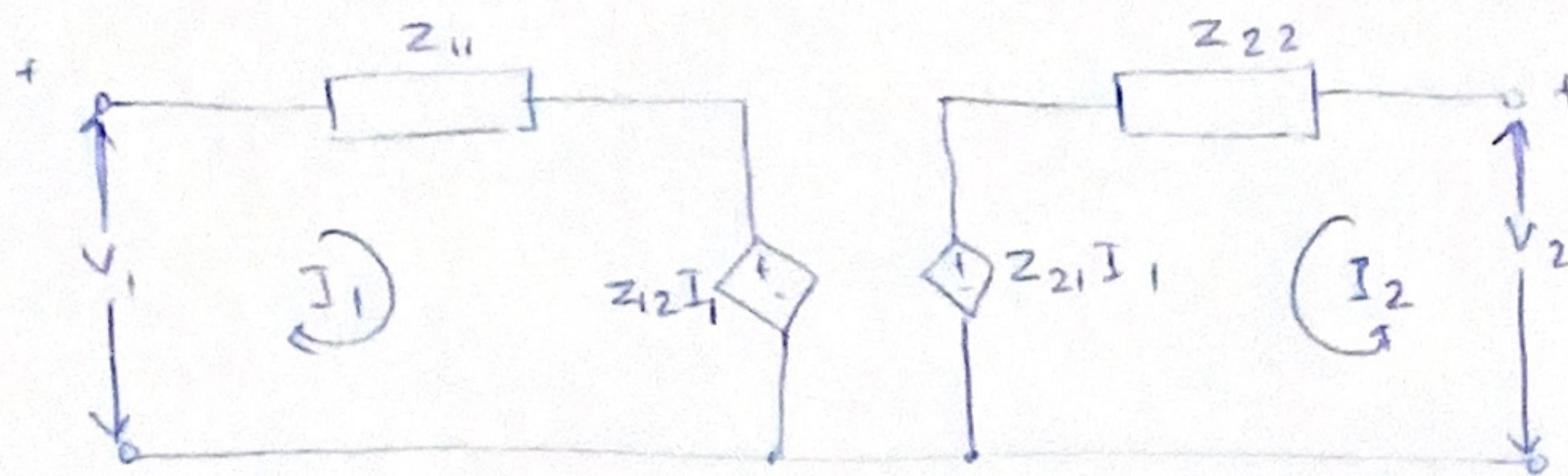\therefore Z parameter equivalent of the circuit,



Thus,

$$Y_{11} = \frac{Z_{22}}{\Delta Z}, \quad Y_{12} = -\frac{Z_{12}}{\Delta Z}$$

$$Y_{21} = -\frac{Z_{21}}{\Delta Z}, \quad Y_{22} = \frac{Z_{11}}{\Delta Z}$$

$$\text{Here, } \Delta Z = Z_{11} Z_{22} - Z_{12} Z_{21}$$

$$= 12 \times 20 - 10 \times 30$$

$$= 240 - 300$$

$$= -60$$

$$Y_{11} = \frac{20}{-60} = -\frac{1}{3}, \quad \text{Eq 20}$$

$$Y_{12} = \frac{10}{60} = \frac{1}{6}$$

$$Y_{21} = \frac{30}{60} = \frac{1}{2}$$


$$Y_{22} = -\frac{20}{60} = -\frac{1}{3}$$

2.

(B)

$$(i) x(t) = 1 + \cos(2\pi t) + \sin(3\pi t)$$
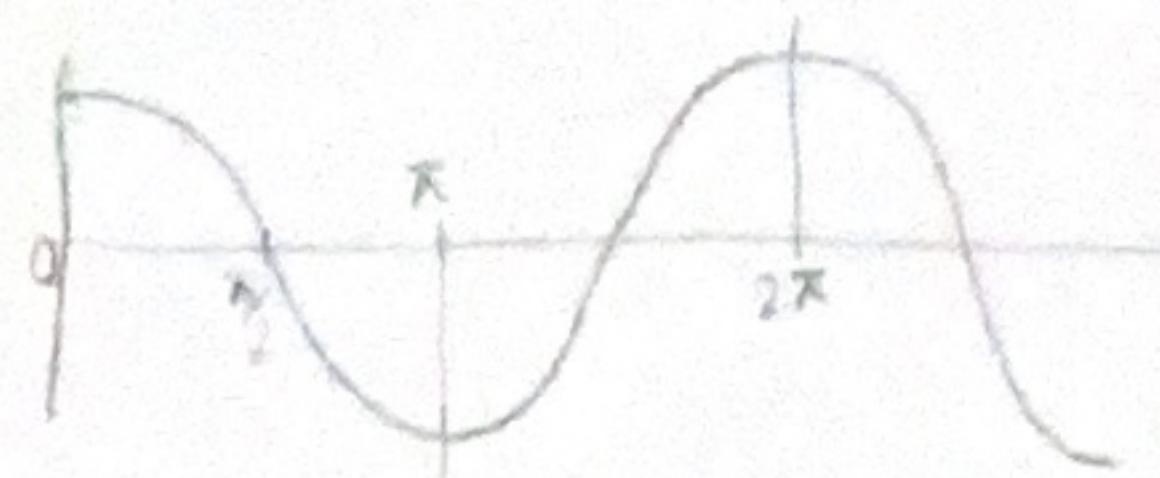
$$x(0) = 1 + \cos(0) + \sin(0) \\ = 1 + 1 + 0 = 2$$




$$x(1) = 1 + \cos 2\pi + \sin 3\pi \\ = 1 + 1 + 0 = 2$$



$$x(2) = 1 + \cos 4\pi + \sin 6\pi \\ = 1 + 1 + 0 = 2$$

$$x(-1) = 1 + \cos(-2\pi) + \sin(-3\pi) \\ = 1 + 1 - 0 = 2$$
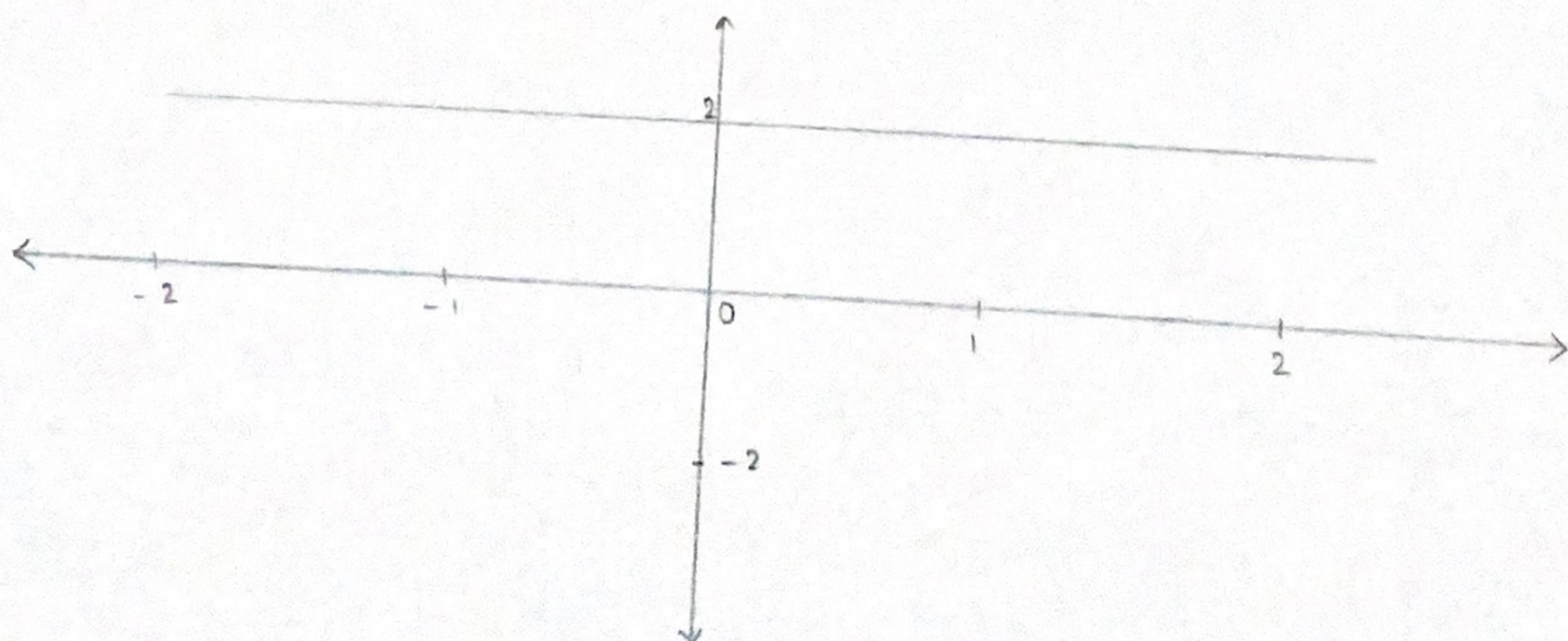
$$x(-2) = 1 + \cos(-4\pi) + \sin(-6\pi) \\ = 1 + 1 - 0 = 2$$



2.

B.

$$(ii) x(t) = e^{3t} u(-t)$$

$$x(0) = e^0 u(0) = u(0)$$

$$x(1) = e^3 u(-1)$$

$$= 20.08 u(-1)$$

$$x(2) = e^6 u(-2)$$

$$= 403.43 u(-2)$$

$$x(-1) = e^{-3} u(1)$$


$$= 0.05 u(1)$$

$$x(-2) = e^{-6} u(2)$$

$$= 2.48 \times 10^{-3} u(2)$$

Q.

(Q2)

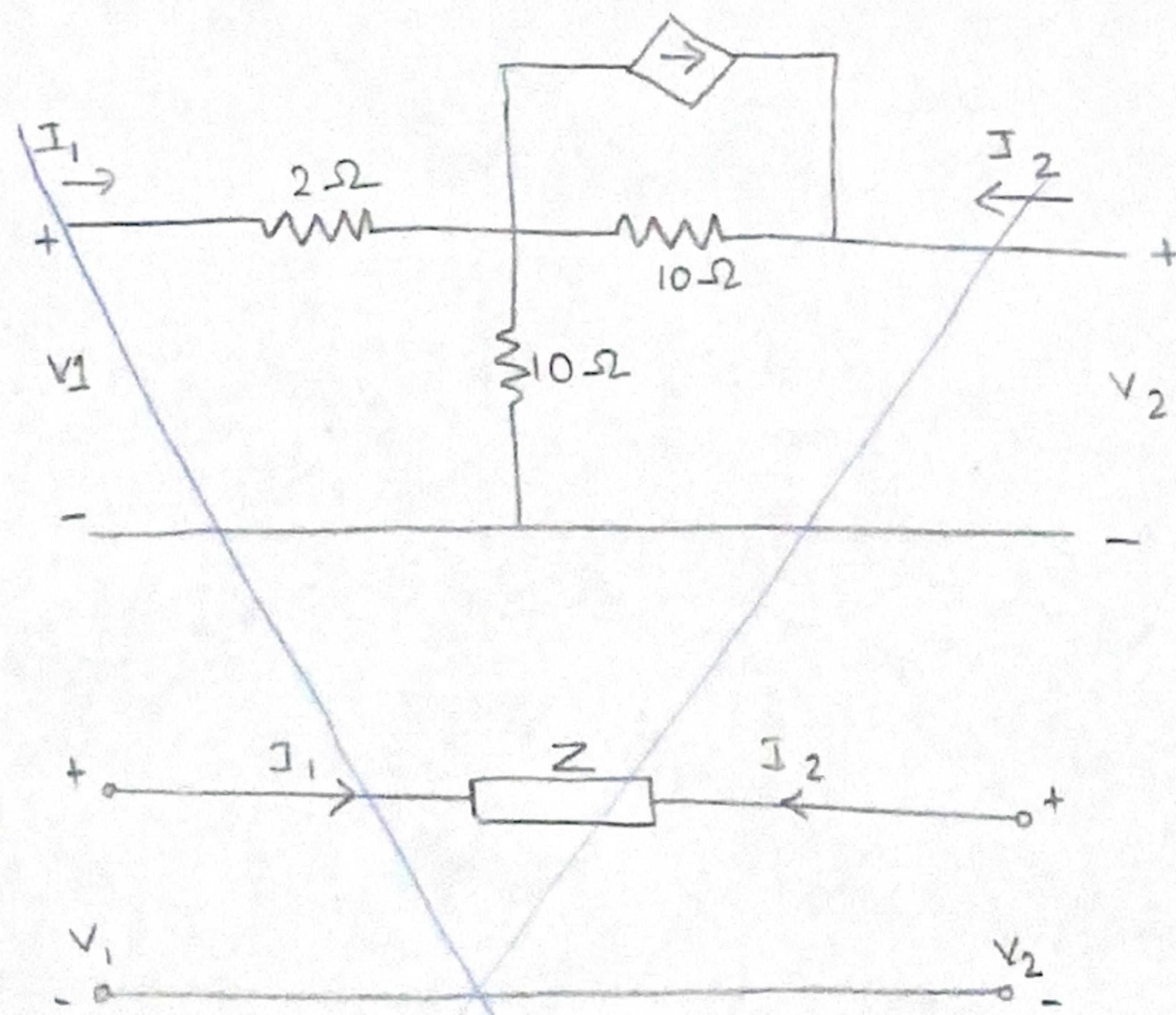

$$I_1 = \frac{V_1 - V_2}{Z}$$

$$I_1 = \frac{V_1}{Z} - \frac{V_2}{Z} \quad \text{--- (i)}$$

$$I_2 = -\frac{1}{Z} V_1 + \frac{1}{Z} V_2 \quad \text{--- (ii)}$$

$$|Y| = \begin{bmatrix} \frac{1}{2} & -\frac{1}{2} \\ -\frac{1}{2} & \frac{1}{2} \end{bmatrix}$$