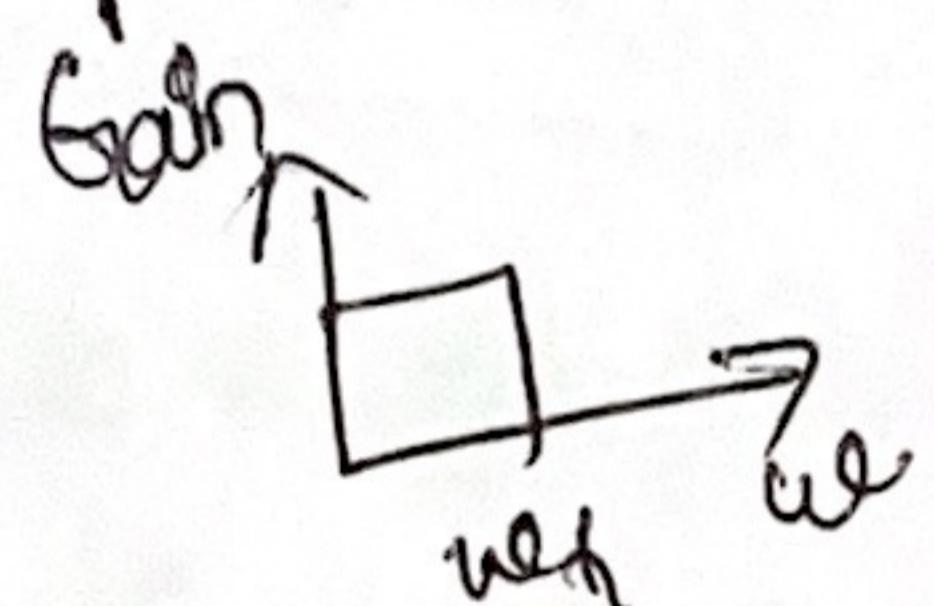


Filters: devices or circuits that pass only certain frequencies & block other frequencies.

Butterworth low pass filters

low pass filter - passes freq. passes less than certain freq.

Passband circuit
Stopband ω_{stop}



[With half power freq.]

at $\omega = \omega_B$, gain = $A/\sqrt{2}$.


$$\text{Differentiator } \frac{V_o}{V_i} = H(s) = -RCS$$

$$\omega_0 = \frac{1}{RC}$$



$|2C| = R$ - provides unity gain at ω_0 .

Integrator


$$H(s) = -\frac{1}{RC}$$

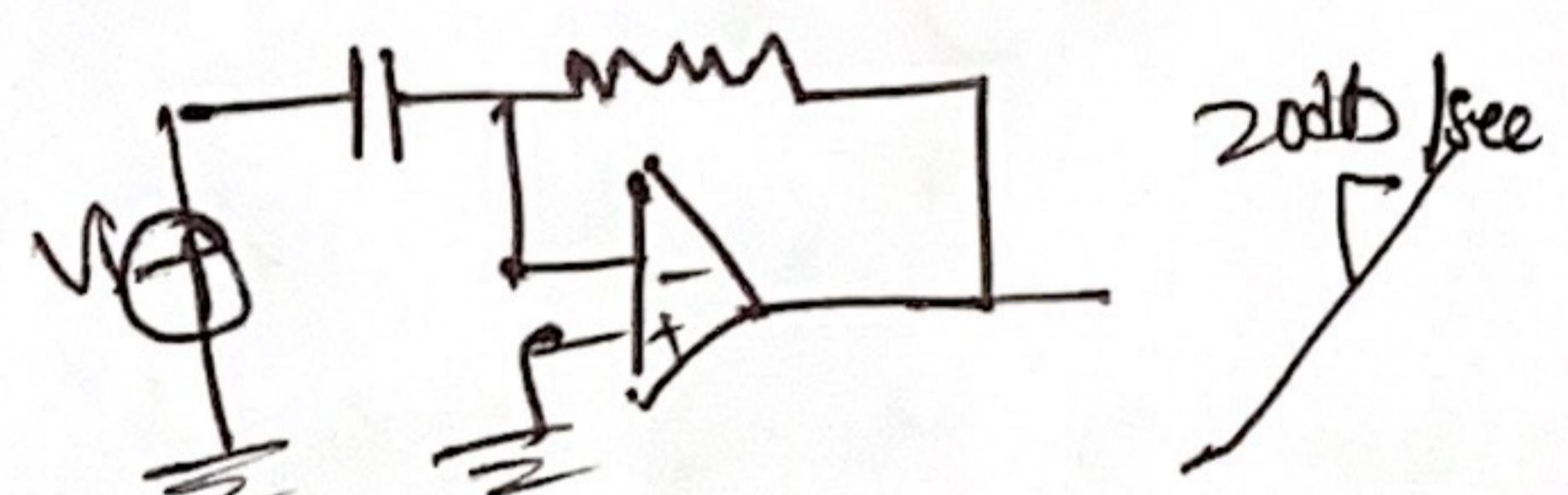

Noninverting and deboost integrator

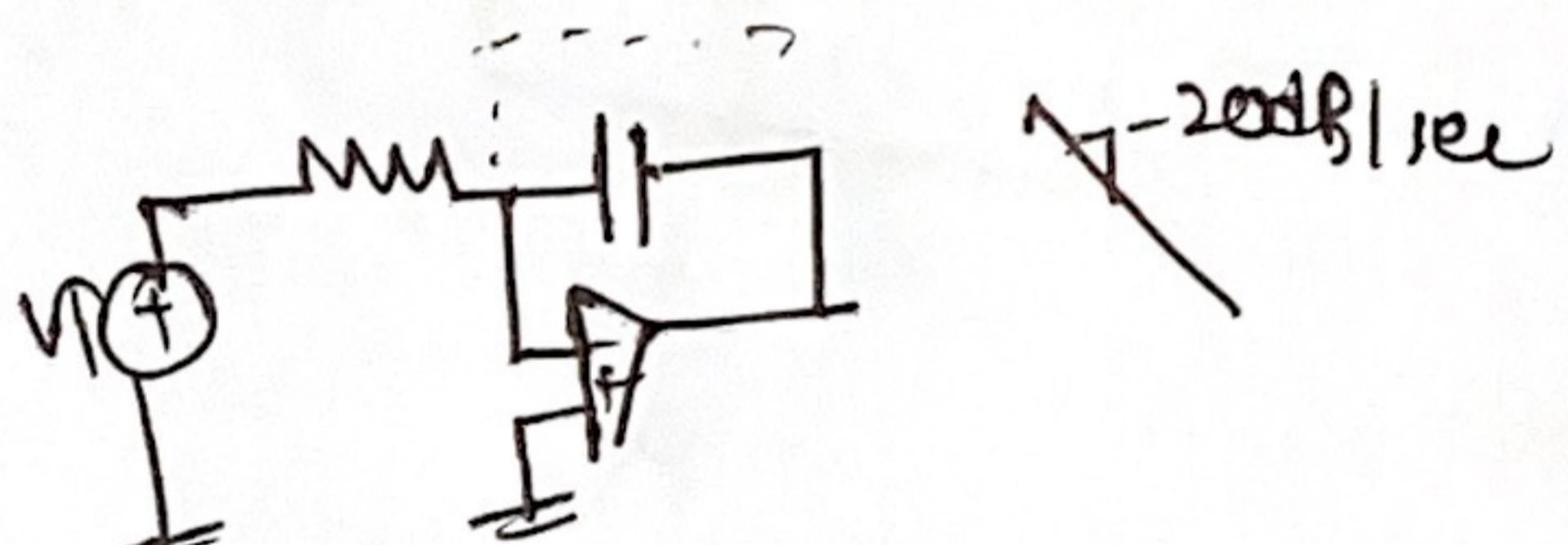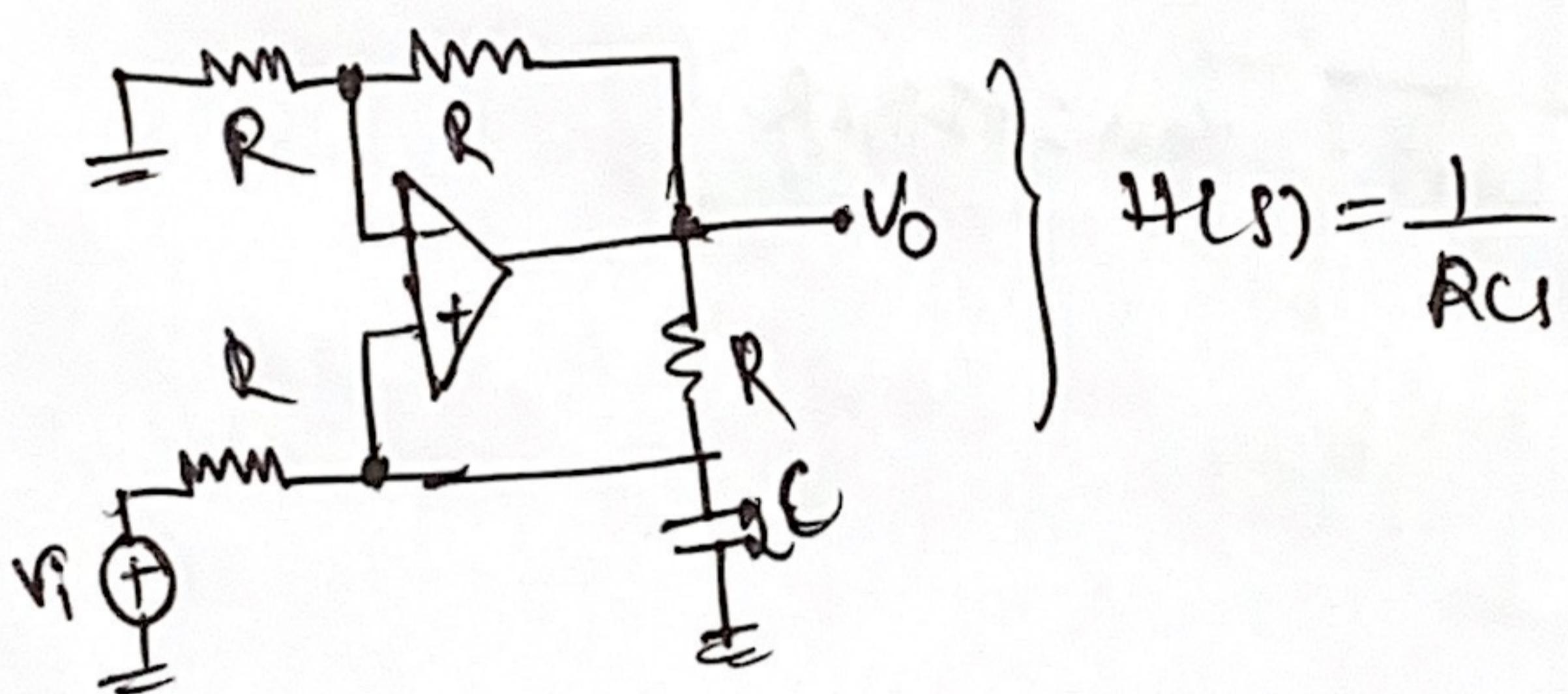

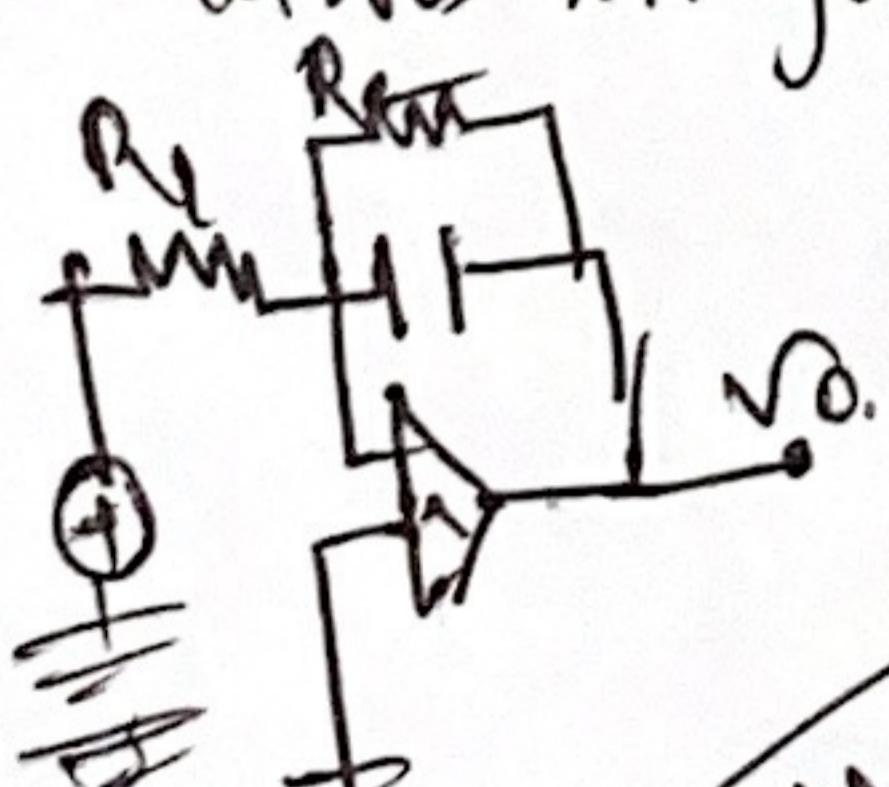
Low pass filter: placing a resistor parallel with feed back capacitor turns integrator into low pass F. with gain $H(s)$.



$$H(s) = -\frac{R_2}{R_1} \frac{1}{R_2 C s + 1}$$

$$H(j\omega) = H_0 \frac{1}{1 + j\omega/\omega_0}$$
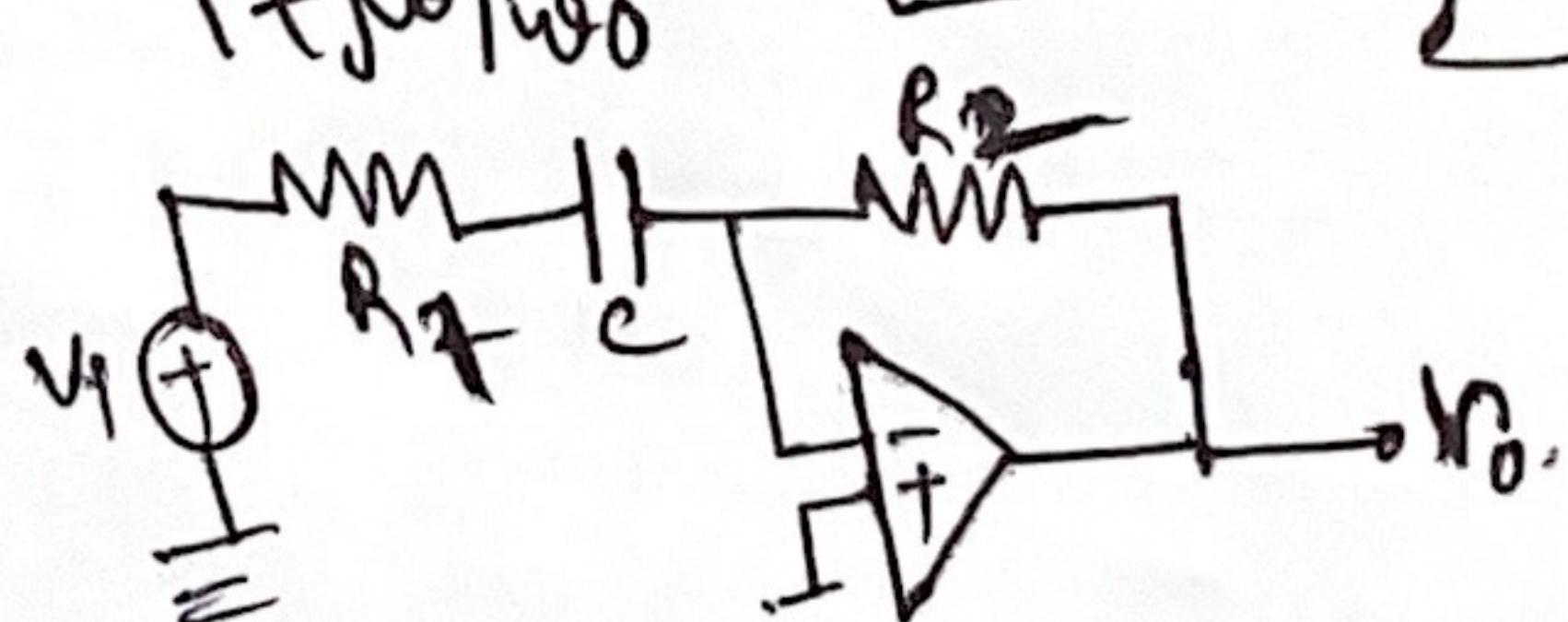
$$\omega_0 = \frac{1}{R_2 C}, \quad H_0 = -\frac{R_2}{R_1}$$



High pass filter: placing a capacitor series with input resistor turns differentiator into HPF with gain,


$$H(s) = -\frac{R_2}{R_1} \frac{R_1 C}{R_1 C + s}$$

$$H(j\omega) = H_0 \frac{j\omega/\omega_0}{1 + j\omega/\omega_0}$$

$$H_0 = -\frac{R_2}{R_1}, \quad \omega_0 = \frac{1}{R_1 C}$$

wide band band pass filters. combine both above circuits to bandpass

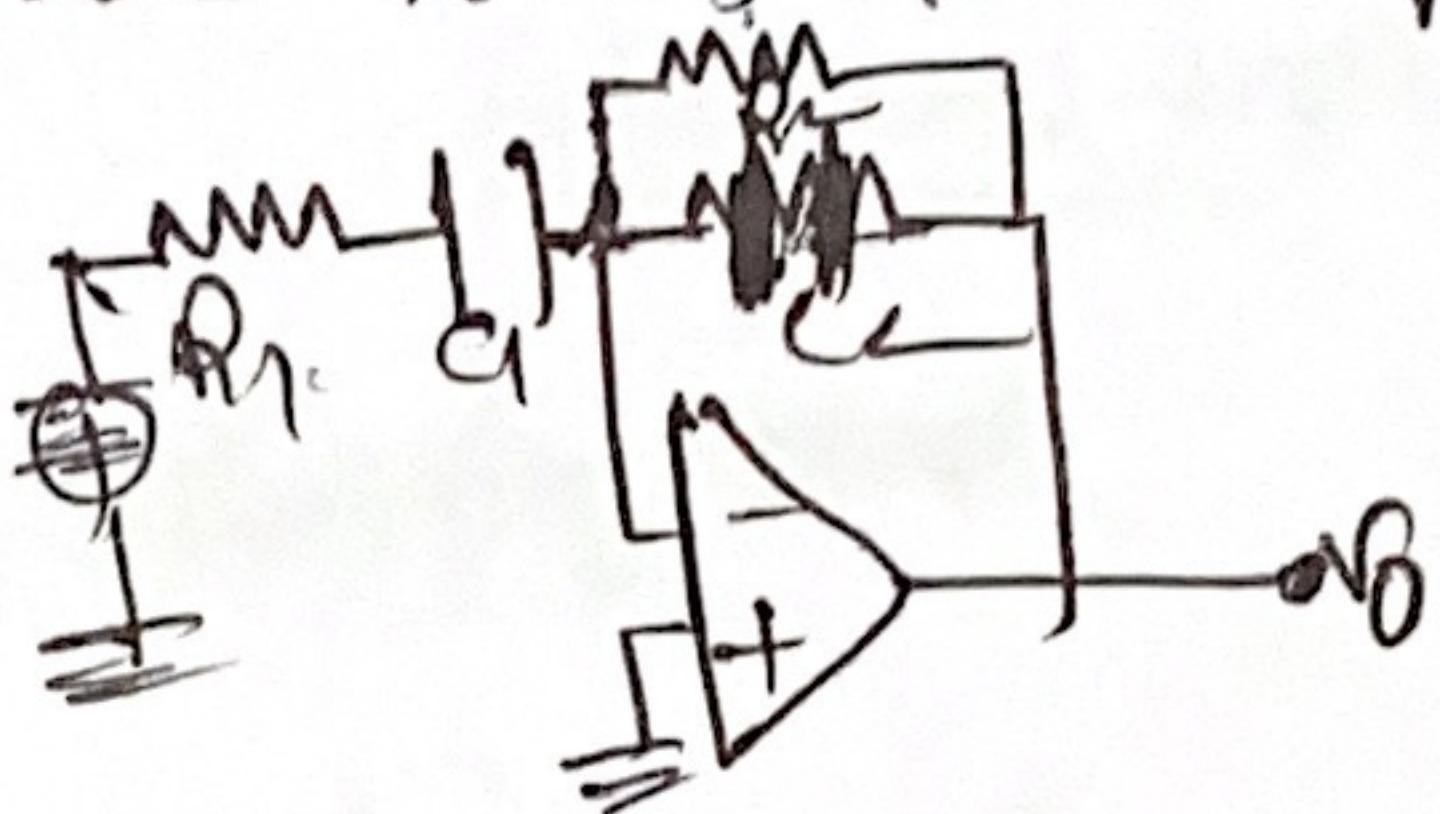
$$\text{response } H(s) = \frac{R_2}{R_1} \frac{R_1 C_B}{s_1(s+1)} \cdot \frac{1}{R_2(s+1)}$$



$$H(V_{o0}) = H_0 \frac{\omega_0^2 \omega_0}{(1 + \omega_0/\omega_L)(1 + \omega_0/\omega_H)}$$

$H_0 = \text{mid frequency gain}$.
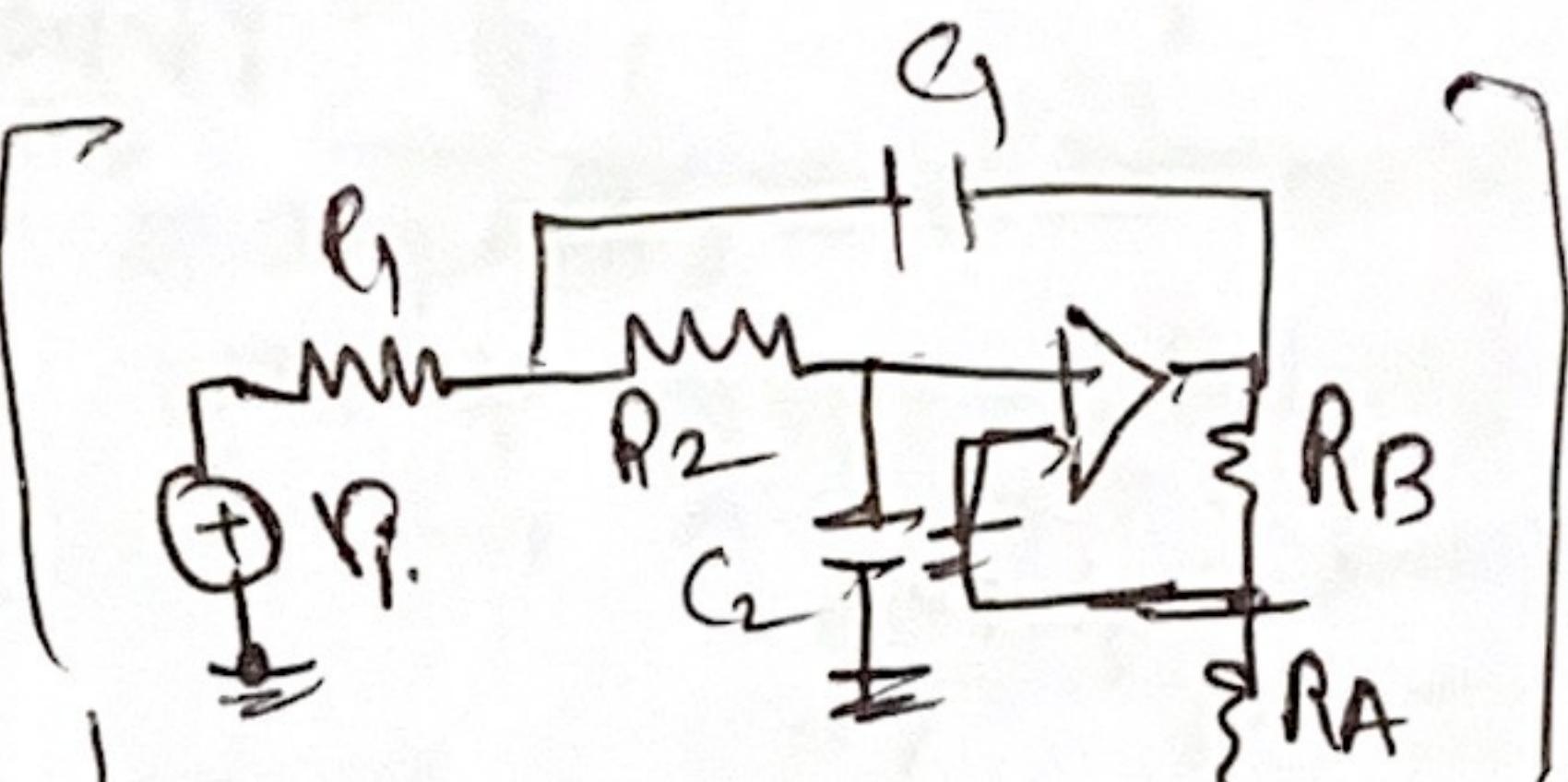
$$H_0 = \frac{R_2}{R_1}, \quad \omega_L = \frac{1}{R_1 C_1}, \quad \omega_H = \frac{1}{R_2 C_2}$$



Lowpass RCL filters:

$$K = 1 + \frac{R_B}{R_A}, \quad H(s) = \frac{1}{R_1 C_1 R_2 C_2 s^2 + ((1-K) R_1 C_1 + R_2 C_2 + R_1 C_2) s + 1}$$

$$(s = j\omega), \quad \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}, \quad Q = \frac{1}{(1-K)\sqrt{R_1 C_1 R_2 C_2} + \sqrt{R_1 C_1 R_2 C_2} + \sqrt{R_2 C_2 R_1 C_1}}$$


If $R_1 = R_2 = R$, $C_1 = C_2 = C$

$$Q = \frac{1}{3-K}, \quad \omega_0 = \frac{1}{RC}, \quad R_2 C_2 (K-1) R_A, \quad K = 3 - 1/Q.$$

High pass RCL filter

$Q = \text{same LPF}$
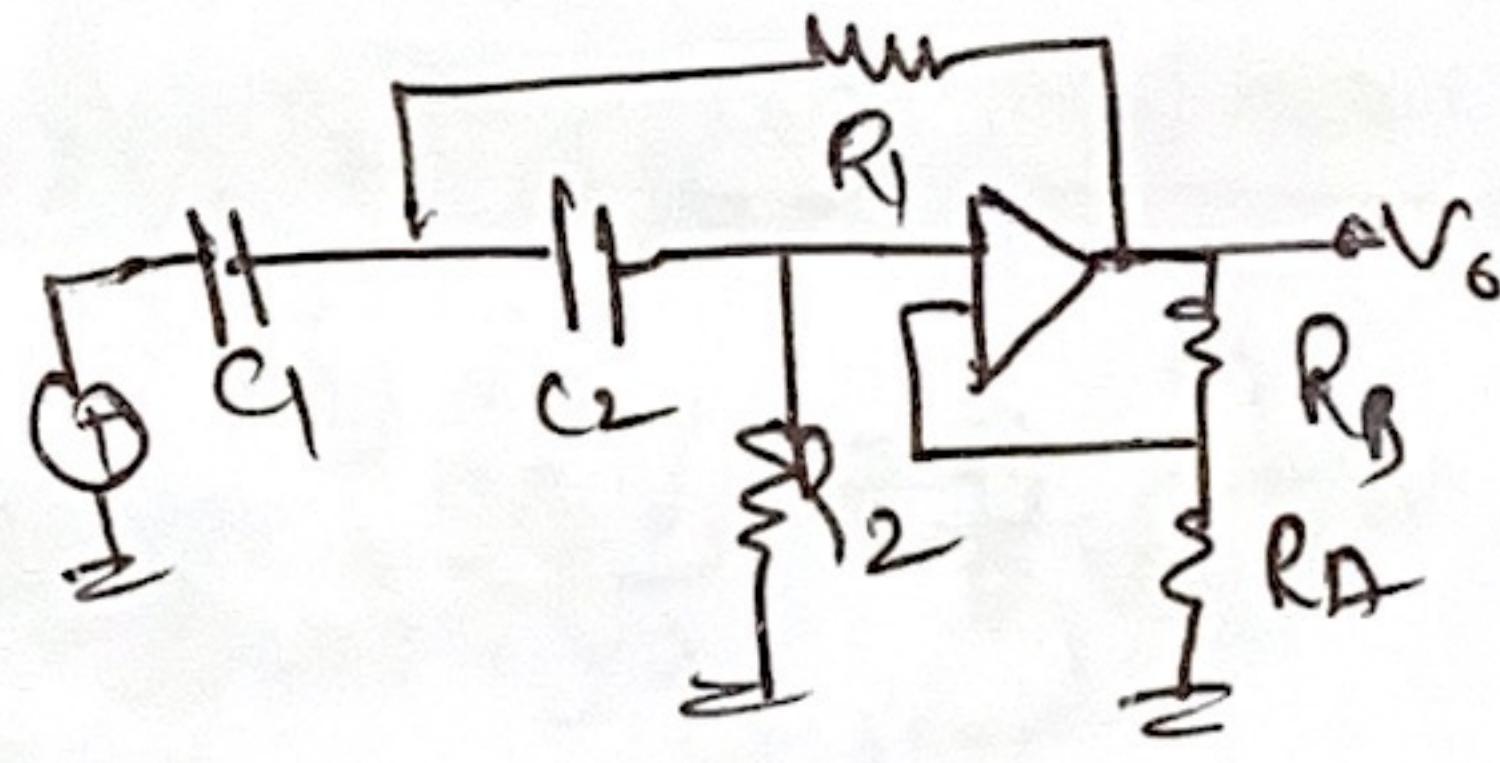
$$H_{HP} = K, \quad H(s) = \frac{H_{HP}}{H_{LP} + H_{LP}}$$



unbiased state of the circuit

2nd order low pass filter

$$\text{Gain}(V_o/V_i) = 1 + \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega C_1 R_1}$$

$$V_{in} = V_o$$

$$f_c = \frac{1}{2\pi R_1 C_1}$$

RC voltage divider

$$f_c^2 = \frac{1}{Q^2 R_1^2 C_1^2}$$

eg. voltage across

active high pass

$$f_o = \frac{1}{2\pi R C}$$

2nd order high pass

$$\text{Gain (AV)} = 1 + \frac{R_2}{R_1}$$

$$\frac{V_o}{V_i} = \frac{D_V}{\sqrt{1 + (f/f_c)^2}}$$

$$\text{Gain (B)} = 20 \log \frac{V_o}{V_i}$$

active band pass (cascading connect)

voltage gain high pass

$$\frac{V_o}{V_i} = A_{\text{high}} \times \left(\frac{f/f_c}{1 + (f/f_c)^2} \right)$$

voltage gain for low pass

$$\frac{V_o}{V_i} = A_{\text{low}} / \sqrt{1 + (f/f_c)^2}$$


$$A_{\text{low}} = A_{\text{max}} \times A_{\text{norm}}^2$$

$Q < 0$, wide band pass } Q = quality factor

$Q > 10$, narrow band pass

3122

Multipole Feedback Filters.

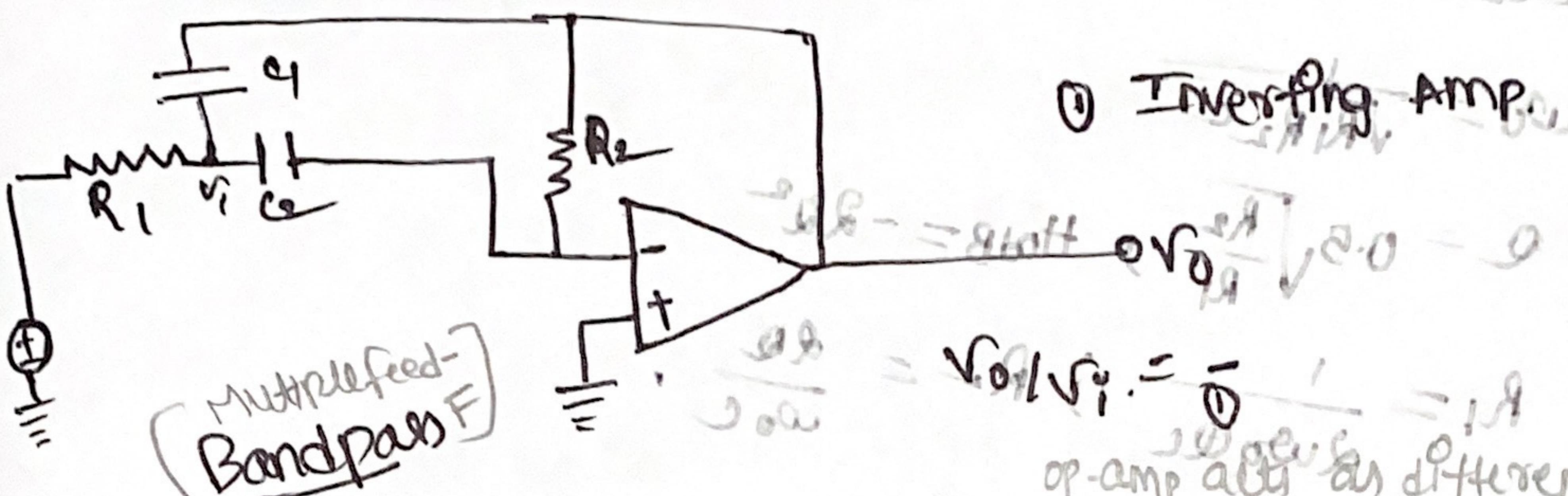

① Inverting Amp.

$$\frac{V_0}{V_i} = -\frac{R_2}{C_2}$$

$$\frac{V_0}{V_i} = \frac{R_2}{C_2} = 10$$

op-amp acts as differentiator

$$W\pi f v_i \text{ so } V_0 = -8R_2(2v_i)$$

$$V_0 = -R_2 C_2 s v_i$$

$$V_i = \frac{V_0}{SR_2 C_2}$$

Node equation V_1

$$\frac{V_0 - V_1}{R_1 + R_2 C_2} = \frac{V_1 - V_0}{S R_2 C_2}$$

$$\frac{V_1 - V_0}{R_1 R_2 C_2} = S C_2 V_1 = S C_2 (V_0 - V_1)$$

$$\frac{V_0}{R_1} = S C_2 (V_1 - V_0) + S C_2 V_1 + V_1 / R_1$$

$$\frac{V_1}{R_1} = -V_0 \left[S_1 + \frac{S_2 V_1}{V_0} + \frac{S_3 V_1}{V_0} + \frac{V_1}{R_1 V_0} \right]$$

$$= -V_0 [B_0 + B_1 C_2 R_1 + B_2 C_2 R_2 + B_3 C_2 R_1 R_2]$$

$$\frac{V_1}{R_1} = -V_0 \left[1 + \frac{S R_1 C_2 R_2 (2 + S R_1 C_2)}{S C_2 R_1 R_2} \right]$$

$$\frac{V_0}{V_1} = \frac{-S C_2 R_1}{B_2}$$

$$H(j\omega) = -\frac{j\omega C R_2}{1 + j\omega R_1 (1 + (2 + \omega^2 R_1 R_2 C_1 C_2))}$$

Take

$$\omega R_1 R_2 C_1 C_2 = \frac{\omega_0^2}{\omega_0}$$

$$\Rightarrow \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

$$j\omega R_1 C_1 + C_2 = \left(\frac{j\omega}{\omega_0}\right) 1 \Omega \Rightarrow Q = \frac{\sqrt{R_2 / R_1}}{\sqrt{C_1 / C_2} + \sqrt{C_2 / C_1}}$$

$$\Rightarrow j\omega C R_2 = H_{dB} \left(\frac{j\omega}{\omega_0}\right) 1 \Omega$$

$$H_{dB} = \frac{-R_2 / R_1}{1 + C_1 / C_2}$$

slow

band g
subtraction


slow

$$c_1 < c_2 = c \Rightarrow$$

$$w_0 = \frac{1}{\sqrt{R_1 R_2}} e^{i\theta}$$

$$d = 0.5 \sqrt{\frac{R_2}{R_1}}, \quad \text{HodB} = -20^\circ$$
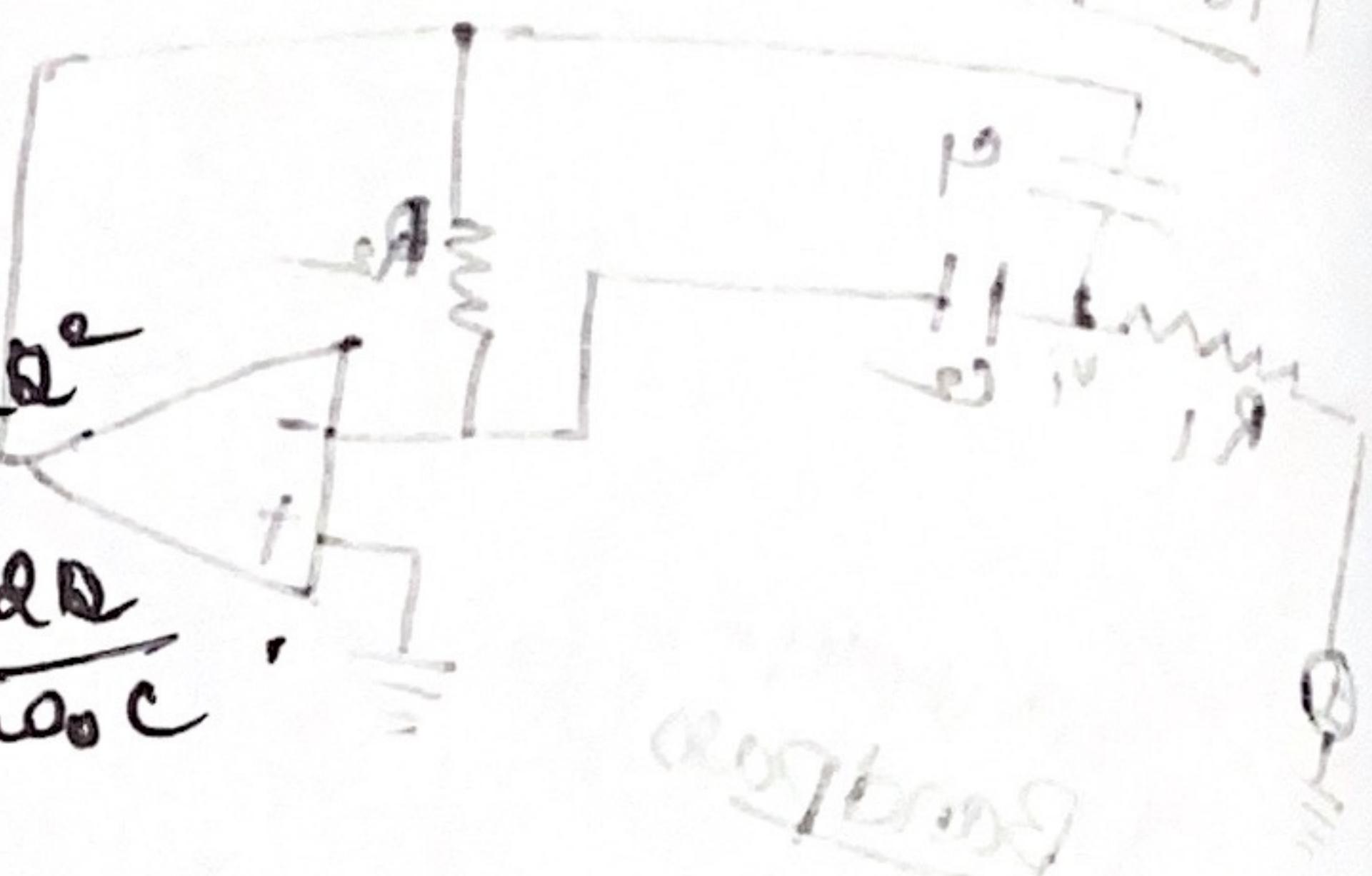
$$R_1 = \frac{1}{2\pi\sigma_0 Qc} ; R_2 = \frac{\alpha D}{\sigma_0 c}$$



Ex: Design a multiple feedback filter with

$$w_0 = \frac{1}{\sqrt{g_{tt}}}$$

$$\omega = \frac{1}{\sqrt{L}}$$

$$R_1 = \frac{1}{2\pi\mu_0\sigma}$$

$$= \frac{4\pi \times 10^3}{244 + 10 \times 79} \underline{\underline{100}}$$

$$= \pi \cdot 100^2 \cdot 0.12 = \pi \cdot 12000 = 37.7 \times 10^3$$

$$\text{Current} = \frac{V}{R} = \frac{12}{0.3} = 40 \text{ A}$$

$$\left[\frac{V_A}{\text{ov}_A} + \frac{V_B}{\text{ov}_B} + \frac{V_C}{\text{ov}_C} + \phi_{12} \right] \text{ov} = \frac{i_V}{\text{ov}}$$

~~Final project page~~

1900. 1. 20. - 1900. 1. 21.

Mr. P. C. G. H. S. and Dr. G. G. Day - 2
182 + 51 = 187 + 187

$H_0 < \alpha Q^2$, then

Paxill House

R45 (20°11'00.3) - 1

IV

show = cauch
superior + (s) + Unit / .

~~September~~

$$\overrightarrow{AB} = \omega C$$

$$\text{Proof: } \text{Let } \frac{w_1}{w_2} = \frac{a+bi}{c+di} \text{ where } a, b, c, d \in \mathbb{R} \text{ and } c^2 + d^2 \neq 0.$$

$$01\left(\frac{w}{\omega}\right) \text{ about } = \text{ Newt}$$

JAN 29 -
- 3119 ft = 8160 ft

16103128

Filter approximations:


- (i) Intro to different type of filters to approach
 (ii) Butterworth Response.

(a) Filter design Approximation


(b) Design of first order BW filter

(c) Design of higher order BW Filter ex.

[1] Butterworth Filter

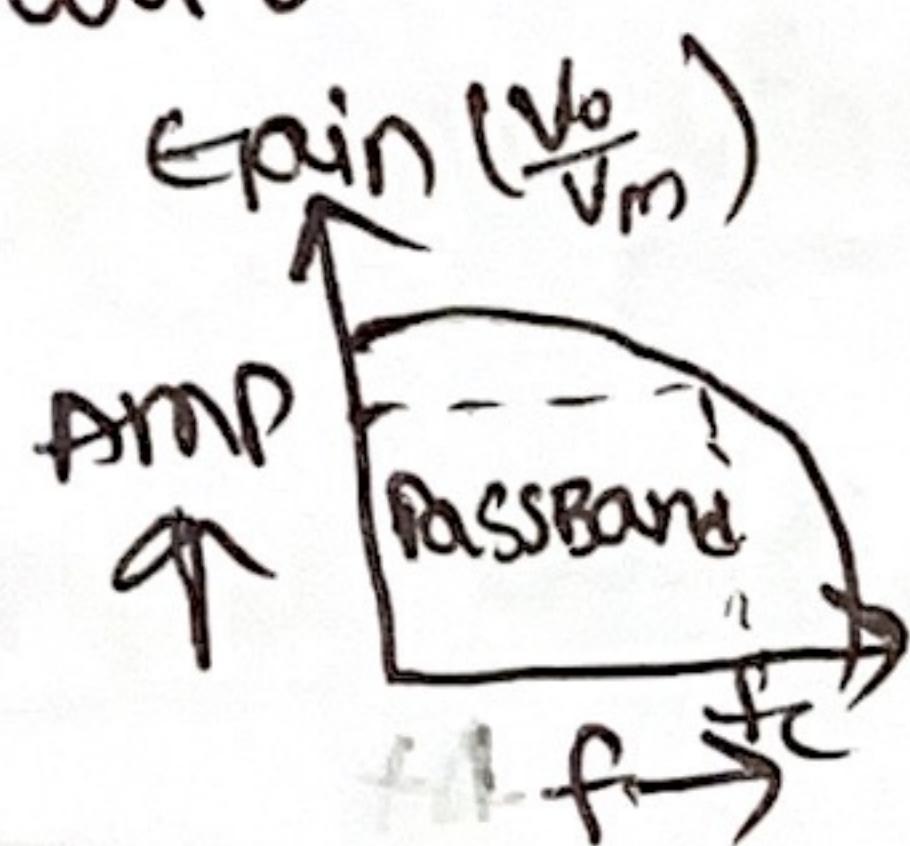

[2] Cheby Filter,

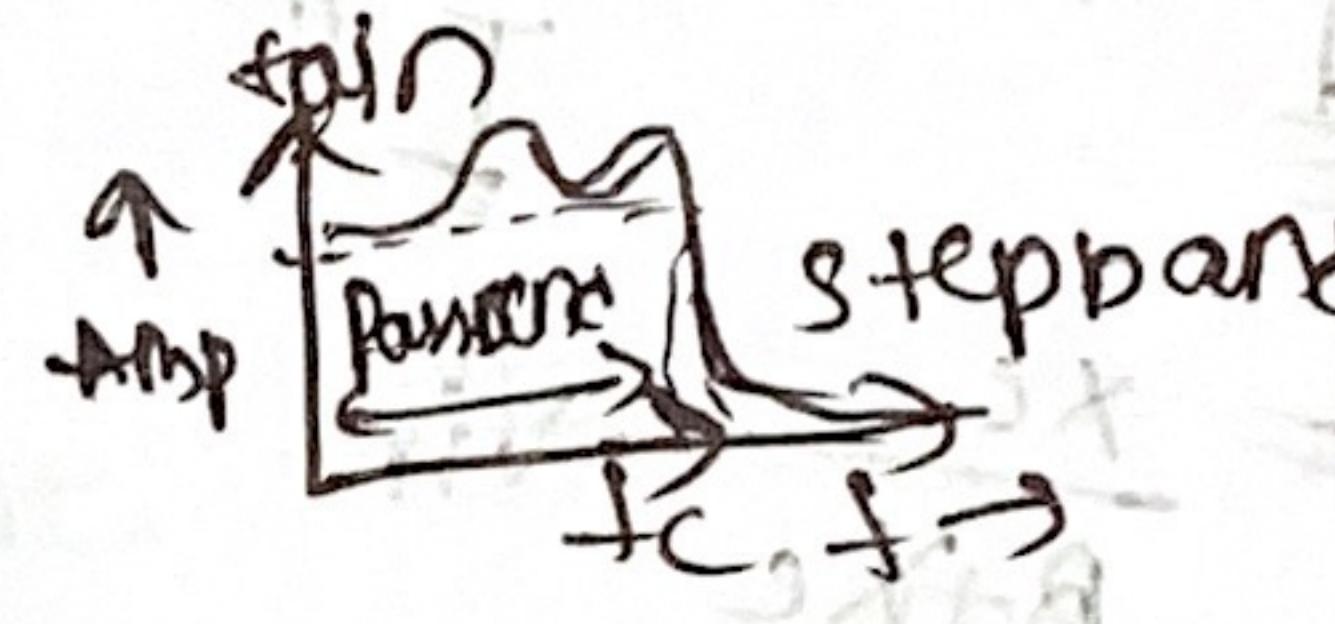


① No. of ripples = $n/2$

② Ripple pass band

③ Transition very fast

- ① Maximally flat approximation
- ② Flat band + fast response
- ③ Roll off rate $\rightarrow 20n \text{ dB/decade}$
- ④ Also, no ripple in stop band


[3] Empirical Filter

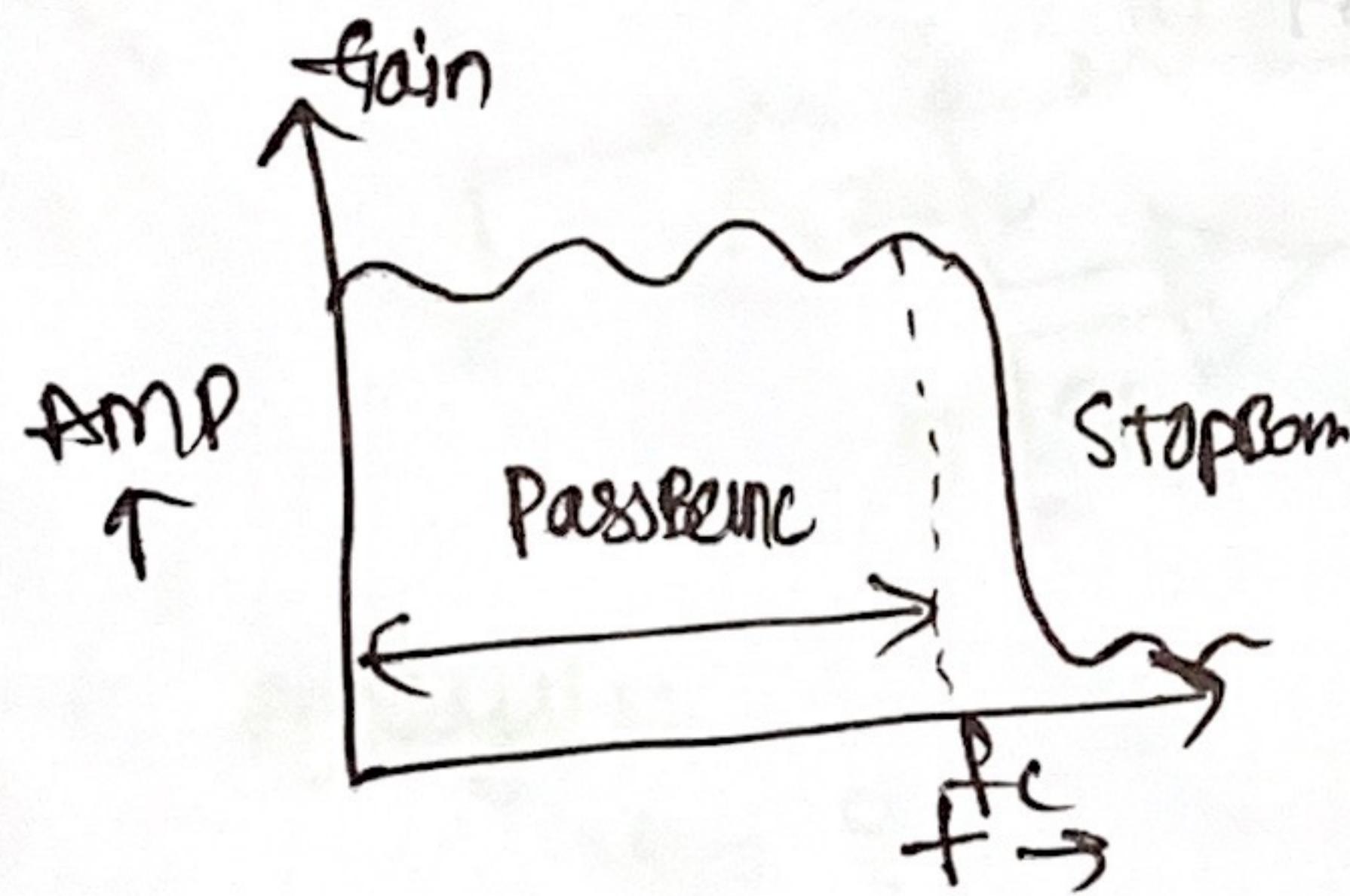

① Fastest transition

② Ripple in passband & stopband

[4] Bessel Filter

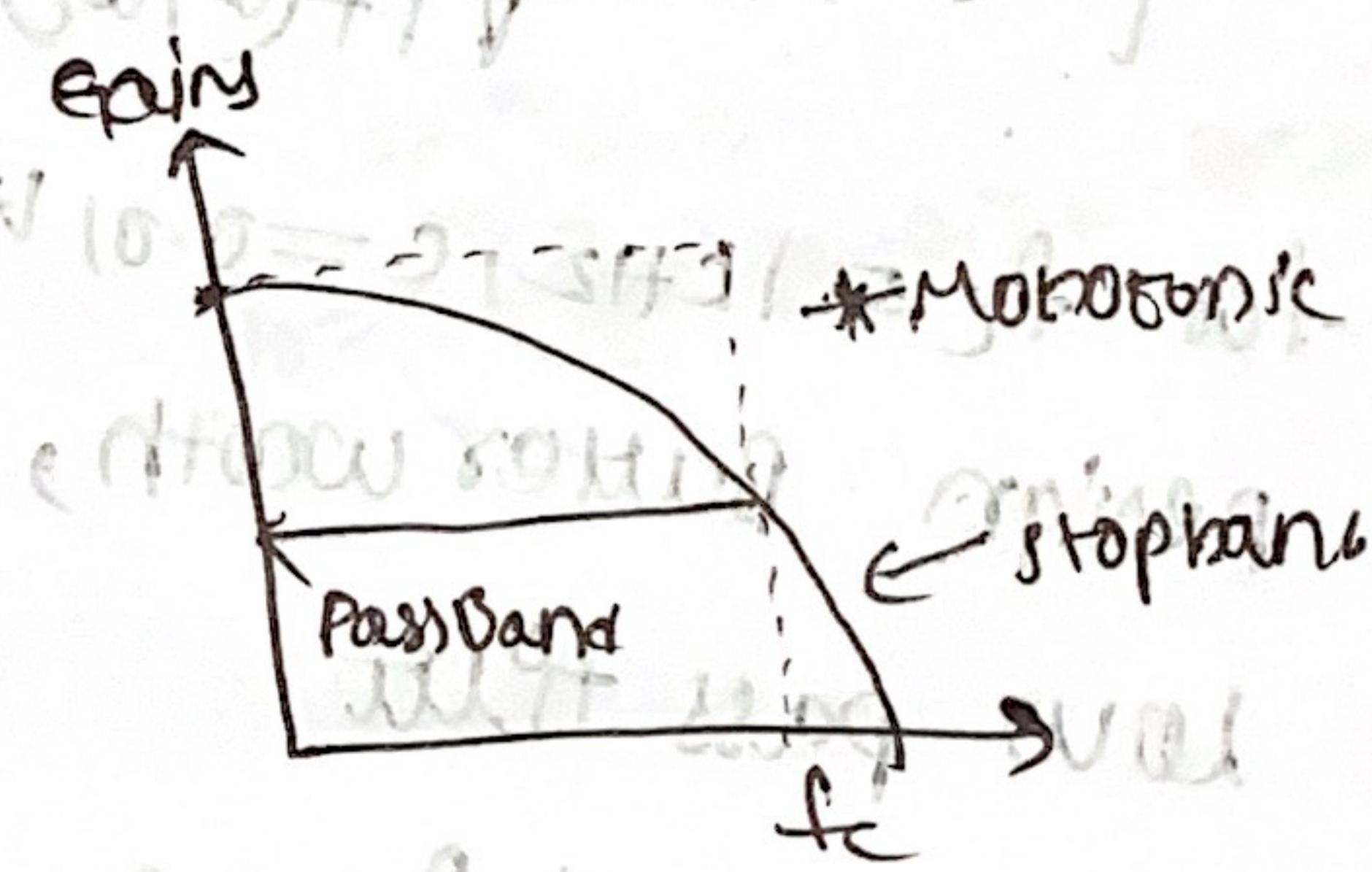

① No ripple in pass band

Stopband


② Phase + frequency variation linear

③ Constant delay [slow transition].

Higher order Butterworth filter design:

The gain of the Butterworth approximation
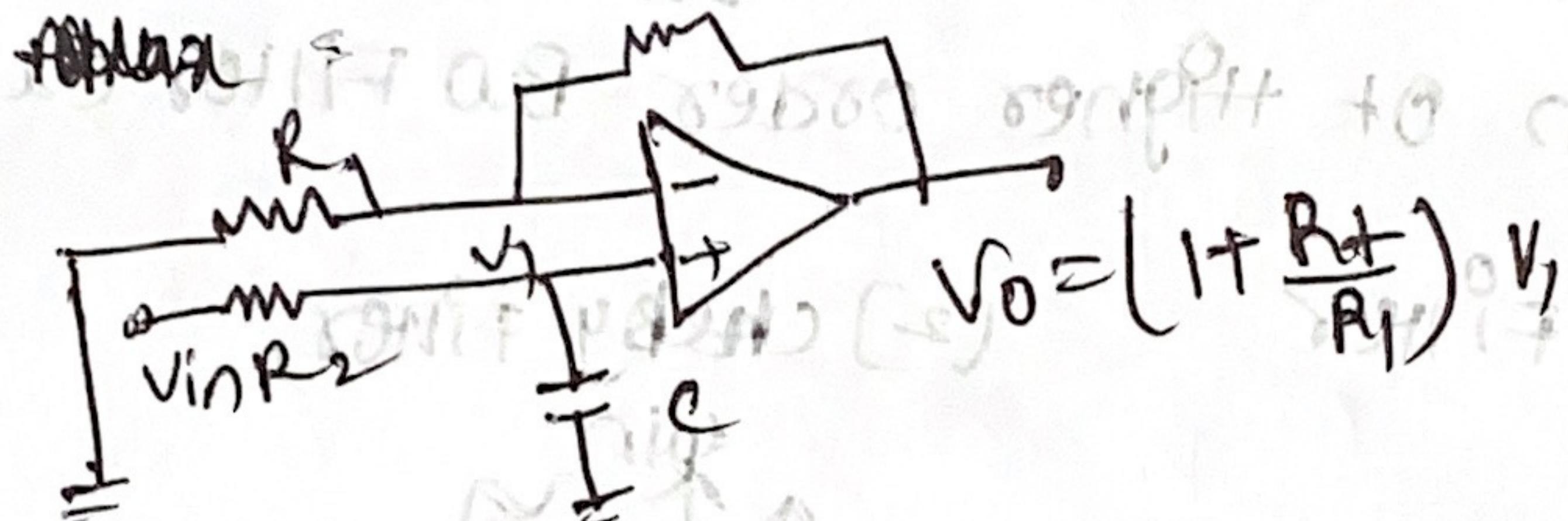
$$\rightarrow H(j\omega) = \frac{1}{\sqrt{1 + c^2(\omega/\omega_c)^2}}$$



$$V_1 = \frac{X_C}{A + j\omega C} \cdot V_{in}$$

$$\rightarrow \boxed{\frac{V_o}{V_{in}} = \frac{A}{1 + (\omega/\omega_c)^2}} \text{ or } \boxed{\frac{V_o}{V_{in}} = \frac{A}{\sqrt{1 + (\omega/\omega_c)^2}}}$$

$$A_f = 1 + R_2/R_1 \quad \omega_c = 1/R_C$$

As per Butterworth approx

$$|H(j\omega)| = \frac{1}{\sqrt{1 + (\omega/\omega_c)^2}} \text{ for 2nd order, } N=2$$

$$\text{for } f_c = 1 \text{ kHz, } c = 0.014 + 1/R_A A_f^2$$

design Butterworth,

low pass filter

$$A_f = \frac{1 + R_2}{R_1} = Q.$$

General low pass equation consider function.

$$\rightarrow H_{LP}(j\omega) = \frac{1}{1 - (\omega/\omega_c)^2 + (Q\omega/\omega_c)^2}$$

2nd order Butterworth LPF with $f_c = 1 \text{ kHz}$

$$\frac{V_o}{V_i} = \frac{1}{(S\omega_c)^2 + S\omega_c(S - k) + 1} \quad k = \text{gain}$$

$$\rightarrow H(s) = \frac{1}{1 + R_1 R_2 s^2 + [1 - k] R_1 s + Q_1 (1 + R_2 s)] s}$$

4th order Butterworth LPF with $f_C = 1\text{kHz}$,

$$\frac{V_o}{V_i} = \frac{1}{(sCR)^2 + sCR(3-K) + 1}$$

$$K = K_1 K_2 = 2.575 \quad (\text{resulting gain})$$

$$K_1 = 2.235$$

$$K_2 = 1.152$$


17/03/23

OP-Amp Limitations:

① Input bias & offset current:

I_B = Bias current


I_{OS} = Offset current

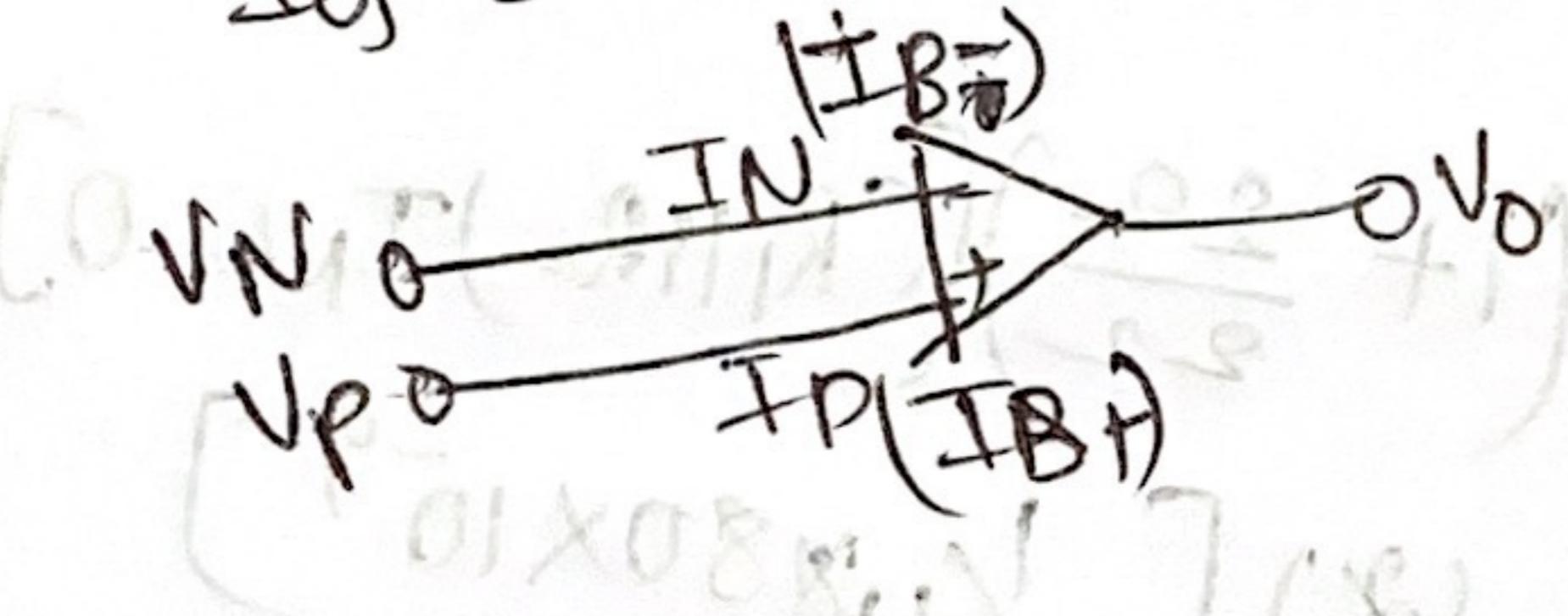

$$I_B = \frac{I_P + I_S}{2}$$

$$I_{OS} = I_P - I_N$$

EFFECT OF I_{OS} & I_B :

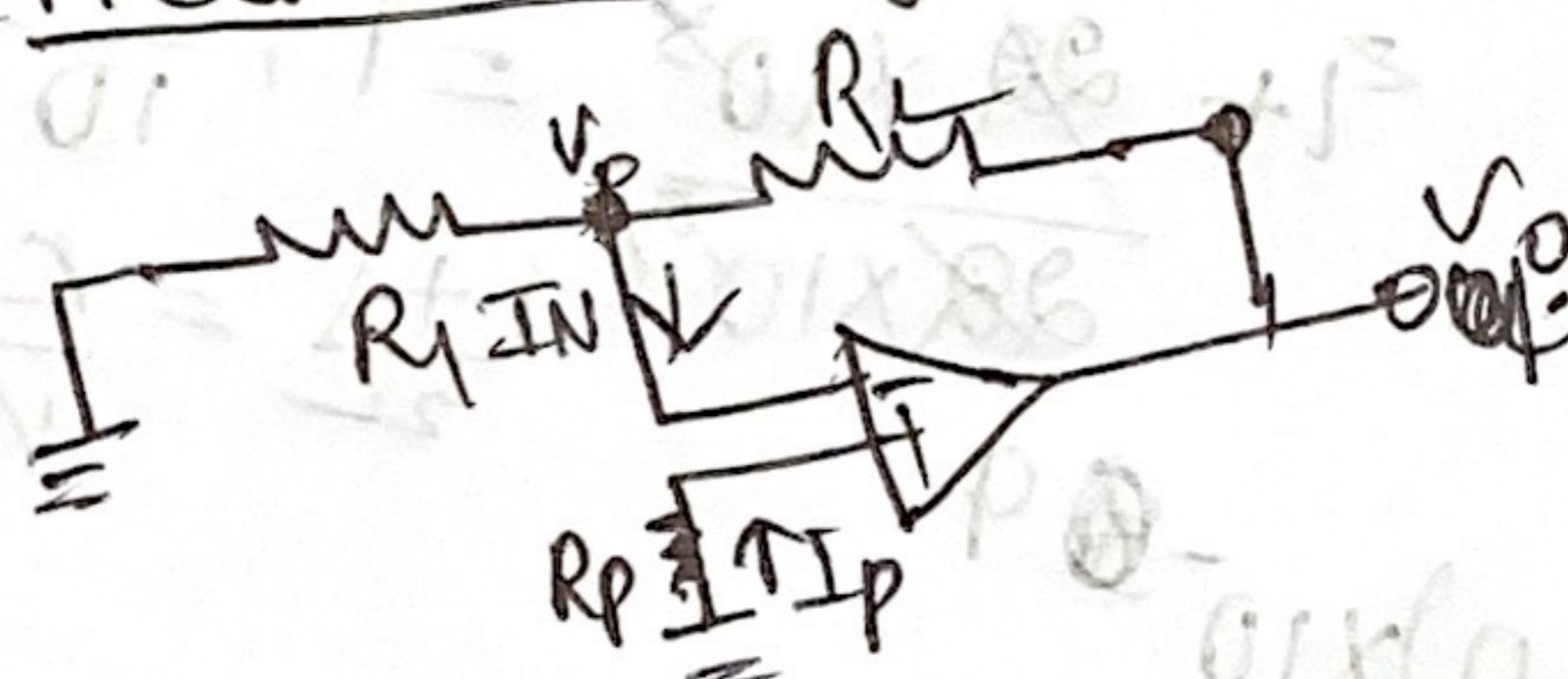

$$V_O = \left(1 + \frac{R_2}{R_1}\right) \left[(R_1 || R_2) I_N - R_P I_P \right]$$

Analysis:

$$V_O = ?$$

Apply superposition theorem.

$$V_P = -R_P I_P$$

$$V_O = \left(1 + \frac{R_2}{R_1}\right) N_P I_N R_L$$

$$V_O = -\left(1 + \frac{R_2}{R_1}\right) I_P R_P + I_N R_L$$

$$V_O = \left(1 + \frac{R_2}{R_1}\right) \left[(R_1 || R_2) I_N - R_P I_P \right] = E_o$$

PC noise gain,

Try to minimize this value else error will be more.

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) \left[(R_1 || R_2) - R_p \right] I_B - \left[(R_1 || R_2) + R_p \right] \frac{I_O}{2}$$

$R_p = R_1 || R_2 (\infty)$ (If we put all dummy resistance)

$$E_0 = \left(1 + \frac{R_2}{R_1}\right) (R_p \cdot I_O)$$

- (Q1) In the circuit shown in previous page, $R_1 = 22K\Omega$, $R_2 = 2.2M\Omega$, ~~let~~ let the opamp rating $I_B = 80nA$, $I_{OJ} = 20nA$:

(a) calculate E_0 for $R_p = 0$

(b) Repeat 'a' with $R_p = R_1 || R_2$

(c) Repeat 'B' with all resistances simultaneously reduced by the factor of 10:

(d) Repeat 'c' with opamp replaced with $I_{OJ} = 3nA$

$$(a) E_0 = \left(1 + \frac{R_2}{R_1}\right) (R_p \cdot I_O) = \left(1 + \frac{2.2}{22}\right) [(R_1 || R_2) I_B - 0]$$

$$= (2) [1 + 0.1] (2.2 \times 10^{-9})$$

$$= 1 + \frac{2.2 \times 10^3}{22 \times 10^2} = 1 + \frac{1}{10^2} \frac{10^2}{10^2}$$

$$= 1 + \frac{1}{10^2} = \frac{11}{10^2} = \frac{1}{10} \times 10^9$$

$$(b) E_0 = \left(1 + 1\right) (R_1 || R_2) (20) \times 10^{-9}$$

$$= 2 (2.2 \times 10^3) \times 10^{-3} + 4 (2.2 \times 10^3) \times 10^{-9}$$

$$= \frac{1+1}{10^2} \left(\frac{1}{11}\right) (20 \times 10^{-9}) = 0.000364$$

$$R_p = 2.2K$$

$$R = 0.22M\Omega$$

(c)

Op-Amp Limitations

- ① Super beta Input op-amps
- ② Fet Input op-amps.
- ③ Input bias current cancellation.

I_{OJ}

I_B

Input Offset Voltage:

$$V_0 = A(V_p - V_N)$$

$$V_p = V_N \Rightarrow V_0 = 0.$$

$$V_{O_s}, V_p \neq V_N \Rightarrow V_0 \neq 0.$$

$$V_0 = A(V_p + V_{O_s} - V_N) = 0.$$

$$V_N = V_p + V_{O_s}$$

$$V_0 = V_{O_s} \left(1 + \frac{R_2}{R_1} \right)$$

↳ Eq.

Power supply Rejection Ratio:

$$V_S + DV_S \Rightarrow V_0.$$

$$\frac{1}{PSRR} = \frac{|V_0|}{S \cdot V_S} \text{ MV/V}$$

Input offset error & compensation Techniques:

$$I_{O_s} \Rightarrow E_0 =$$

$$V_{O_s} \Rightarrow E_0 =$$

$$E_0 = \left(1 + \frac{R_2}{R_1} \right) (R_1 || R_2) I_{O_s}$$

$$E_0 = \left(1 + \frac{R_2}{R_1} \right) V_{O_s}$$

$$E_0 = \left(1 + \frac{R_2}{R_1} \right) [V_{O_s} - \underbrace{(R_1 || R_2) I_{O_s}}_{E_i}]$$


$$V_0 = A_f V_i + E_0$$

$$A_f = -R_2/R_1$$



$$A_f = 1 + R_2/R_1$$

① Internal offset null:

$$V_I = 0 \Rightarrow V_O = 0.$$

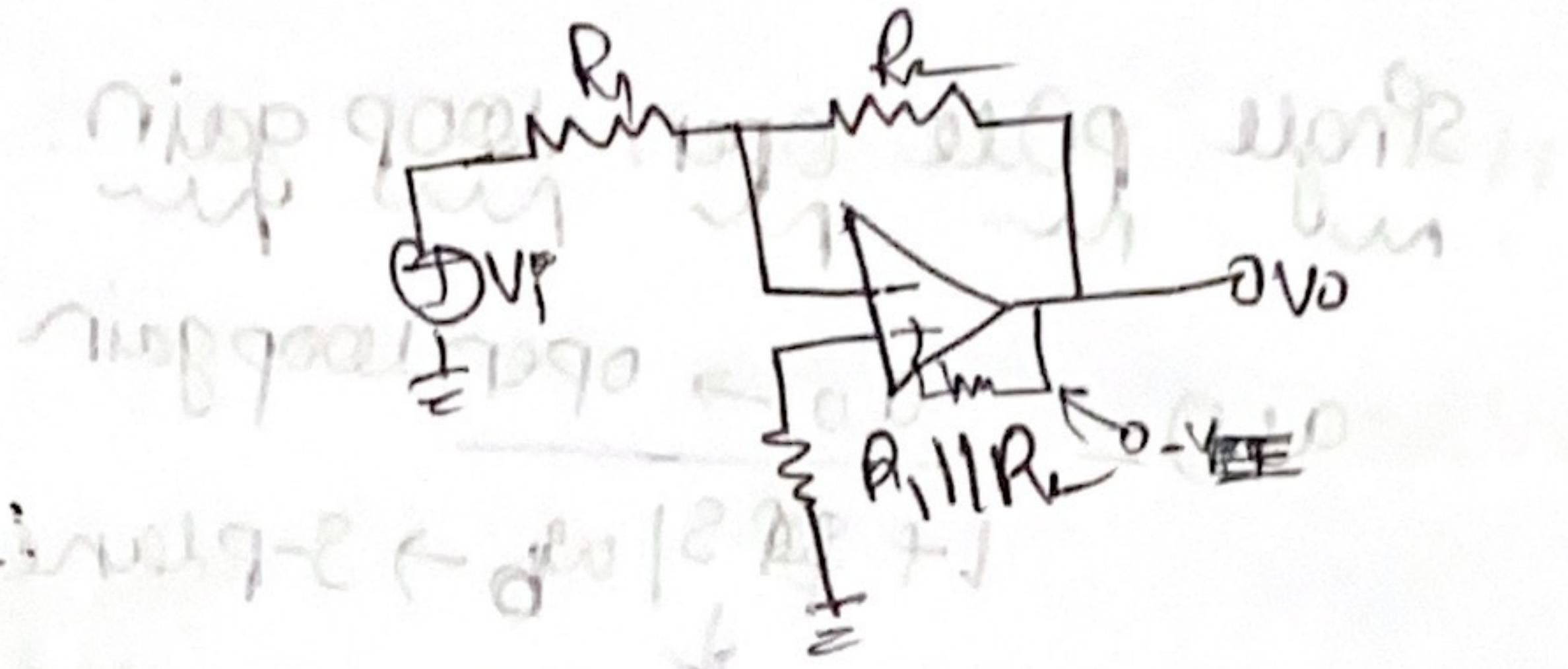


② External offset null:

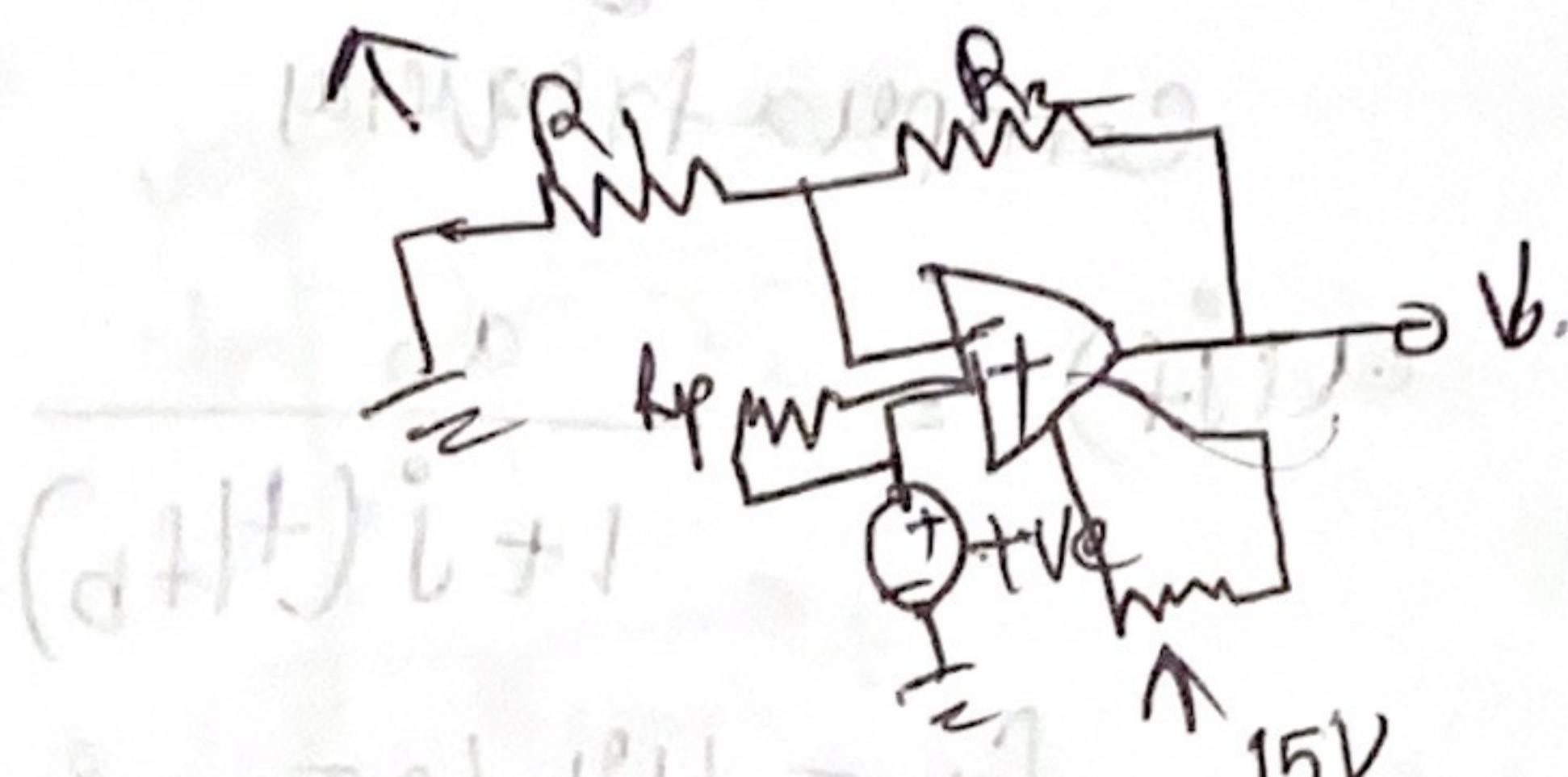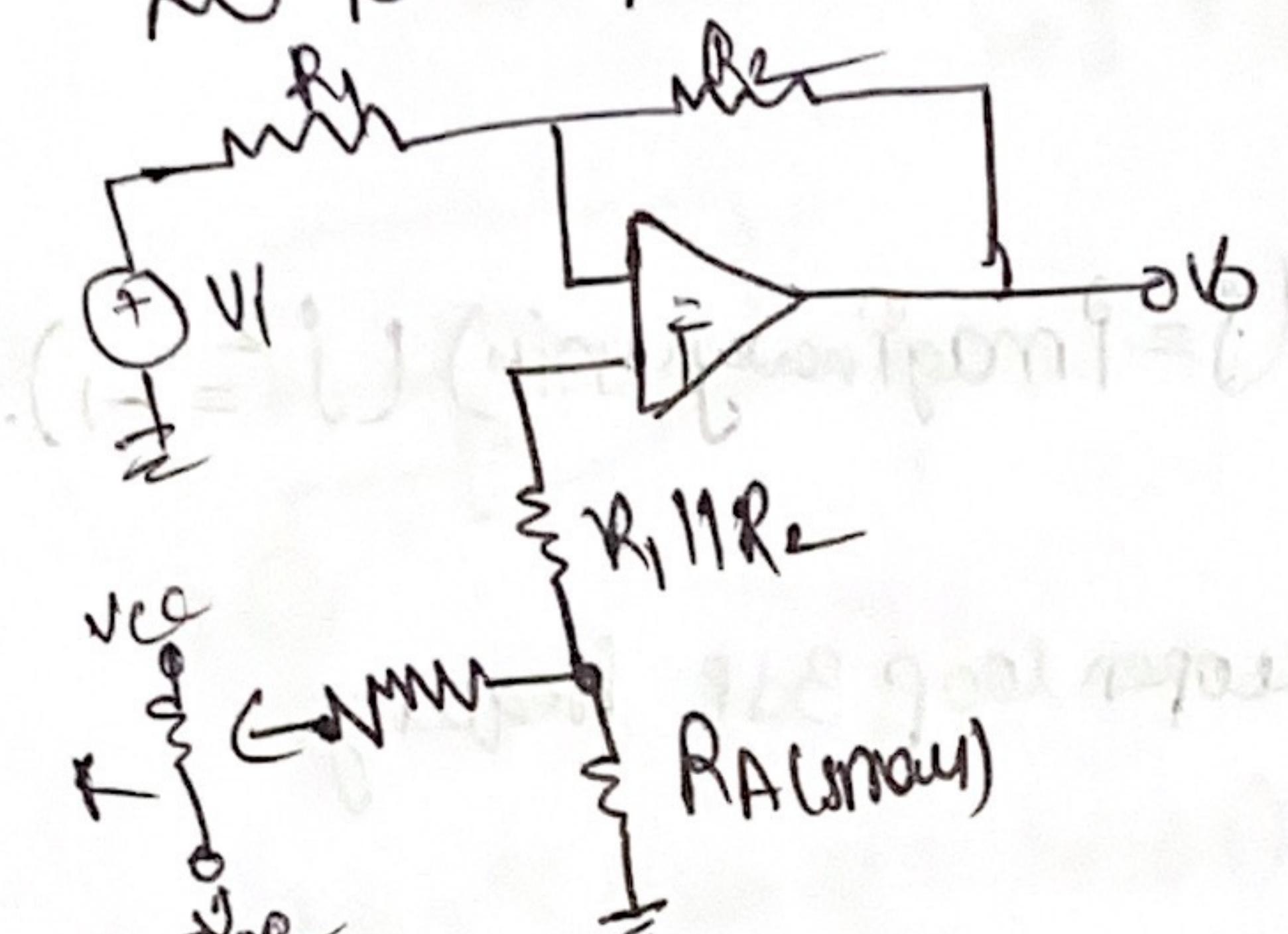

$$R_B > R_E.$$

Dynamic opamp limitations:

→ Open loop response.

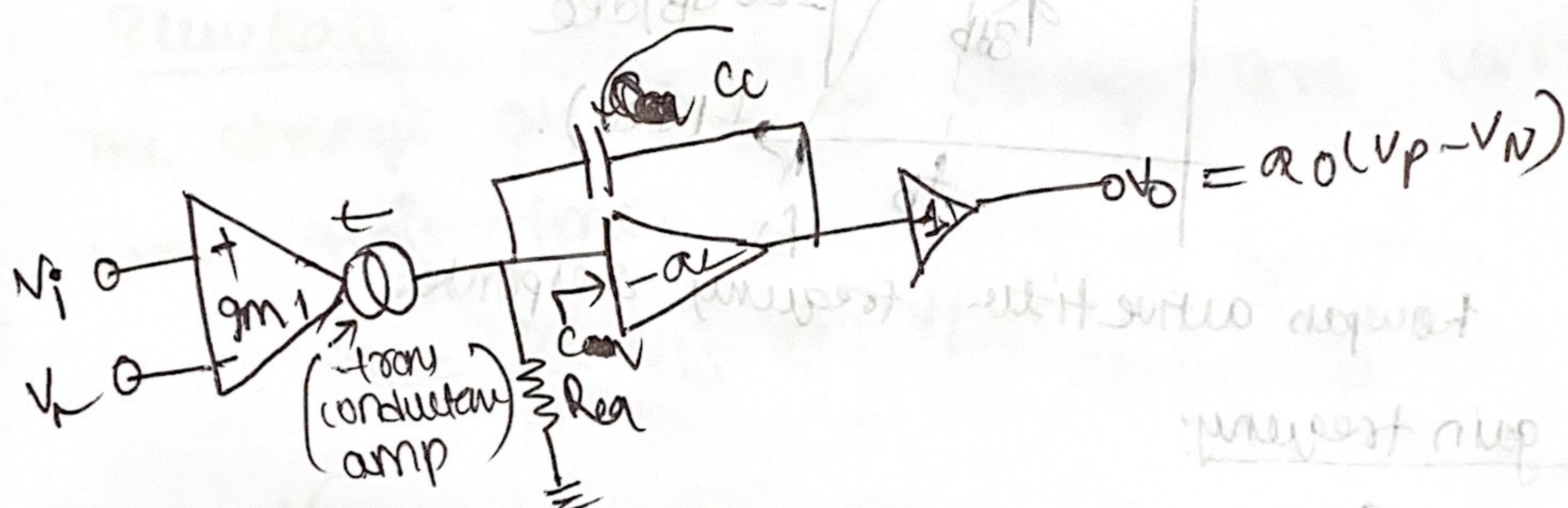

$$V_o = a_0(V_P - V_N)$$

$$V_o = 1 + a_2 \frac{1}{R_EA} \times -90^\circ$$

$$\Rightarrow V_o = a_2 R_EA g_m 1 (V_P - V_N)$$

$$a_0 = a_2 R_EA g_m 1$$

$$\frac{d\omega}{dt} = 1$$

$$d\omega = f$$

$$d\omega = f$$

(roll off frequency)

$$\rightarrow f_b = \frac{1}{2\pi R_E A}, \text{ (dominant pole freq)}$$

23/3/22

single pole open loop gain:

$$a(s) = \frac{a_0}{1 + s/a_b} \rightarrow \text{open loop gain}$$

$s = j\omega$ → s-plane pole location.

Complex frequency

$$a(jf) = \frac{a_0}{1 + j(f/f_b)} \quad (j = \text{maginary unit}), (j^2 = -1).$$


$f_b = \omega_b / 2\pi \rightarrow$ is the open loop 3dB frequency.

Magnitude & phase:

$$|a(jf)| = \text{mag}(a(jf)) = \frac{a_0}{\sqrt{1 + (f/f_b)^2}}$$

$$\Rightarrow a(jf) = \text{ph}(a(jf)) = -\tan^{-1}(f/f_b).$$

$|a(jf)|(\text{dB})$.

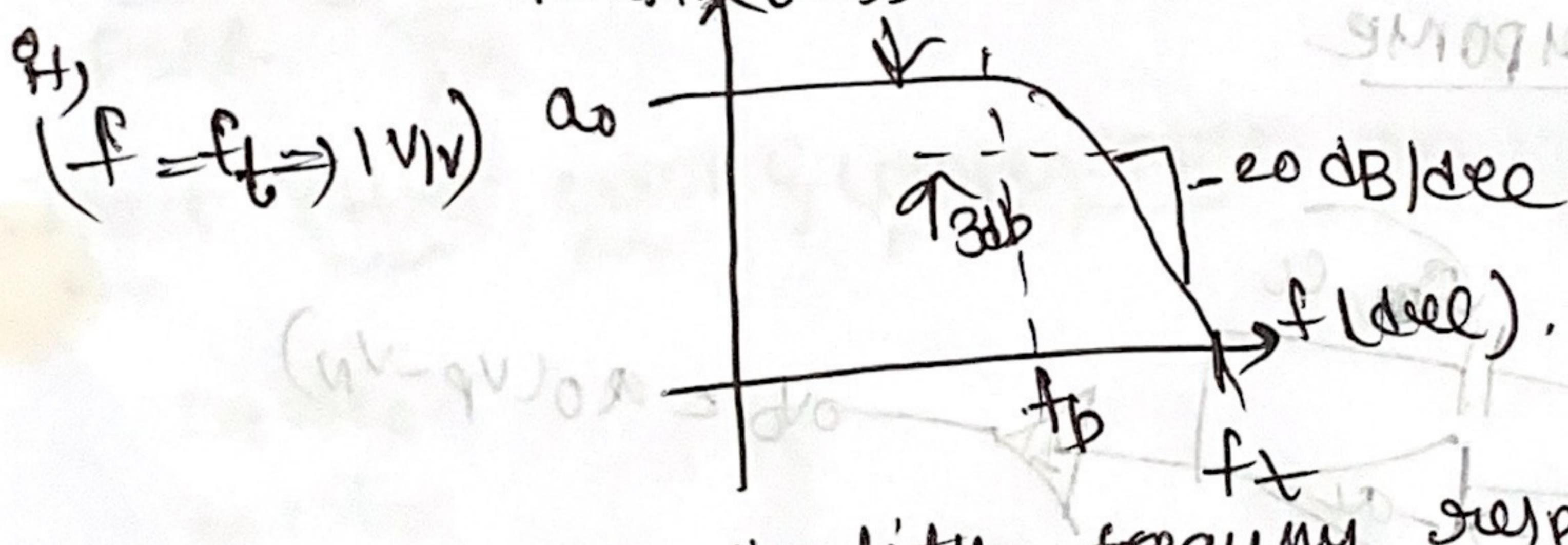

unity gain frequency:

$$f_u = \frac{a_0}{\sqrt{1 + 1}} = \sqrt{a_0}$$

$f_u \gg f_b$

$$(f_u = a_0 + b)$$

$$\begin{aligned}
 & \text{R1} = \text{R2} = 10k\Omega \\
 & U_{out} = 0V \\
 & U_{in} = 0V \\
 & U_{out} = 0V
 \end{aligned}$$

(current 40 mA)



(0.04 mA normal, $\frac{1}{100000} = 0.04$)

24/3/22

Transient Response:

→ Rise time - T_R
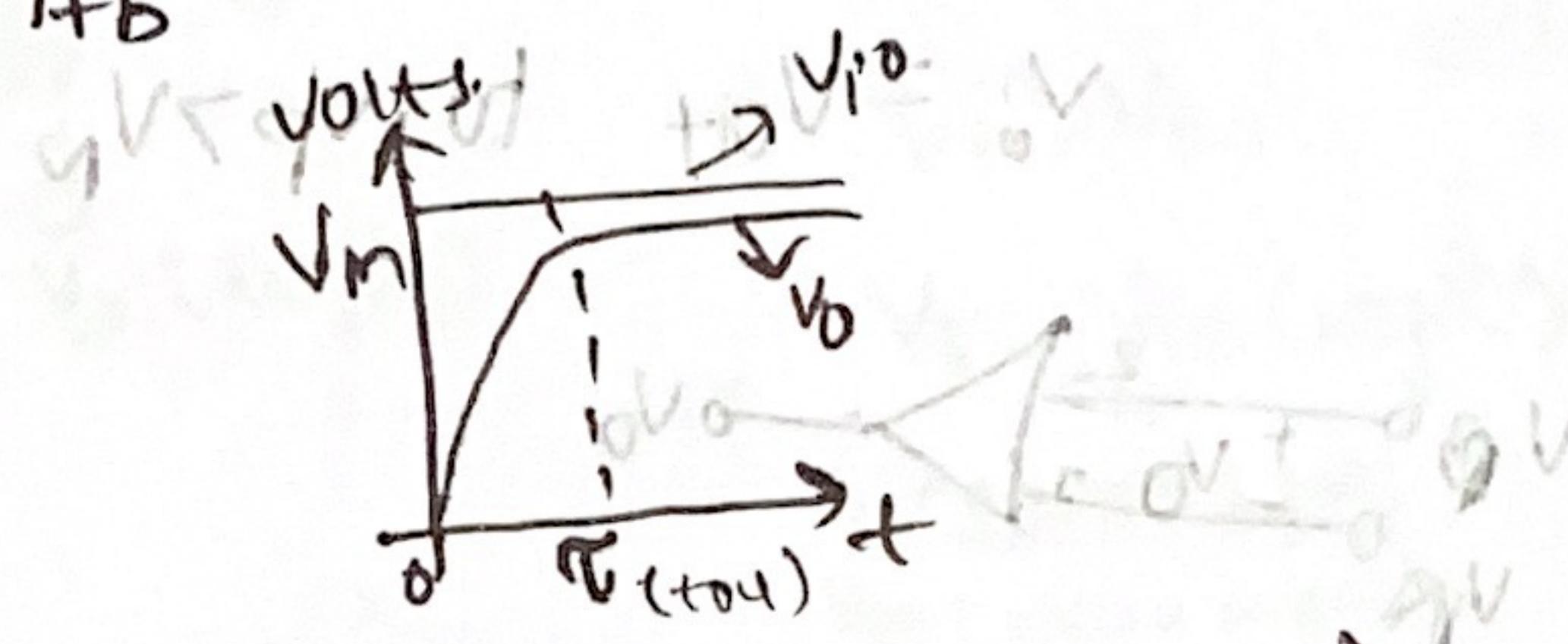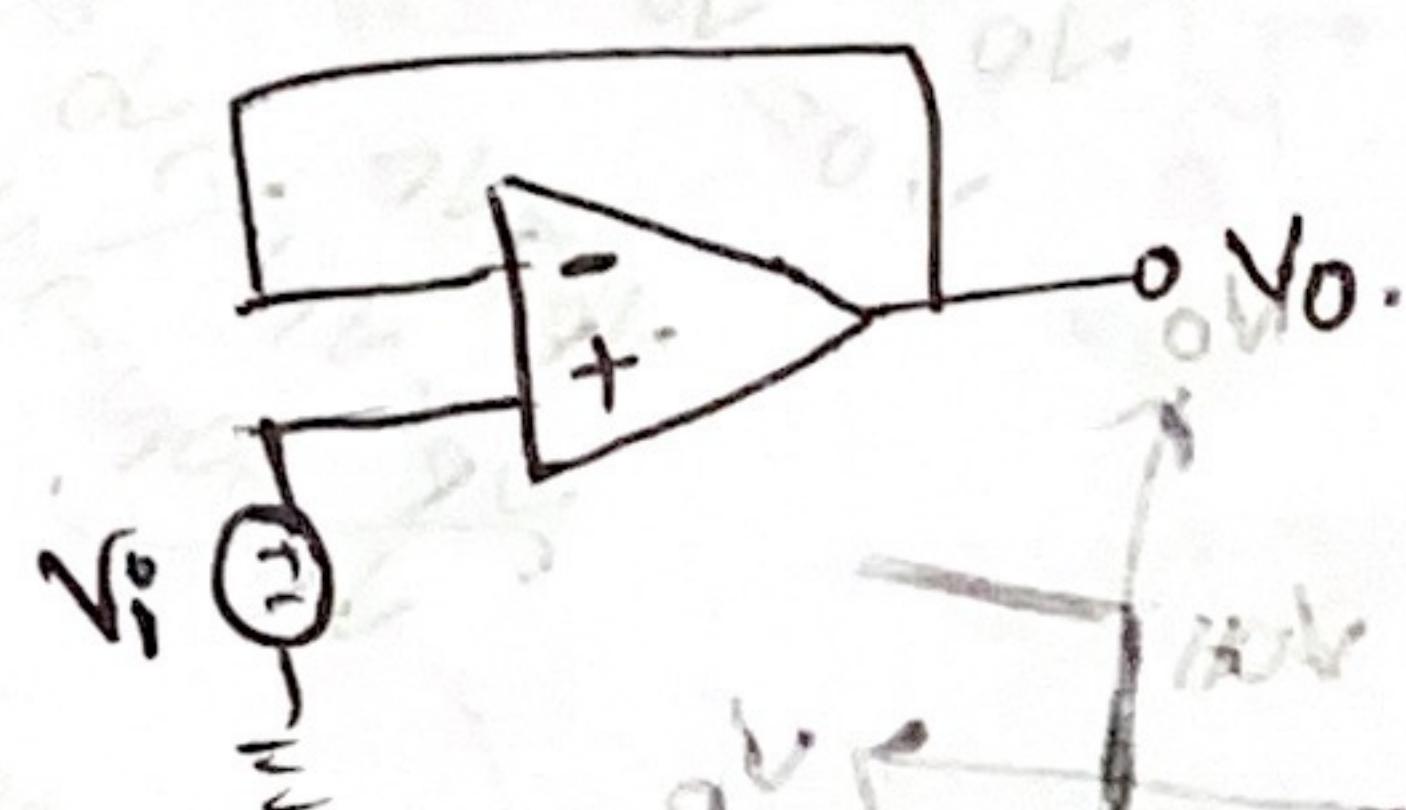
$$A(\text{if}) = \frac{a_0}{1 + j\omega_f/f_b}$$



$$T_R = \tau (\ln 0.9 - \ln 0.1) = \frac{1}{2\pi f_L} (\ln 0.9 - \ln 0.1)$$

$$\tau = \frac{1}{2\pi f_L} \Rightarrow V_o(t) = V_m (1 - e^{-t/\tau})$$



$$T_R = \frac{0.35}{f_L}$$

Non-inverting no group

Slew Rate:


The change or Rate of Voltage are current wrt unit time.

$$SR = \frac{DV}{Dt} \text{ V/μs}$$

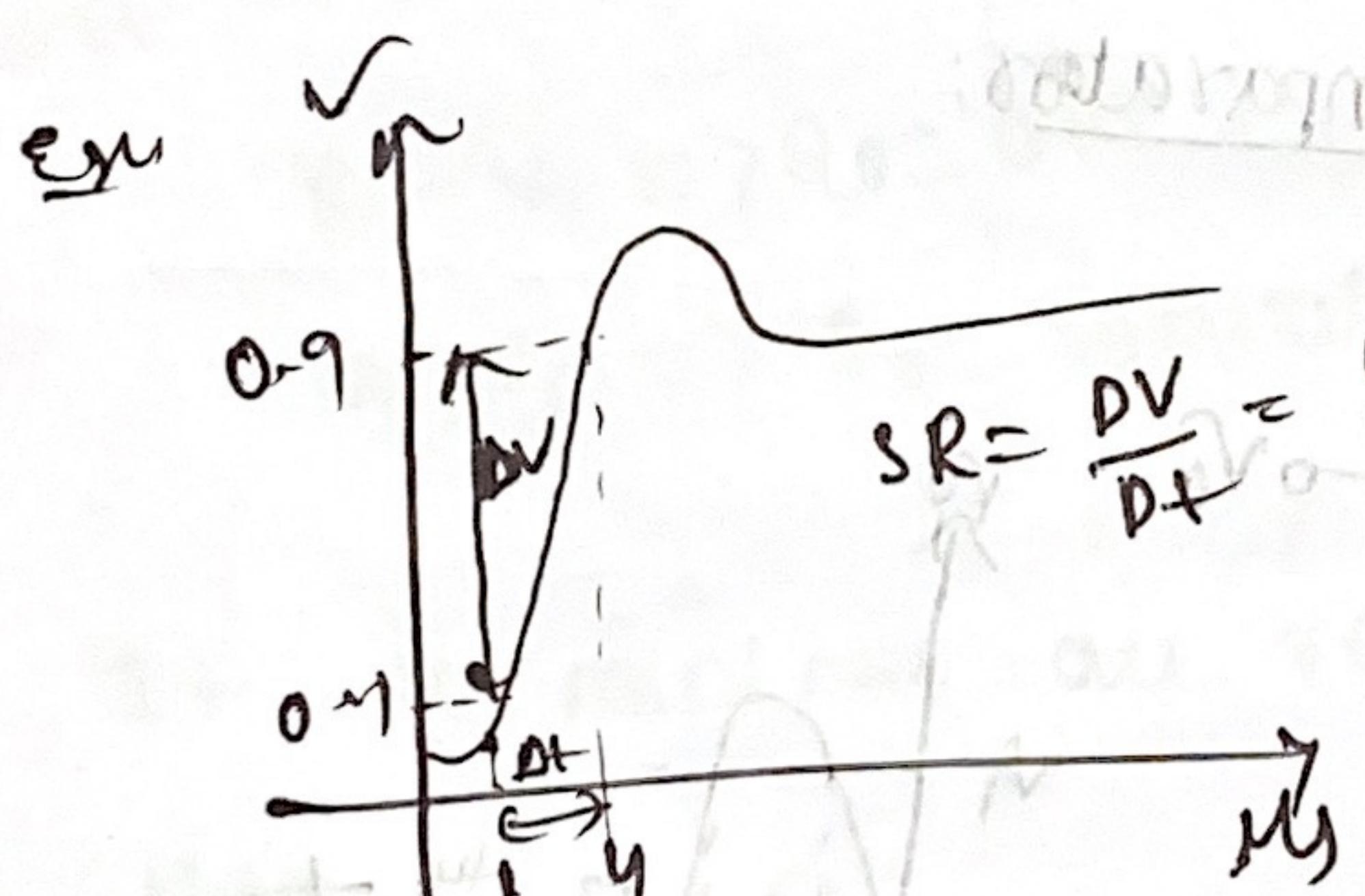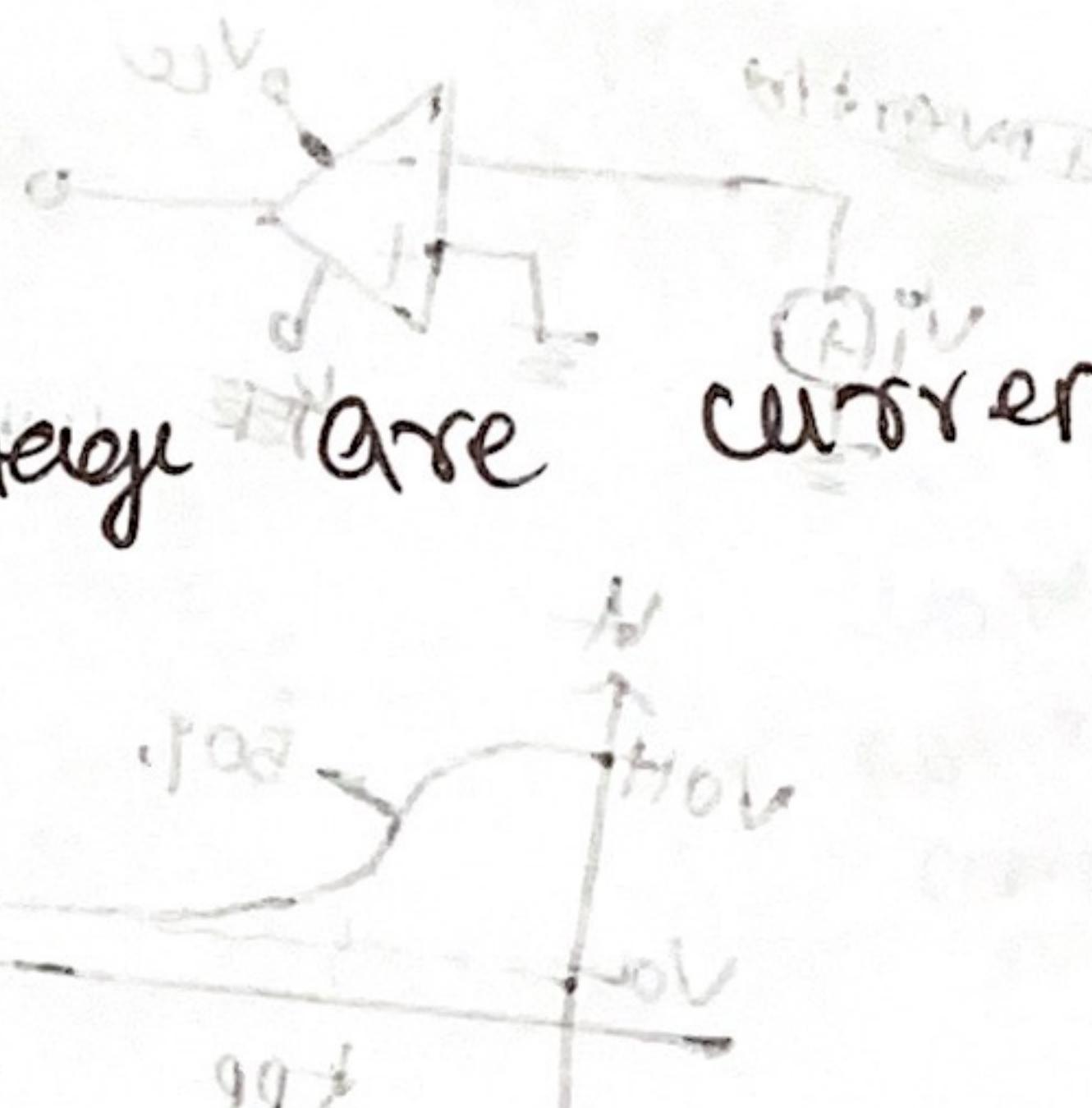

$$SR = \frac{DV}{Dt} = \frac{0.9 - 0.1}{1/3} = \frac{0.8}{3} \text{ V/μs}$$

Slew rate limitation

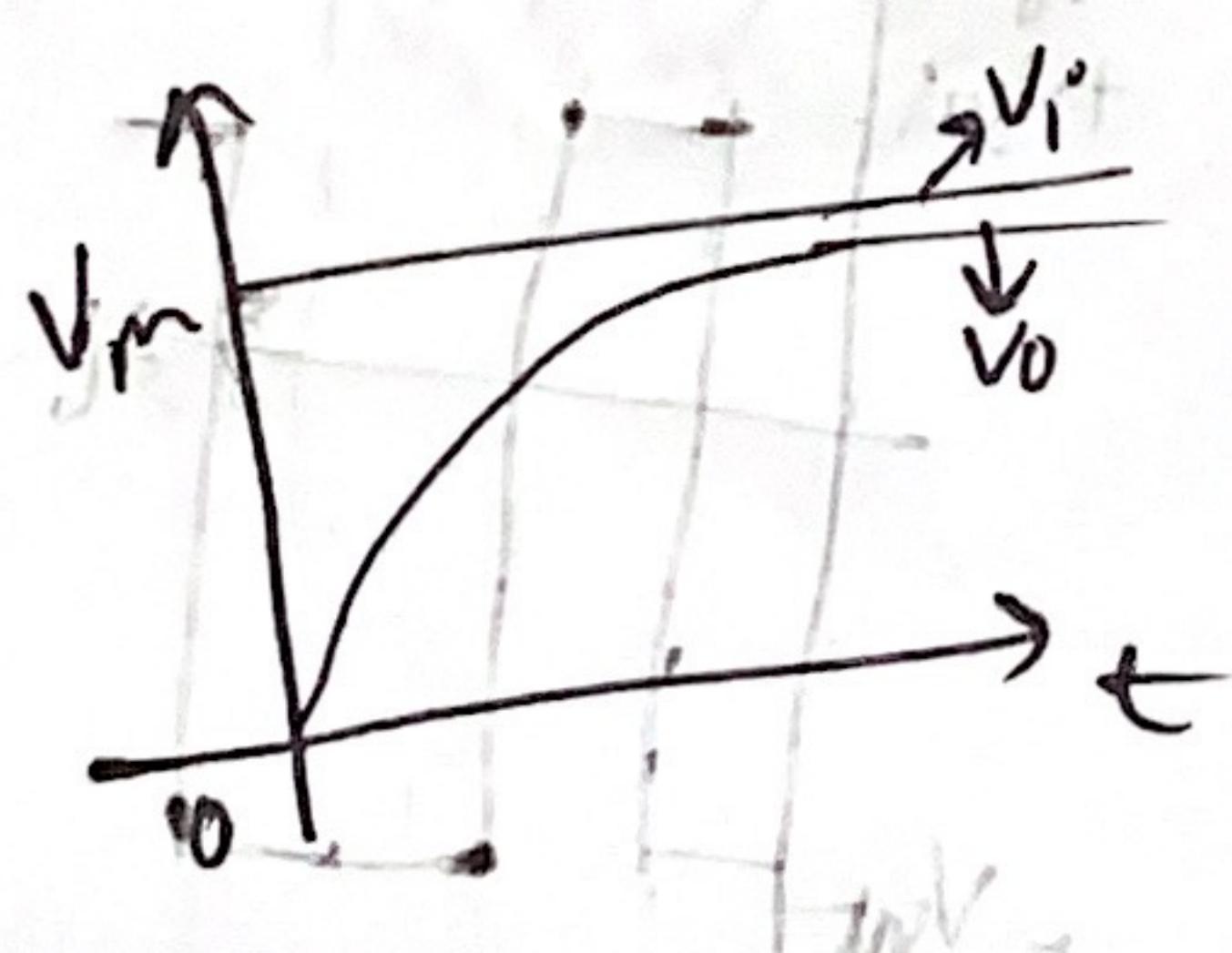

$$V_o(t) = V_m [1 - e^{-(t/\tau)}]$$

$$\frac{dV_o}{dt} \Big|_{t=0} = \frac{V_m}{\tau}$$

One better if $\tau \rightarrow \infty$, $0 = \tau \rightarrow \infty$