

8.40 Transform network

$$I(s) = \frac{1/5 - 1/5 e^{-5s}}{(2 + 2/5)} = \frac{1}{2} \left[\frac{-1 - e^{-5s}}{(5+1)} \right]$$

$$I(s) = \frac{-(1 + e^{-5s})}{2(s+1)} \quad (14)$$


$$i(t) = \mathcal{L}^{-1}[I(s)] = \mathcal{L}^{-1} \left[\frac{1}{2} \left[\frac{-1 - e^{-5s}}{(s+1)} \right] \right] \quad (15)$$

$$V(t) = 5A(t-1) - 10A(t-2) + 5A(t-3) \quad (21)$$

EX. Y PARAMETER

$$I_1 = Y_{11}V_1 + Y_{12}V_2$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2$$

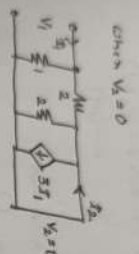


$$V_1(1+0.5) - V_2(0.5) = I_1$$

$$V_1(1.5) = I_1 \Rightarrow Y_{11} = I_1/V_1 = 1.5 \text{ S} \quad (16)$$

$$V_2(0.5+0.5) - V_1(0.5) = I_2 - 3I_1$$

$$-V_1(0.5) + 3(1.5V_1) = I_2$$
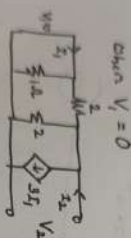
$$4V_1 = I_2 \Rightarrow Y_{21} = I_2/V_1 = 4 \text{ S} \quad (17)$$



$$V_1(1.5) - V_2(0.5) = I_1$$

$$\Rightarrow Y_{12} = I_1/V_2 = -0.5 \text{ S}$$

$$V_2(1) - V_1(0.5) = I_2 - 3I_1$$

$$V_2 + 3(-0.5V_2) = I_2$$

$$\Rightarrow \frac{I_2}{V_2} = Y_{22} = -0.5 \text{ S}$$


58

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$


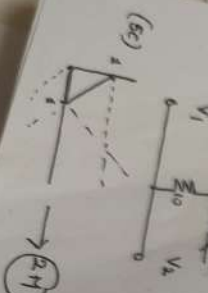
$$\frac{h_{11} = 1.5 \Omega}{h_{21} = -2} = \frac{V_1}{I_1} \quad (18)$$



$$V_2 = I_2(20) \Rightarrow h_{22} = \frac{I_2}{V_2} = \left(\frac{1}{20} \text{ S} \right)$$

$$h_{12} = \frac{V_1}{V_2} = 0.5 \quad (19)$$

$$314 \times \frac{1}{19} = 3.4$$

$$5 = 0.314$$

$$R = 5 \Omega$$

$$L = 10 \text{ mH}$$

$$C = 10 \mu\text{F}$$


$$f_s = \frac{1}{2\pi RC} = \frac{1}{2\pi \times 5 \times 10^{-6}} = 1591.5 \text{ Hz}$$

$$f_s = \frac{1}{2\pi RL} = \frac{1}{2\pi \times 5 \times 10^{-3}} = 15.915 \text{ Hz}$$

$$R = \frac{X_L}{X_C} = \frac{2\pi f L}{\frac{1}{2\pi f C}} = 2\pi f L C$$

$$I = I_{\text{max}} \sin \omega t$$
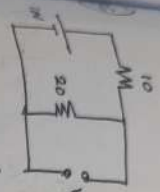
$$P_{\text{max}} = (I_0)^2 \times 5 = 500 \text{ W}$$



$$V_c(0^-) = \left(\frac{10}{30}\right) \times 20 = 6.667 \text{ V} = V_c(0^+)$$

When switch is opened and again S.S.I's reached

$$V_c(t) = V_c(\infty) - [V_c(\infty) - V_c(0)] e^{-t/\tau}$$

$$= 0 - [0 - 6.667] e^{-t/20 \times 10^{-6}}$$

$$V_c(t) = 6.667 e^{-25000t}$$

Since no current flows


$$V_a(0^+) = 5 \text{ V}$$

$$V_b = 5 \text{ V}, V_c = 5 \text{ V}$$


$$V_a \left(\frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right) - 5 \left(\frac{1}{10} \right) - \left(\frac{5}{20} \right) = 0$$

$$V_a(0.25) = 0.75$$


$$V_a(0^+) = 3 \text{ V}$$

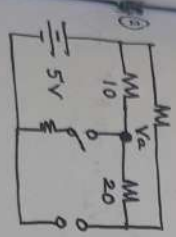

At $t = 0^+$

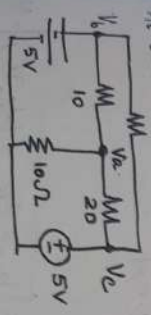






$$V_a(0^+) = 3 \text{ V}$$

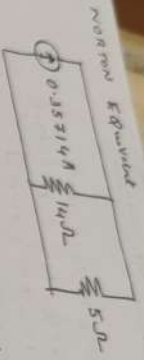

$$I_{5\Omega} = 0.35714 \times \frac{15}{19}$$

$$= 0.263A$$

$$P = (0.263)^2 \times 5 = 0.345W$$

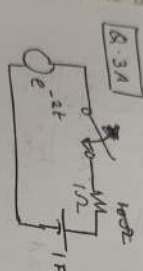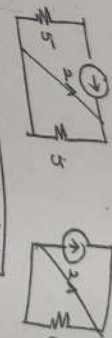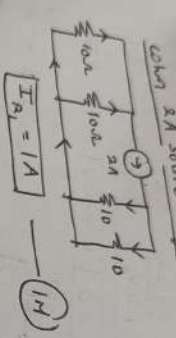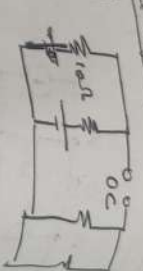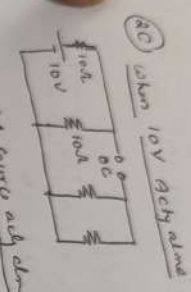

$$Ri' + \frac{1}{L} \int i' dt = e^{-2t}$$

$$i' + \int i' dt = e^{-2t}$$

$$\frac{di'}{dt} + i' = -2e^{-2t}$$

$$(D+1)i' = -2e^{-2t}$$

Thm 11 in RLF form

$$i' = e^{-pt} \int qe^{pt} dt + k e^{-pt}$$

$$i' = e^{-t} \int -2e^{-2t} (e^t) dt + k e^{-t}$$




$$= -2e^{-t} \int e^{-t} dt + k e^{-t}$$

$$At t=0, i'=0$$

$$0 = 2(1) + k(1) \Rightarrow k = -2$$

$$i' = \frac{2e^{-2t} - 2e^{-t}}{(PI + Comp.F)}$$

(14)

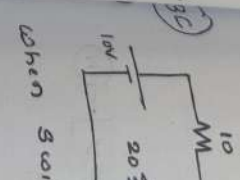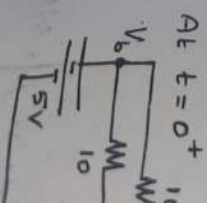
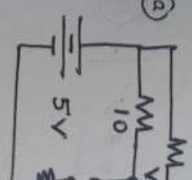


$$R = 5$$

$$f_x = \frac{1}{10}$$

$$Q = \frac{1}{10}$$

$$I = I$$

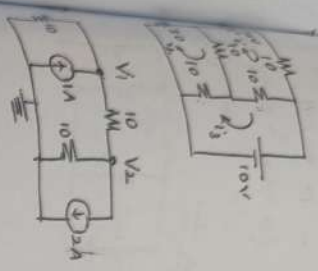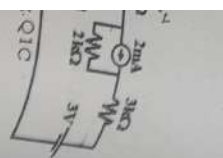

$$30 \begin{matrix} 2' \\ 1' \end{matrix} - 10 \begin{matrix} 2' \\ 1' \end{matrix} - 10 \begin{matrix} 2' \\ 1' \end{matrix} = 10 \quad \text{--- (3M)}$$

$$\begin{matrix} -10 \begin{matrix} 1' \\ 1' \end{matrix} + 40 \begin{matrix} 2' \\ 1' \end{matrix} - 10 \begin{matrix} 2' \\ 1' \end{matrix} = 0 \\ -10 \begin{matrix} 1' \\ 1' \end{matrix} - 10 \begin{matrix} 2' \\ 1' \end{matrix} + 20 \begin{matrix} 2' \\ 1' \end{matrix} = -10 \end{matrix} \quad \text{--- (2M)}$$

$$\begin{matrix} 2' = 0.1538 \\ 1' = -0.0767 \end{matrix} \quad \begin{matrix} 2' = -0.4615 \end{matrix}$$



$$V_1 \left(\frac{1}{10} + \frac{1}{10} \right) - V_2 \left(\frac{1}{10} \right) = 1$$

$$0.2V_1 - 0.1V_2 = 1 \Rightarrow 2V_1 - V_2 = 10 \quad \text{--- (1M)}$$

$$V_2 \left(\frac{1}{10} + \frac{1}{10} \right) - V_1 \left(\frac{1}{10} \right) = -2$$

$$-0.1V_1 + 0.2V_2 = -2$$

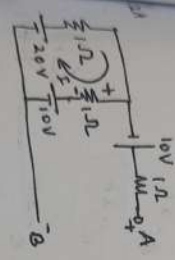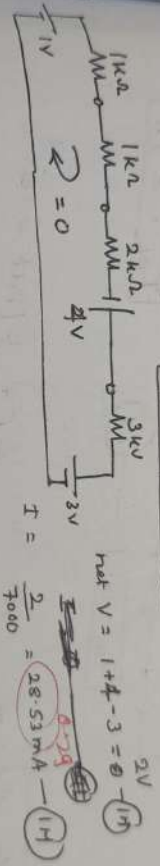
$$\begin{matrix} -V_1 + 2V_2 = -20 \\ V_1 = 0, V_2 = -10 \end{matrix} \quad \text{--- (1M)}$$



$$I = \frac{20 - 10}{2} = 5A$$

$$-V_{AB} + 10 + 5(1) + 10 = 0 = R_{AB}$$


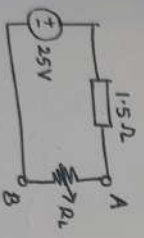
$$\Rightarrow V_{AB} = 25V \quad \text{--- (5M)}$$



$$R_L = R_{S_{\text{open}}} = R_{AB} \text{ for } P = P_{\text{max}}$$


$$\therefore R_L = 1.5\Omega \quad \text{--- (1M)}$$
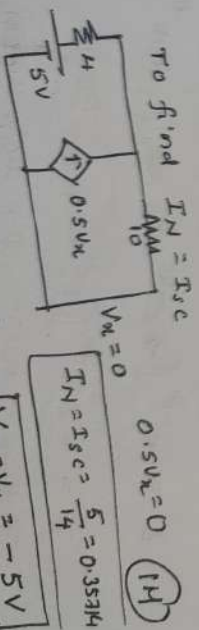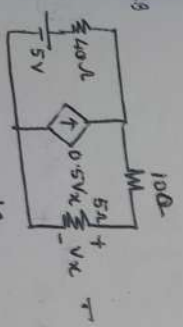
$$P_{\text{max}} = I^2 R_L = \left(\frac{25}{3} \right)^2 \times 1.5 = 104.16W \quad \text{--- (1M)}$$




$$-V_{AB} + 5 + 2V_{AB} = 0 \Rightarrow V_{AB} = V_{AB} = -5V \quad \text{--- (1M)}$$
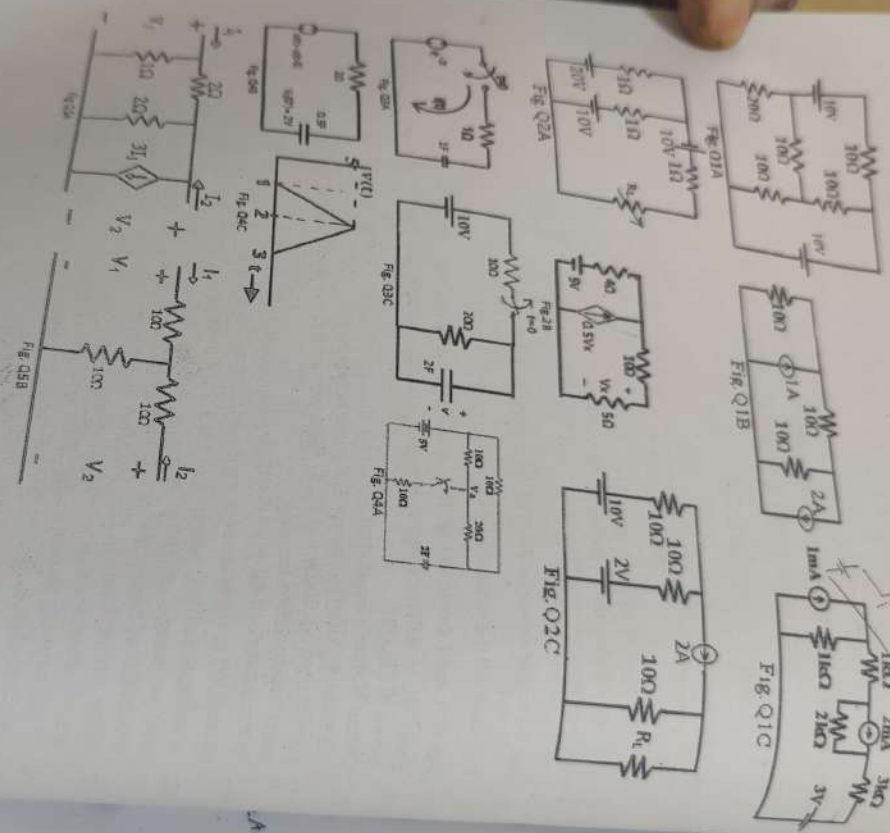
$$R_N = -14\Omega \quad \text{--- (1M)}$$



2.9

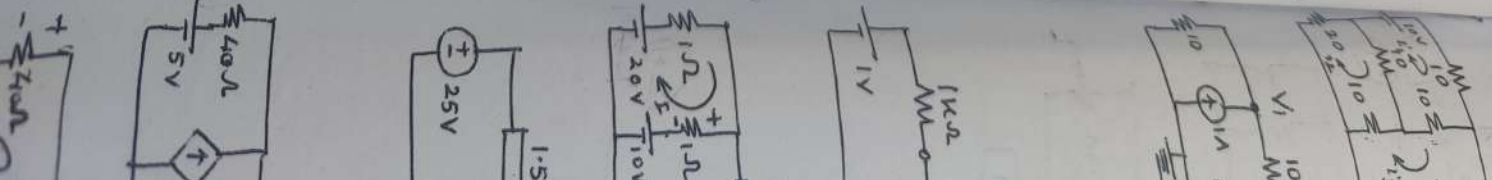



MANIPAL INSTITUTE OF TECHNOLOGY

THIRD SEMESTER B. TECH. (INSTRUMENTATION AND CONTROL ENG.G.)
END SEMESTER EXAMINATIONS, DEC - 2017

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ICE 2101] - *Made Easy*

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer ALL the questions.
- ❖ Missing data may be suitably assumed.

- 1A. For the circuit shown in Fig. Q1A, determine the mesh currents. 5
- 1B. Calculate all the node voltages for the circuit shown in Fig. Q1B 3
- 1C. For the circuit shown in Fig. Q1C calculate the current in $3k\Omega$ resistor 2
- 2A. Find R_L to deliver maximum power and the corresponding power in the circuit shown in Fig. Q2A. 5
- 2B. Obtain Norton's equivalent circuit for the network shown in Fig. Q2B with respect to 5Ω resistor. Also find power dissipated in 5Ω resistor. 3
- 2C. For the network shown in Fig. Q2C, determine the current through $R_L = 10\Omega$ resistor using superposition theorem 2
- 3A. In the network of the Fig. Q3A the switch is closed at $t=0$. Obtain expression for current $i(t)$ in complementary and particular solution form. 5
- 3B. A resistance of 5Ω , capacitor of $10\mu F$ and Inductance of $10mH$ is connected in series with ac source of $50V$. Determine the resonating frequency, quality factor and bandwidth of the circuit. Also determine maximum power dissipated in the circuit. 3
- 3C. In the circuit shown in Fig. Q3C, find the expression for V for $t \geq 0$, if switch is opened at $t = 0$ assuming that a steady state having previously been attained. 2
- 4A. In the network shown in Fig. Q4A, steady state is reached with switch open. At $t=0$ switch is closed. Determine the values of $V_a(0^-)$ and $V_a(0^+)$. 5
- 4B. Use Laplace transform to obtain expression for current in the circuit shown in Fig. Q4B. 3
- 4C. Express the waveform shown in Fig. Q4C using basic signals. 2
- 5A. For the network shown in Fig. Q5A find Y parameters. 4
- 5B. Obtain h parameters for the circuit network shown in Fig. Q5B 4
- 5C. Plot $x(t) = u(t) - t(t) + t(t-1)$. 2