



$$I_3 - I_1 = 2I_2$$

$$2I_3 + I_2 = 0$$

$$v_2 + v_3 = v_2$$


solving

$$I_1 = -3I_2 \quad I_3 = 2I_2$$

$$v_1 = -3v_2 \quad v_2 = 2v_3$$

$$Z = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix}^{-1} = \begin{bmatrix} 2/3 & 1 \\ -1/3 & 0 \end{bmatrix}$$

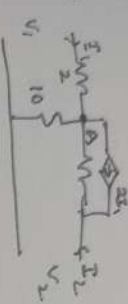1-Row  $\rightarrow 2/3$   
2-Row  $\rightarrow 1/3$   
4th




Short  $v_2$ ,  $v_2 = 0$   $\Rightarrow \frac{V_1}{10} + \frac{V_1}{10} + 2I_1 = I_1$

$\Rightarrow V_1 = -5I_1$   
 $V_1 = 2I_1 + V_2 = 2I_1 - 5I_1 = -3I_1 \Rightarrow \frac{V_1}{I_1} = h_{11} = -3\Omega$

$\frac{V_2}{10} + 2I_1 = -I_2 \Rightarrow \frac{I_2}{I_1} = h_{21} = -\frac{3}{2}$

Make  $I_1 = 0$ :

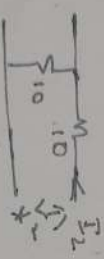

$V_2 = I_2 \times (10 \parallel 20)$   
 $\frac{I_2}{V_2} = h_{22} = \frac{1}{20} = 0.05 \text{ S}$


$V_1 = 2I_2 \times 10 = 20I_2$

$h_{12} = \frac{V_1}{V_2} = \frac{20I_2}{I_2(20)} = \frac{1}{1} = 1$

Each  $0.5 \text{ mV}$

1m

43.

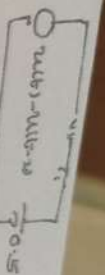

$$iR + \frac{1}{s} \int i dt = 20.5 - u(t)$$

Take LT.

$$s I(s) + 2 \frac{I(s)}{s} - \frac{20.5}{s} = \frac{1}{s} - \frac{e^{-2s}}{s}$$

$\Rightarrow$

$$I(s) = \frac{-e^{-2s}}{2(s+1)}$$

$$i(t) = -\frac{1}{2} e^{-(t-2)} u(t-2)$$


4C

$$v(t) = 5 \times (t-1) - 10 \times (t-2) + 5 \times (t-3) + 5 \times (t-5) - 10 \times (t-6) + 5 \times (t-7)$$

$$\therefore V(s) = \frac{5}{s^2} [e^{-s} - 5e^{-2s} + e^{-3s} + e^{-5s} - 5e^{-6s} + e^{-7s}]$$

Note: Mark is given if it is considered as partial

5A

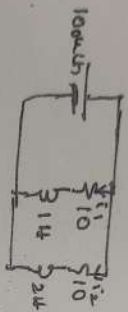

$$i_1 \Rightarrow i_1 R + L \frac{di_1}{dt} = 100$$

$$10 i_1 + \frac{di_1}{dt} = 100$$

$$I_1(s) = \frac{100}{s(s+10)}$$

$$I_1(s) = \frac{10}{s} - \frac{10}{s+10}$$

$$i_1(t) = 10 u(t) - 10 e^{-t} u(t)$$


$$-i_2 R_2 + L_2 \frac{di_2}{dt} = 100$$

$$I_2(s) = \frac{50}{s(s+5)}$$

$$\Rightarrow i_2(t) = 10(1 - e^{-5t}) u(t)$$

Q.5Q

Short  $v_2 \Rightarrow v_2 = 0$

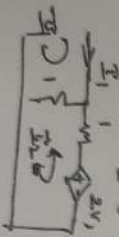


$$\Rightarrow I_1 + I_2 = V_1$$

$$I_1 + 2I_2 = 2V_1$$

$$\Rightarrow V_1 = \frac{I_1}{V_1} = 0V$$

$$\Rightarrow I_2 = 1V_1$$

$$V_2 = \frac{I_2}{V_1} = 1V$$

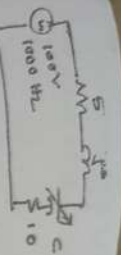

$$X_L = \omega L = 2\pi f L$$

$$\Rightarrow C = 53 \mu F$$

$$P = I^2 R_L = \left(\frac{100}{5+10}\right)^2 \times 10$$


$$= 444 W$$

- (2M)
- (1M)
- (3M)
- (2M)

switch is closed at  $t=5ms$ , inductor is open at  $t=5ms$

$$\therefore \frac{dV}{dt} \bigg|_{t=5ms} = 0 A$$

Note: No Partial Marks

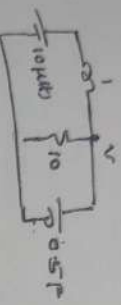

$$\text{For } t > 0 \quad \frac{1}{s} \int (V-10) dt + \frac{V}{10} + 0.5 \frac{dV}{dt} = 0$$


$$\text{applying } \frac{1}{s} [V(s) - 10] + \frac{V(s)}{10} + 0.5 s V(s) = 0$$

$$\Rightarrow V(s) = \frac{20}{s(s^2 + 0.2s + 2)}$$


$$V(s) = \frac{A}{s} + \frac{Bs+C}{(s+0.1)^2 + (\sqrt{3})^2}$$

$$\Rightarrow v(t) = 10 \cos(2t) - 10 e^{-0.1t} \{ \cos \sqrt{3}t + 0.067 \sin \sqrt{3}t \}$$

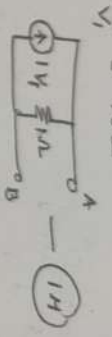
$$\frac{V_{oc}}{I_{sc}} = \frac{V_1}{I_1} = 1 \Omega$$



2. B

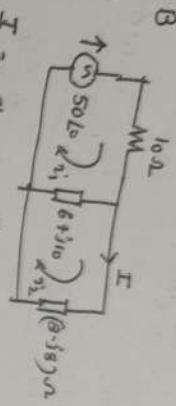
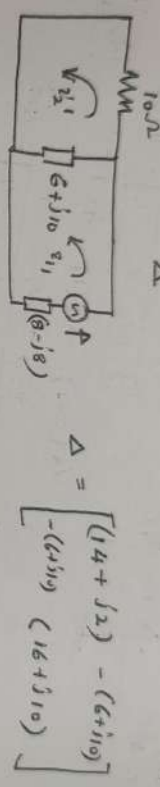
$$I = I_2 = \frac{\begin{vmatrix} 16+j10 & 50 \\ -(6+j10) & 0 \end{vmatrix}}{\Delta} = \frac{2.135 \angle 48^\circ \text{ A}}{(1.5)}$$



$$V_2' = \frac{\begin{vmatrix} 50 & -(6+j10) \\ 0 & (16+j10) \end{vmatrix}}{\Delta} = \frac{2.135 \angle 48^\circ \text{ A}}{(1.5)}$$


$V_2 = V_2'$  Hence Reciprocity theorem verified

2C


$$V_{TH} = 2 \times 10 = 20 \text{ V} - (1H)$$




3. A

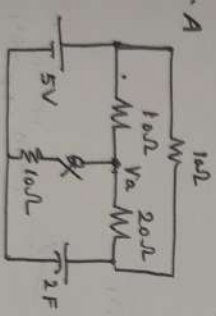

At  $t=0^+$

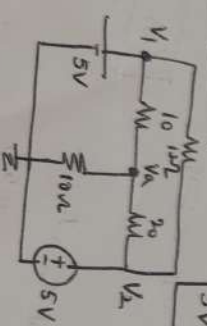

At  $t=0^-$  circuit reduces to

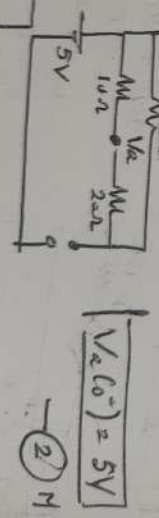

$$V_1 = V_2 = 5 \text{ V}$$

$$V_A \left( \frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right) - \frac{5}{10} - \frac{5}{20} = 0$$


$$V_A \left( \frac{5}{20} \right) = \frac{10+5}{20} = \frac{15}{20}$$

$$V_A = \frac{15}{20} \cdot \frac{20}{5} = 3 \text{ V}$$

(3) M

ECA

Scheme of VALUATION

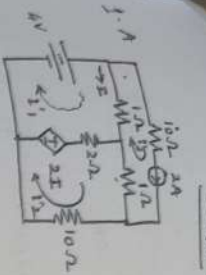

$$V_1 = 4V \quad (1H) \quad I = V_1 - V_2 = (V_1 - 2) \quad (1H)$$

$$5V_1 - 2V_2 - 2 = 4 - 2(V_1 - 2) \quad (1H)$$


$$5V_1 - 2V_2 = 10 \quad (1H)$$

$$-2V_1 + 13V_2 - 2 = 2(V_1 - 2) = 2V_1 - 4$$

$$-4V_1 + 13V_2 = -2 \quad (1H)$$

$$4V_1 - 13V_2 = 2 \quad (1H)$$
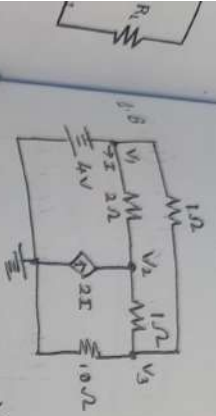
$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2.210A \\ 0.5263A \end{bmatrix} \quad (1H)$$



$$V_2 = 4V \quad (1H) \quad I = (V_1 - V_2) \quad (1H)$$

$$V_2(1.5) - (V_1 - V_2) - V_3 = 2I = 2(V_1 - V_2) = 2V_1 - 2V_2$$


$$2.5V_2 - V_3 = 6 \quad (1H)$$

$$V_3(2.5) - V_2(1) - 4(1) = 0$$

$$-V_2 + 2.5V_3 = 4 \quad (1H)$$

$$V_2 - 2.5V_3 = -4 \quad (1H)$$
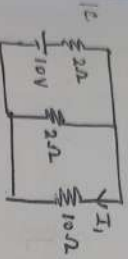
$$\begin{bmatrix} V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 3.90V \\ 3.76V \end{bmatrix} \quad (1H)$$




$$I_1 = \left[ \frac{10}{2 + \frac{2 \times 10}{12}} \right] \cdot \frac{2}{12} = 0.4545A \quad (1H)$$

$$I_2 = \left[ \frac{2}{2 + \frac{2 \times 10}{12}} \right] \cdot \frac{2}{12} = 0.09090A \quad (1H)$$

$$I_3 = 1 \times \left( \frac{1}{11} \right) = 0.09090A \quad (1H)$$
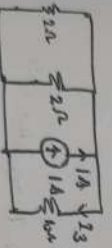
$$I = I_1 + I_2 + I_3 = 0.63636 \quad (1H)$$




$$2V_1 = V_1 - 0.5V_1 = 0.5V_1$$

$$V_1 = 0.25V_1 \quad (A)$$

$$V_1 = I = 0.25V_1$$

$$-V_{AB} + 0.5V_1 + 0.25V_1 + 0.25V_1 = 0$$

$$V_{AB} = 1V_1 = V_1 \quad (2H)$$

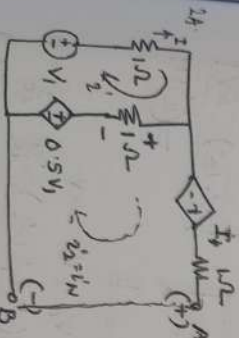

To find  $R_{TH}$  apply short and  $I_N = I_{sc} = I_2$















$$2V_2 - V_2 = V_1 - 0.5V_1 = 0.5V_1$$

$$-V_2 + 2V_2 = 0.5V_1 + 0.25V_1 = 0.75V_1$$


$$-2V_2 + 2V_2 = 0.5V_1 \quad \text{Add } V_2 = 0.5V_1 + 0.5V_1 = 1V_1$$
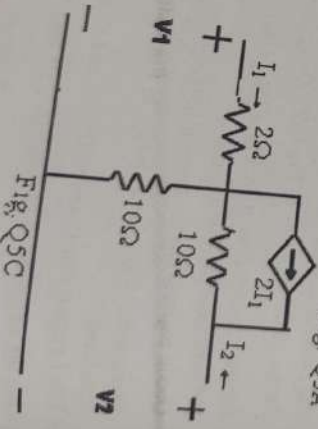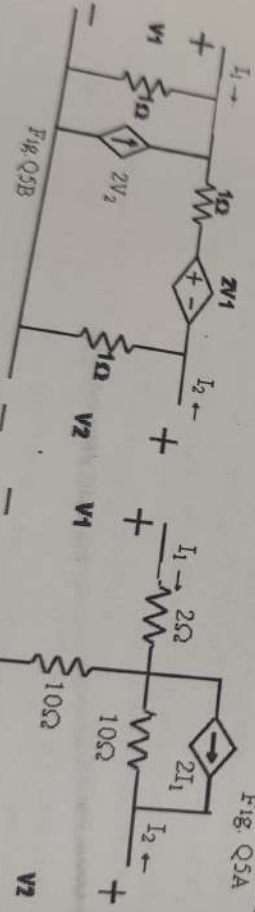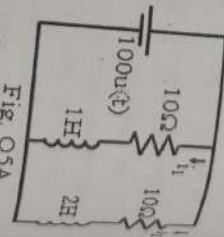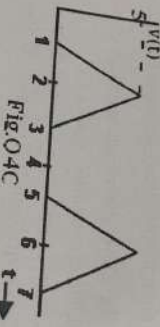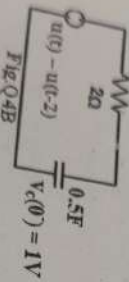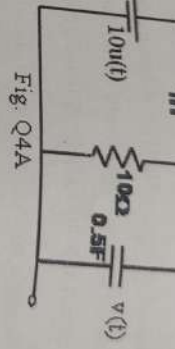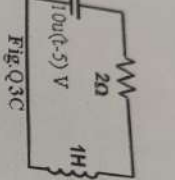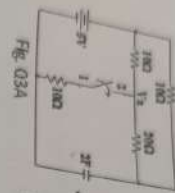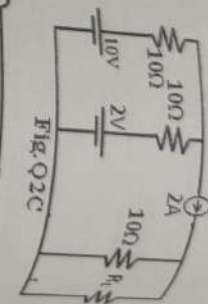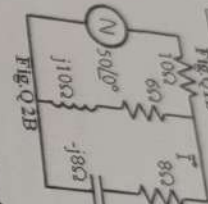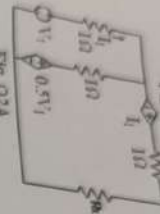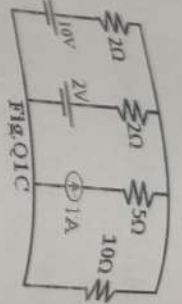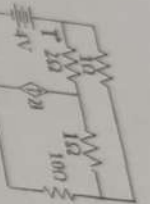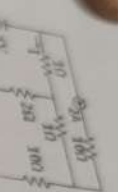
$$\therefore I_N = (V_1) A \rightarrow (2H)$$





\*\*\*\*\*

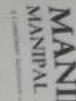

MANIPAL INSTITUTE OF TECHNOLOGY

THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)  
END SEMESTER EXAMINATIONS, NOV/DEC 2016

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ICE 2101]

Time: 3 Hours

MAX. MARKS: 50

**Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed

- 1A. For the circuit shown in Fig. Q1A, determine the mesh currents. 5
- 1B. determine the node voltages for the circuit shown in Fig. Q1B 3
- 1C. For the circuit shown in Fig. Q1B, find the current in  $10\Omega$  resistor using superposition theorem. 2
- 2A. Obtain Norton's equivalent for the circuit shown in Fig. Q2A, with respect to  $R_L$ . 5
- 2B. In the circuit shown in Fig. Q2B, find current  $I$  and verify reciprocity theorem. 3
- 2C. Obtain Thevenin's equivalent for the circuit shown in Fig. Q2C, with respect to  $R_L$ . 2
- 3A. In the network shown Fig. Q3A, the switch is closed at  $t=0$ , a steady state having previously been attained. Determine  $v_a(0^+)$  and  $v_a(0^-)$ . 5
- 3B. A source of  $100V$  with source impedance  $5+j3$  and frequency  $1000$  Hz is connected to a load of capacitor  $C$  in series with  $10\Omega$  resistor. At what value of  $C$ , power in the  $10\Omega$  resistor is maximum? What is the power? 2
- 3C. For the circuit shown in Fig. Q3C, find current in the circuit at  $5$  seconds. 5
- 4A. For the circuit shown in Fig. Q4A, obtain expression for current in complementary and particular solution form. 3
- 4B. Obtain expression for current in the circuit shown in Fig. Q4B. 3
- 4C. Express the waveform shown in Fig. Q4C using basic signals and write the Laplace transform. 4
- 4A. Use Laplace transform to find  $i_1$  and  $i_2$  in the circuit shown in Fig. Q5A 4
- 5B. For the network shown in Fig. Q5B find  $V$  parameters. Hence find  $Z$  parameters 4
- 5C. Find  $h$  parameters for the circuit shown in Fig. Q5C 2