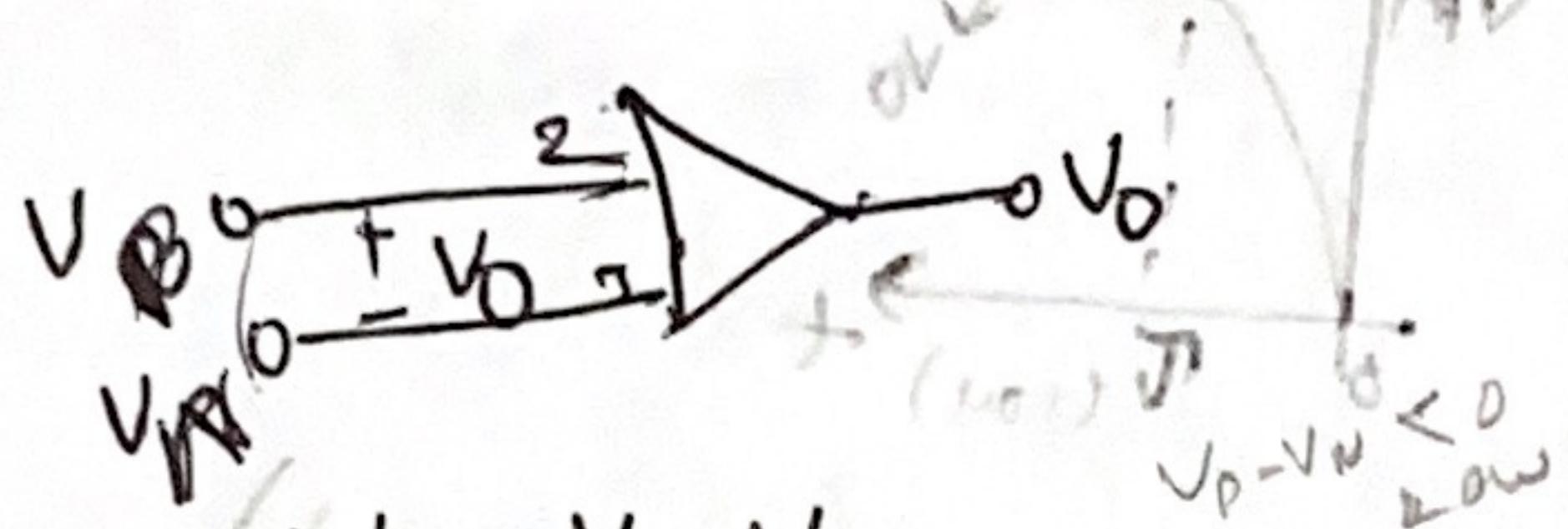


NON-LINEAR CIRCUITS

Voltage Comparators

$$V_p = V_u = V_{OL} \text{ for } V_i < V_N$$

$$V_o = V_{OH} \text{ for } V_p > V_N$$





$$(V_D = V_p - V_N)$$

$$V_o = V_{OL} \text{ if } V_D < 0$$

$$V_o = V_{OH} \text{ if } V_D > 0$$

Opamp as a Comparator

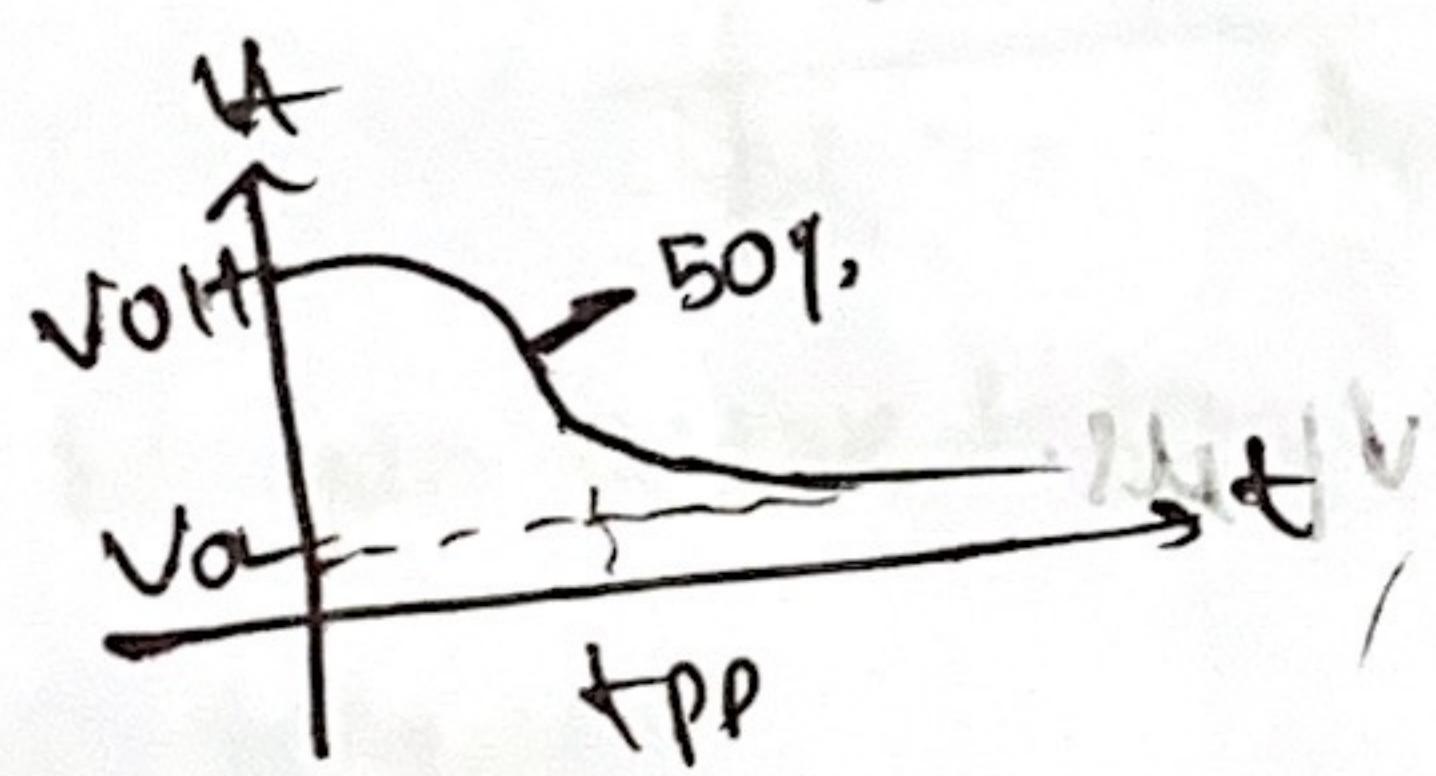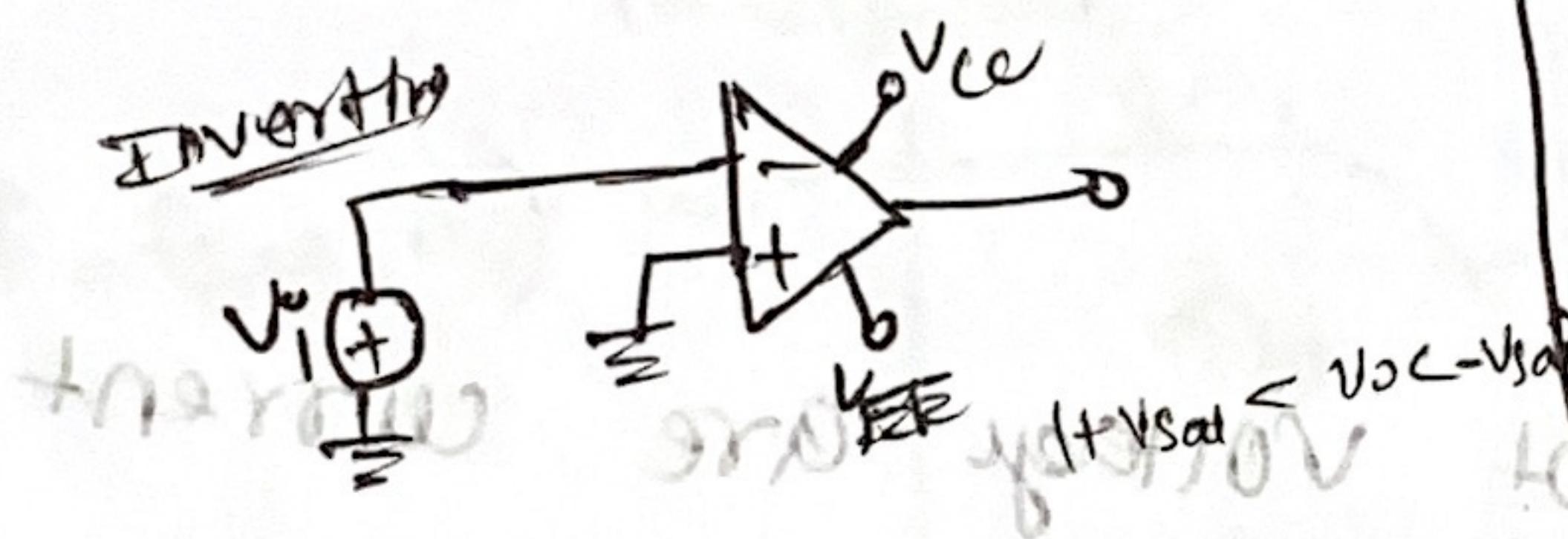


Open loop circuit,

Open loop mean gain $\approx 10^6$ so
P+ will be operating in
non-linear range

• enter finite \rightarrow w


Opamp as Voltage Comparators

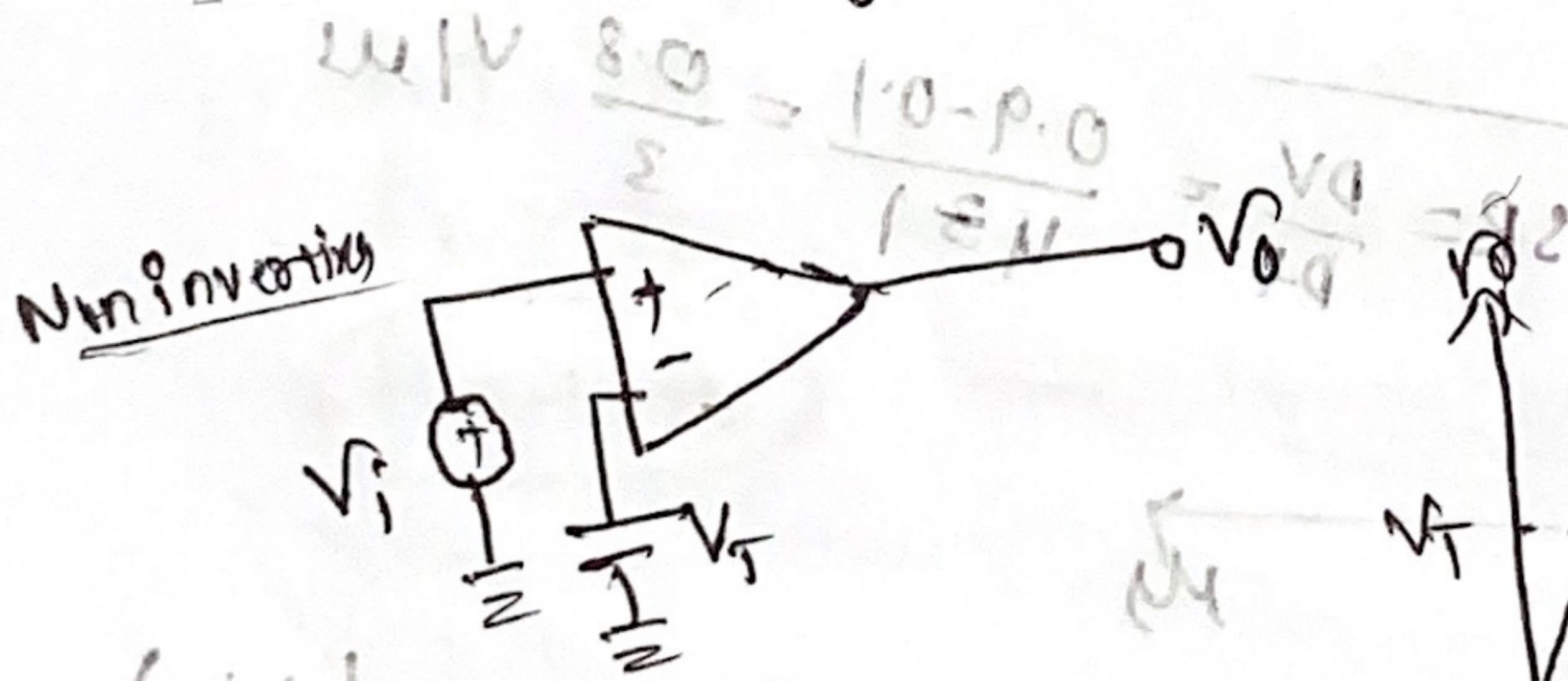


$$V_p > V_T \Rightarrow V_o = +V_{sat}$$

$$V_p < V_T \Rightarrow V_o = -V_{sat}$$

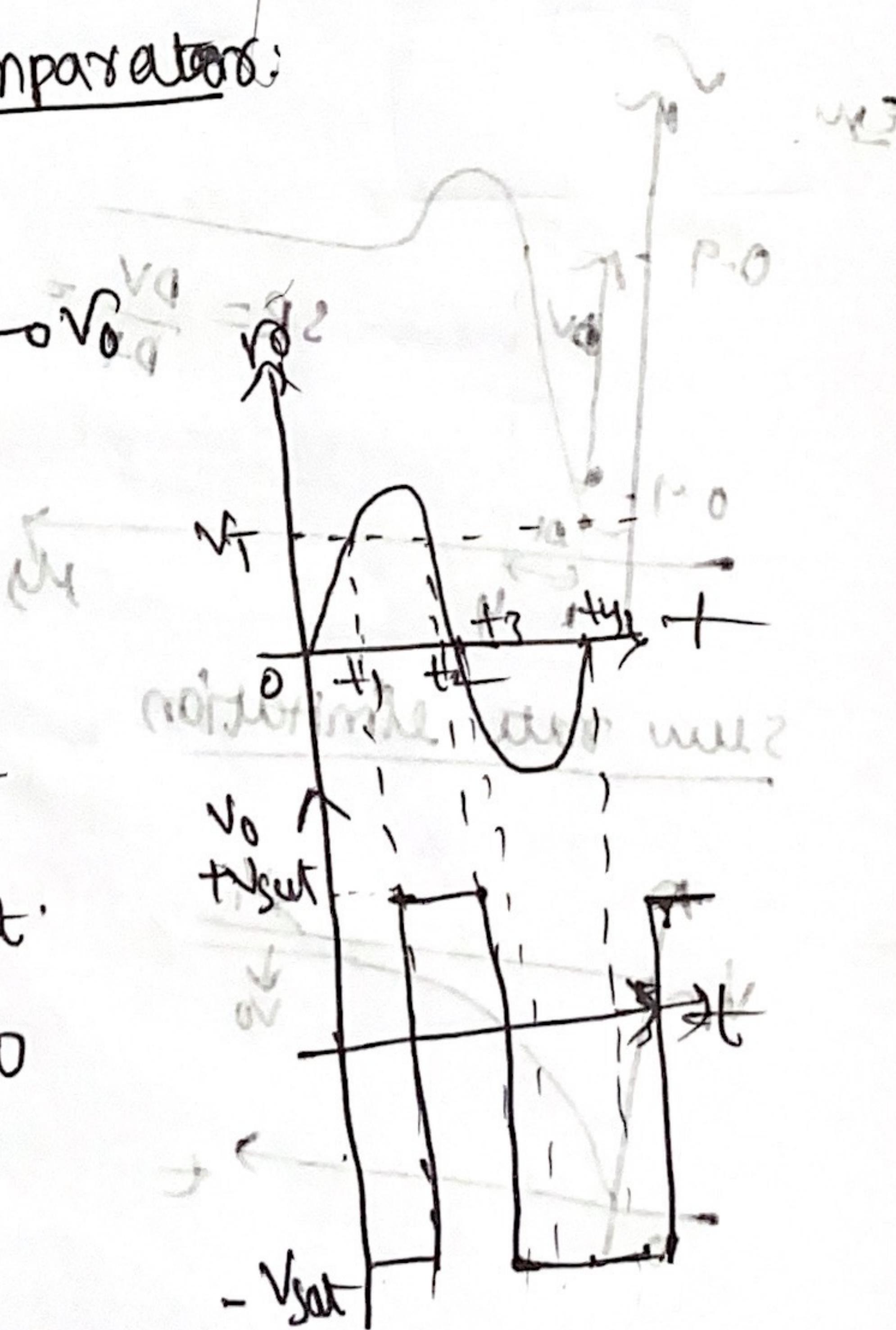$\rightarrow V_T = 0$, then it is called zero crossing detector.




General Response IC Configuration

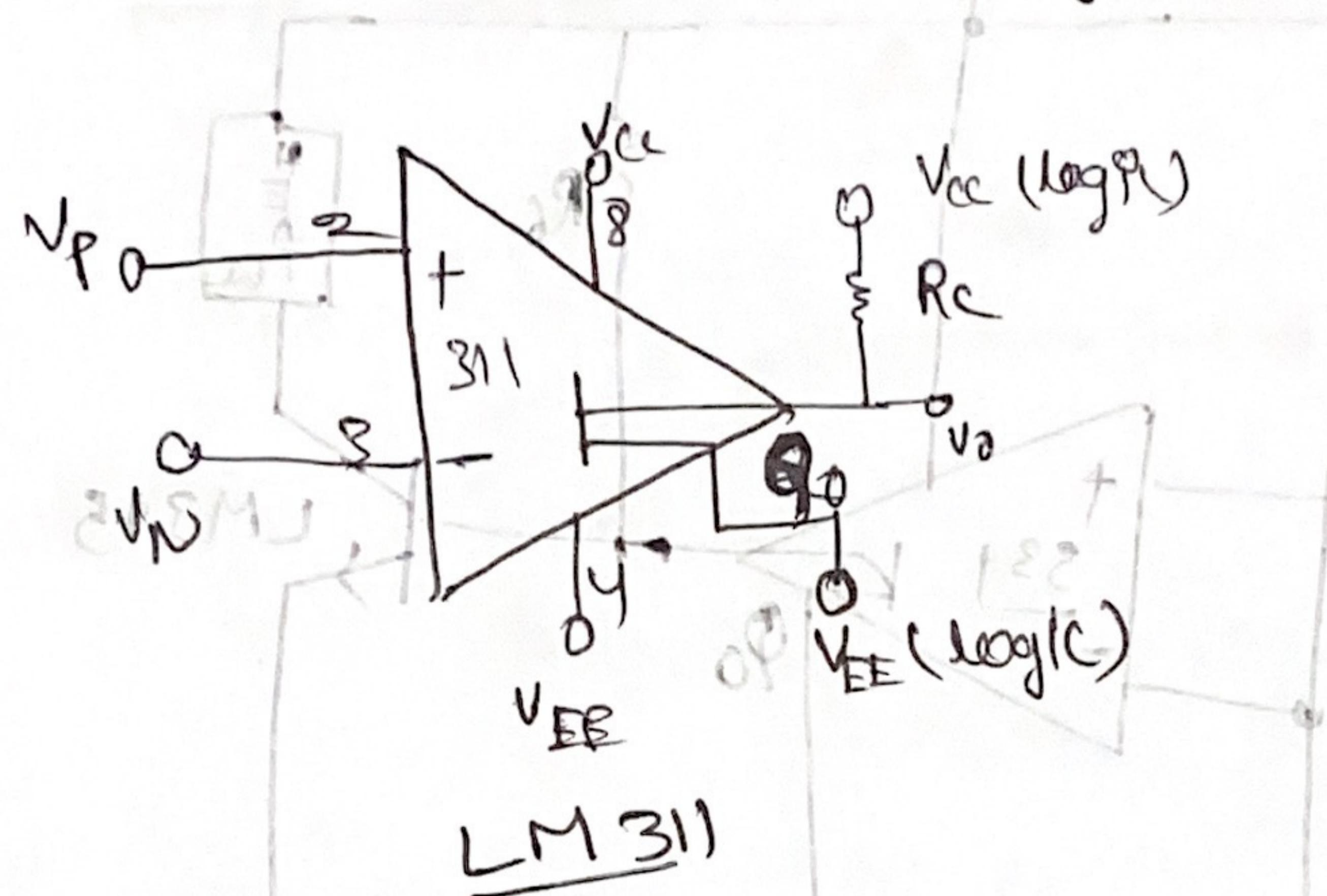

$V_P < V_N$,
 $V_0 = V_{CE(\text{sat})} + V_{EE(\text{logic})}$
 $V_0 = V_{OL} \approx V_{EE(\text{logic})}$.
 $V_P > V_N$,
 $V_I = V_{CC(\text{logic})} = V_{OH}$.
 VOH (output Low)
 VOH (output High)

Comparator Applications:

① user detector | I thus should detect or:

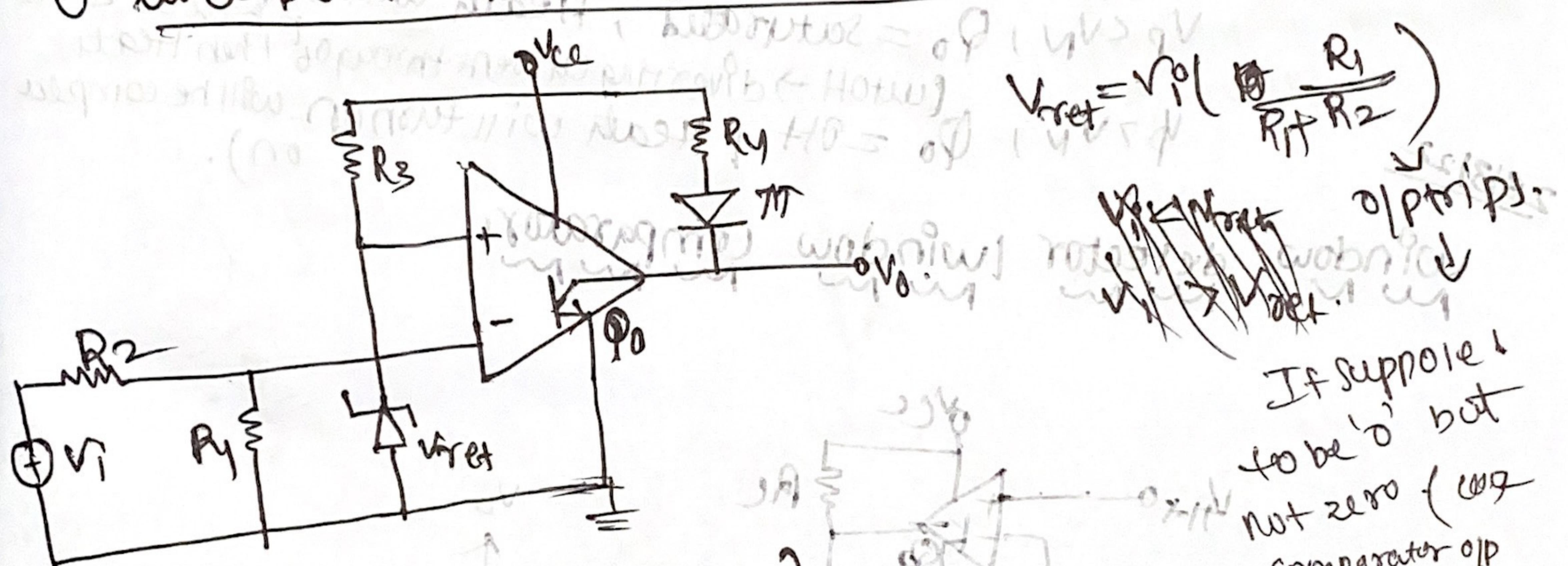

$$\text{Voltage (w.r.t } v_0) = V_T = \frac{R_1 + R_2}{R_1} \times V_{\text{out}}$$

$\gamma_0 < k \Rightarrow Q_0 = 0^{++}$, LEP is 0^{++}

$N < N_T \Rightarrow \varrho_0 = 0$ +, ϱ_0 ~~saturated~~, UEP grows.


It terminates all reversed the opij reversed

Then.

$V_i < V_T$ = saturated, LED glow,

$V_i > V_T$, $\phi_D = \text{off}$, LED is off.


inverting
and
non inverting
reversed

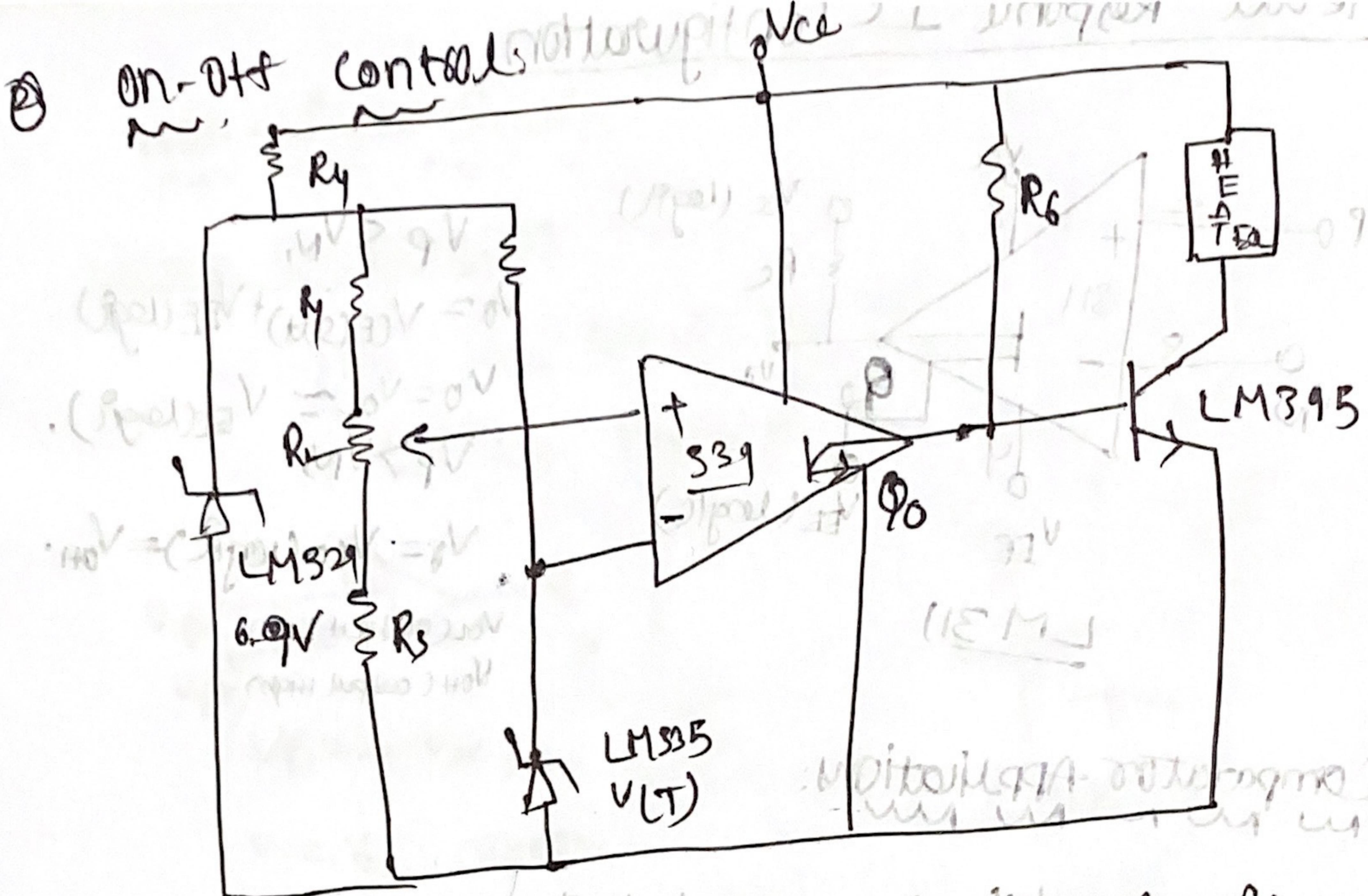

rotated blower will off to base of LM391
V_P < V_N, Q₀ = saturated, Heater will turn on
cutoff \rightarrow drawing current through then Heater
 $V_P > V_N$, Q₀ = off, Heater will turn on. will be complete
on).

29/3/22

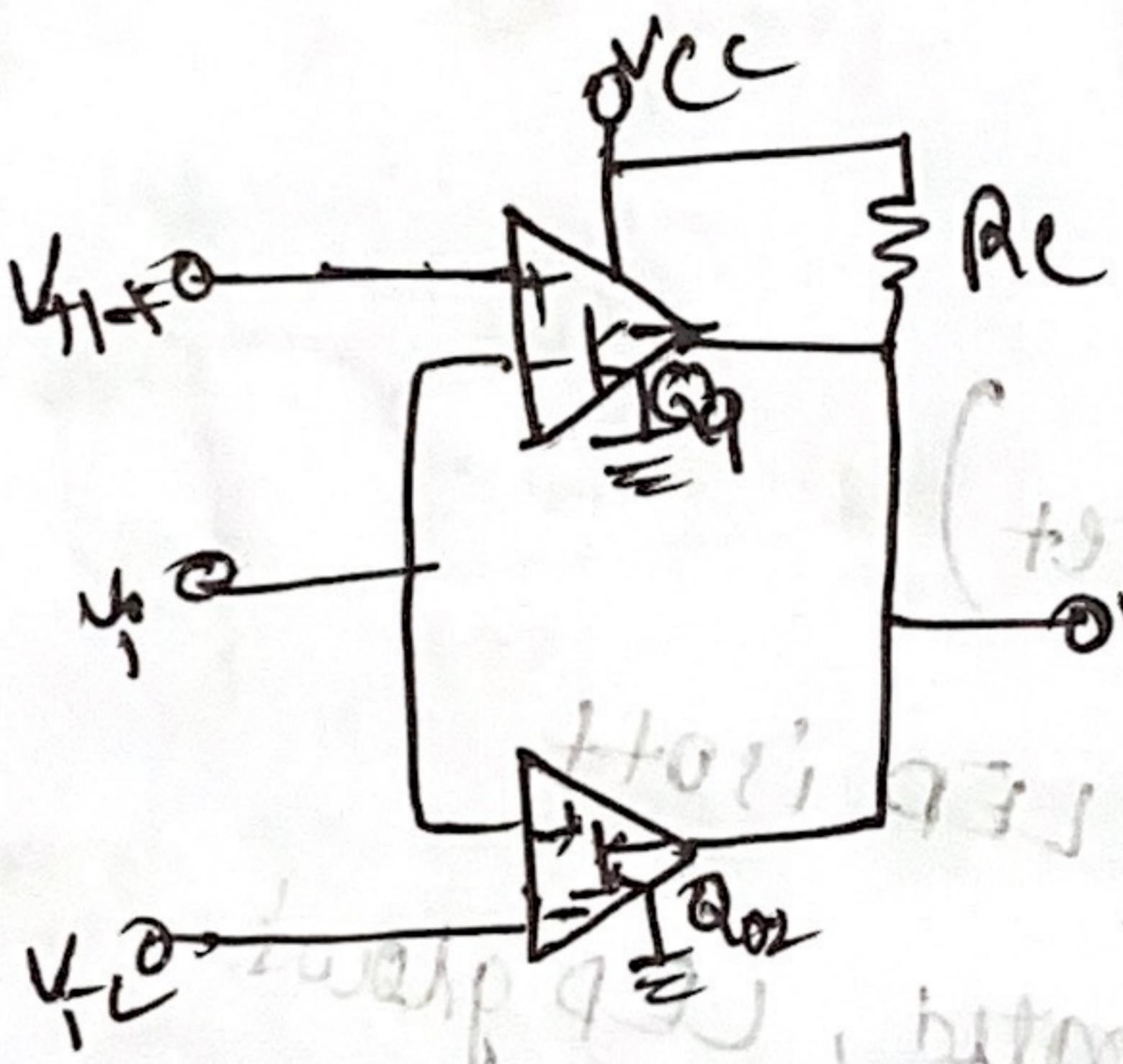~~312~~ window detector window compensator




$V_i > V_{\text{TH}} \Rightarrow Q_0$ (Saturated). ~~$V_{TL} < V_P < V_{TH}$~~

$$\forall i \in V, v_i < v_{TH},$$

→ window comparator is to indicate the when a given voltage falls within a specific band or window

Pulse width Modulation

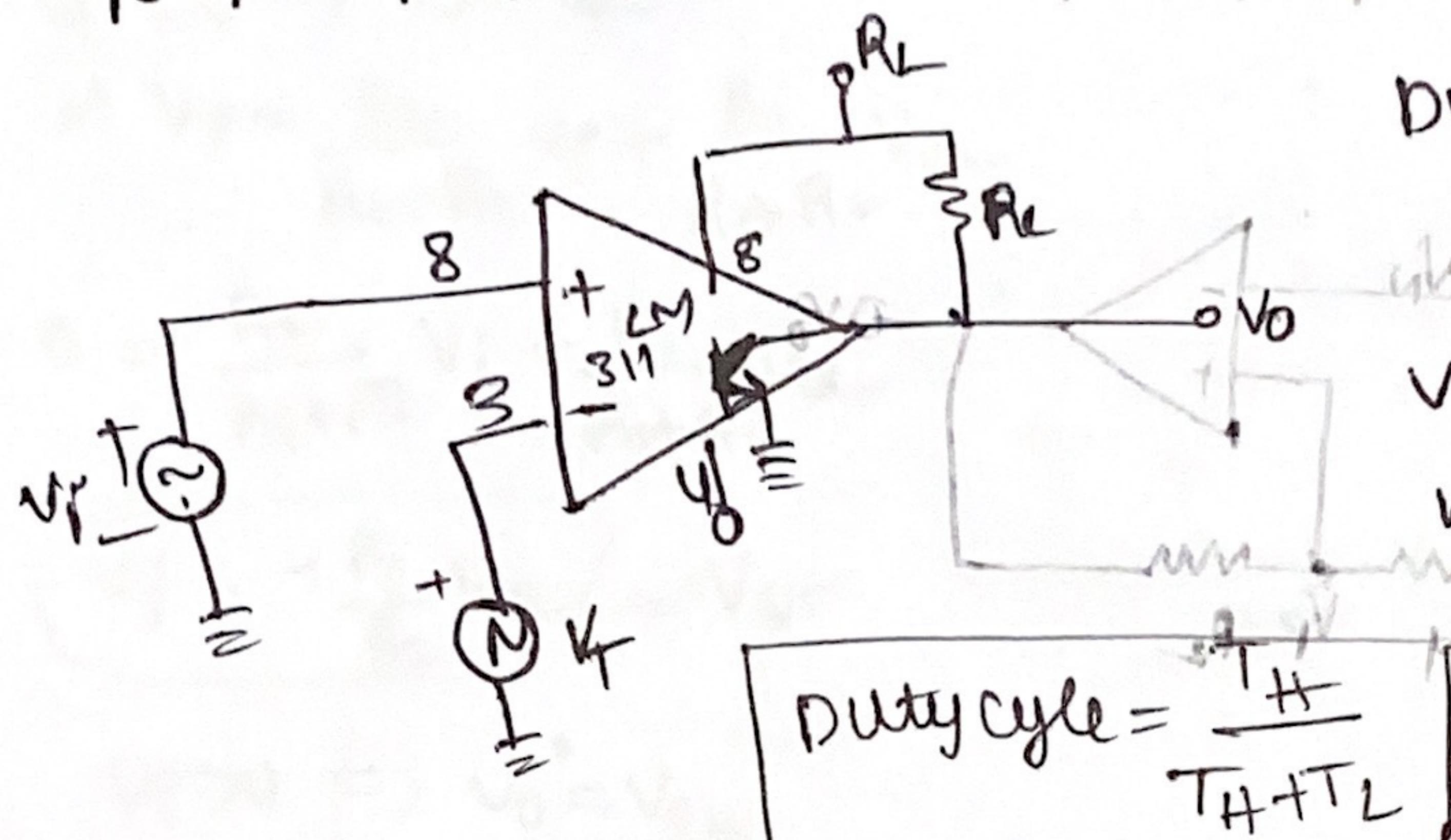

$$\text{Duty cycle} = \frac{T_H}{T_H + T_L} \times 100\% \quad (1)$$

$$V_P < V_T \Rightarrow Q_0$$

$$V_i > V_T \Rightarrow Q_1$$

$$\boxed{\text{Duty cycle} = \frac{T_H}{T_H + T_L}}$$


Schmitt Trigger:

Inverting summing trigger:

(+Vsat)

$$V_{CE} = R_3 = R_1 // R_2$$

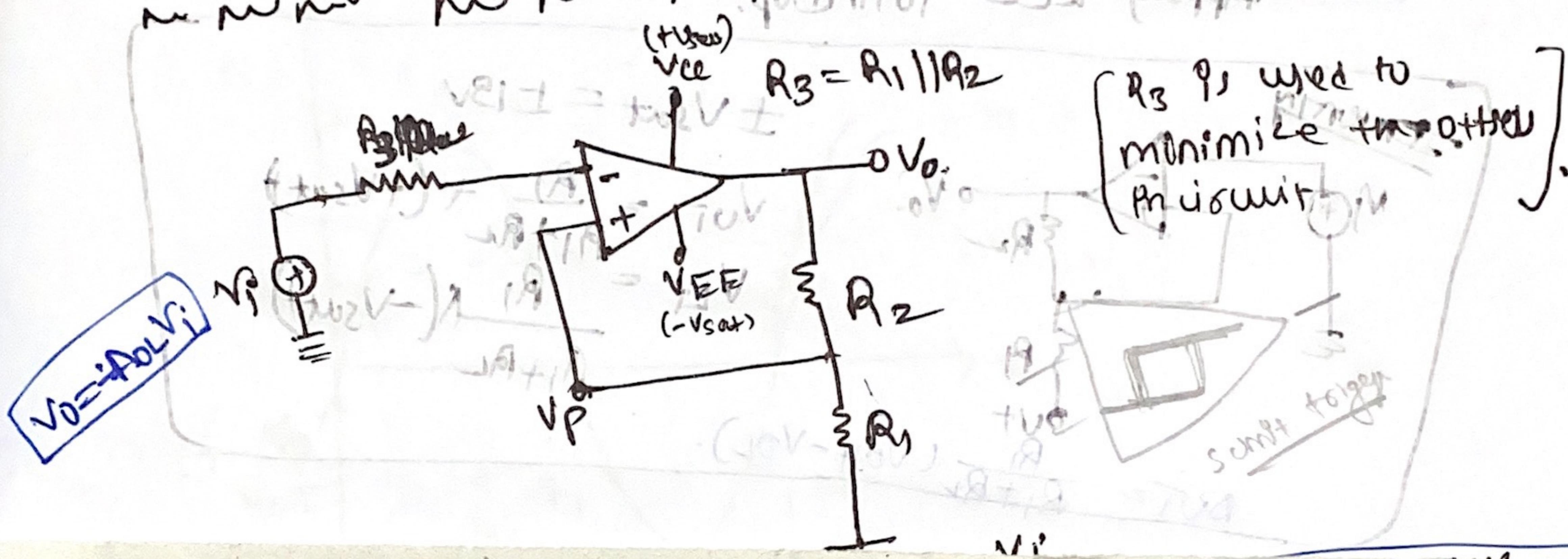R_3 is used to minimize the distortion in the circuit.



Assume,

$$V_0 = +Vsat \Rightarrow V_d = +Ve$$

$$V_f = V_{LT}$$

As soon as $V_i > V_{LT}$, $V_d = -Ve$

$$V_0 = -Vsat$$

$$V_f = V_{LT}$$

As long as $V_i > V_{LT}$ | $V_d = -Ve$

$$V_0 = -Vsat$$


$$V_f = V_{LT}$$

As soon as, $V_i < V_{LT} \Rightarrow V_d = +Ve$

$$V_0 = +Vsat$$


$$V_f = V_{LT}$$

Condition	P/P-V	O/P-V
$V_i < V_{LT}$	$V_d = +Ve$	$V_0 = +Vsat$
$V_i > V_{LT}$	$V_d = -Ve$	$V_0 = -Vsat$
$V_i < V_{LT}$	$V_d = -Ve$	$V_0 = -Vsat$
$V_i > V_{LT}$	$V_d = +Ve$	$V_0 = +Vsat$

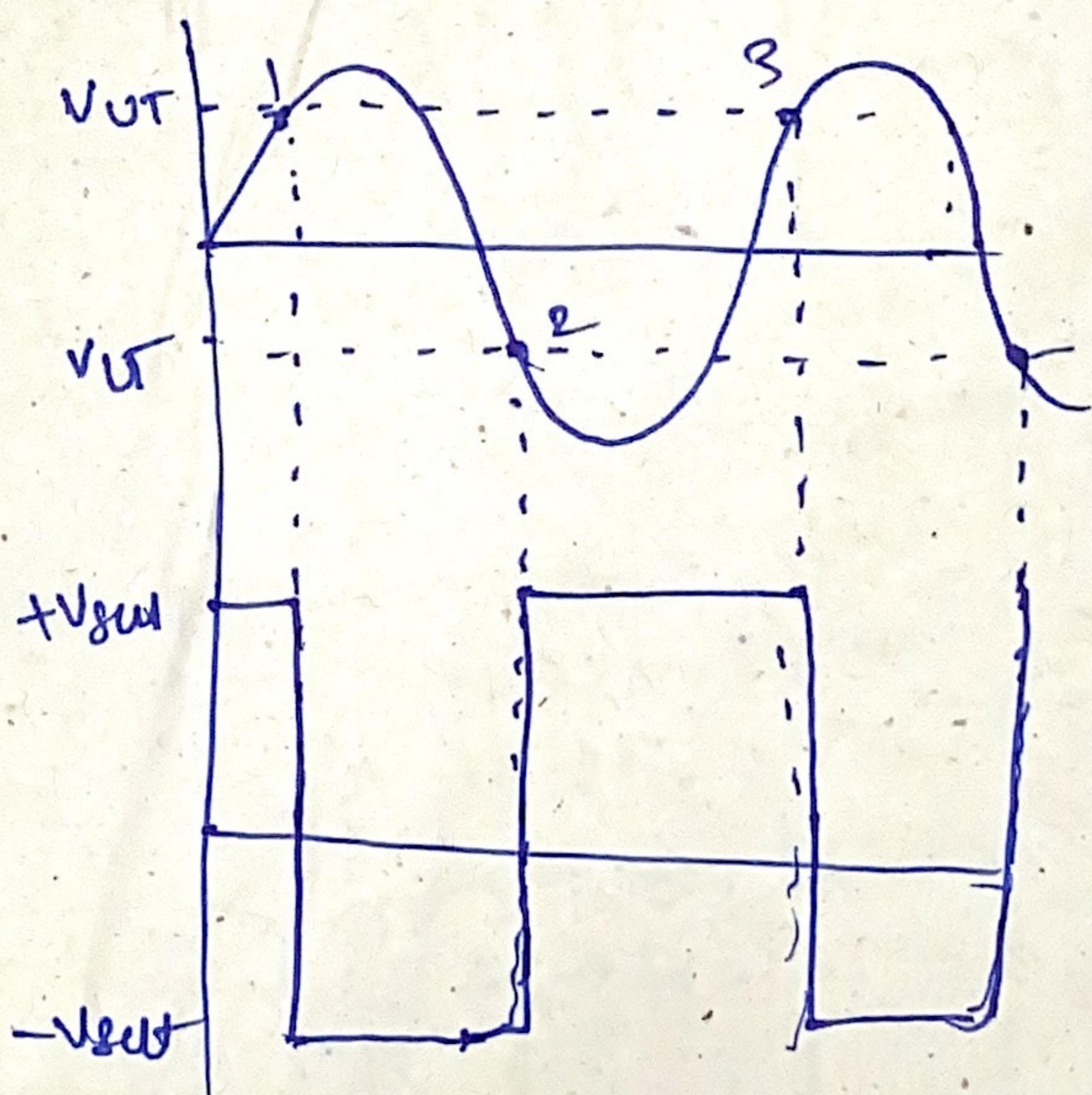

NON-INVERTING schmitt trigger: nichtinvertierendes Schmitt-Trigger

$$V_{out} = \frac{R_2}{R_1+R_2} V_{in}$$

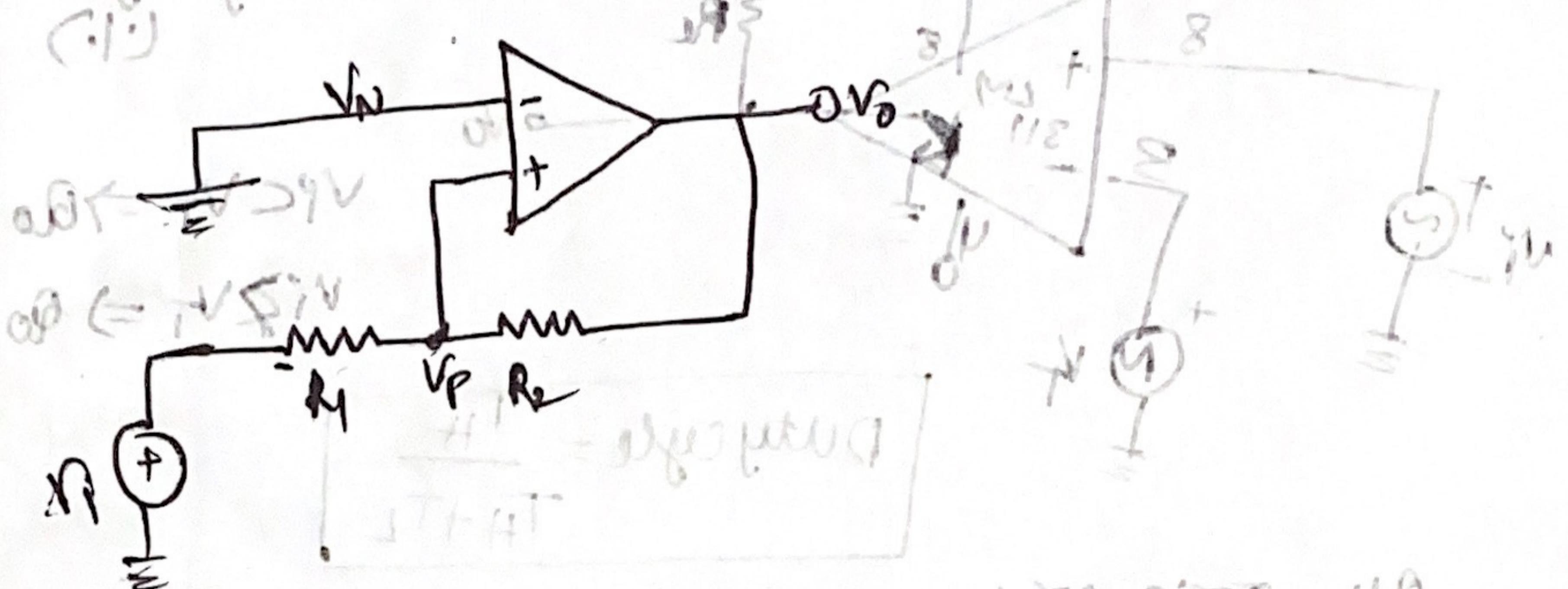

$$\text{Assume } V_i < V_p \Rightarrow V_o = V_{OH}$$

Apply KCL at node Np.

$$\pm V_{sat} = \pm 15V$$

$$V_{OT} = \frac{R_1}{R_1+R_2} + (+V_{sat})$$

$$V_{LT} = \frac{R_1}{R_1+R_2} (-V_{sat})$$

$$DV_T = \frac{R_1}{R_1+R_2} (V_{OH} - V_{OL})$$

$$\begin{cases} V_i > 0, V_o = V_{OH} \\ V_i < 0, V_o = V_{OL} \end{cases}$$

$$\frac{V_{OT}}{18} = \frac{18}{18+18} = 9V$$

$$\frac{V_i - V_p}{R_1} + \frac{V_o - V_p}{R_2} = 0$$

$$V_{iR_L} = V_{pR_2} + V_{oR_1} - V_{pR_1} = 0$$

$$V_{p(R_2 - R_f)} + V_{oR_1} + V_{iR_L} = 0$$

$$V_p = \frac{V_o R_1 + V_i R_2}{R_1 + R_2}$$

$$V_p = \frac{R_2}{R_1 + R_2} V_{iR_L} + \frac{R_1}{R_1 + R_2} V_o$$

3019122

$$V_i < 0 \Rightarrow V_o = V_{OL}$$

$$\Rightarrow V_p = \frac{R_2}{R_1+R_2} V_i + \frac{R_1}{R_1+R_2} V_{OL}$$


$$0 = \frac{R_2}{R_1+R_2} V_i + \frac{R_1}{R_1+R_2} V_{OL}$$

$$V_i = -\frac{R_1}{R_2} V_{OL} = V_{UR}$$


$$V_i > 0 \Rightarrow V_o = V_{OH}$$

$$V_i = \frac{R_1}{R_2} V_{OH} = V_{LT}$$

$$V_o = V_{OL}$$

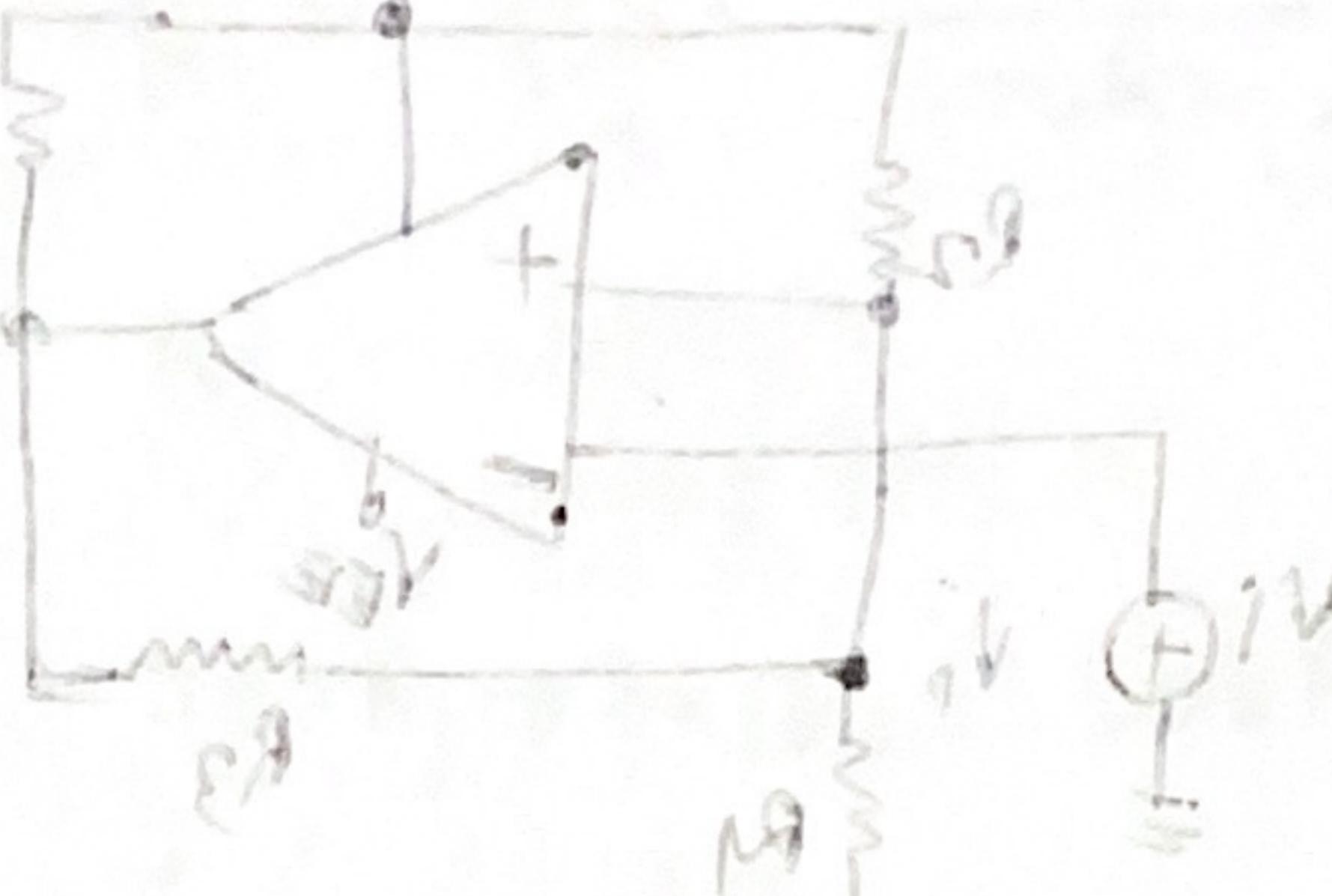

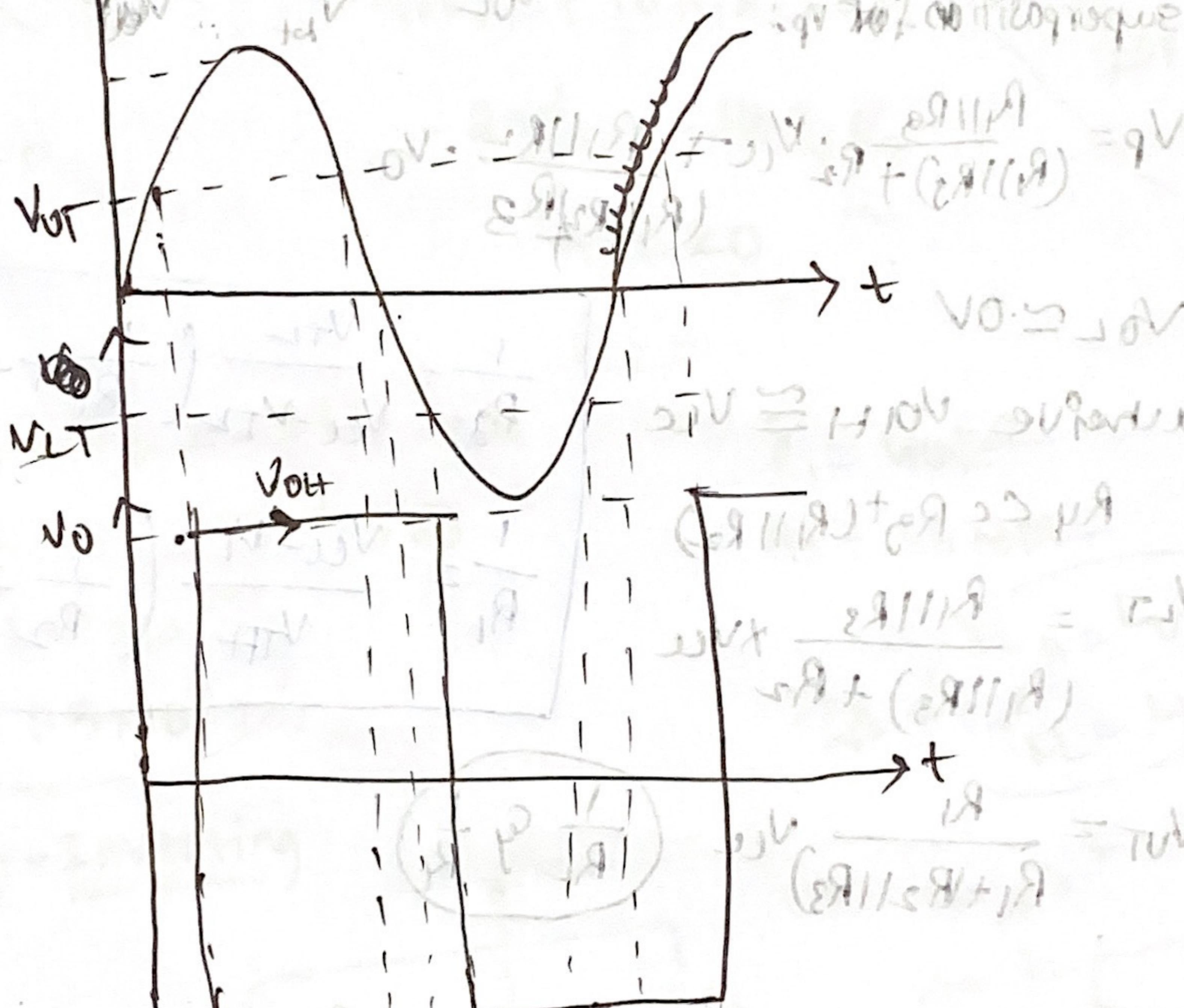
$$DV_T = \frac{R_1}{R_2} (V_{OH} - V_{OL})$$




Stable) $V_o = 10V$, after P88M4 rotarumos so robimos 10V
 $V_{OL} = 0V$, $V_{LT} = 10V$, $V_{UR} = 0V$, $V_{OH} = 10V$ rot M88M4 eti


Inverting

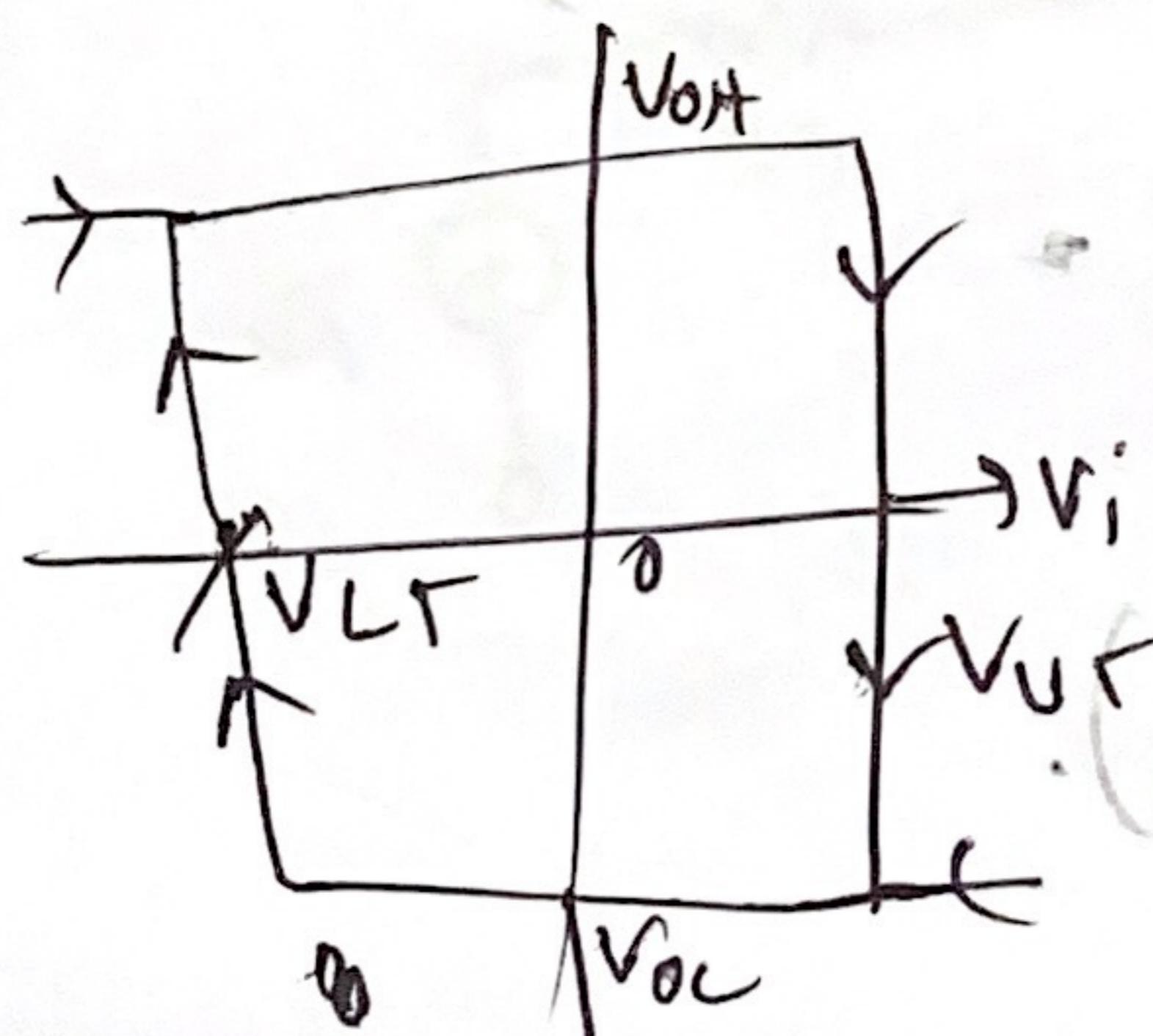

NonInverting

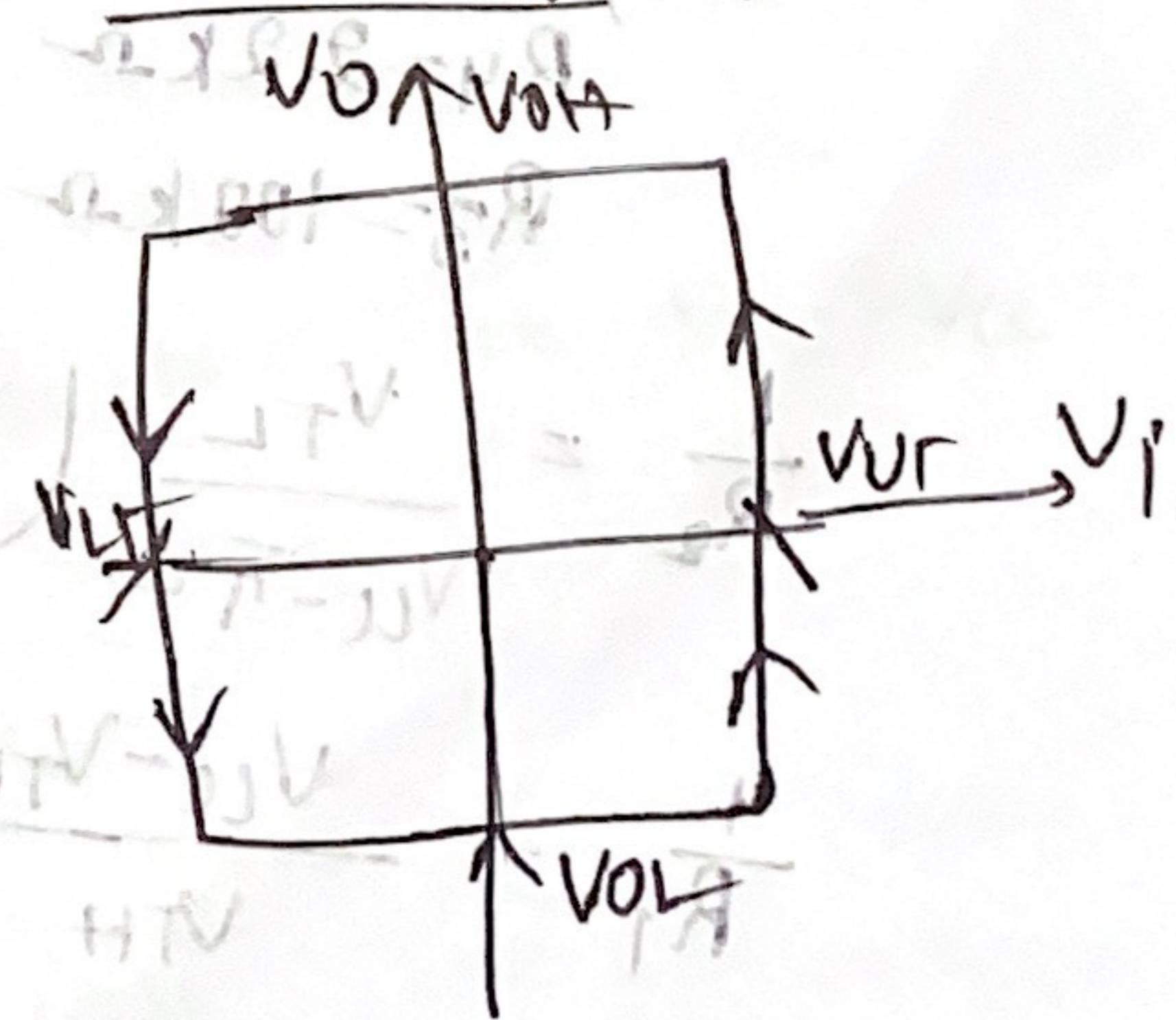

VTC offsetting (Voltage transfer curve)

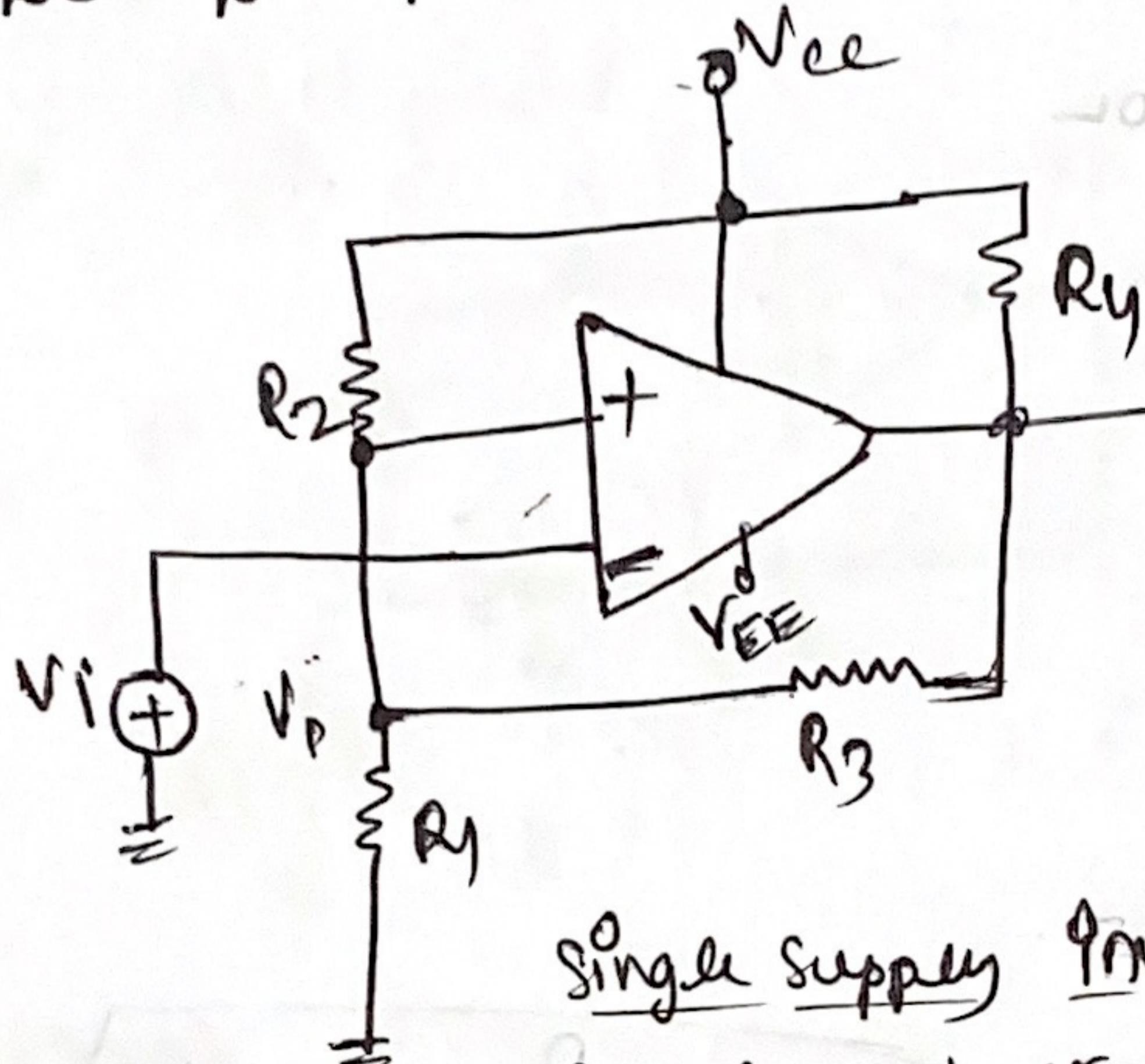

- apply superposition for v_p :


$$v_p = \frac{R_1 || R_3}{(R_1 || R_3) + R_2} v_{cc} + \frac{R_1 || R_2}{(R_1 || R_2) + R_3} v_o.$$

$$v_{ol} \approx 0V$$

to achieve $v_{oh} \approx v_{cc}$

$$\begin{aligned} v_o = v_{ol} = 0. \\ R_4 \ll R_3 + (R_1 || R_2) \\ \Rightarrow v_{lt} = \frac{R_1 || R_3}{(R_1 || R_3) + R_2} v_{cc} \end{aligned}$$

$$\begin{aligned} v_o = v_{oh} = v_{cc} \\ \Rightarrow v_{lt} = \frac{R_1}{R_1 + R_2 || R_3} v_{cc} \end{aligned}$$

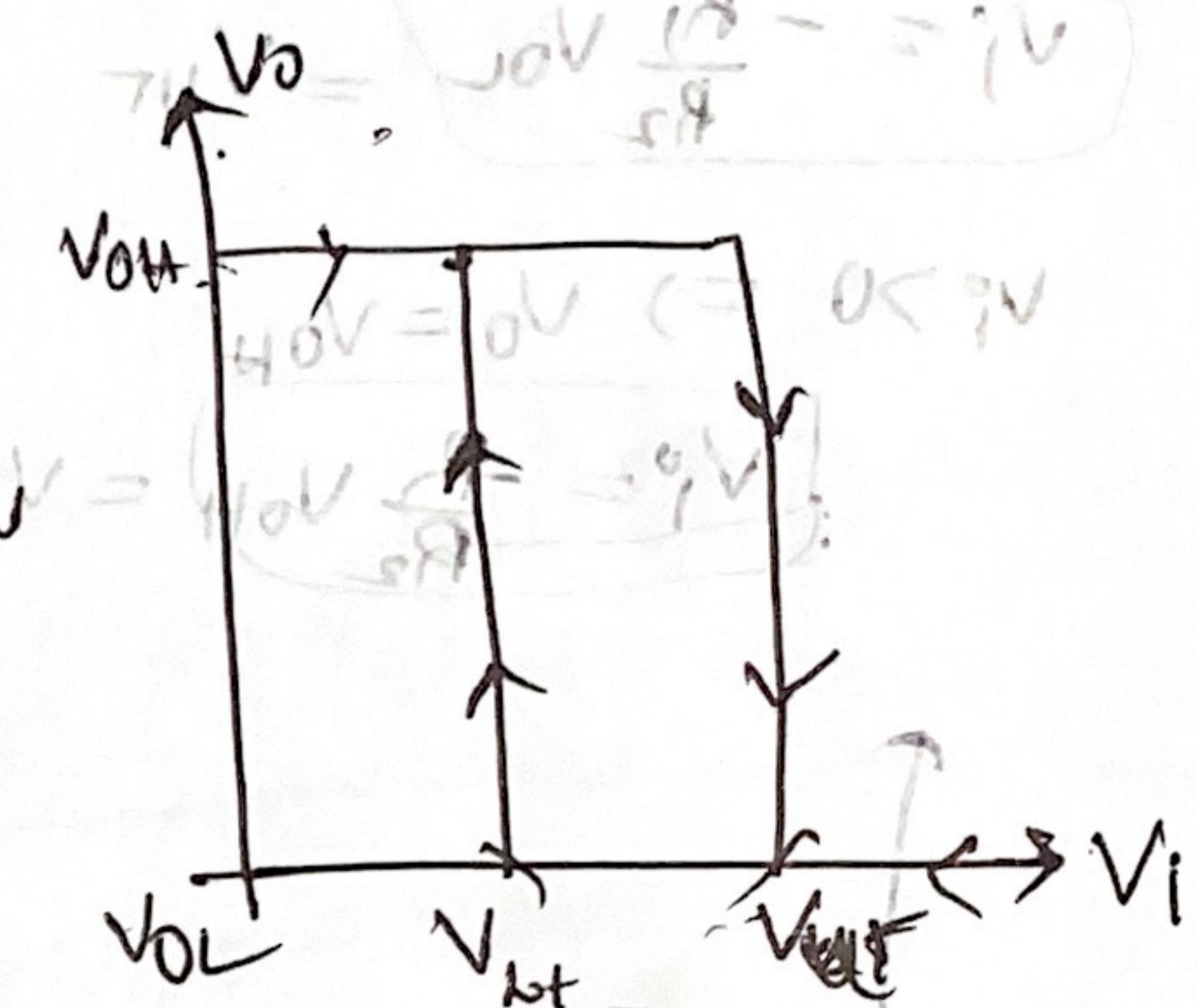

$$\begin{aligned} \frac{1}{R_2} &= \frac{v_{tl}}{v_{cc} - v_{tl}} \left(\frac{1}{R_1} + \frac{1}{R_3} \right) \\ \frac{1}{R_1} &= \frac{v_{cc} - v_{th}}{v_{th}} \left(\frac{1}{R_2} + \frac{1}{R_3} \right). \end{aligned}$$

$$\frac{1}{R_2} \approx \frac{1}{R_3}$$

31/3/22

Q1) consider a comparator LM339 with $v_{cc} = 5V$. calculate the resistances for $v_{ol} = 0V$, $v_{oh} = 5V$, $v_{tl} = 1.5V$, $v_{th} = 2.5V$

Ans)


assume,

$$R_4 = 2.2k\Omega \quad \text{so } R_4 \ll R_3 (R_1 || R_2)$$

$$R_3 = 100k\Omega$$

$$\frac{1}{R_2} = \frac{v_{tl}}{v_{cc} - v_{tl}} \left(\frac{1}{R_1} + \frac{1}{R_3} \right)$$
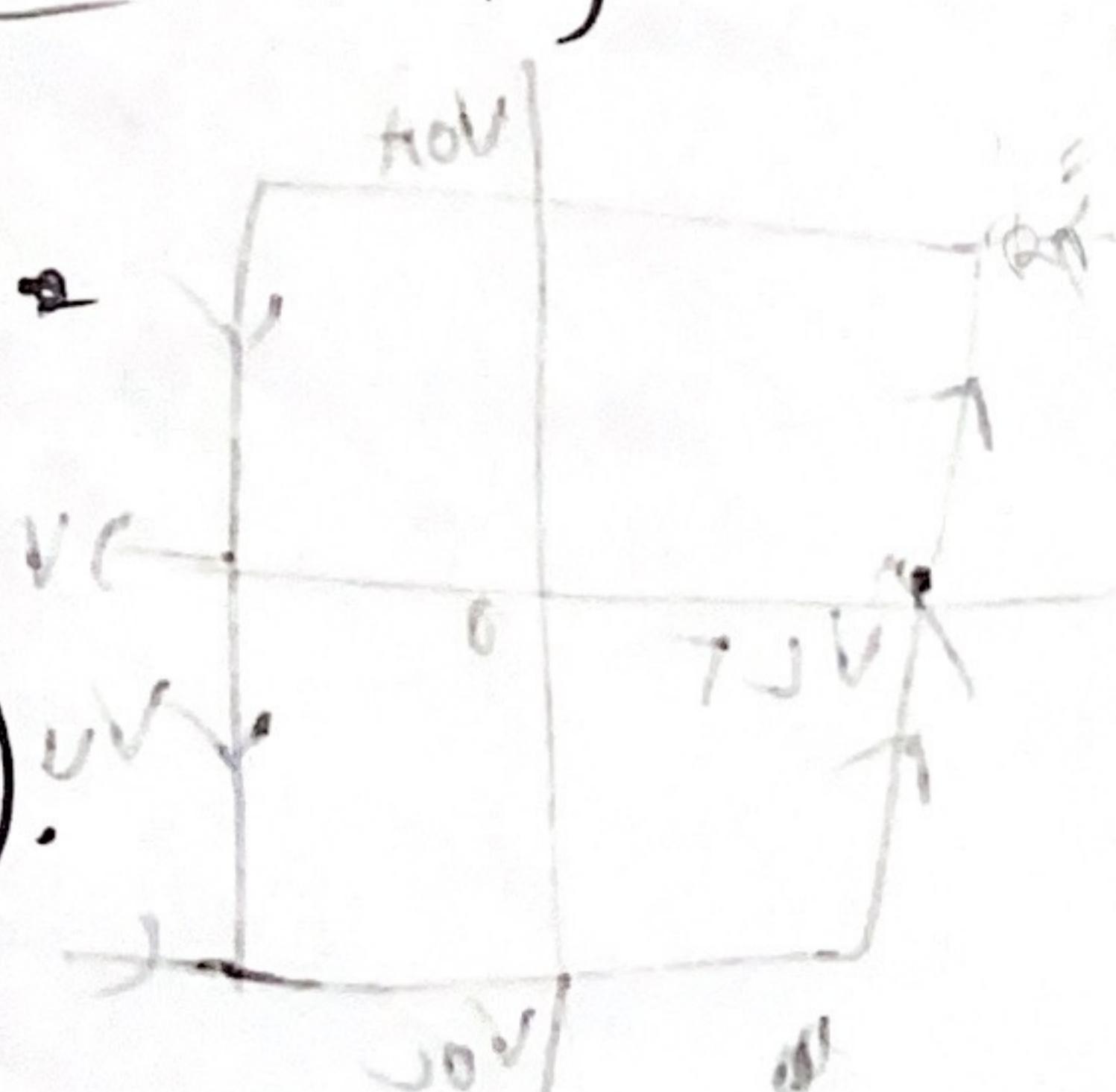
$$\frac{1}{R_1} = \frac{v_{cc} - v_{th}}{v_{th}} \left(\frac{1}{R_2} + \frac{1}{R_3} \right).$$



$$\frac{1}{R_2} = \frac{1.5}{5-1.5} \left(\frac{1}{R_1} + \frac{1}{100} \right) \quad \frac{1}{R_1} = \frac{5-2.5}{2.5} \left(\frac{1}{R_2} + \frac{1}{100} \right)$$

$$\frac{1}{R_2} = \frac{1.5}{3.5} \left(\frac{100+R_1}{100R_1} \right) \quad \frac{1}{R_1} = \frac{3.5}{2.5} \left(\frac{100+R_2}{100R_2} \right)$$

$$R_2 = \frac{7}{3} \left(\frac{100R_1}{100+R_1} \right) \quad R_1 = \frac{500R_2}{700+7R_2}$$

$$300R_2 + 3R_1R_2 = 700R_1 \quad 700R_1 + 7R_1R_2 = 500R_2 \rightarrow \textcircled{2}$$

~~$$-700R_1 + 300R_2 + 3R_1R_2 = 0$$~~

~~$$700R_1 - 500R_2 + 7R_1R_2 = 0$$~~

~~$$-200R_2 + 10R_1R_2 = 0$$~~

~~$$-20R_2 = -10R_1R_2$$~~

~~$$R_1 = 20$$~~

~~$$R_2 =$$~~



~~$$R_1 = 40\text{ k}\Omega$$~~

~~$$R_2 = 66.66\text{ k}\Omega$$~~

$$a = 2.5 \times 10^{-5}$$

$$b = 1.5 \times 10^3$$

NON-INVERTING

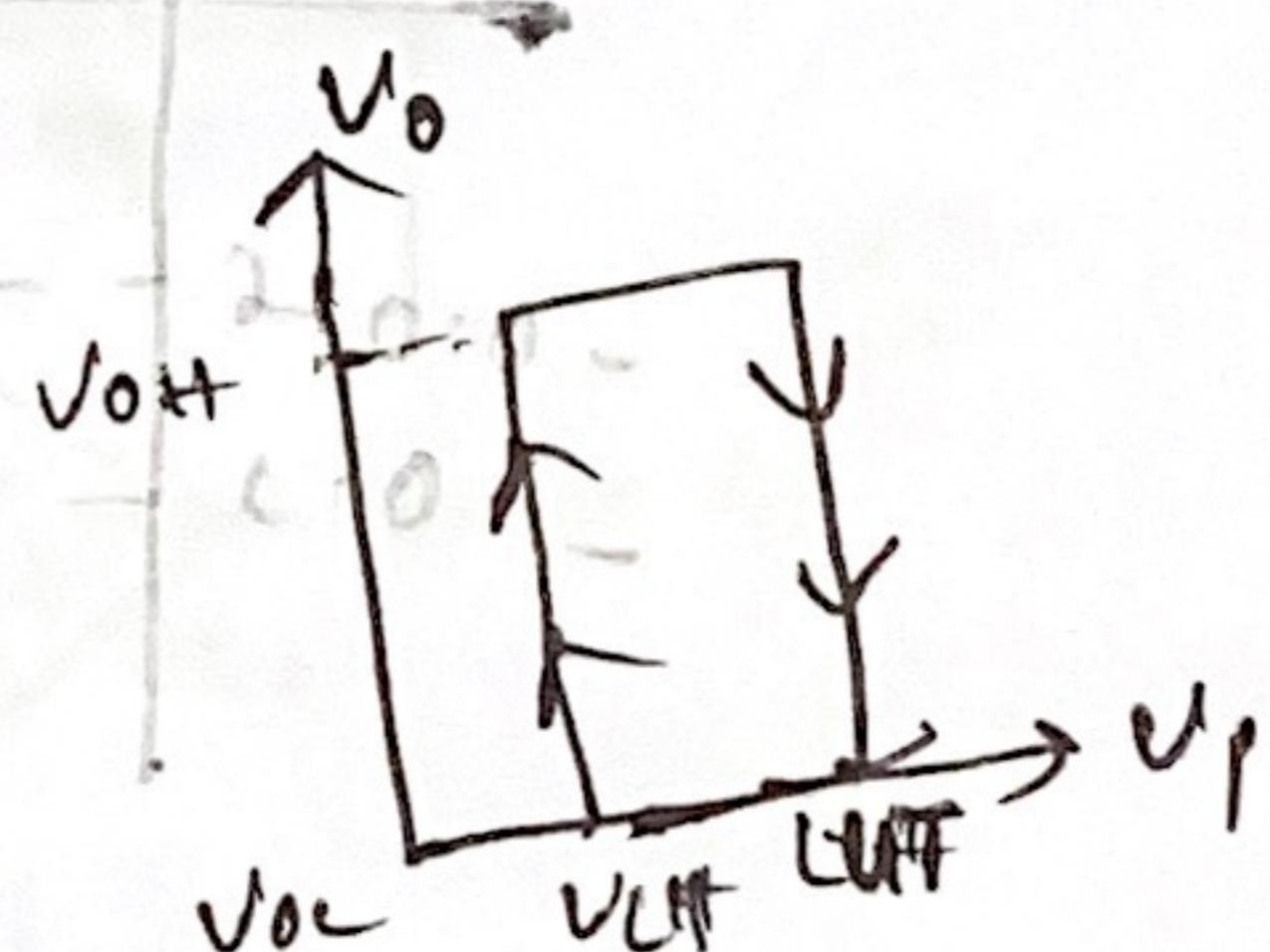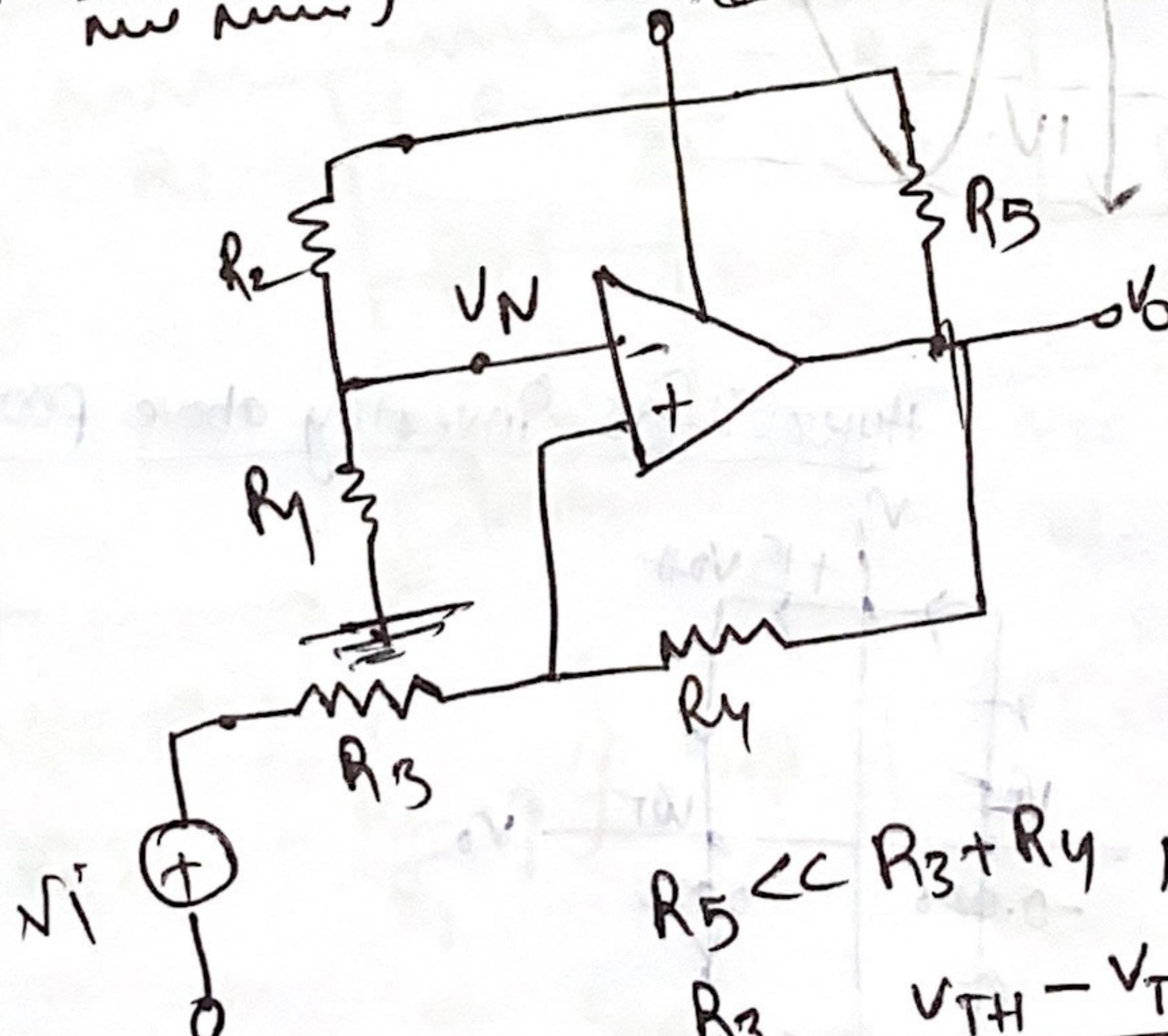

$R_5 \ll R_3 + R_4$, to ensure $V_{OH} = V_{CC}$

$$\frac{R_3}{R_4} = \frac{V_{TH} - V_{TL}}{V_{CC}}$$

$$\frac{R_2}{R_1} = \frac{V_{CC} - V_{TL}}{V_{TH}}$$

(Q2) Consider a ^{No. 3} inverting Schmitt trigger circuit with $R_1 = 100\text{ k}\Omega$, $R_2 = 56\text{ k}\Omega = 56 \times 10^3$, $V_{in} = 1\text{ V P-P}$, $\pm V_{cc} = \pm 15\text{ V}$ and determine threshold voltages, V_{LT} and V_{HT} and draw the hysteresis graph. O/P waveform

Ans)

$$V_{out} = \frac{R_1 R_3}{R_1 R_3 + R_2} \times V_{cc}$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} \times V_{cc}$$

$$= \frac{R_1 R_3}{R_1 R_3 + R_2 (R_1 + R_3)} \times V_{cc} \quad (\text{Assume } R_3 = 100\text{ k}\Omega)$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_{cc} \quad \pm V_{cc} = \pm 15$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} V_{cc} \quad + V_{cc} = 15\text{ V}$$

$$- V_{cc} = V_{OL}$$


$$V_{LT} = \frac{100 \times 10^3}{100 + 56 \times 10^3} \times 15$$

$$V_{LT} = \frac{100}{56 \times 10^3} \times 15$$

$$= -0.026$$

$$= \frac{100}{56 \times 10^3} \times 15 \approx 0.026$$


V_{HT}

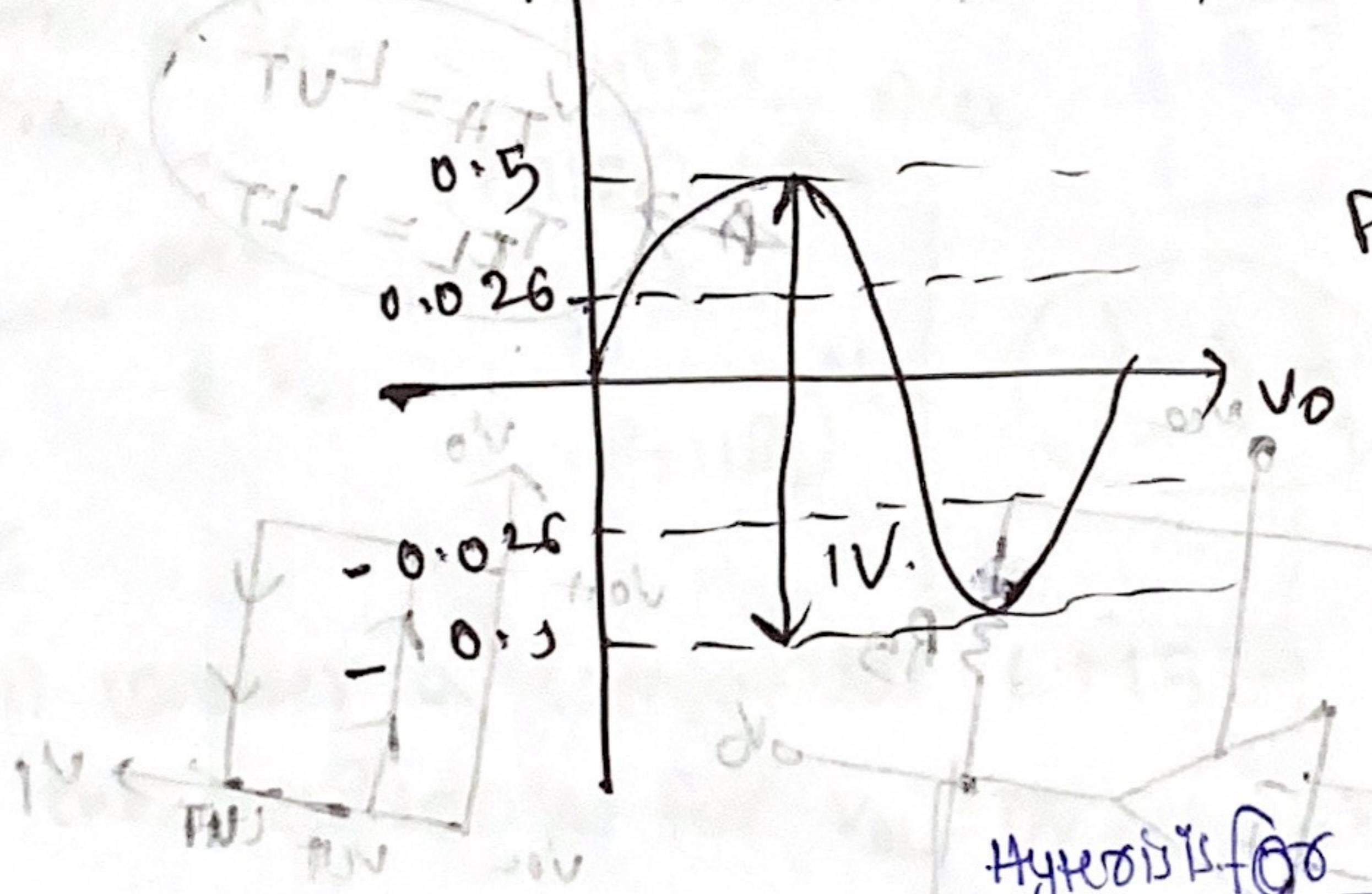

Peak to Peak is 1


so, 0.5 = peak

Hysteresis for Inverting above point.

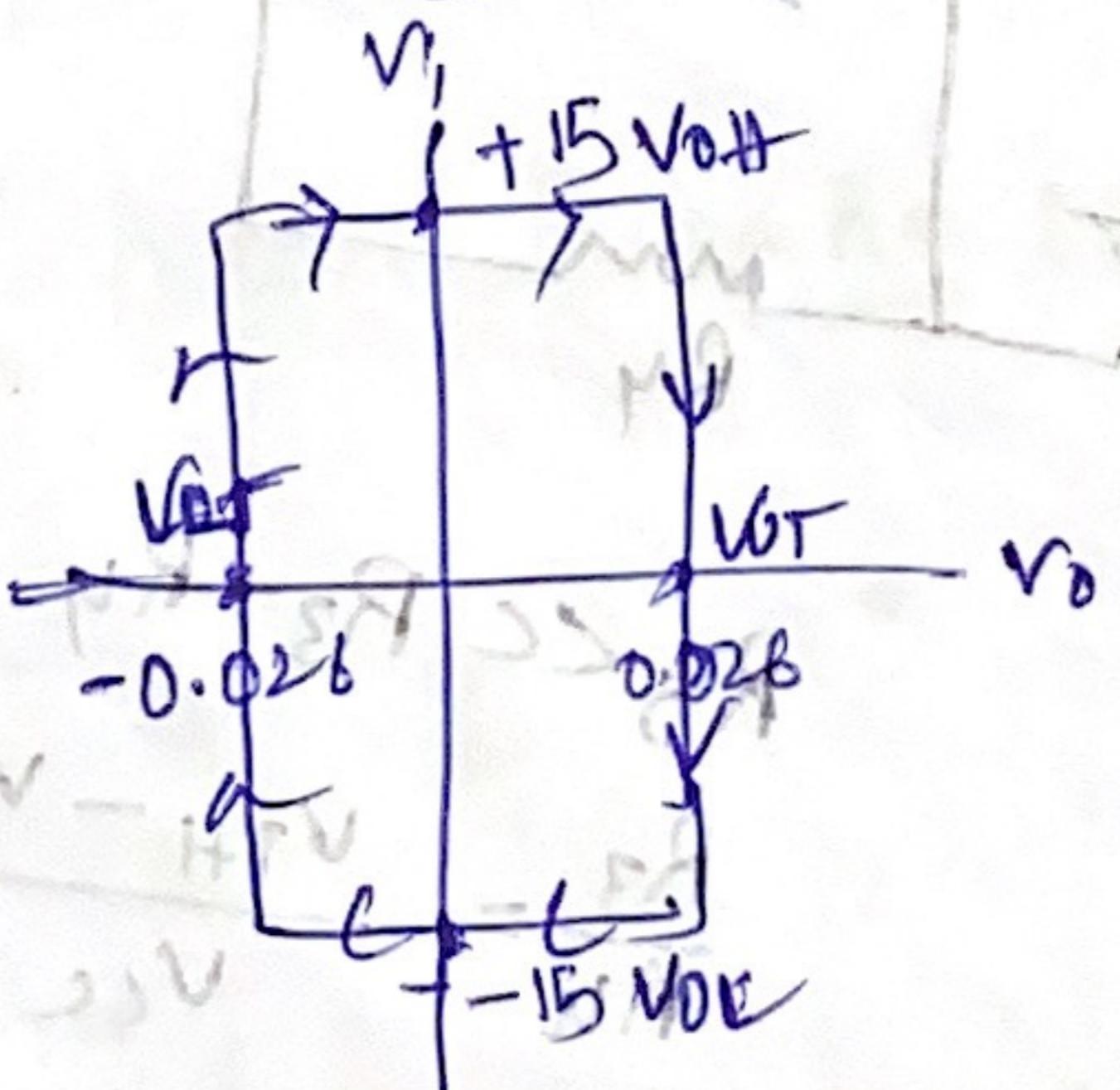

Precision Rectifiers

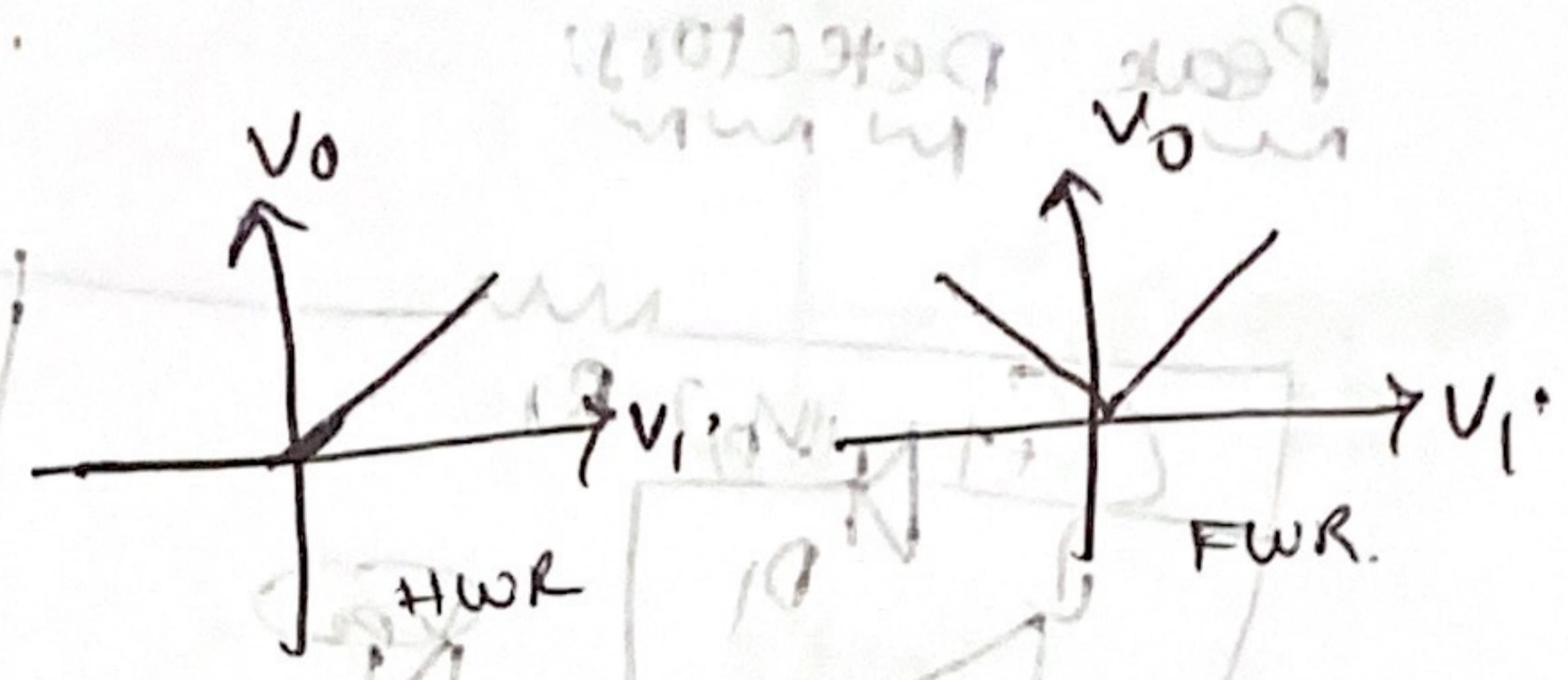- ① Half wave Rectifier.
- ② full wave Rectifier.




- ① Half wave Rectifier:

$$V_{OA} = V_0 + V_{D(ON)}$$


$$\Rightarrow V_i < 0 \Rightarrow V_0 \approx V_0 + 0.7V$$

$$V_i > 0 \Rightarrow +ve \text{ PIP} \Rightarrow V_0 = V_i$$

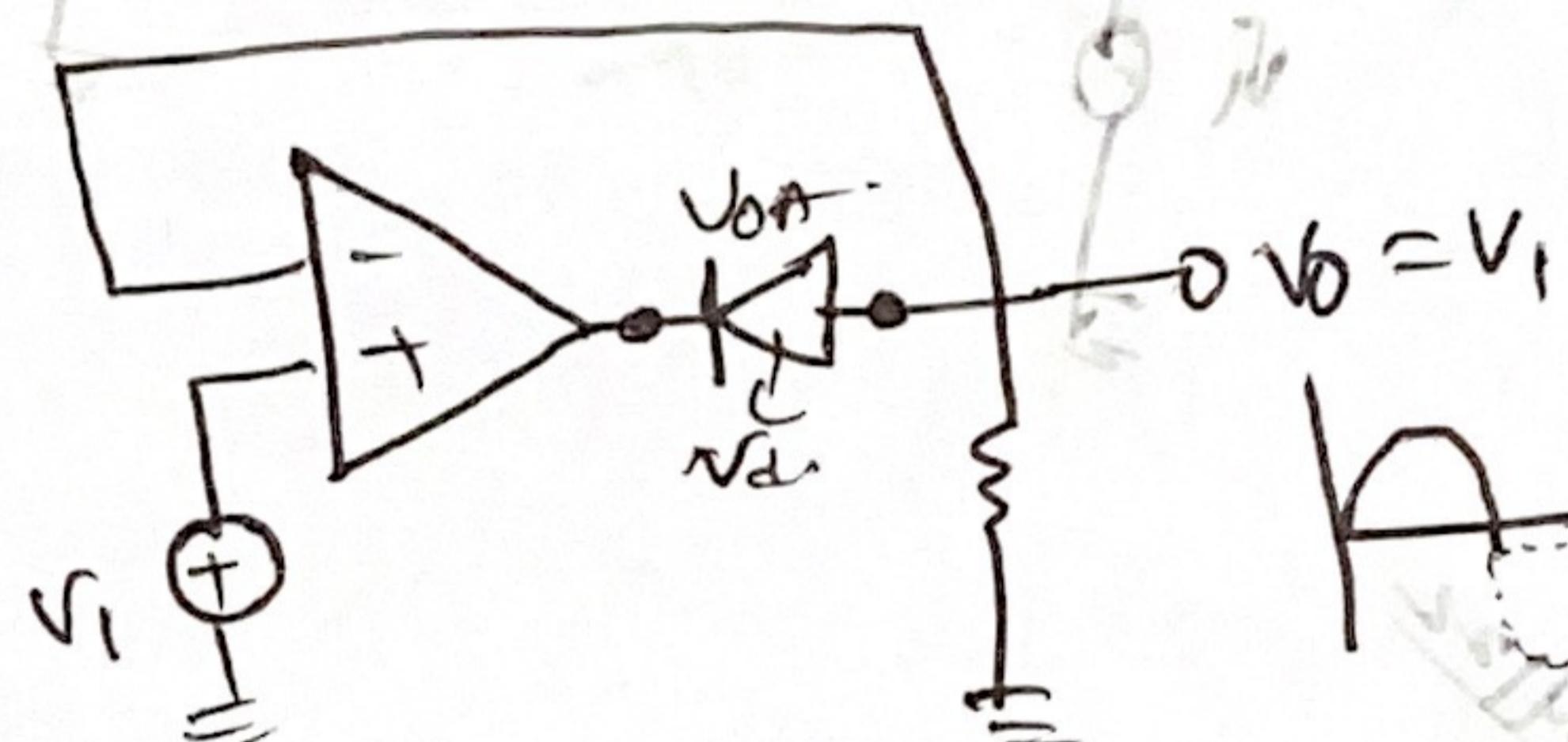$V_0 = V_i$ for $V_i > 0$
 $V_0 = -V_i$ for $V_i < 0$ $\Rightarrow V_0 = -V_i$



Improved HWR:

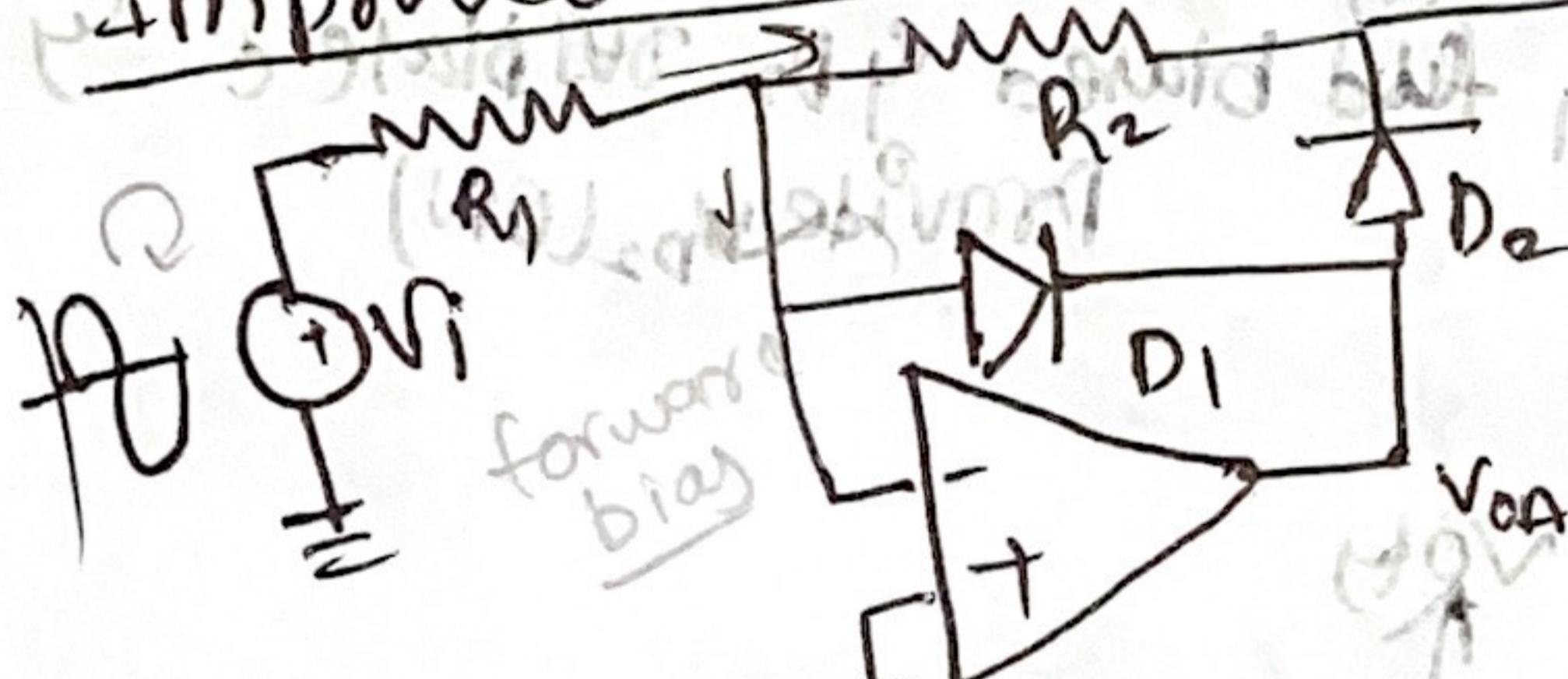


$$V_{OA} = V_i + V_{D(ON)}$$

$$V_i > 0 \Rightarrow V_{OA} = V_i + V_{D(ON)}$$

$$V_i < 0 \Rightarrow V_0 = -\frac{R_2}{R_1} V_i$$

- ② Full wave Rectifier:

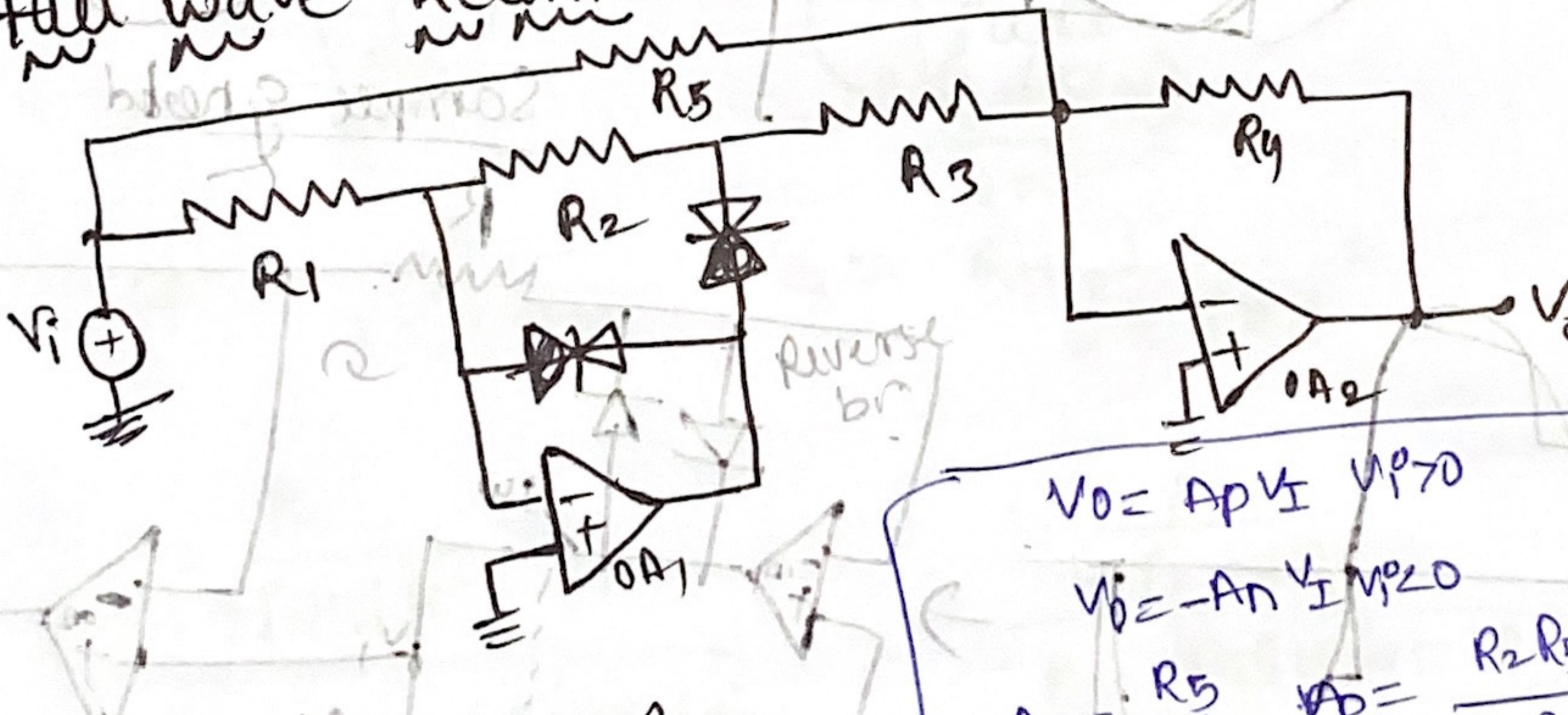

$$V_0 = AP V_i \quad V_i > 0$$

$$V_0 = -AP V_i \quad V_i < 0$$

$$AP = \frac{R_2 R_5}{R_1 R_3} \quad A_n = \frac{R_5}{R_3}$$


$$V_0 = -\frac{R_2}{R_5} V_i - \frac{R_1}{R_3} V_{HW}$$

$$V_{HW} = V_{D(ON)} + \frac{R_2}{R_1} V_i$$

$$V_{D(ON)} = V_D \quad V_{HW} = V_D + \frac{R_2}{R_1} V_i$$

$$V_0 = V_i / A_n$$



Peak Detectors

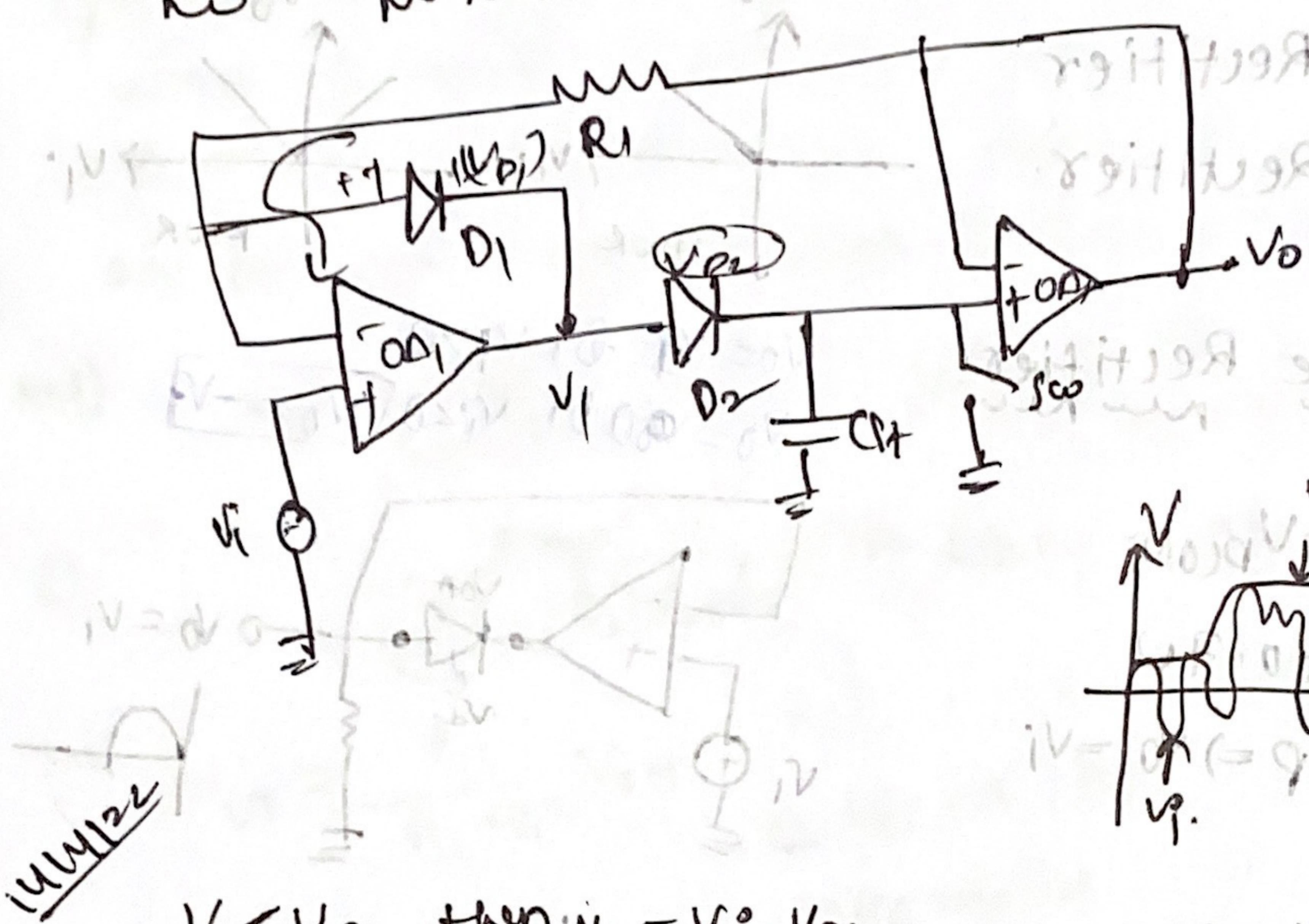



$$V_1 < V_{D2}, \text{ then } V_1 = V_i - V_{D1}.$$

$V_1 < 0$, $V_0 = V_1 + V_{D2}$. $V_1 > 0$, D_1 feed biased by D_2 dissipate energy provide $V_{D2}(\text{ON})$.

Sample & Hold Amplifiers

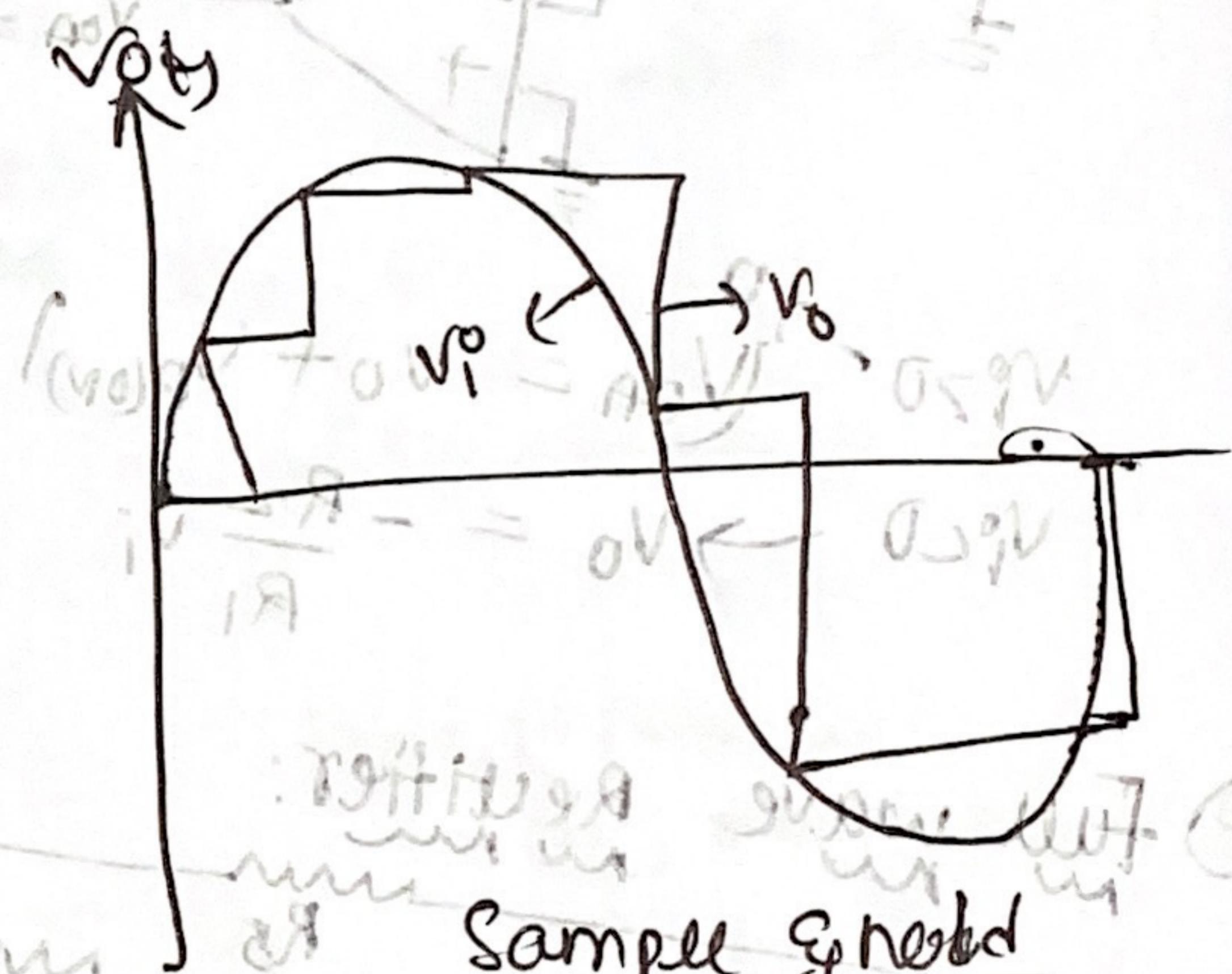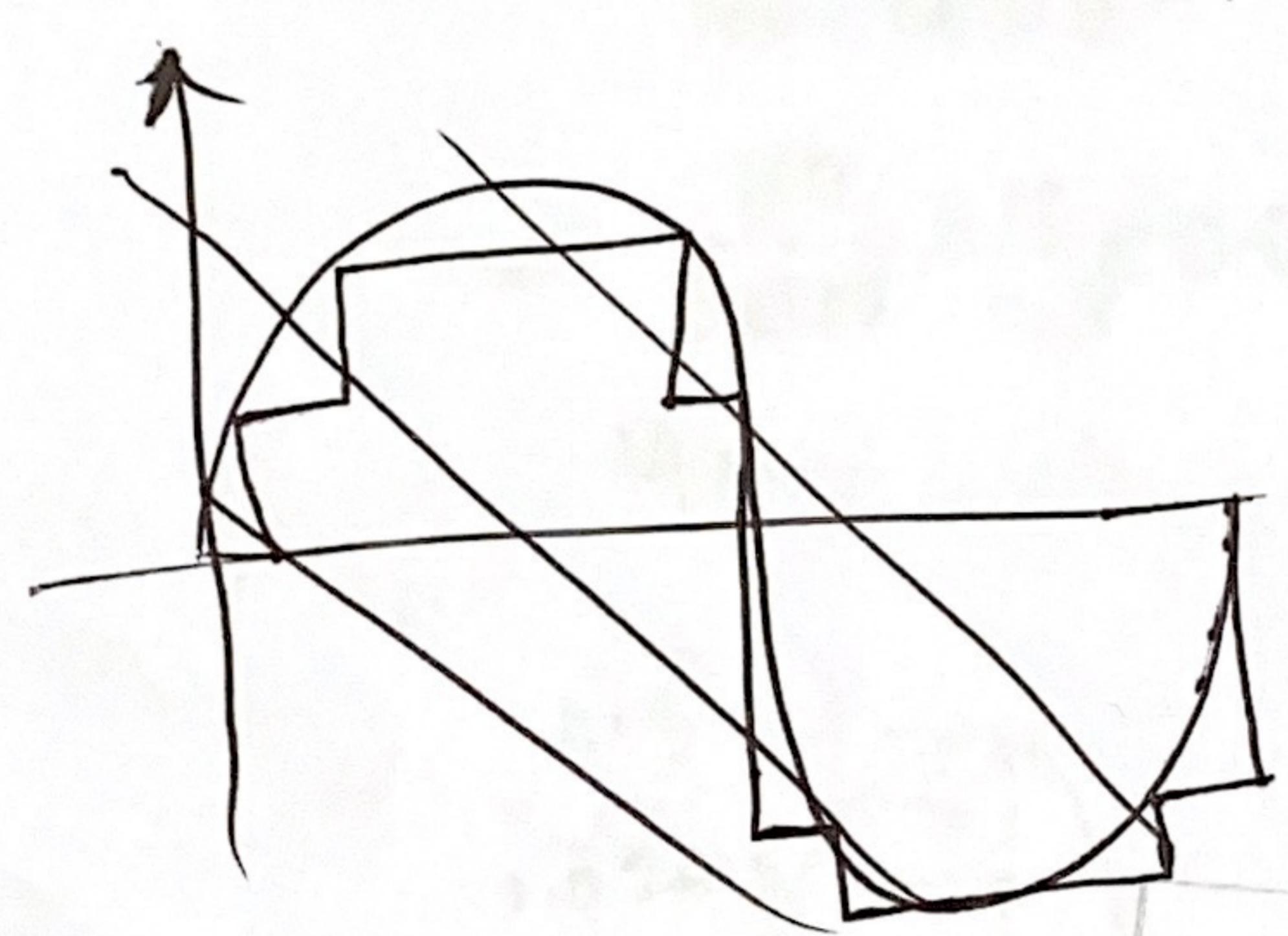

Sample & Hold

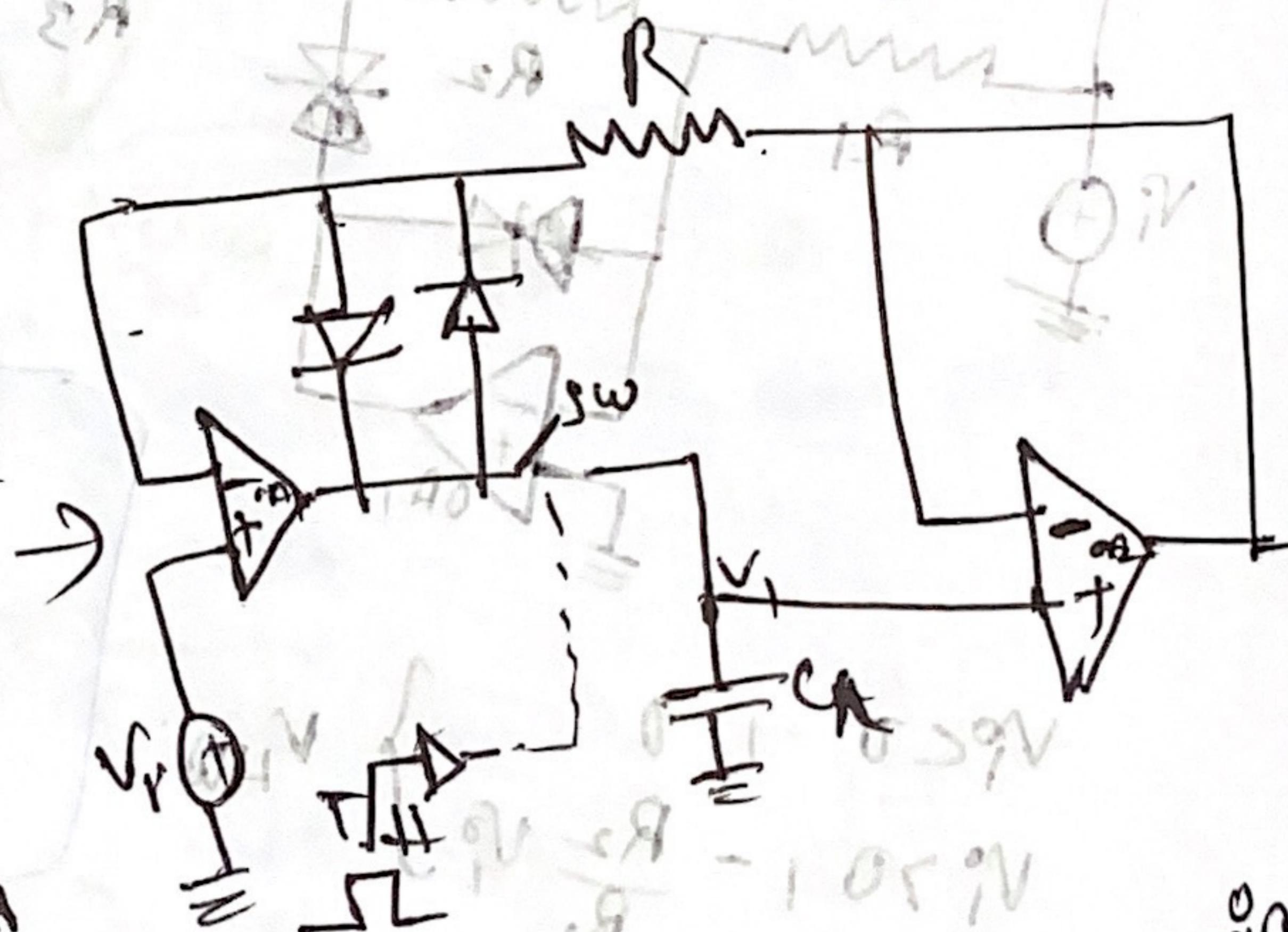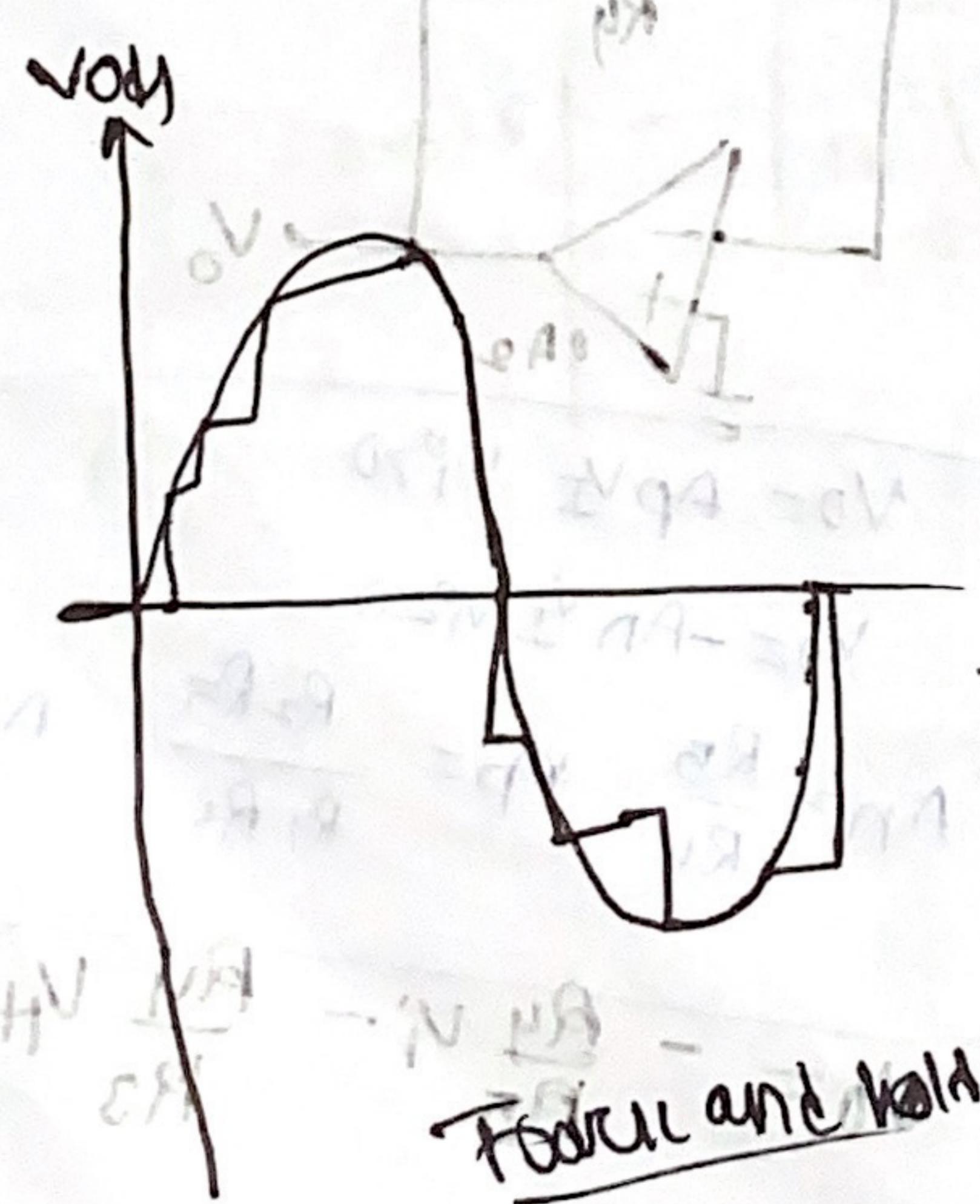



for track switch is closed, then the feedback path is switch - R_f - R_{f2} they

For hold the voltage at 4 point will be V_0 as switches open.

(At $N=0$)

Sine wave generators.

when Bridge oscillators:

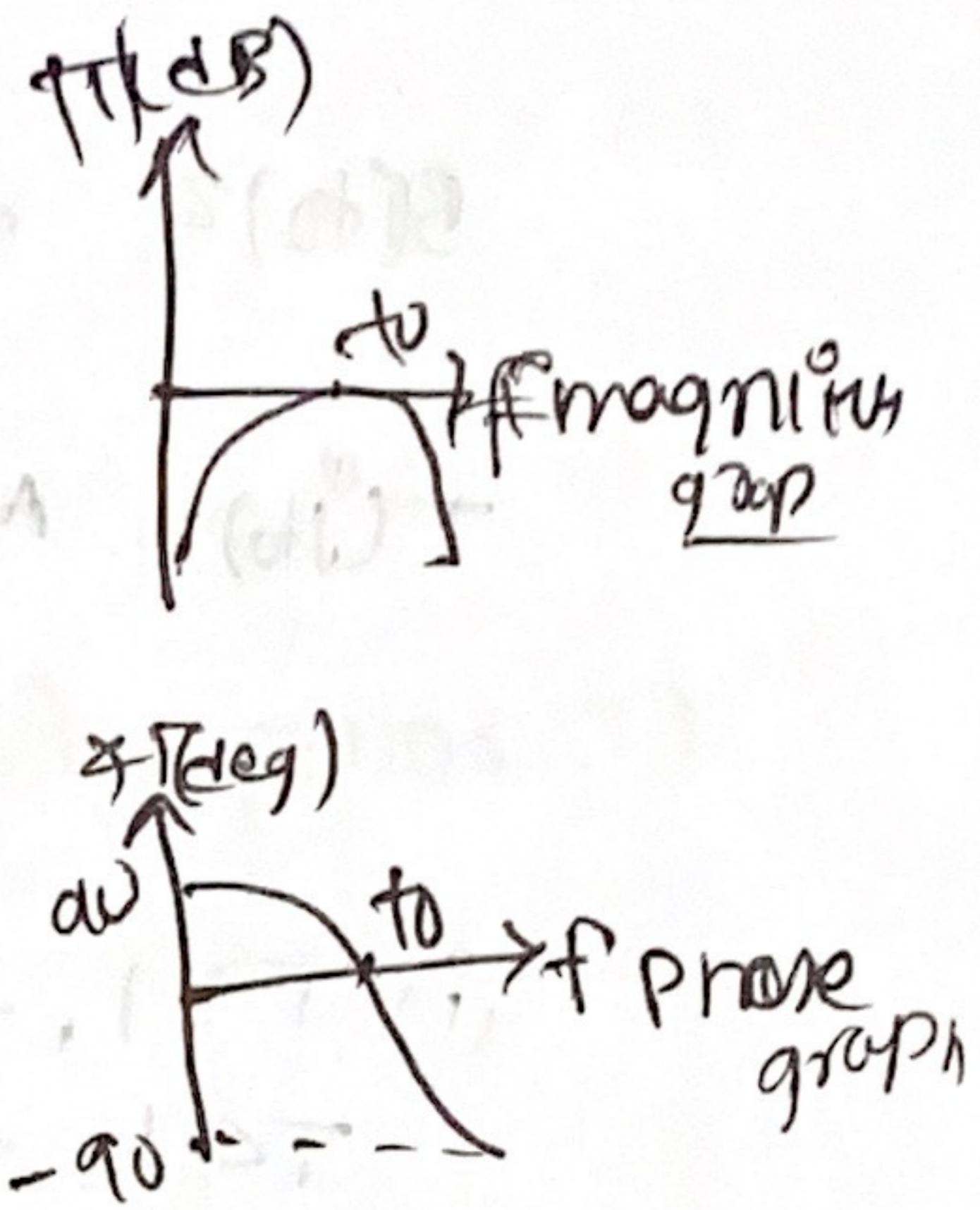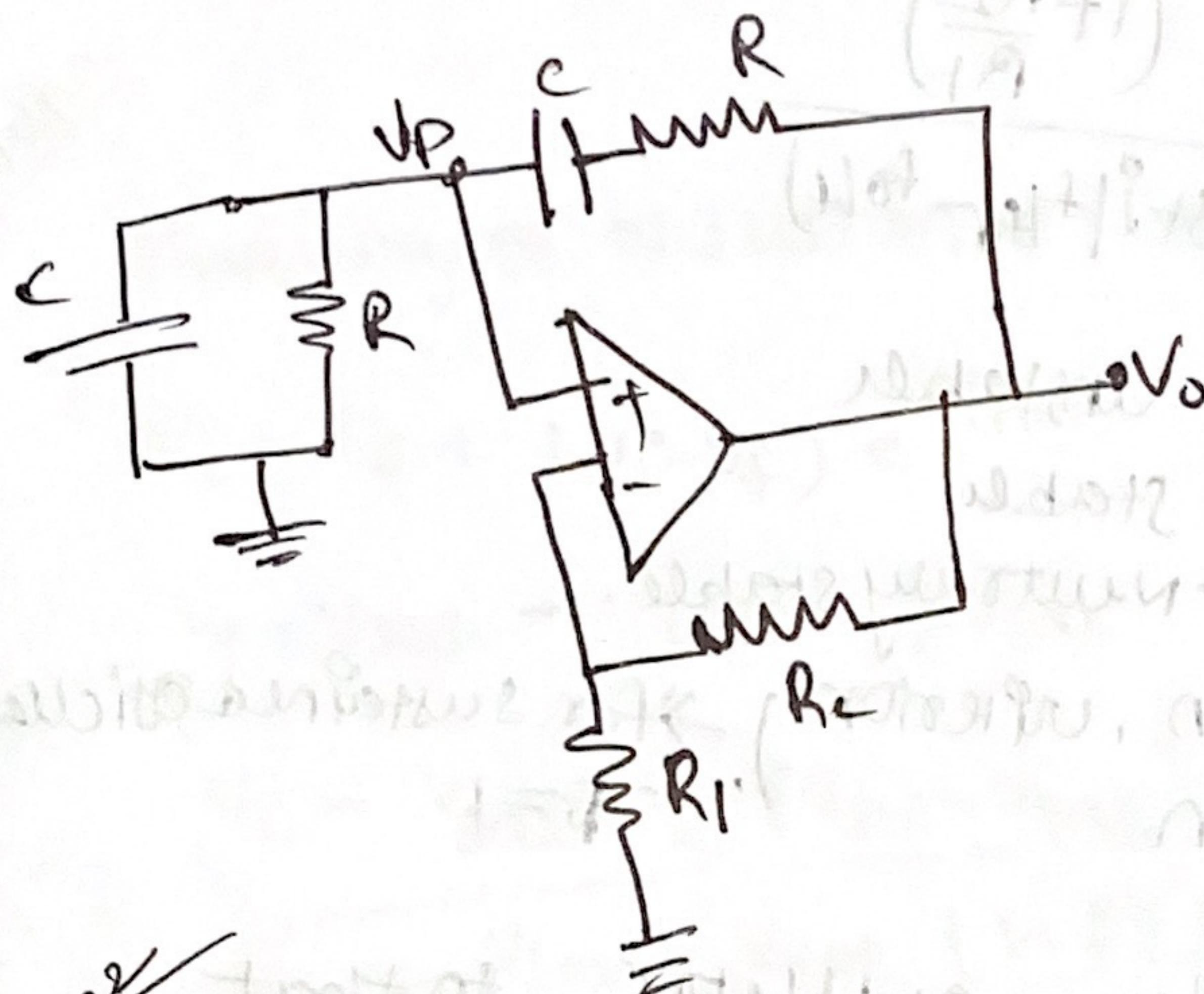

~~1.8.14.12~~ consider non-inverting amp:

$$B = \frac{V_P}{V_0}, \quad A = 1 + \frac{R_2}{R_1} = \frac{V_0}{V_P} \quad Z_P, 2s$$

$$\textcircled{B} \quad V_P = \frac{2P}{2P+2s} \times V_0. \quad \Leftrightarrow \quad B(jf) = \frac{V_P}{V_0} = \frac{2P}{2P+2s}$$

$$Z_P = R_{II} \times C \quad Z_f = R + j \omega C$$

$$= R_{II} \frac{1}{j \omega C}$$

$$= R + \frac{1}{j \omega C}$$

$$= R \cancel{\left(\frac{1}{j \omega C} \right)}$$

$$= \frac{R(j\omega C + 1)}{j \omega C}$$

$$Z_P = \frac{R}{1 + j \omega f R C}$$

$$Z_f = R + \frac{1}{j \omega f C} = \frac{1 + R j \omega f C}{j \omega f C}$$

$$\frac{V_P}{V_0} = \frac{\frac{R}{1 + j \omega f R C}}{\frac{R}{1 + j \omega f R C} + \frac{1 + j \omega f R C}{j \omega f C}} = \frac{R}{R + (R + 1)(1 + j \omega f R C)}$$

$$= \frac{R}{R + (R + 1)(1 + j \omega f R C)}$$

$$\frac{V_P}{V_0} = \frac{2 \pi f R C}{1 + (Q_f \omega f R C)^2 + 2(Q_f \omega f R C) + j^2 \omega^2 f^2 R^2 C^2}$$

$$B(jf) = \frac{1}{\frac{1}{2 \pi f R C} + j^2 \omega^2 f^2 R^2 C^2 + 1}$$

$$\Rightarrow f_0 = \frac{1}{2 \pi R C}$$

$$Q_f = \frac{2R}{C}$$

$$B(f_0) = \frac{1}{3 + j(f/f_0 - f_0/f)}$$

$$T(jf_0) = A \times B = \frac{(1 + R_2/R_1)}{3 + j(f/f_0 - f_0/f)}$$

(i) $T > 1$, $A > 3\text{V/V}$, Unstable

$T < 1$, $A < 3\text{V/V}$, Stable

$T = 1$, $A = 3\text{V/V}$, Neutrally stable.

$(AB=1 \Rightarrow \text{Barkhausen criterion})$ for sustained oscillation.

(ii) Design a Wien-bridge oscillator, so that

$$f_0 = 965\text{ Hz}, C = 0.054\text{F}$$

$$R_2 = 2R_1$$

assume

A) Assume that sustained oscillator

$$T = AB$$

$$A = \frac{1}{B}$$

$$3 = \frac{1}{B}$$



$$B = \frac{1}{3}$$

$$A = 3$$

$$R_2 = 2R_1$$

Multivibrators:

① A stable Multi-vibrator using opamp:

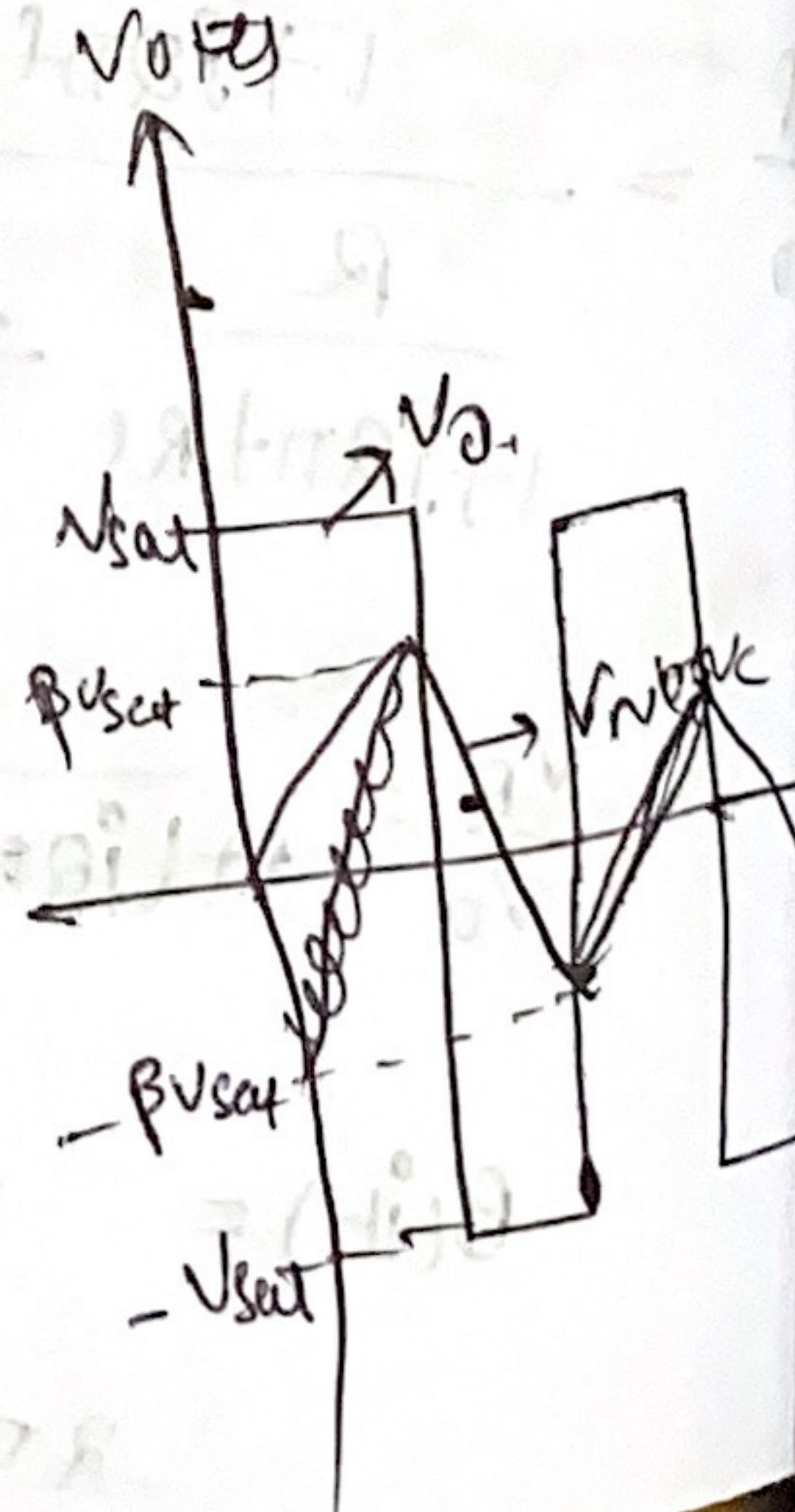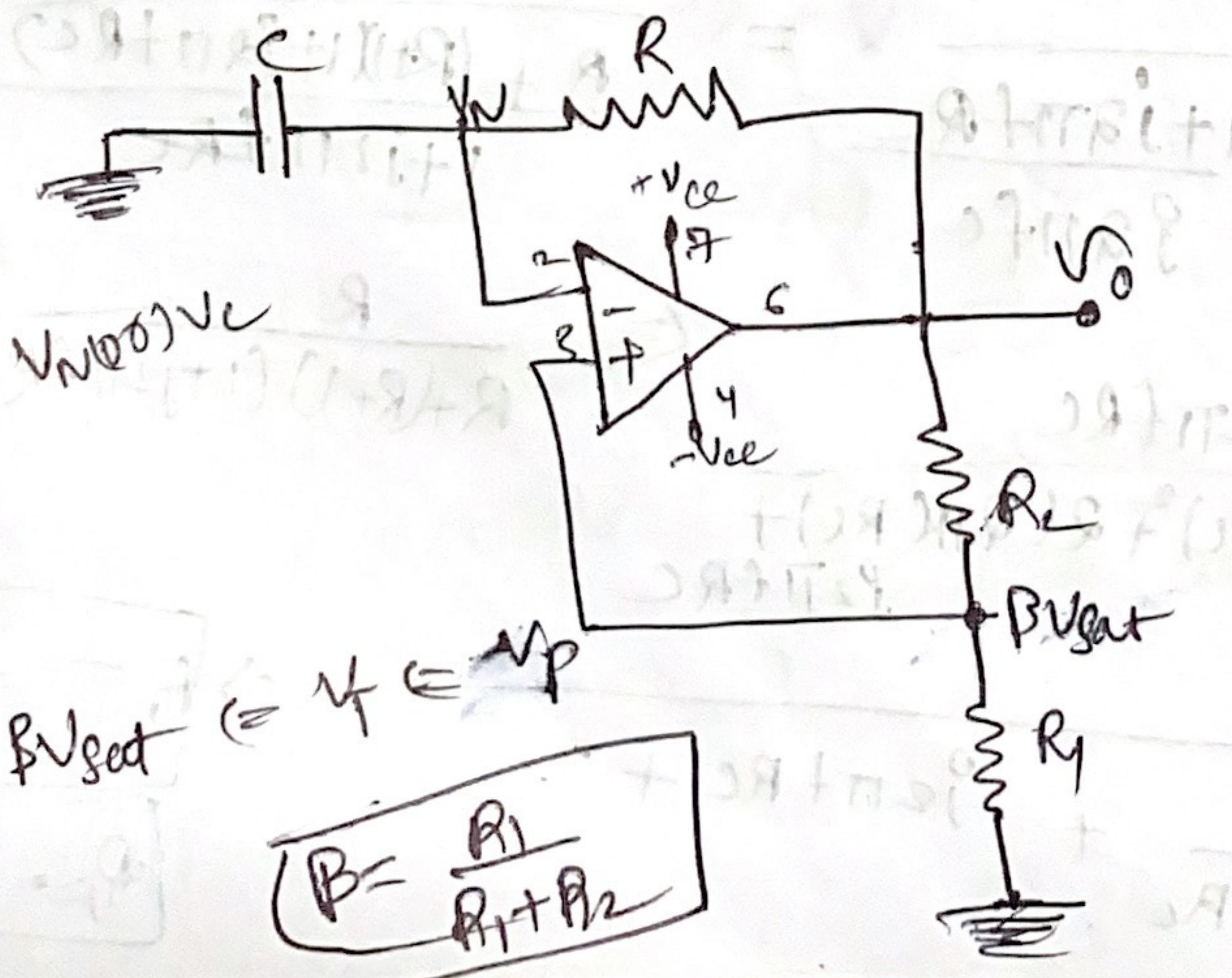

$$\text{Duty cycle (D)} = \frac{T_{on}}{T_{on} + T_{off}}$$

~~Frequency of oscillation (f) or total time period (T).~~

$$V_C = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_f = V_{sat} - (1 + \beta) V_{sat}$$

$$V_C = V_{sat} + (-\beta V_{sat} - V_{sat}) e^{-t/RC}$$

$$\boxed{V_C = V_{sat} - V_{sat} (1 + \beta) e^{-t/RC}}$$

$$\text{At } t = T_1, V_C = \beta V_{sat}$$

$$\beta V_{sat} = V_{sat} - V_{sat} (1 + \beta) e^{-T_1/RC}$$

$$\beta = 1 - (1 + \beta) e^{-T_1/RC}$$

$$\frac{\beta}{1 + \beta} = -e^{-T_1/RC}$$

$$T_1 = RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)$$

$$\overline{T} = 2T_1$$

$$\boxed{T = 2RC \ln \left(\frac{1 + \beta}{1 - \beta} \right)}$$

$$\boxed{T = 2RC \ln \frac{V_{sat} + V_f}{V_{sat} - V_f}}$$

$$\text{If, } R_1 = R_2$$

$$\text{then, } \beta = 0.5$$

$$T = 2RC \ln \left(\frac{1 + 0.5}{1 - 0.5} \right)$$

$$= 2RC \ln 3$$

$$R_1 = 1.16 R_2$$

$$\text{then } \beta = \frac{1.16 R_2}{2.16 R_2}$$

$$\boxed{f = \frac{1}{T}}$$

$$\boxed{f = \frac{1}{2RC \ln (1 + \beta) / R_2}}$$

$$T = 2RC, f_0 = \frac{1}{2RC}$$

(Q1) An op-amp Astable Multivibrator circuit is constructed using following component $R_2 = 35\text{ k}\Omega$, $R_1 = 30\text{ k}\Omega$, $R = 50\text{ k}\Omega$, $C = 0.01\text{ MF}$. calculate frequency of oscillation.

$$\text{Ans} \quad \beta = \frac{R_4}{R_1 + R_2} = \frac{30}{30 + 35}.$$

$$\beta = 0.461$$

$$T = 2 \times 50 \times 0.01 \times 10^{-6} \times \ln \left(\frac{1+0.461}{1-0.461} \right)$$

$$= \frac{100 \times 0.01 \times 10^{-6}}{0.99 \times 10^4} \times 0.99 \times 10^4 = \frac{8 \times 50 \times 10^4 \times 10^{-6}}{10^2 \times 10^4}$$



$$T = 0.99 \times 10^{-6} \text{ s}$$

$$f = \frac{1}{0.99 \times 10^{-6}} \quad T = 0.99 \times 10^{-6}$$

$$f = \frac{10^3}{0.99}$$

$$= 1\text{ kHz}$$

Monostable Multivibrator using op-amp:

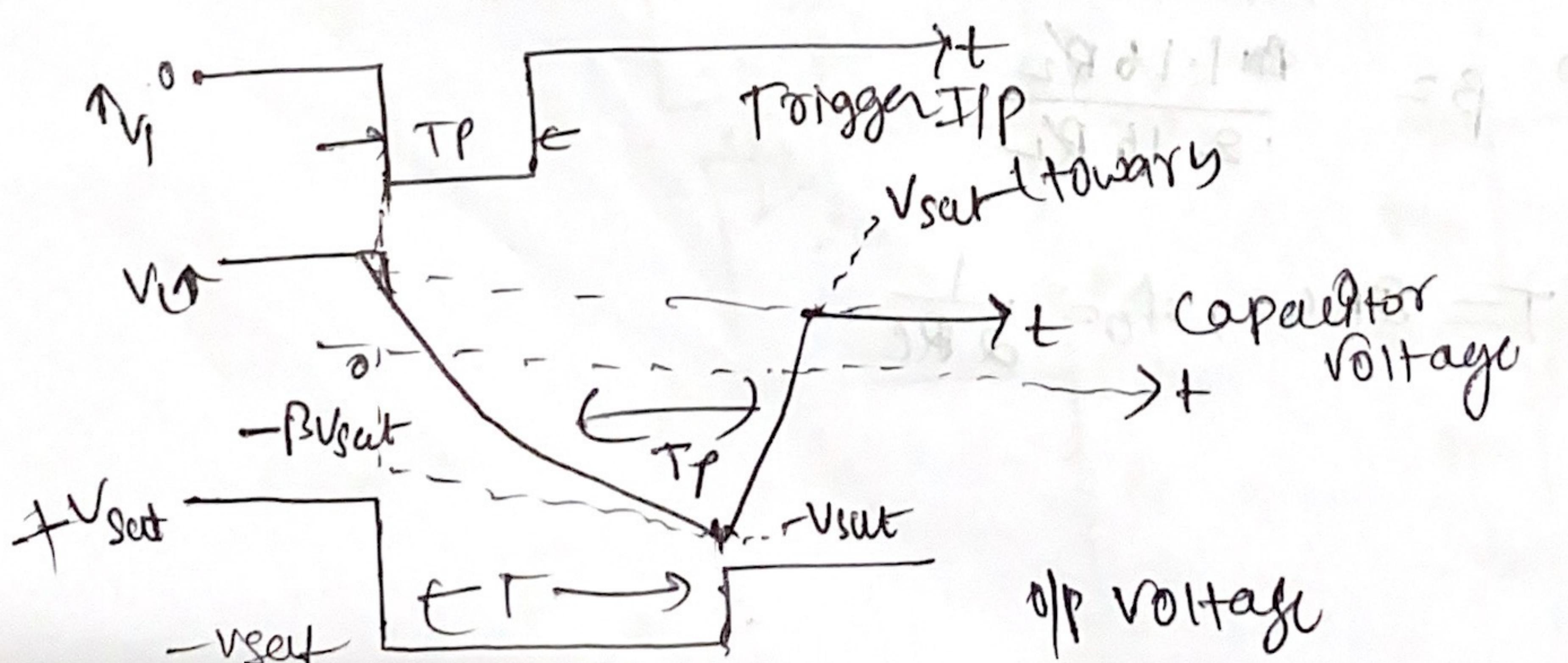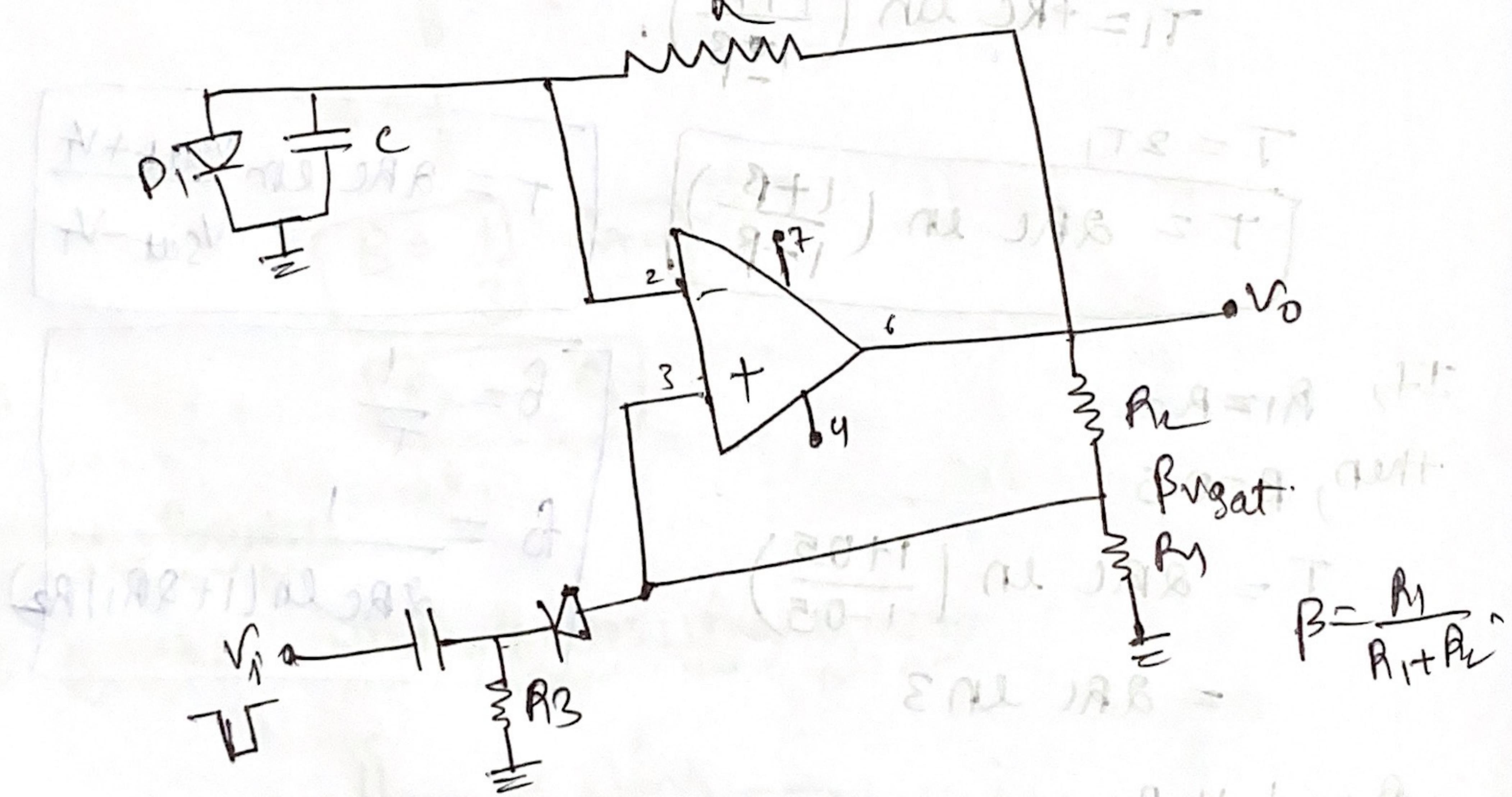

21/4/22

$$V_O = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_f = -V_{sat}$$

$$V_i = V_D.$$

$$V_C \approx V_O = -V_{sat} (V_D + V_{sat}) e^{-t/RC}$$

$$t=T \Rightarrow V_C = -\beta V_{sat}$$

$$+\beta V_{sat} = \beta V_{sat} (V_D + V_{sat}) e^{-T/RC}$$

$$\beta = (V_D + V_{sat}) e^{-T/RC}$$

$$T = RC \ln \left(\frac{1 + V_D/V_{sat}}{1 - \beta} \right)$$

$$V_D \ll V_{sat}$$

$$T = +RC \ln \left(\frac{1}{1 - \beta} \right)$$

$$T = 0.69 RC$$

$$T_{discharge} = RC \ln \left(1 + \frac{R_1}{R_2} \right).$$

Q1) An op-amp Mono stable Circuit is constructed using a following components $R_1 = R_2 = 30 \text{ k}\Omega$, $R = 150 \text{ k}\Omega$, $C = 1 \mu\text{F}$. If opamp is supplied $\pm 12 \text{ V}$ and timing pulse $t_p = 10 \text{ ms}$ initiates 10ms pulse calculate the circuit time period and capacitor recovery time and T_B w/ TP & V's.

A)

$$t_p = 10 \text{ ms} \quad C = 1 \mu\text{F} \quad R = 150 \text{ k}\Omega$$

$$T = 0.69 \times 150 \times 10^3 \times 1 \times 10^{-6}$$

$$= 0.1035$$

$$T = 150 \times 10^3 \times 10^{-6} \ln \left(\frac{1 + \frac{0.7}{12}}{1 - \frac{1}{2}} \right)$$

$$= 0.15 \ln \left(\frac{1.05}{0.5} \right) = 0.15 \ln (2 \times 1.05) = 0.315$$

$$= 112 \text{ ms.}$$

$$T_{discharge} = RC \ln \left(1 + \frac{R_2}{R_1} \right) = 103 \text{ ms.}$$

$$T = T_{charge} + T_{discharge} = 215 \text{ ms.}$$