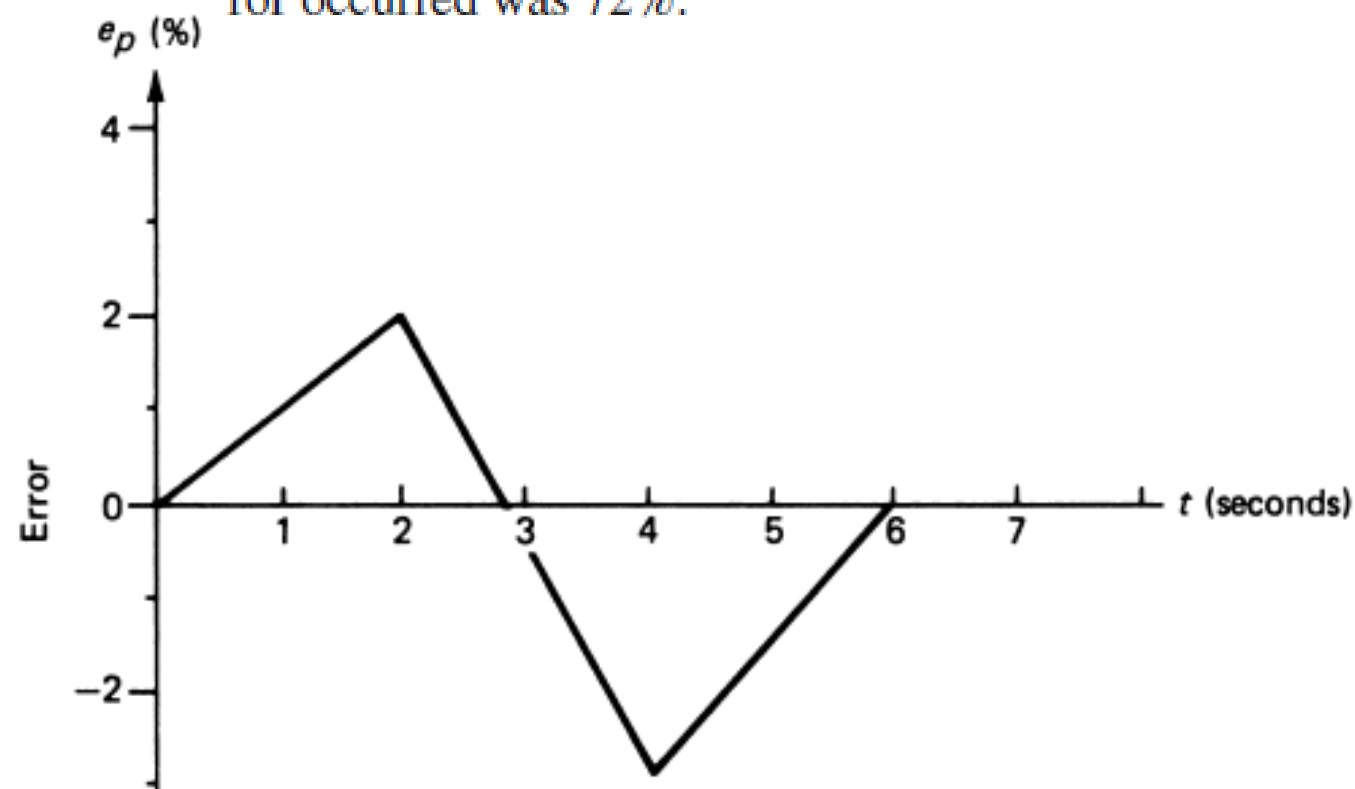


## Section 6

- 13 A PI controller has  $K_P = 2.0$ ,  $K_I = 2.2 \text{ s}^{-1}$ , and  $p_I(0) = 40\%$ . Plot the output for an error given by Figure 26.
- 14 A PD controller has  $K_P = 2.0$ ,  $K_D = 2 \text{ s}$ , and  $p_0 = 40\%$ . Plot the controller output for the error input of Figure 26.
- 15 A PID controller has  $K_P = 2.0$ ,  $K_I = 2.2 \text{ s}^{-1}$ ,  $K_D = 2 \text{ s}$ , and  $p_I(0) = 40\%$ . Plot the controller output for the error of Figure 26.
- 16 A PI controller is reverse acting,  $PB = 20$ , 12 repeats per minute. Find (a) the proportional gain, (b) the integral gain, and (c) the time that the controller output will reach  $0\%$  after a constant error of  $-1.5\%$  starts. The controller output when the error occurred was  $72\%$ .



# Design of analog Controllers

Reference:

Process Control Instrumentation Technology

Curtis D. Johnson


# Electronic controllers

- An analog controller is a device that implements different controller modes using analog signals to represent the loop parameters.
- The analog signal may be in the form of an electric current or a pneumatic air pressure.
- The controller accepts a measurement expressed in terms of one of these signals, calculates an output for the mode being used, and outputs an analog signal of the same type.


- Electronic method of realizing controller modes necessitates the use of **OPAMPs** as the primary circuit elements.
- For pneumatics the **nozzle/flapper system** forms the basis of controller mode implementation.
- Thus, electronic controllers are designed to input and output the standard 4- to 20-mA signal.
- For pneumatic controllers the signal standard is 3 to 15 psi for U.S. installations and 20 to 100 kPa in many other locations throughout the world.
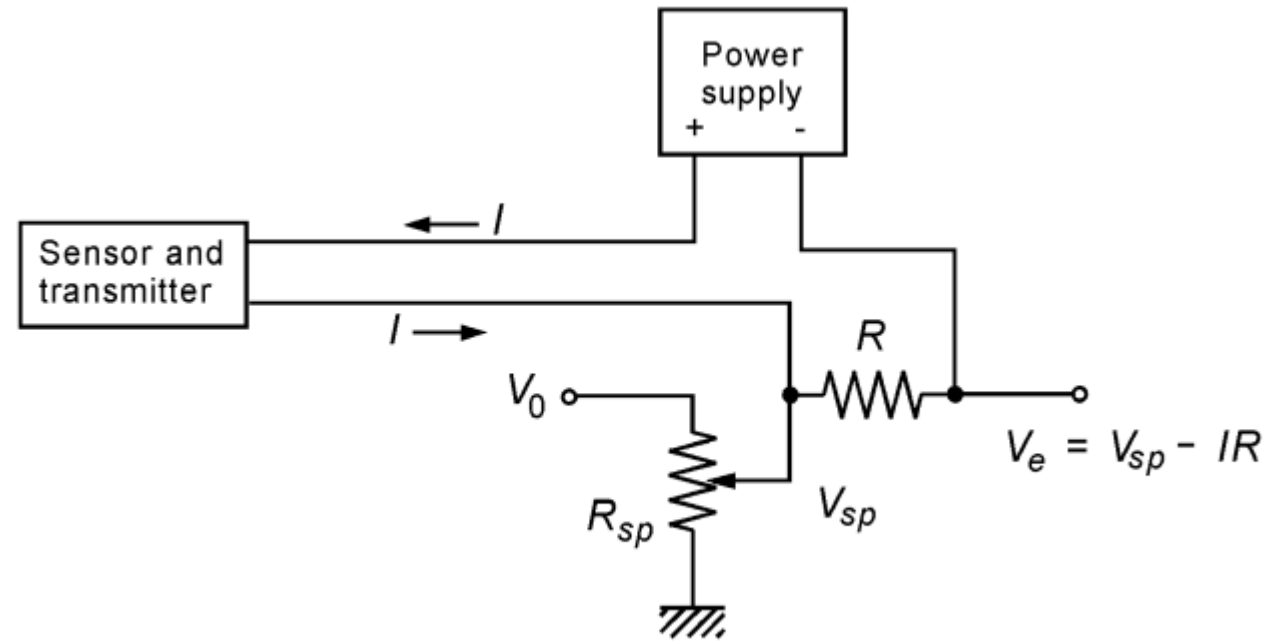
# Error Detector

- The detection of an error signal is done in electronic controllers by taking the difference between voltages.
- One voltage is generated by the process signal current passed through a resistor.
- The second voltage represents the set point, which is usually generated by a voltage divider using a constant voltage as a source.



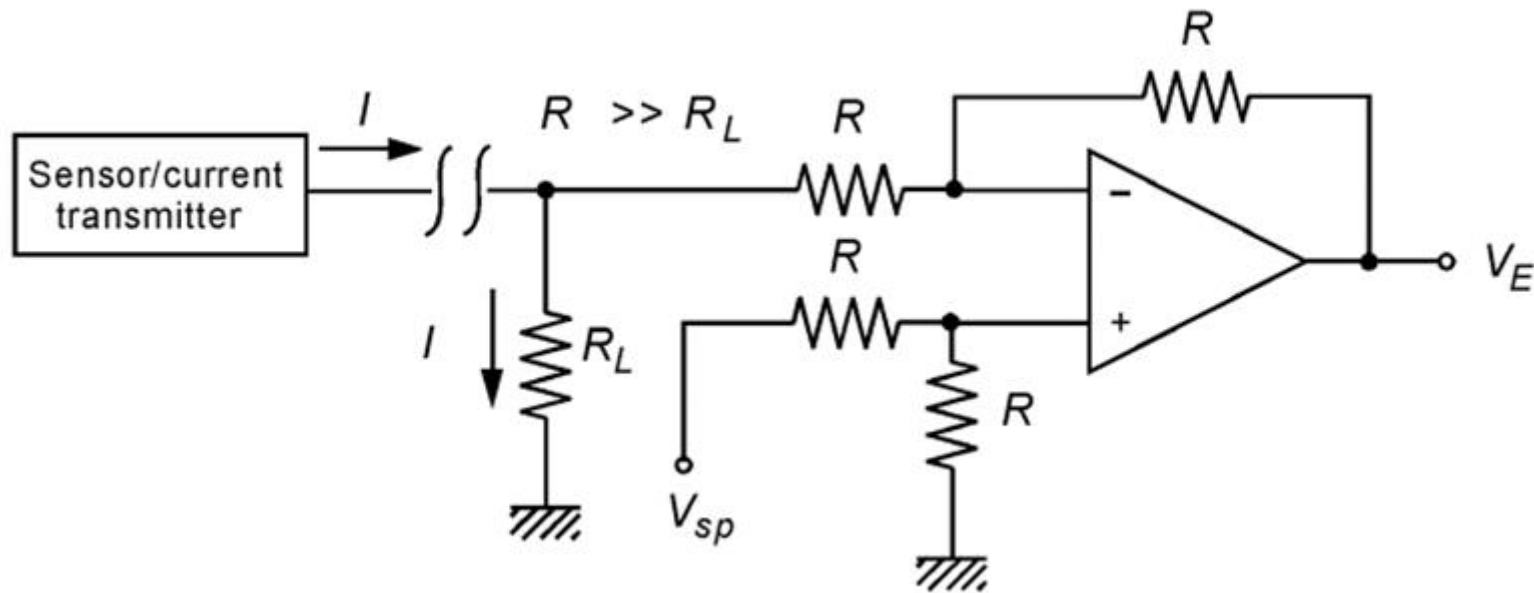
Error detector using a ground-based current and a differential amplifier.


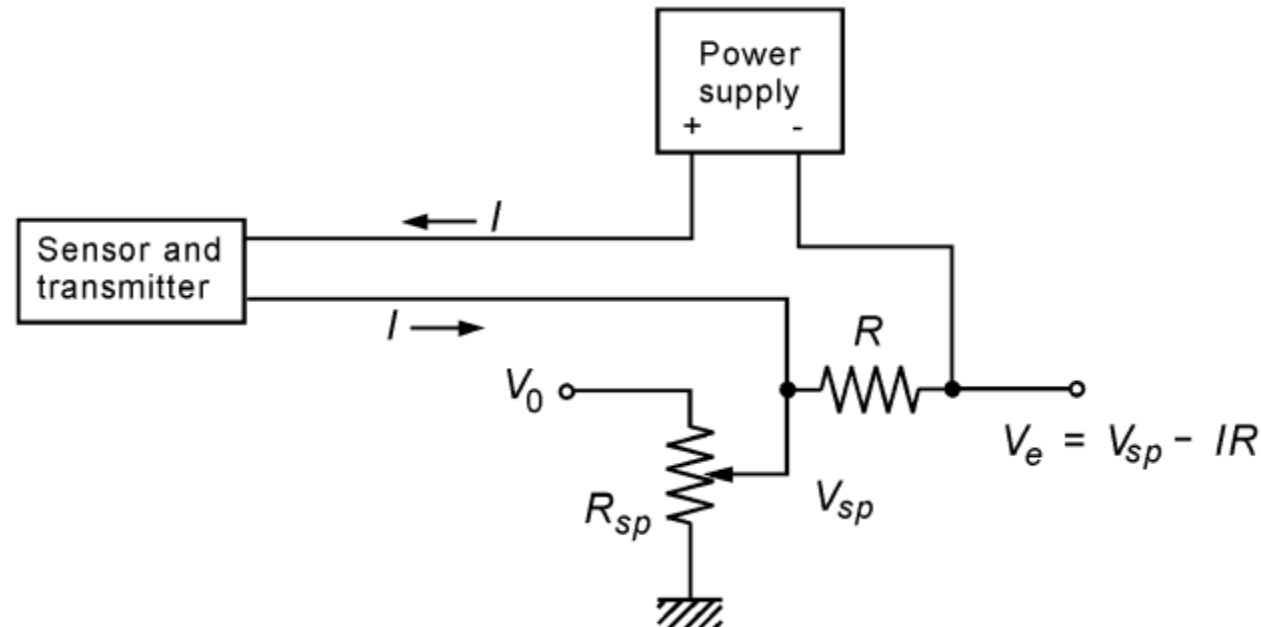
# Problem #1


A sensor converts from 0 to 2.0 m in to a 4 to 20 mA current. An error detector such as shown in Fig. is used with  $R = 100\ \Omega$ ,  $V_0 = 5.0\text{ V}$  and  $R_{sp} = 1\text{K}\Omega$  pot.

- If the setpoint is 0.85 m what is  $V_{sp}$ ?
- If  $V_{sp} = 1.5\text{ V}$ , what is the range of error voltage as position varies from 0 to 2.0m?



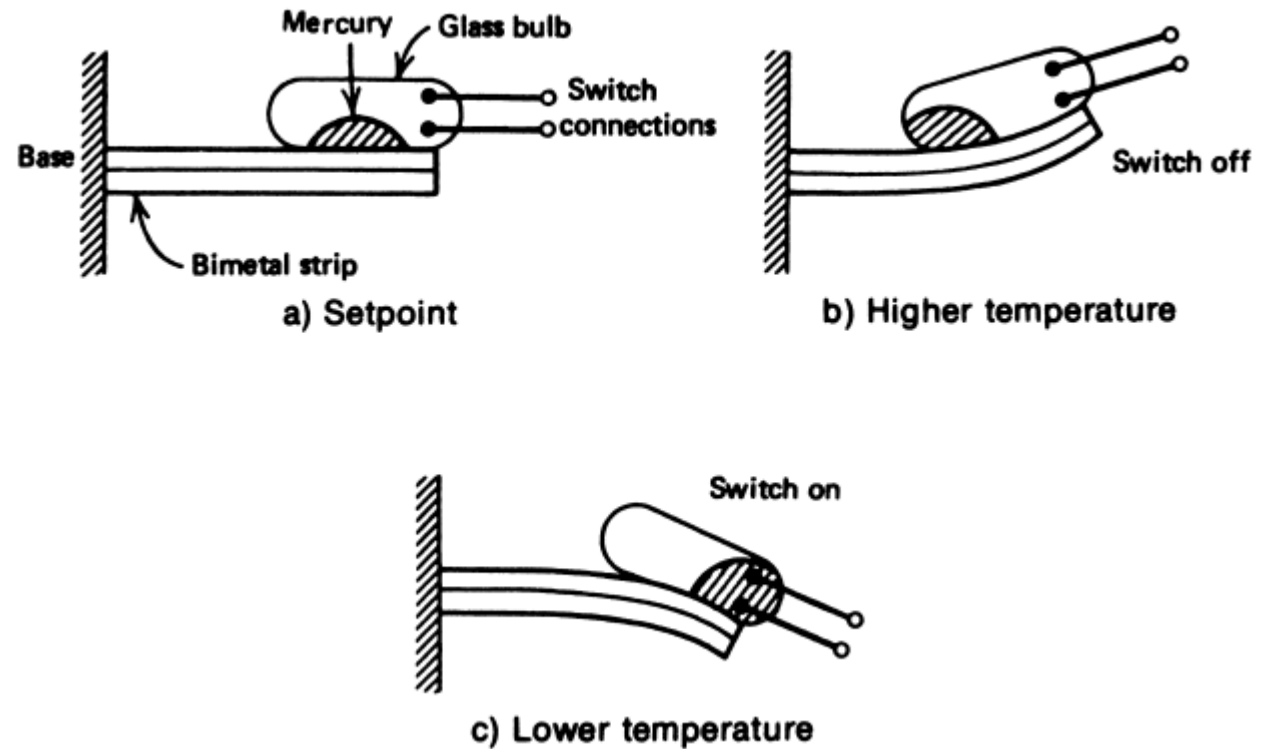
# Single mode : Two position Controllers

- A two position controller can be implemented by electronic and electromechanical designs.
- Many house hold air-conditioning and heating systems employ a two position controller constructed from bimetal strip and mercury switch as shown.





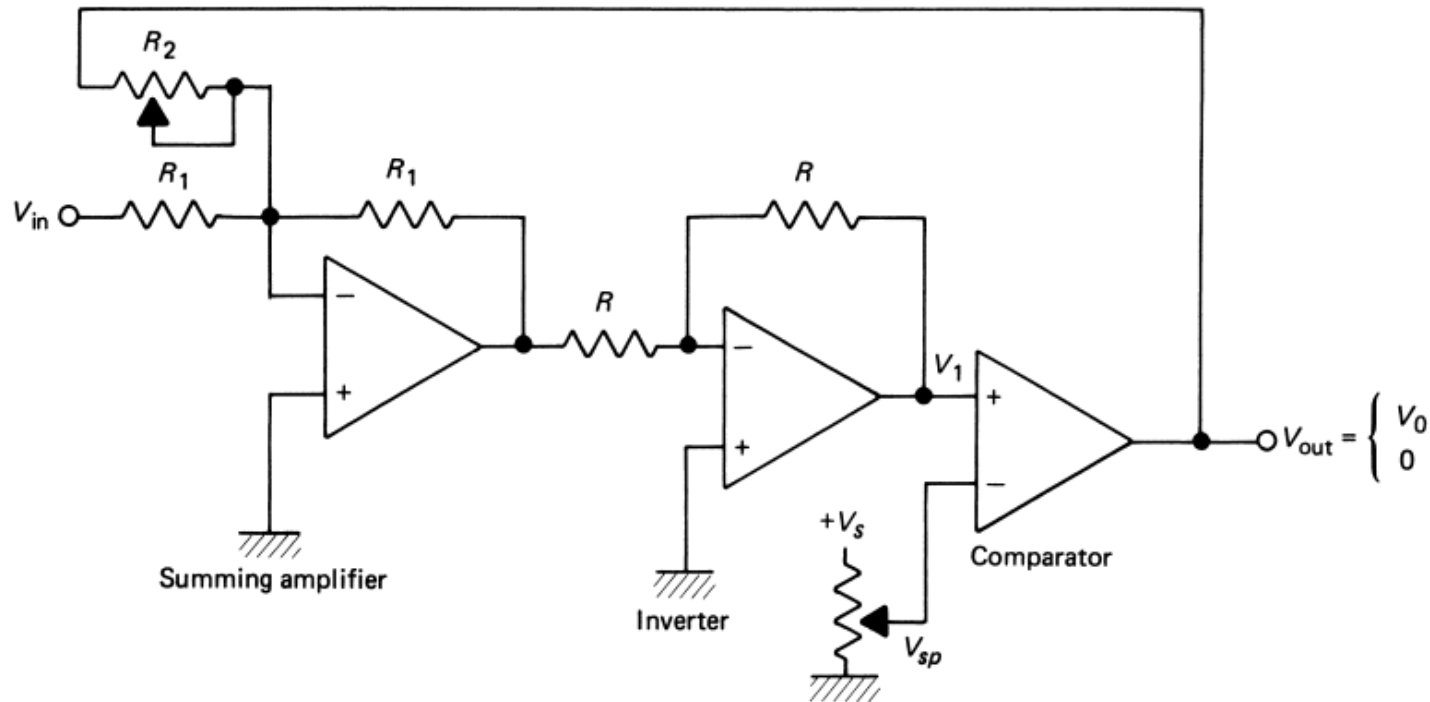
# Op-Amp implementation of ON/OFF control:



Circuit

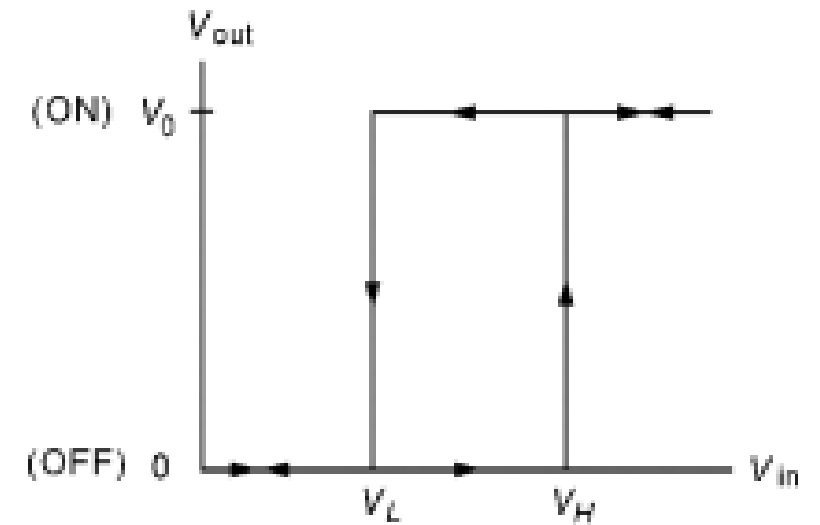

Output

# Op-Amp implementation of ON/OFF control:

Assume that, in the beginning, the comparator is in the OFF state

$$V_{\text{out}} = 0$$

The comparator output switches states when the voltage on its input,  $V_1$  is equal to the set point value  $V_{\text{sp}}$ . Analyzing this circuit,

$$V_1 = V_{\text{in}} + \frac{R_1}{R_2} V_{\text{out}}$$

Substituting

$$V_1 = V_{\text{in}}$$

The comparator changes to ON state when  $V_1 = V_{\text{in}} = V_{\text{H}}$ . Thus, the high (ON) switch voltage is

$$V_{\text{H}} = V_{\text{sp}}$$

$$V_{\text{out}} = V_0$$

With this  $V_1$  changes to

$$V_1 = V_{\text{in}} + \frac{R_1}{R_2} V_0$$

If  $V_{\text{in}} = V_{\text{L}}$  the comparator changes to OFF state, giving the relation,

$$V_1 = V_{\text{sp}} = V_{\text{L}} + \frac{R_1}{R_2} V_0$$

This gives the low (OFF) switching voltage of

$$V_{\text{L}} = V_{\text{sp}} - \frac{R_1}{R_2} V_0$$

## Problem No:2

Level measurement in a sump tank is provided by a transducer scaled as 0.2 V/m. A pump is to be turned on by application of + 5 V when the sump level exceeds 2.0 m. The pump is to be turned back off when the sump level drops to 1.5 m. Develop a two position controller.

Calculations:

$$V_H = (0.2 \text{ V/m}) \times (2.0 \text{ m}) = 0.4 \text{ V}$$

$$V_L = (0.2 \text{ V/m}) \times (1.5 \text{ m}) = 0.3 \text{ V}$$

So, using the relations given in Eqs. 2.4 and 2.8,

$$0.4 \text{ V} = V_{SP}$$

$$0.3 \text{ V} = V_{SP} - \frac{R_1}{R_2} V_0$$

Therefore,

$$V_{SP} = 0.4 \text{ V}$$

$$0.3 \text{ V} = 0.4 - \frac{R_1}{R_2} 5$$

$$\text{Or, } \frac{R_1}{R_2} = 0.02$$



There are two unknowns and only condition to be satisfied. So, one unknown can be selected.

$$\text{Let } R_1 = 5 \text{ K}\Omega \quad \text{then, } R_2 = 250 \text{ K}\Omega$$

## Problem #3

Using a system of Fig. 2.5 design a two position controller with a 0 to 10 V input and a 0 or 10 V output. The setpoint is 4.3 V and the neutral zone is to be  $\pm 1.1$  V about this setpoint.

# Three position

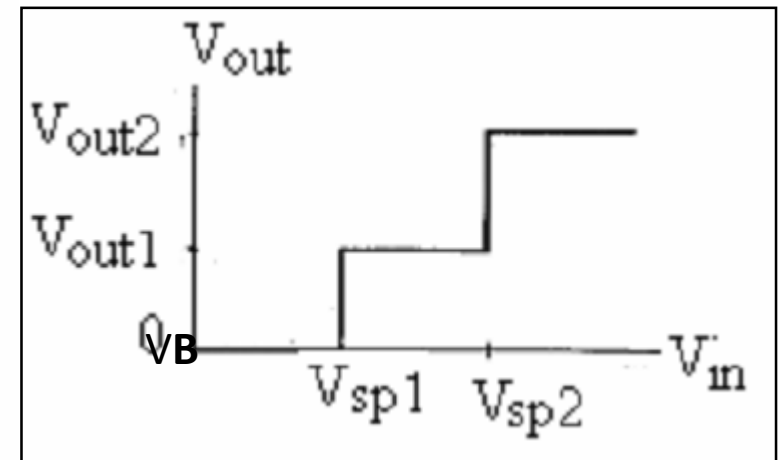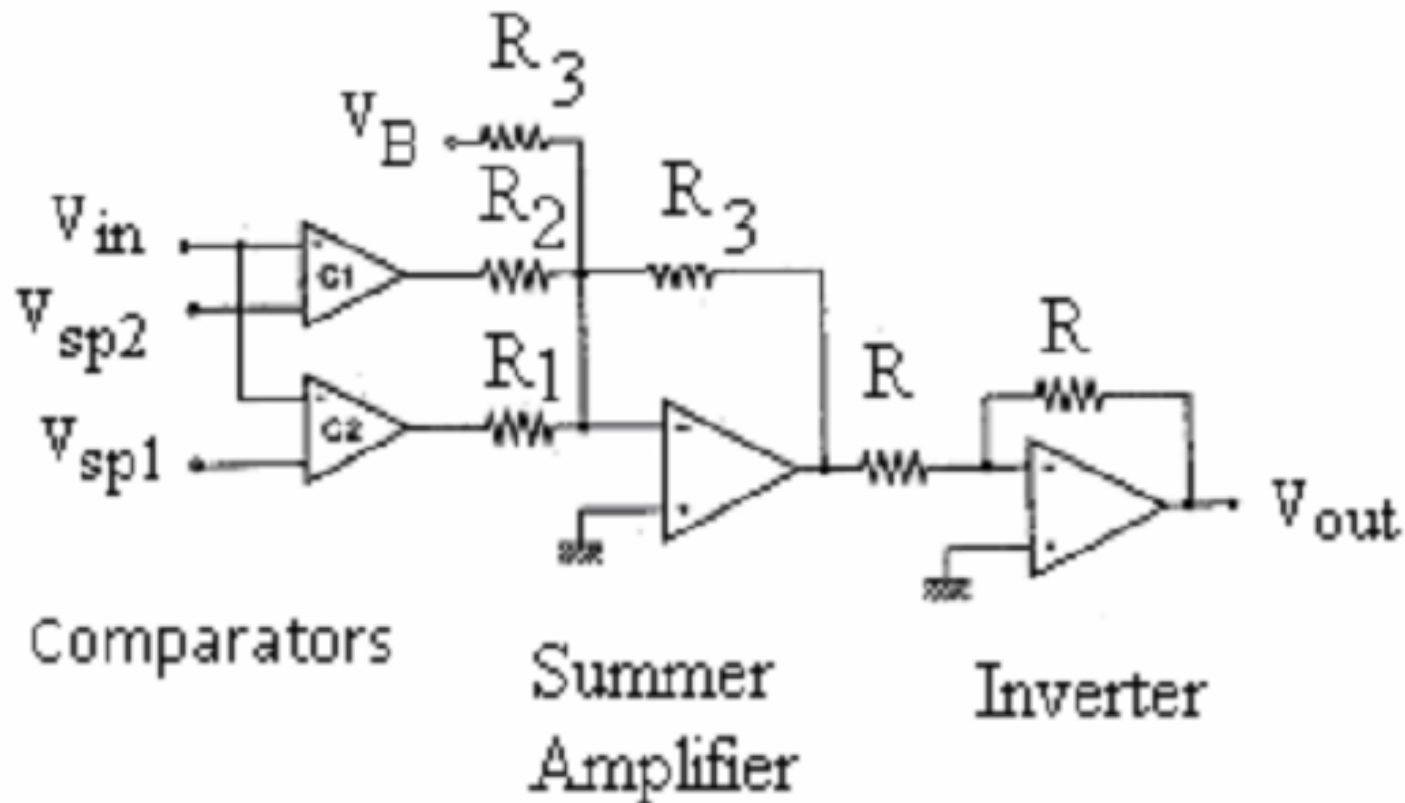

Response with  $V_B=0$

# Three position

When  $V_{in} < V_{SP1}$ ,

Comparator C1 is OFF, C2 is OFF (Because  $V_{SP1} < V_{SP2}$ )

Outputs of both comparators are 0 V. Thus,

$$V_{out} = V_B$$

When  $V_{SP1} < V_{in} < V_{SP2}$ ,

Comparator C1 is OFF, C2 is ON

Outputs of comparator C1 = 0 and Output of Comparator C2 =  $\frac{R_3}{R_1} V_0$  Volts. Thus,

$$V_{out} = V_B + \frac{R_3}{R_1} V_0$$

# Three position

When  $V_{in} > V_{SP2}$ ,

Comparator C1 is ON, C2 is ON

Outputs of comparator C1 =  $\frac{R_3}{R_2} V_0$  and Output of Comparator C2 =  $\frac{R_3}{R_1} V_0$  Volts. Thus,

$$V_{out} = V_B + \frac{R_3}{R_1} V_0 + \frac{R_3}{R_2} V_0$$

Thus,

$$\text{When } V_{in} < V_{SP1}, \quad V_{out} = V_B \quad (2.9)$$

$$V_{SP1} < V_{in} < V_{SP2}, \quad V_{out} = V_B + \frac{R_3}{R_1} V_0 \quad (2.10)$$

$$V_{in} > V_{SP2}, \quad V_{out} = V_B + \frac{R_3}{R_1} V_0 + \frac{R_3}{R_2} V_0$$



# Proportional Mode

- Implementation of this mode requires a circuit that has a response given by

$$p = K_P e_p + p_0$$

$p$  = controller output 0–100%

$K_P$  = proportional gain

$e_p$  = error in percent of variable range

$p_0$  = controller output with no error

- If we consider both the controller output and error to be expressed in terms of voltage, we see that is simply a summing amplifier with the analog electronic equation for the output voltage as

$$V_{\text{out}} = G_P V_e + V_0$$


$V_{\text{out}}$  = output voltage

$G_P = R_2/R_1$  = gain

$V_e$  = error voltage

$V_0$  = output with zero error

# Proportional Mode

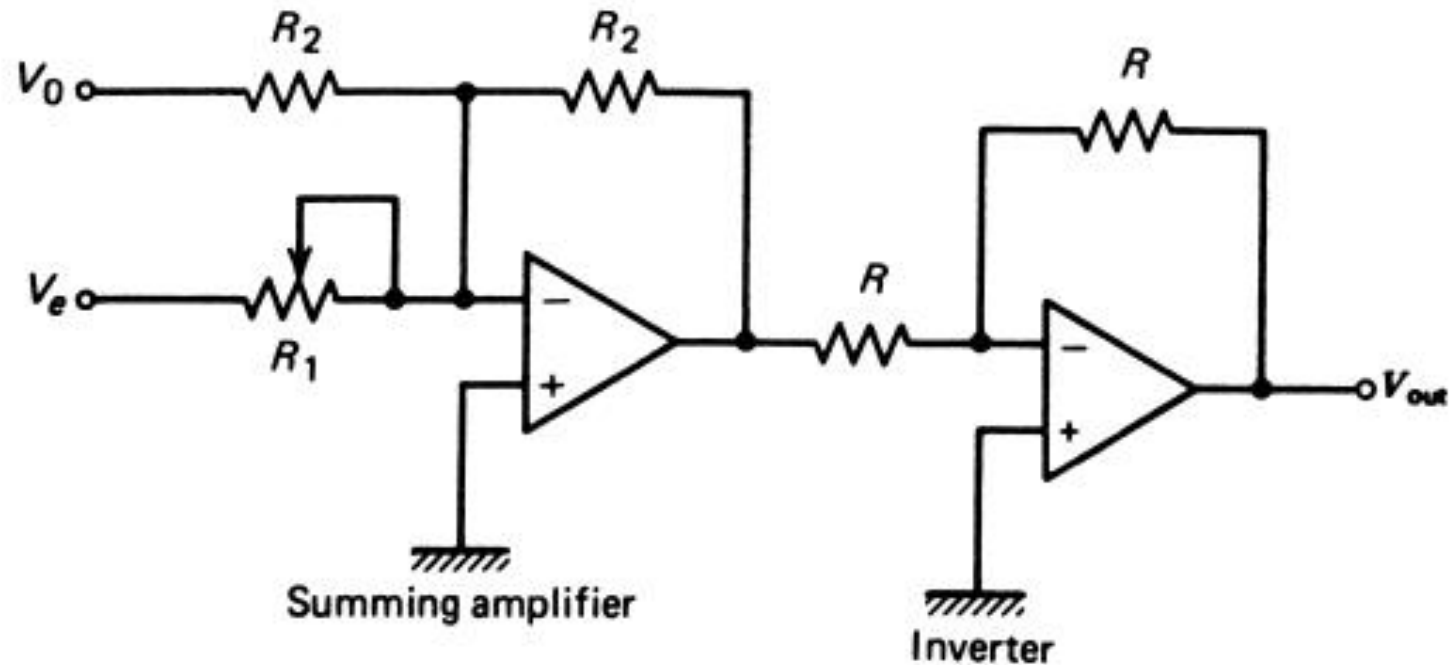

**FIGURE 7**

An op amp proportional-mode controller.

## Design Procedure:

- The design of a proportional controller calls for specification of the proportional gain described by  $K_P$  that expresses the percent of output for an error of 1% of the measurement range.
- Alternatively it could be described as the proportional band,  $PB=100/K_P$ .
- This must now be expressed in terms of the voltage gain,  $G_P$  in The relationship between  $G_P$  and  $K_P$  is given by,

$$G_P = K_P \frac{\Delta V_{\text{out}}}{\Delta V_{\text{m}}}$$

# Integral Mode

- The integral mode was characterized by an equation of the form

$$p(t) = K_I \int_0^t e_p dt + p(0)$$

Where

$p(t)$  = controller output in percent of full scale

$K_I$  = integration gain ( $s^{-1}$ )

$e_p$  = deviations in percent of full-scale variable value

$p(0)$  = controller output at  $t = 0$

- The corresponding equation relating input to output is

$$V_{\text{out}} = G_I \int_0^t V_e dt + V_{\text{out}}(0)$$


$V_{\text{out}}$  = output voltage

$G_I = 1/RC$  = integration gain

$V_e$  = error voltage

$V_{\text{out}}(0)$  = initial output voltage

# OpAmp integral-mode controller

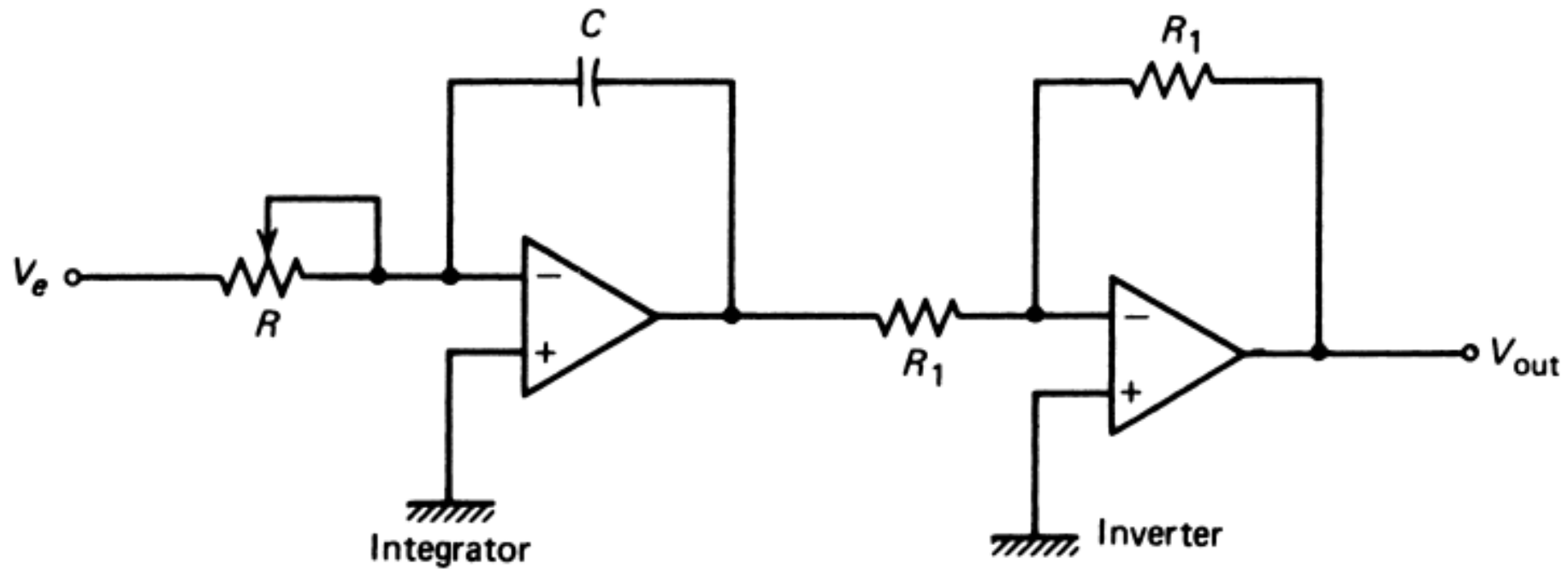

# Determination of $G_I$

- The actual value of  $G_I$  and therefore  $R$  and  $C$ , is determined from  $K_I$  and the input and output voltage ranges.
- Integral gain says that, an input error of 1 % must produce an output that changes as  $K_I$  % per second.
- Or if an error of 1 % lasts for 1 s, the output must change by  $K_I$  percent.

# Steps to find out $G_I$ value

- Find out the input range and the output range.
- Convert  $K_I$  to units of seconds
- Find the error 1% of the input for 1 s
- Find  $K_I$  percent of the output (using the seconds expression for gain).
- Integral gain = Ratio of  $K_I$  percent of the output to 1% of the input for 1 s to.
- The values of  $R$  and  $C$  can be selected from that.

# Derivative Mode

- Is never used alone because it cannot provide a controller output when the error is zero.
- The control mode equation is given by

$$P(t) = K_D \frac{de_p}{dt}$$

where,  $P$  = Controller output in percent of full output

$K_D$  = Derivative time constant ( s)

$e_p$  = error in percent of full scale range




## Implementation of derivative controller using OPAMP:

- Consider an OPAMP differentiator circuit shown in Fig The theoretical transfer function for this circuit will be given by:

$$V_{out} = -RC \frac{dV_e}{dt}$$

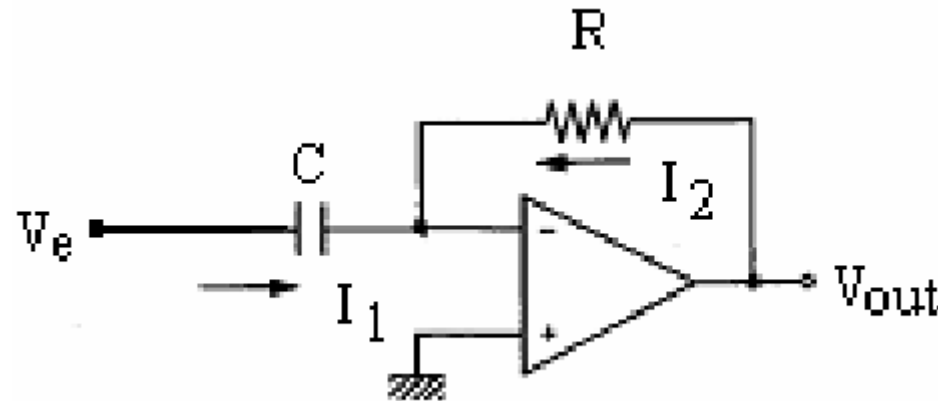- where, the input voltage has been set equal to the controller error voltage



# Implementation of derivative controller using OPAMP:

- From a practical perspective, this circuit can not be used because it tends to be unstable, that is, it may begin to exhibit spontaneous oscillations in the output voltage.
- The reason for this instability is the occurrence of very large gain at high frequencies where the derivative is very large.
- Consider the input voltage


$$V_e = V_0 \sin(2\pi ft).$$
$$V_{out} = \frac{R}{-jX_c} V_e = -j2\pi fRC V_e$$

The magnitude of the output is expressed as,

$$|V_{out}| = 2\pi fRC |V_e|$$
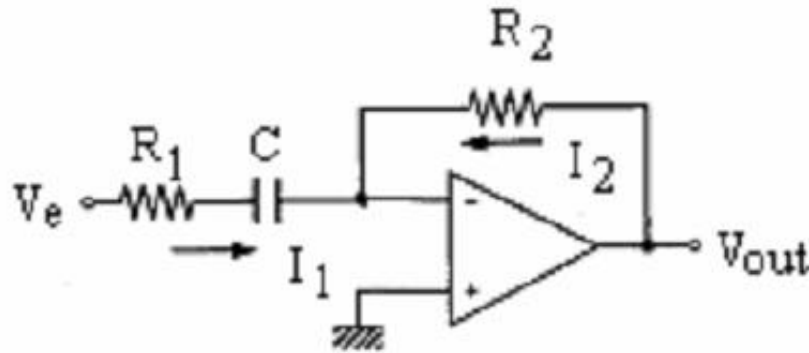
# Practical derivative mode op amp controller

- In order to make a practical circuit, a modification is provided that essentially clamps the gain above some frequency to a constant value.



## Working principle:

- Assume a sinusoidal input voltage and use ac analysis. The input impedance is now given by:

$$X_{in} = R_1 + \frac{1}{j2\pi fC}$$

$$\text{Or, } X_{in} = R_1 - \frac{j}{2\pi fC}$$

Now  $V_{out}$  is given by

$$V_{out} = -\frac{R_2}{R_1 - \frac{j}{2\pi fC}} V_e$$

$$V_{out} = -\frac{2\pi fCR_2}{2\pi fCR_1 - j} V_e$$

$$|V_{out}| = \frac{2\pi fR_2C}{\sqrt{(2\pi fR_1C)^2 + 1}} |V_e|$$

## Working principle:

- For frequencies for which,  $2\pi fR_1C \ll 1$   
The circuit takes the derivative as required.  
But for frequencies for which,  $2\pi fR_1C \gg 1$
- The response reduces to

$$|V_{out}| = \frac{R_2}{R_1} |V_e|$$

- showing no derivative action.
- Therefore when using a derivative action circuit, we must estimate the maximum physical frequency,  $f_{max}$  at which the system can respond.

# Guidelines to design derivative mode controller

- The value of  $G_D = R_2 C$  is determined from  $K_D$  and knowledge of the measurement and output voltage ranges.
- For this mode, the interpretation of  $K_D$  is that, for an error change of 1% in 1 s, the output should change by  $K_D$  percent.
- Thus,  $G_D$  is found from the quotient of percent of the output voltage and 1% of the input voltage.
- $K_D$  must be expressed in seconds

# Guidelines to design derivative mode controller

- 1. Estimate the maximum frequency at which the physical system can respond,  $f_{\max}$ .
- 2. Set  $2\pi f_{\max} R_1 C = 0.1$  and solve for  $R_1$  ( $C$  is found from the mode derivative gain requirement)
- 3. Equation shows that the following responses will result from this selection:

• $f = 0.1 f_{\max}$	$V_{\text{out}} = 0.995 (2\pi f R_2 C)  V_e $	Derivative action
• $f = f_{\max}$	$V_{\text{out}} = 0.707 (2\pi f R_2 C)  V_e $	Transition action
• $f = 10f_{\max}$	$V_{\text{out}} = 0.0995 (2\pi f R_2 C)  V_e $	No Derivative action

Define the circuit derivative gain or derivative time in seconds as  $G_D = R_2 C$ .  $G_D$  will be determined from the design controller derivative gain  $K_D$ .

An integral controller has an input range of 1 to 8 V and an output range of 0 to 12 V. If  $K_I = 12\%/(\%\text{-min})$ , find  $G_I$ , R and C.

$$K_I = 12\%/(\%\text{-min}) = K_I = [12\%/(\%\text{-min})] [1\text{min}/60\text{s}] = 0.2 \text{ s}^{-1}$$

$$1 \% \text{ of the input for } 1 \text{ sec} = (0.01)(8-1) \text{ V}(1\text{s}) = 0.07 \text{ V-s}$$

$$0.2 \% \text{ of the output} = (0.002)12\text{V} = 0.024 \text{ V}$$

$$\text{Thus the gain is, } G_I = 0.024\text{V}/0.07\text{V-s} = 0.3428 \text{ s}^{-1}$$

$$\text{Or, } RC = 2.92 \text{ s} \text{ If } C = 10 \mu\text{F}, R = 292 \text{ K}\Omega$$




# Composite Controller Modes


- The combination of several controller modes was found to combine the advantages of each mode and, in some cases, eliminate disadvantages.
- Composite modes are implemented easily using op amp techniques
- Basically, this consists of simply combining the mode circuit
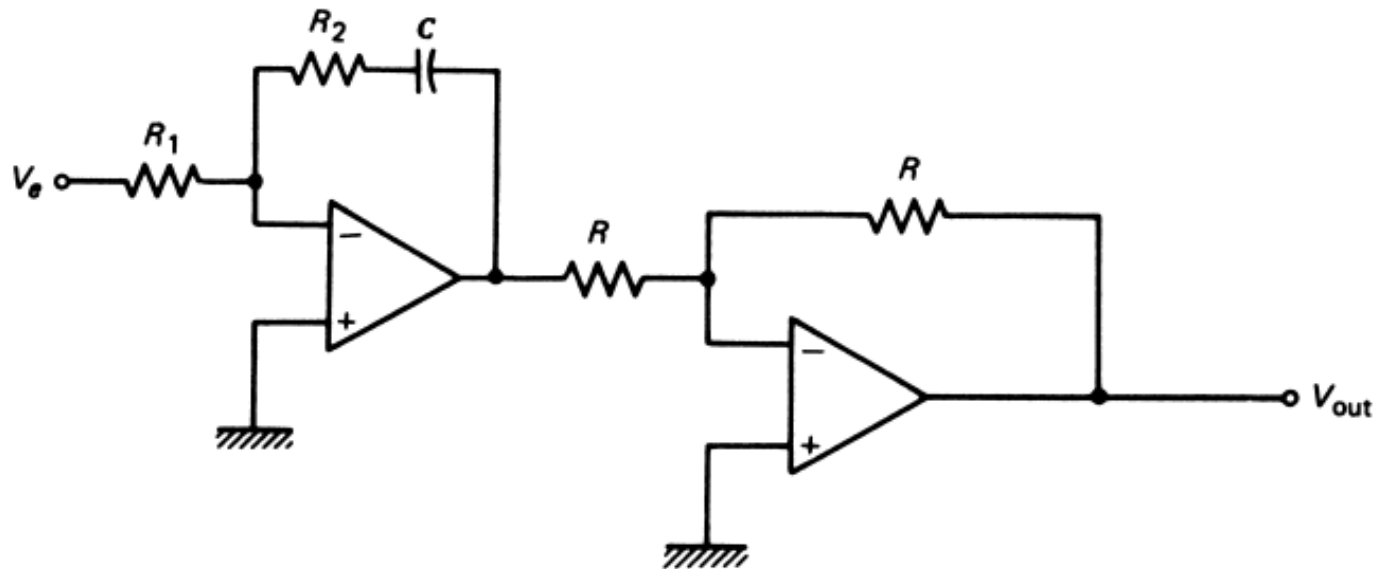
# Proportional-Integral

- A simple combination of the proportional and integral circuits provides the proportional-integral mode of controller action.


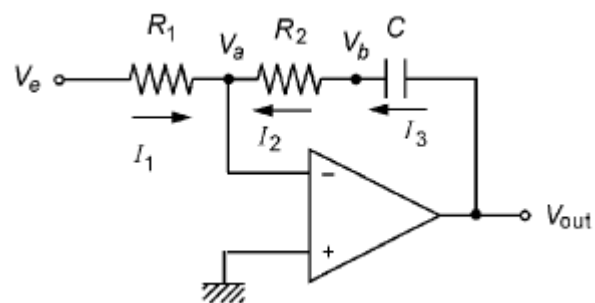
$$P = K_p e_p + K_p K_I \int_0^t e_p dt + P_I(0)$$



$$I_1 + I_2 = 0$$

$$I_3 - I_2 = 0$$

The relationship between the voltage across the capacitor is given by

$$I_c = C \frac{dV_c}{dt}$$

Where  $V_c$  is the voltage across the capacitor

$$\frac{V_e}{R_1} + \frac{V_b}{R_2} = 0$$

$$C \frac{d}{dt} [V_{out_1} - V_b] - \frac{V_b}{R_2} = 0$$

The Eq. can be solved for  $V_b$  as:

$$V_b = -\frac{R_2}{R_1} V_e$$

Substituting this in to Eq.

$$C \frac{dV_{out_1}}{dt} - C \frac{d}{dt} \left( -\frac{R_2}{R_1} V_e \right) - \frac{1}{R_2} \left( -\frac{R_2}{R_1} V_e \right)$$

$$C \frac{dV_{out_1}}{dt} + C \frac{R_2}{R_1} \frac{d}{dt} V_e + \frac{1}{R_1} V_e = 0$$

$$\text{Or, } \frac{dV_{out_1}}{dt} + \frac{R_2}{R_1} \frac{d}{dt} V_e + \frac{1}{R_1 C} V_e = 0$$

In order to solve for  $V_{out}$ , integrate this eq

$$V_{out_1} = -\frac{R_2}{R_1} V_e - \frac{1}{R_1 C} \int_0^t V_e dt + V(0)$$

$$V_{out_1} = -\frac{R_2}{R_1} V_e - \frac{R_2}{R_1} \frac{1}{R_2 C} \int_0^t V_e dt + V(0)$$

- Equation has the same form as for PI mode. The adjustments of this controller are the *proportional band* through  $G_p=R_2/R_1$ ,

$$V_{\text{out}} = \left( \frac{R_2}{R_1} \right) V_e + \frac{1}{R_1 C} \int_0^t V_e dt$$


and the *integration gain* through  $G_I=1/R_2 C$ .

$$V_{\text{out}} = \left( \frac{R_2}{R_1} \right) V_e + \left( \frac{R_2}{R_1} \right) \frac{1}{R_2 C} \int_0^t V_e dt + V_{\text{out}}(0)$$
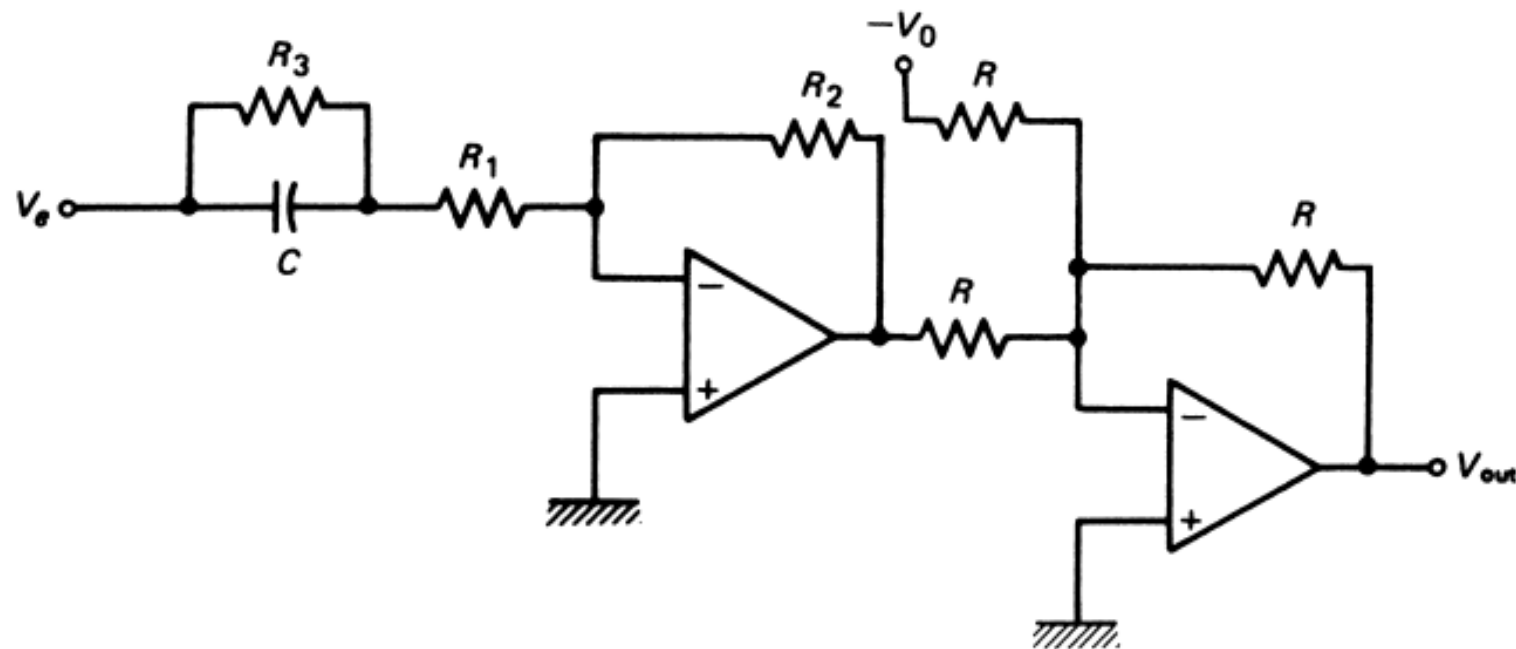
# Proportional Derivative Mode of controller

- PD controller is the combination of proportional and derivative mode of controllers. The general definition of PD controller is:

$$P(t) = K_p e_p + K_p K_D \frac{de_p}{dt} + P(0)$$



$$R = \frac{R_1 R_3}{R_1 + R_3}$$

$$V_{\text{out}} = \left( \frac{R_2}{R_1 + R_3} \right) V_e + \left( \frac{R_2}{R_1 + R_3} \right) R_3 C \frac{dV_e}{dt} + V_0$$


$$2\pi f_{\text{max}} RC = 0.1.$$

$$G_p = R_2 / (R_1 + R_3),$$

$$G_D = R_3 C.$$
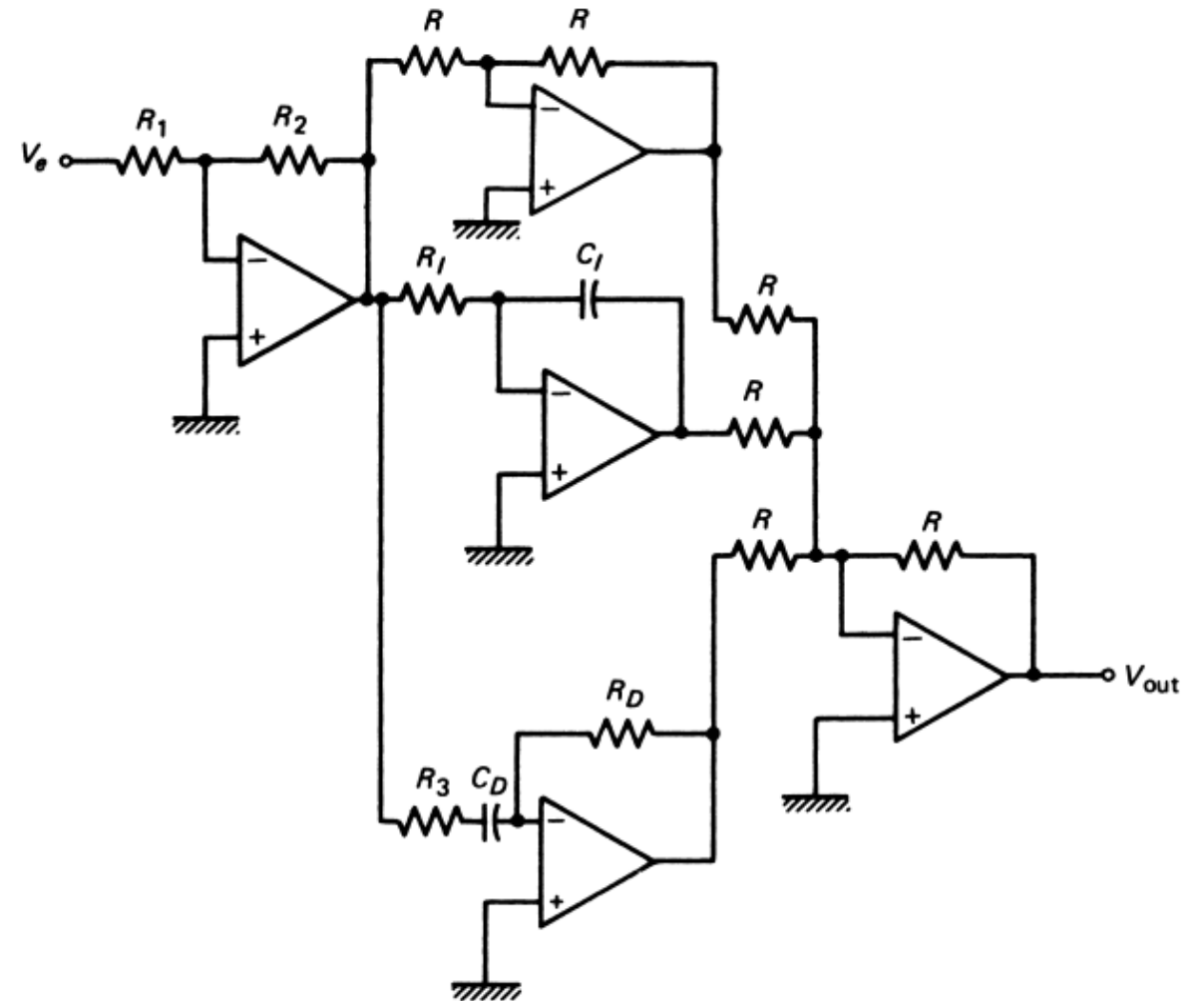
# PID (Three-Mode)

$$p = K_p e_p + K_p K_I \int_0^t e_p dt + K_p K_D \frac{de_p}{dt} + p_I(0)$$



$$V_{p1} = -\frac{R_2}{R_1} V_e$$

$$V_p = \frac{R_2}{R_1} V_e$$

$$V_I = -\frac{1}{R_I C_I} \int_0^t V_{p1} dt \quad \text{or, } V_I = \frac{R_2}{R_1} \frac{1}{R_I C_I} \int_0^t V_e dt$$

$$V_D = -R_D C_D \frac{d}{dt} V_{p1} \quad \text{or, } V_D = \frac{R_2}{R_1} R_D C_D \frac{d}{dt} V_e$$

$$-V_{out} = V_p + V_I + V_D$$

$$-V_{out} = \left( \frac{R_2}{R_1} \right) V_e + \left( \frac{R_2}{R_1} \right) \frac{1}{R_I C_I} \int V_e dt + \left( \frac{R_2}{R_1} \right) R_D C_D \frac{dV_e}{dt} + V_{out} (0)$$

$$G_p = \left( \frac{R_2}{R_1} \right), \quad G_I = \left( \frac{1}{R_I C_I} \right) \quad \text{and} \quad G_D = R_D C_D$$

$$-V_{out} = G_p V_e + G_p G_I \int V_e dt + G_p G_D \frac{dV_e}{dt} + V_{out} (0)$$

Adding an inverter at the output stage,

$$V_{out} = G_p V_e + G_p G_I \int V_e dt + G_p G_D \frac{dV_e}{dt} + V_{out} (0)$$





# Pneumatic controllers

- Reason for using pneumatic controllers:
  - 1. Competitive in cost and reliability
  - 2. Safety (Danger of explosion from electrical malfunctions exists.)
  - 3. Final control element is often pneumatically or hydraulically operated, which suggests that an all pneumatic process control loop might be advantageous.
- It appears that analog or digital electronic methods will eventually replace most pneumatic installations. But we will still have pneumatic equipment for many years until these are depreciated in industry

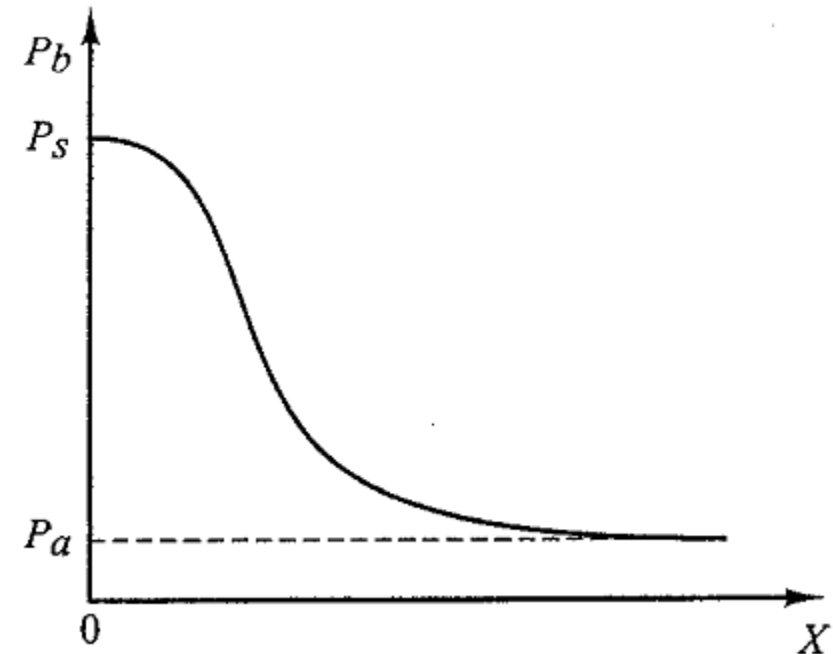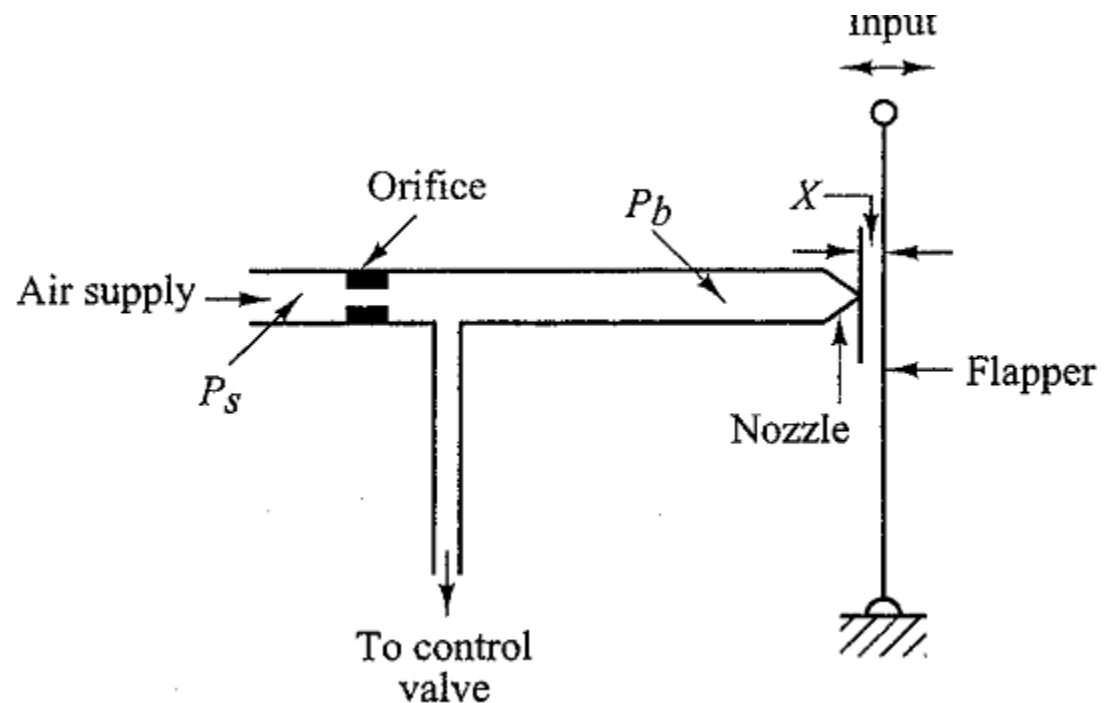
# Pneumatic Nozzle-Flapper systems. (Nozzle/baffle)

- signal conversion is from pressure to mechanical motion and vice versa



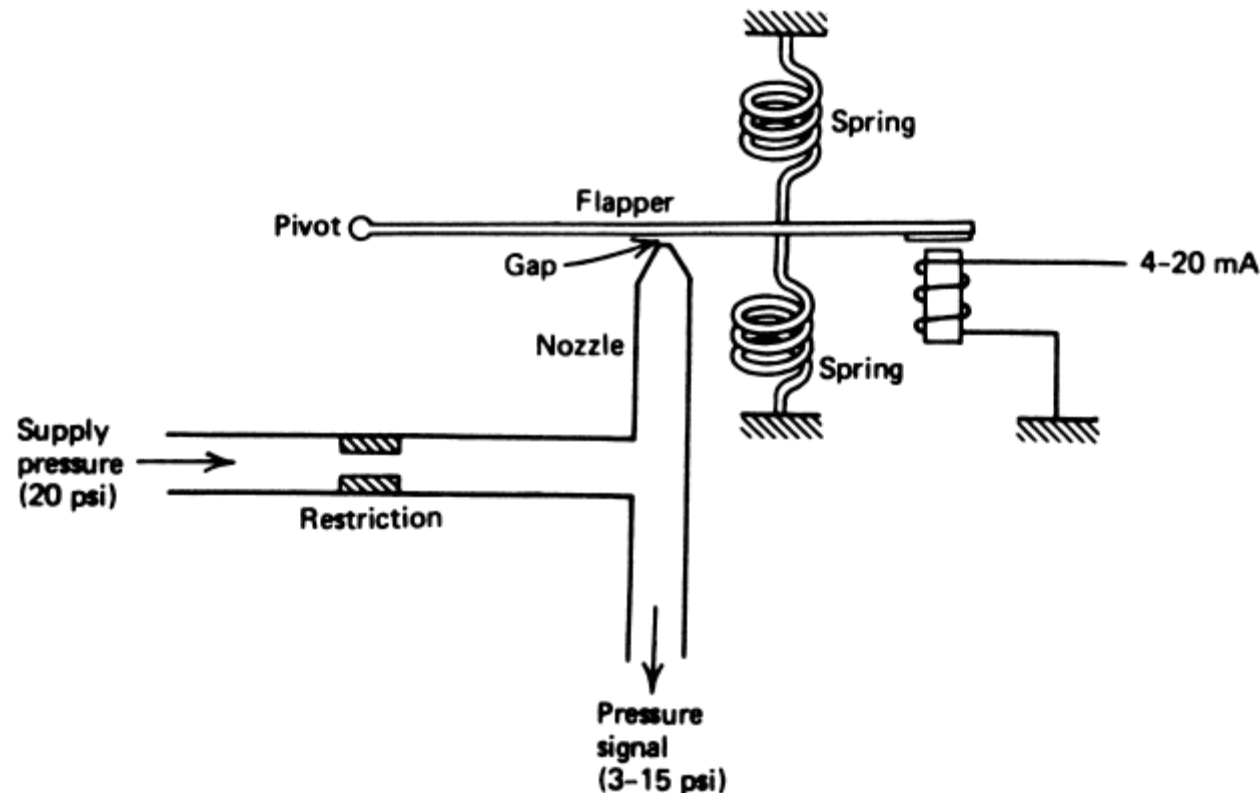
# Using a nozzle/flapper for a current-to-pressure converter

- A linear way of translating the 4- to 20-mA current into a 3- to 15-psig signal






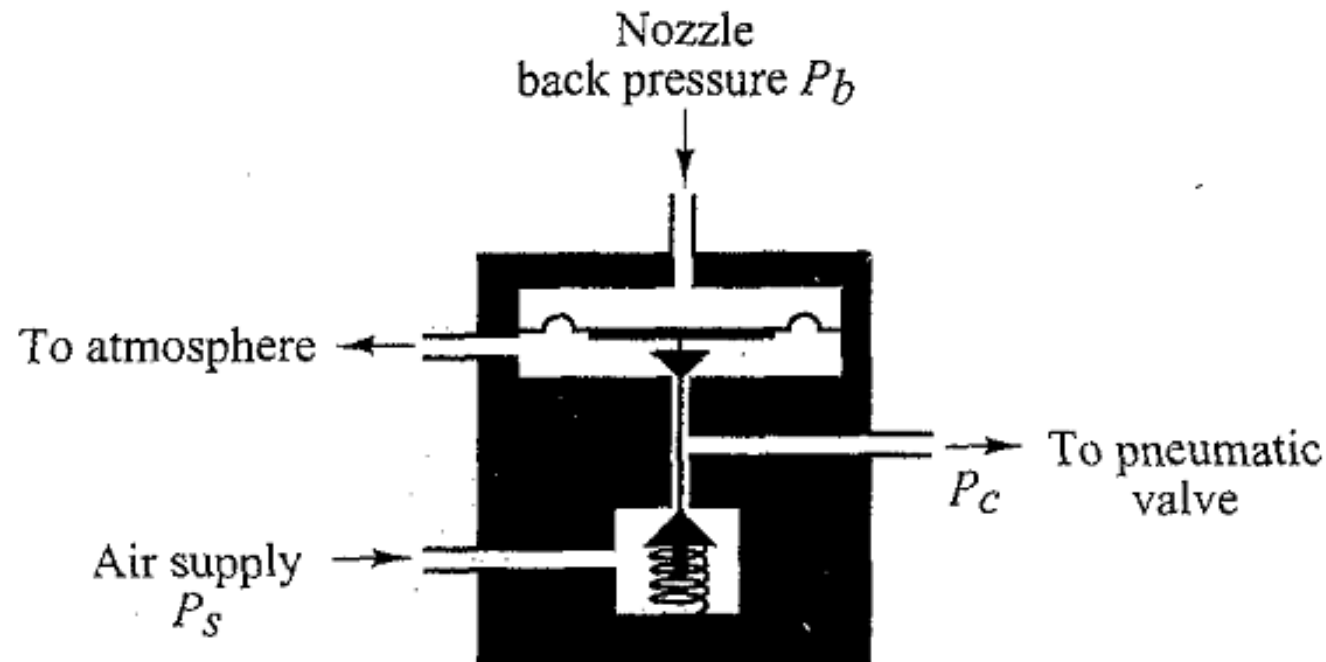
# Pneumatic Relays

- In a pneumatic controller, a nozzle-flapper amplifier acts as the first-stage amplifier and a pneumatic relay as the second-stage amplifier.


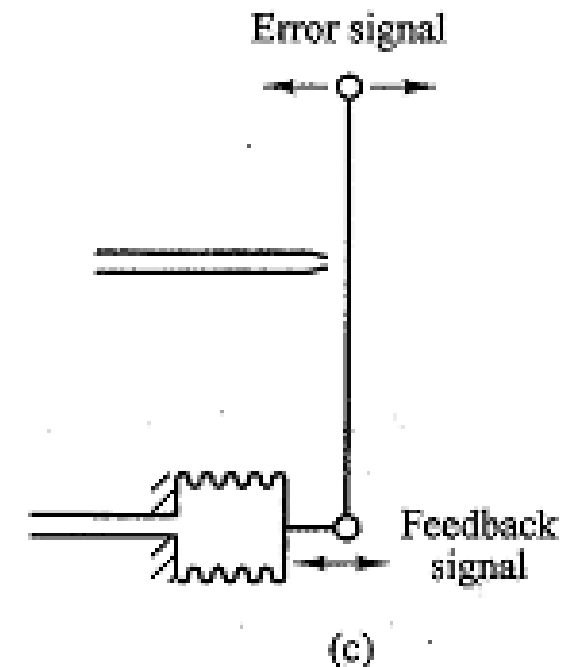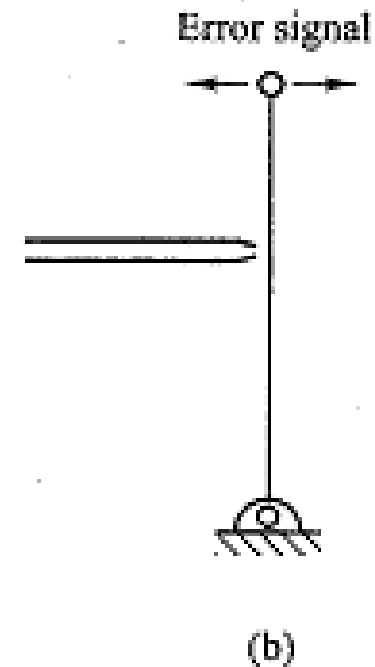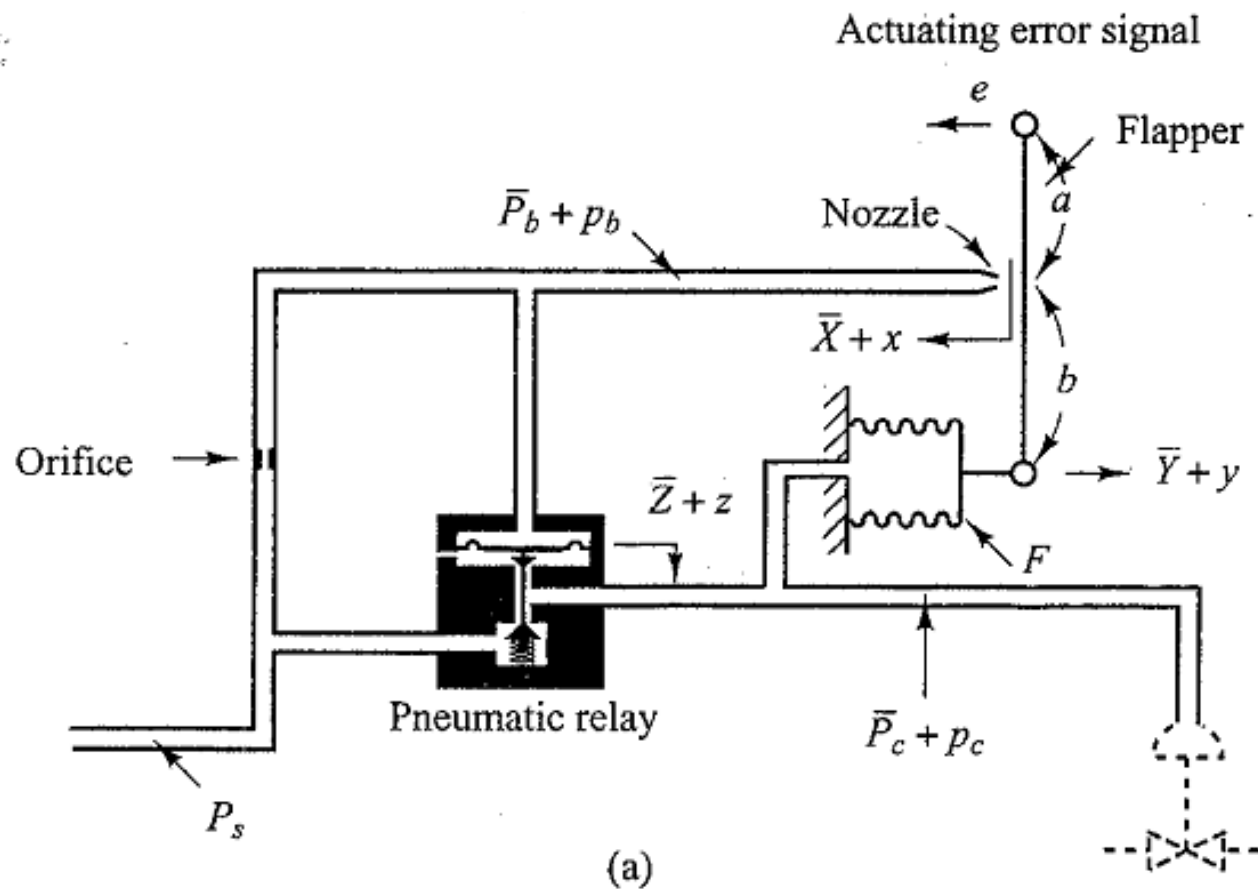
# Pneumatic Proportional Controllers (Force-Distance Type)



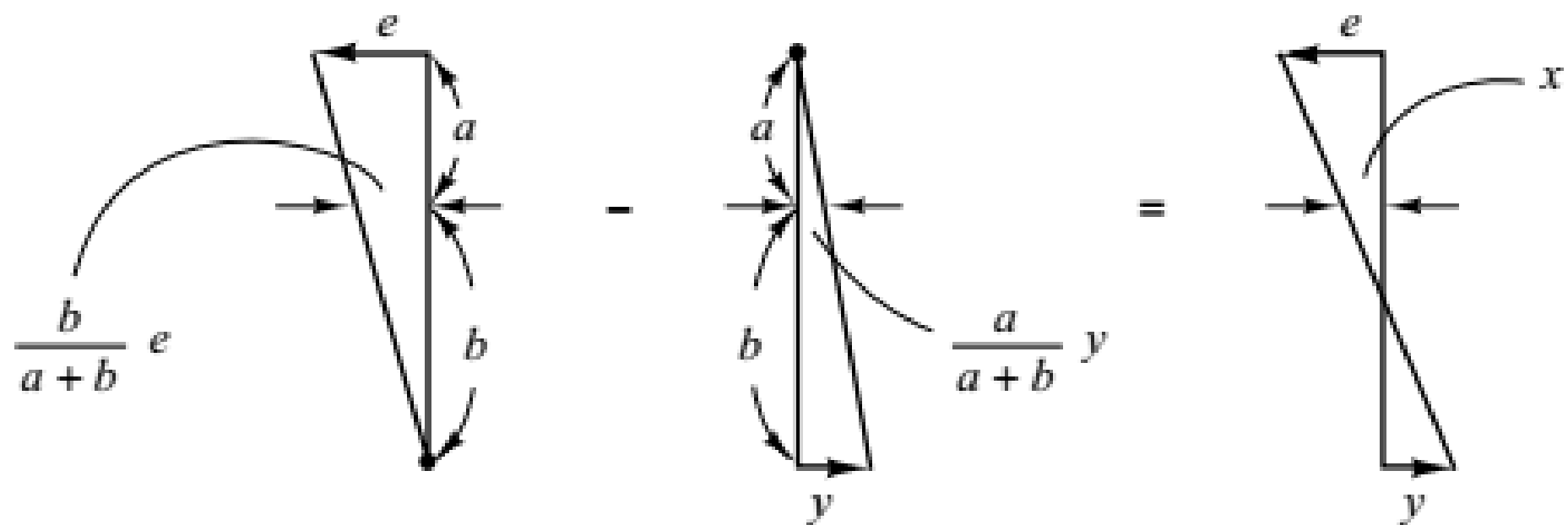

$$p_c = K_3 z$$


$$p_c = \frac{K_3}{K_2} p_b = \frac{K_1 K_3}{K_2} x = K x$$

$$x = \frac{b}{a+b} e - \frac{a}{a+b} y$$

$$A p_c = k_s y$$


$$\frac{P_c(s)}{E(s)} = \frac{\frac{b}{a+b} K}{1 + K \frac{a}{a+b} \frac{A}{k_s}} = K_p$$

## Block diagram for the controller

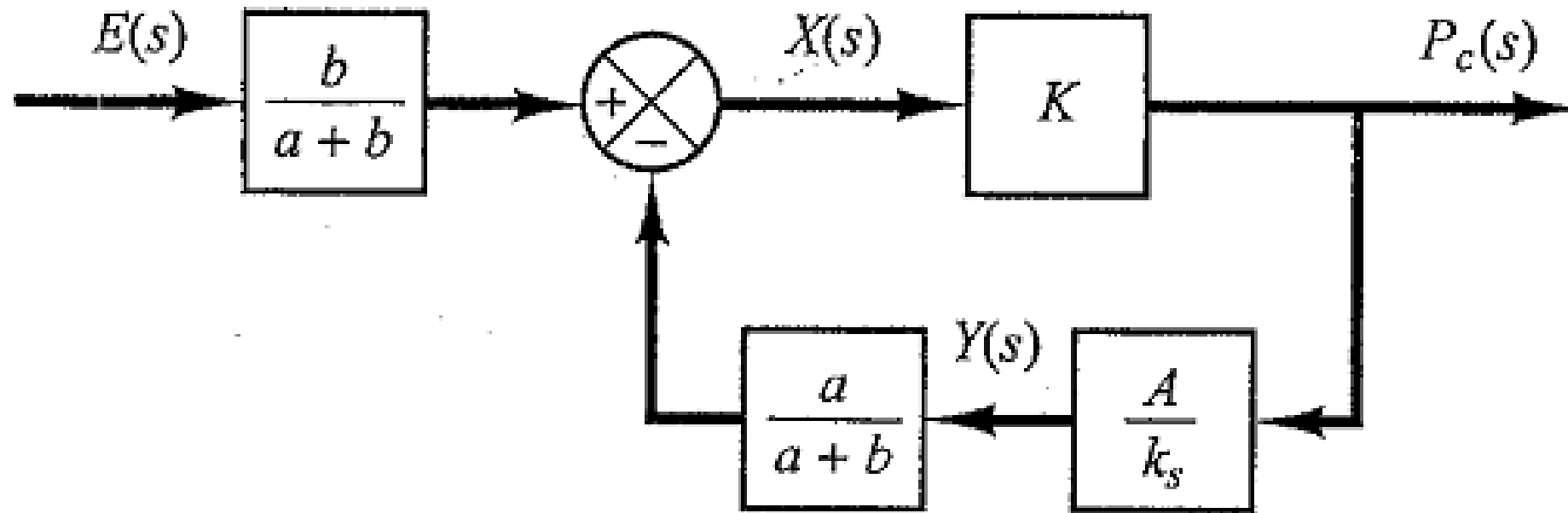




# Pneumatic two-position controllers or pneumatic on–off controllers

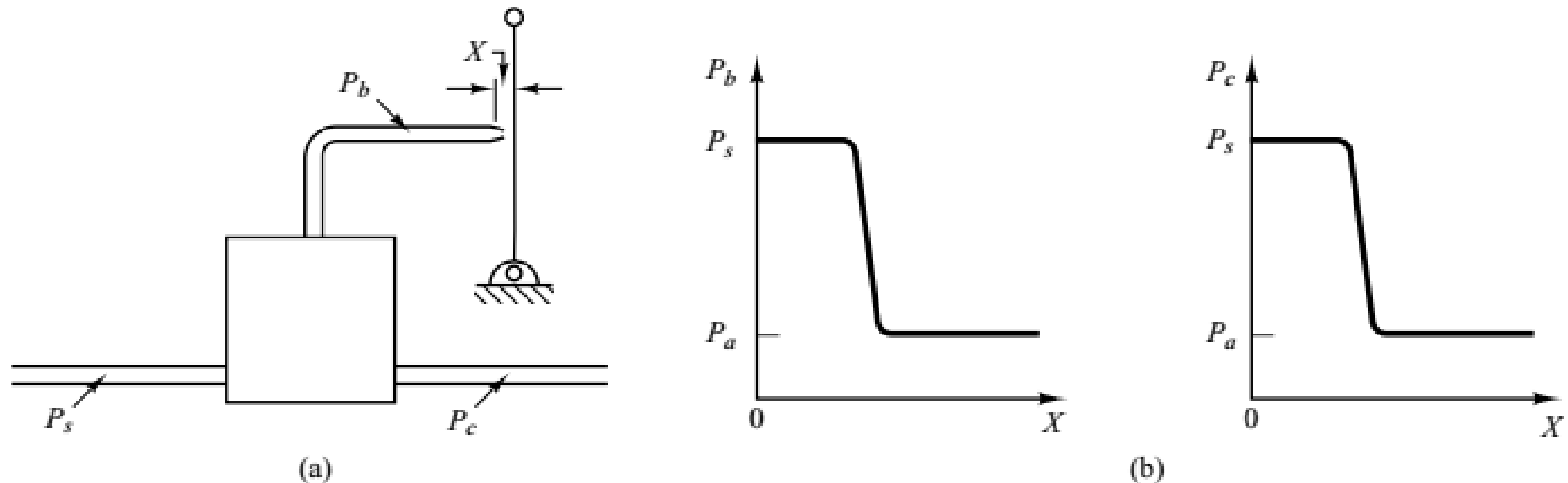

**Figure 4–9**

(a) Pneumatic controller without a feedback mechanism; (b) curves  $P_b$  versus  $X$  and  $P_c$  versus  $X$ .
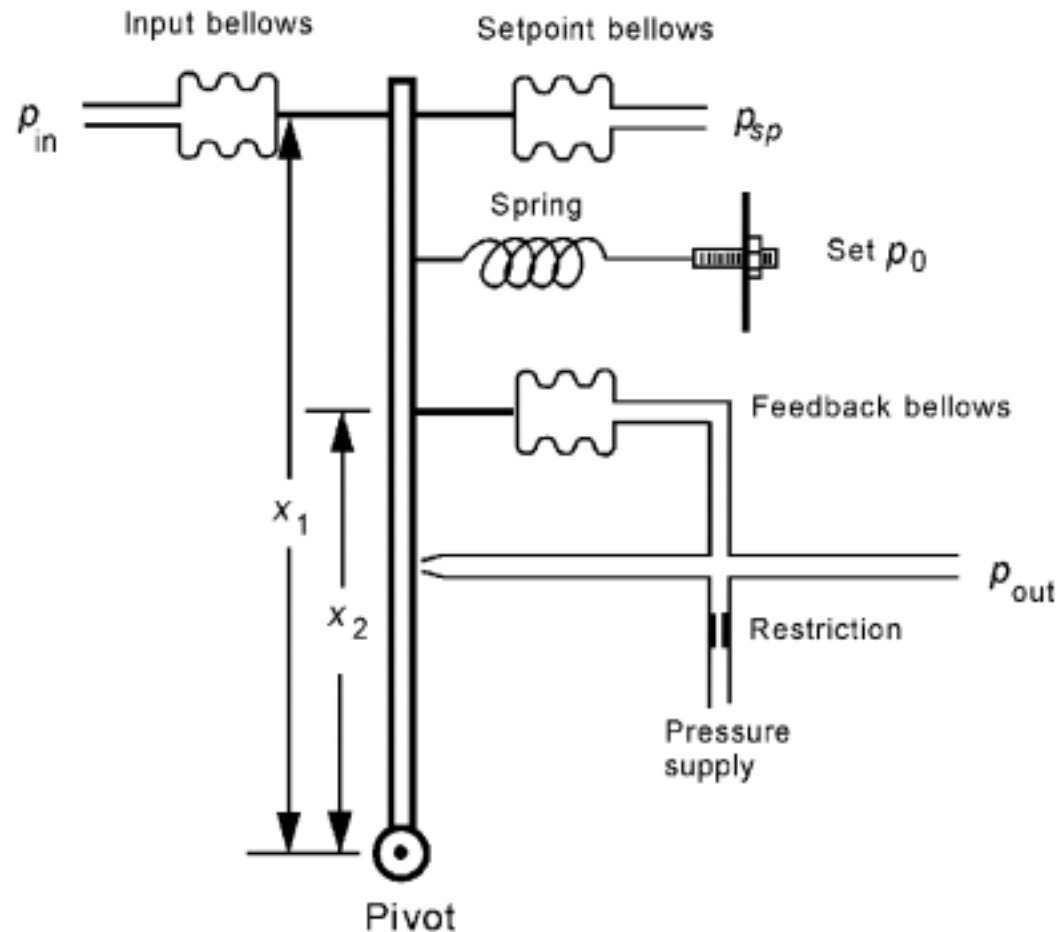
# Second implementation of Proportional Controllers



$$(p_{out} - p_0)A_2x_2 = (p_{in} - p_{sp})A_1x_1$$

$$p_{out} = \frac{x_1}{x_2} \frac{A_1}{A_2} (p_{in} - p_{sp}) + p_0$$

$p_0$  = pressure with no error

$p_{in}$  = input pressure (Pa)

$A_1$  = input and setpoint bellows effective area

$x_1$  = level arm of input (m)

$p_{out}$  = output pressure (Pa)



$A_2$  = feedback bellows effective area ( $m^2$ )

$x_2$  = feedback lever arm (m)

$p_{sp}$  = setpoint pressure

$$K_p = \left( \frac{x_1}{x_2} \right) \left( \frac{A_1}{A_2} \right)$$


# PD Mode

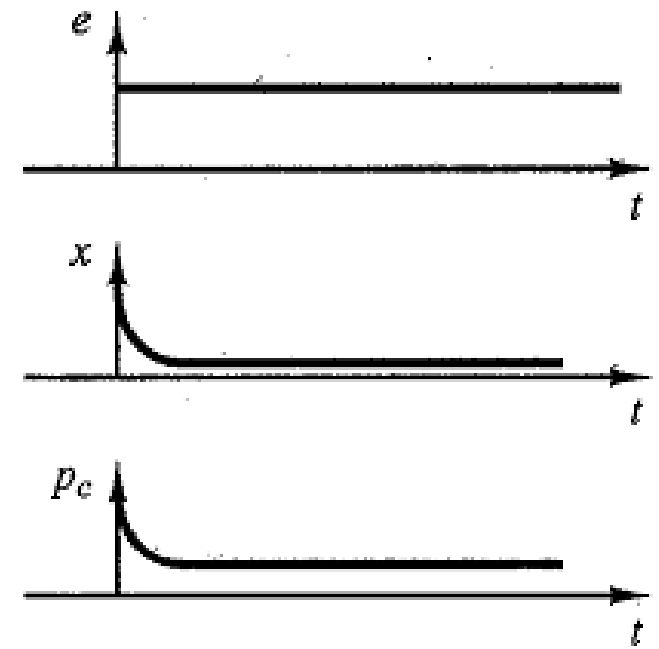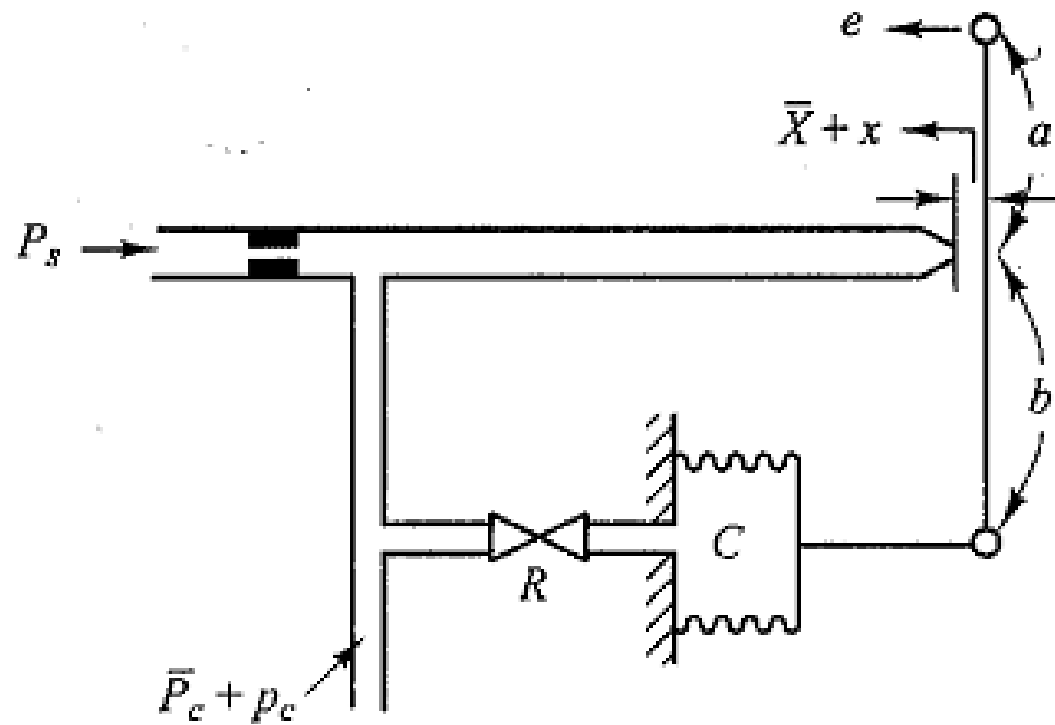

(h)


$$\frac{P_c(s)}{E(s)} = \frac{\frac{b}{a+b} K}{1 + \frac{Ka}{a+b} \frac{A}{k_s} \frac{1}{RCs + 1}}$$
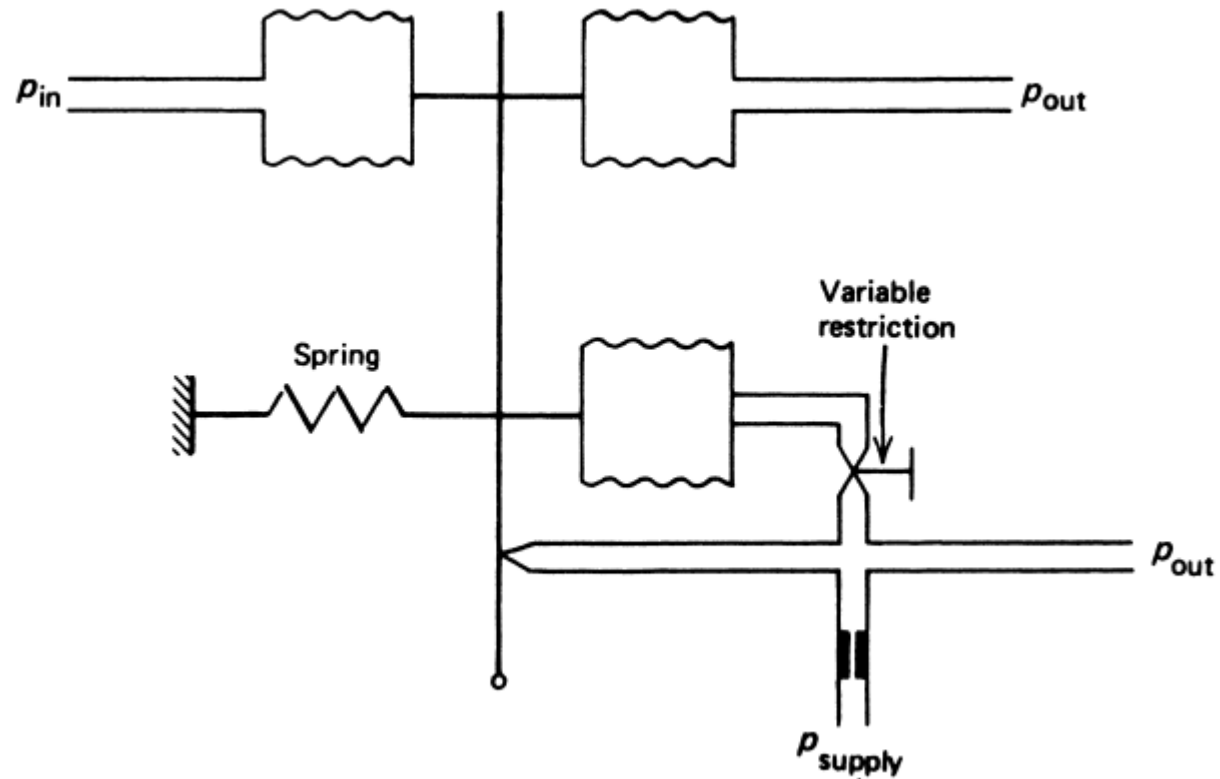
# Pneumatic **proportional-derivative** controller.


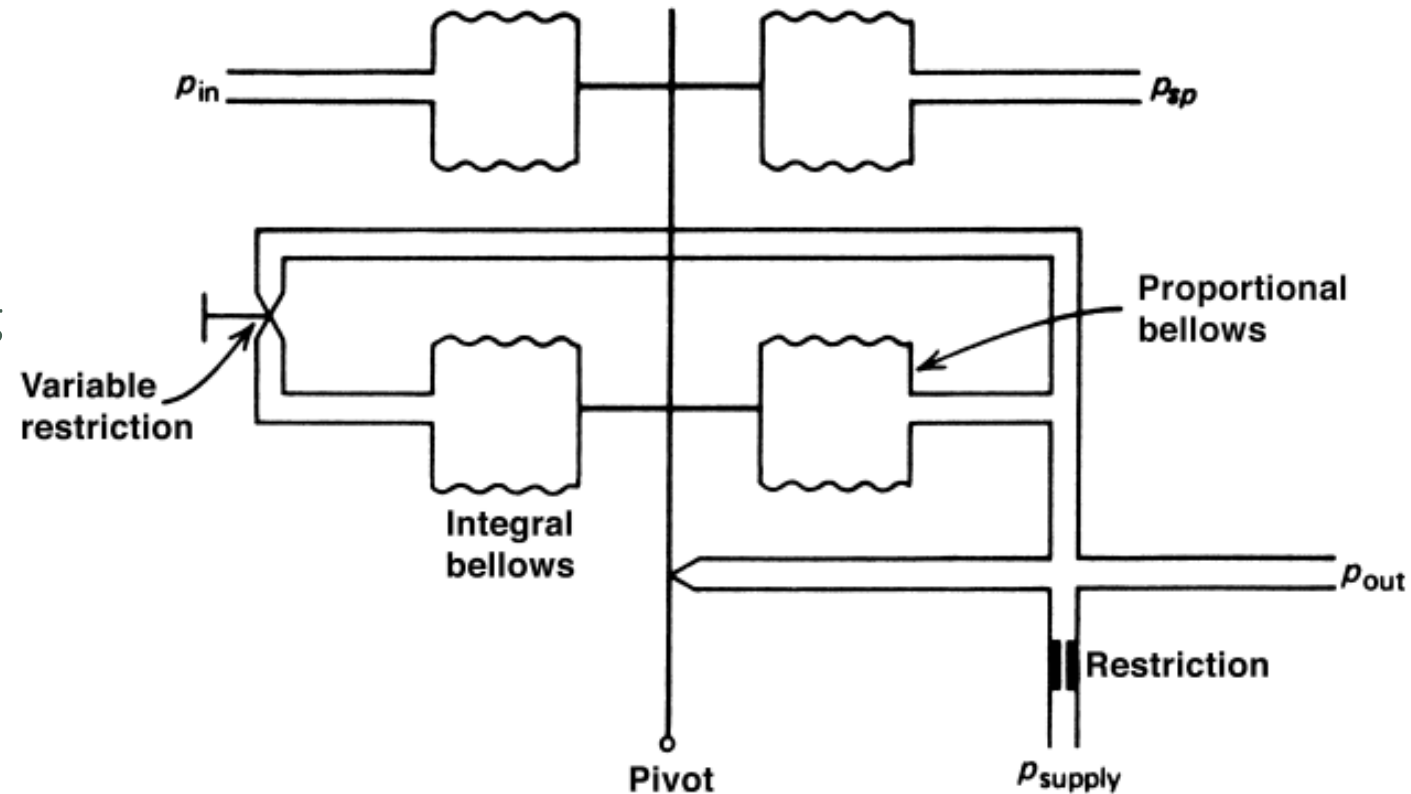
# Proportional-Integral

- An extra bellows with a variable restriction is added to the proportional system.
- The integral bellows slowly moves the Flapper closer to the nozzle, thereby causing a steady increase in output pressure (as dictated by the integral mode).



# Three-Mode

