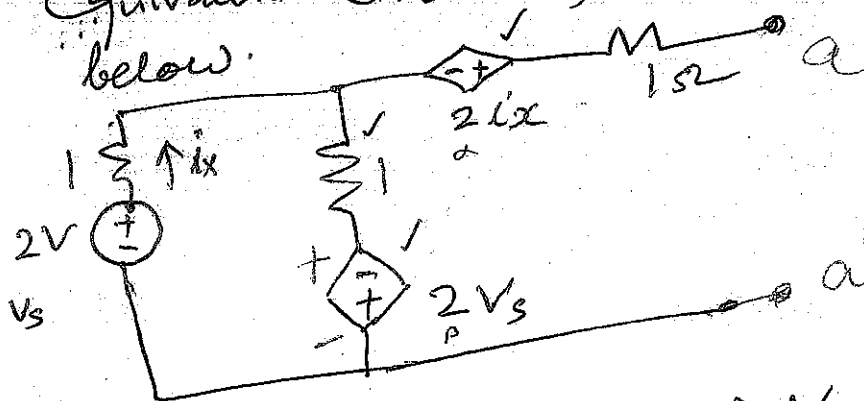


1A) Draw the Thevenin Equivalent Circuit and Norton Equivalent Circuit for the Circuit shown in figure below.




$$i_x = \frac{V_s - 2V_s}{2} = \left(\frac{1-2}{2}\right) V_s = -\frac{1}{2} \times 2 = -1$$


$$\begin{aligned} V_{th} &= 2V_s + 2i_x + 1 \cdot i_x \\ &= 2V_s + (1+2)i_x \\ &= 2V_s + 3\left(-\frac{1}{2}\right)V_s \end{aligned}$$

$$V_{th} = V_s \left[2 - \frac{3}{2} \right] = \frac{V_s}{2} = \frac{2}{2} = 1V$$

Calculation for Z_{th}

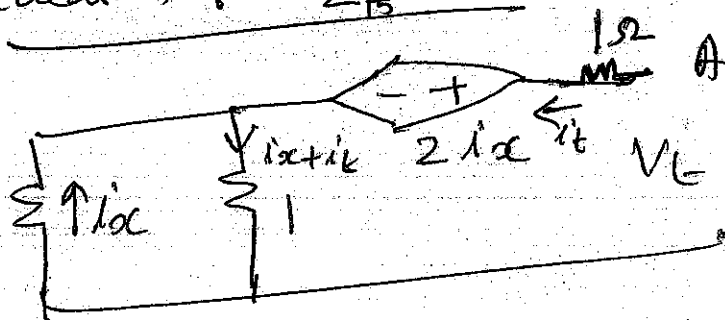

$$Z_{th} = \frac{V_{th}}{i_{th}}$$


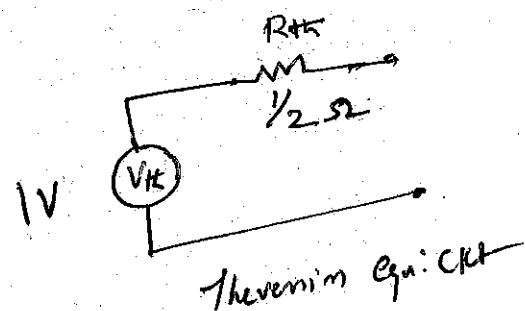


loop 1: $I_x + I_x + I_t = 0$
 $\therefore I_x = -\frac{I_t}{2}$

loop 2: $V_t = 1 \cdot I_t + 2I_x + 1 \cdot I_t + I_t$

$$V_t = I_t - 2 \cdot \frac{I_t}{2} - \frac{I_t}{2} + I_t = \frac{I_t}{2}$$
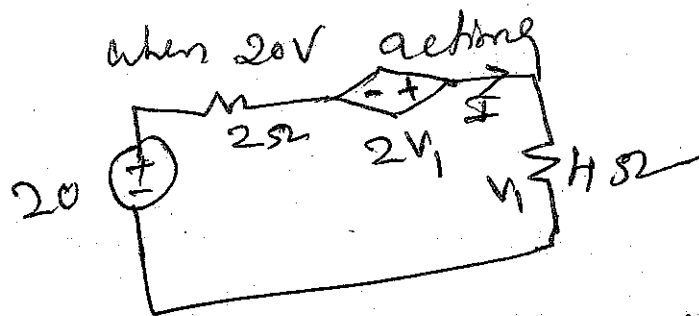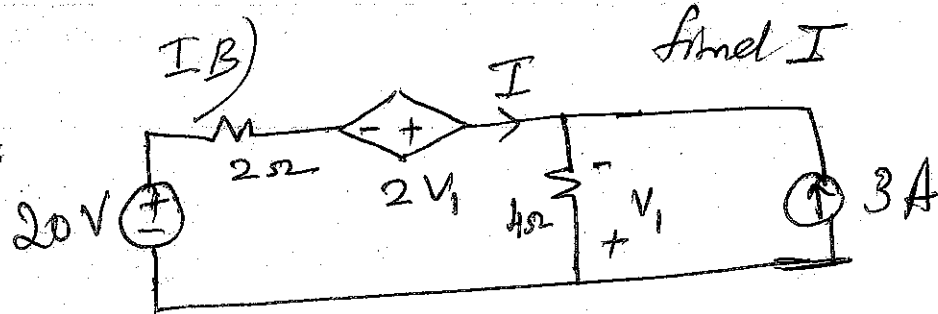
$$\therefore Z_{th} = \frac{V_{th}}{I_{th}} = \frac{1V}{2A} = \frac{1}{2} \Omega \text{ Ans.}$$



$$6I = 20 + 2V_1 \quad (1)$$

$$\text{But } V_1 = -4I \quad (2)$$

(1) gives $6I + 8I = 20$

$$I = \frac{20}{14}$$

when 3A active

$$2I + (I + 3)4 = 2V_1 \quad (3)$$


$$\text{But } V_1 = -(3I + 4)4 \quad (4)$$

∴ (3) gives


$$2I + 4I + 12 = -24 - 8I$$

$$\therefore I = -\frac{36}{14}$$

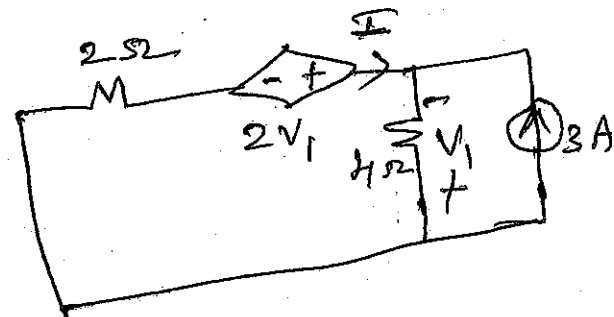∴ Total Current $= I = \frac{20}{14} - \frac{36}{14} = -\frac{16}{14} = -\frac{8}{7} \text{ A}$



IC)

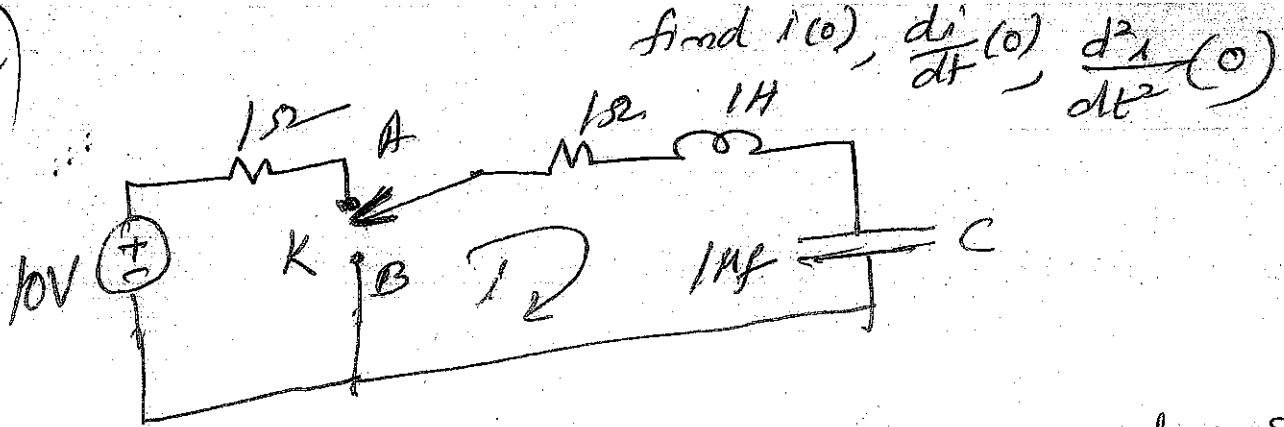

at $t=0$, $i=0$, \therefore capacitor is already charged to 10V and open circuited $\therefore i=0$

$\therefore \underline{i(0) = 0}$ Ans

at position 2

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad (1)$$

$$R(0) + \frac{di}{dt} + 10 = 0$$

$$\therefore \frac{di(0)}{dt} = \underline{\underline{-10 \text{ A/sec}}}$$

diff Eqn (1)



$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

$$\text{at } t=0, i=0, \frac{di}{dt}(0) = -10$$

$$\therefore -10 + \frac{d^2i}{dt^2}(0) + 0 = 0$$

$$\therefore \underline{\underline{\frac{d^2i}{dt^2}(0) = 10 \text{ A/sec}^2}}$$

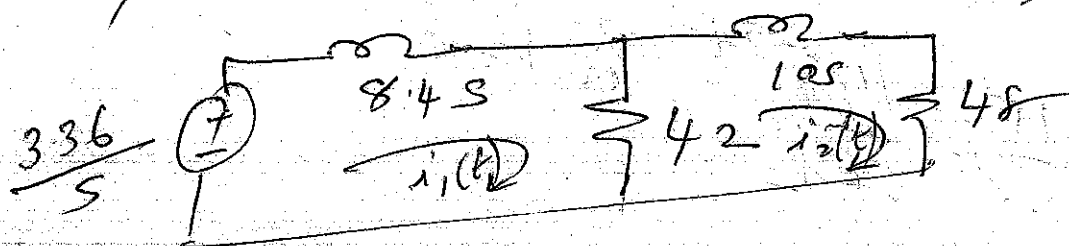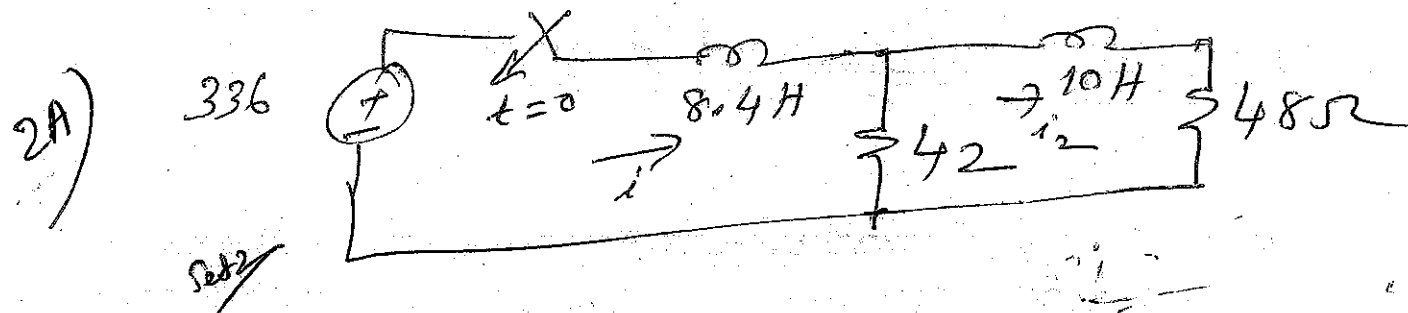1A) Obtain the expression for i_1 and i_2 in the circuit shown in figure 9. when a DC voltage is applied suddenly. Assume that ~~the~~ the initial energy stored in the circuit is zero. Use transform method.



KVL, mesh eqn

$$\frac{336}{s} = (42 + 8.4s)i_1 - 42i_2$$


$$0 = -42i_1 + (90 + 10s)i_2$$

$$\Delta = \begin{vmatrix} 42 + 8.4s & -42 \\ -42 & 90 + 10s \end{vmatrix} = 0, \quad \Delta = 84(s^2 + 14s + 24) = 84(s+2)(s+12)$$

$$i_1 = \frac{\begin{vmatrix} 336s & -42 \\ 0 & 90 + 10s \end{vmatrix}}{\Delta} = \frac{40(s+9)}{s(s+2)(s+12)}$$

$$\text{Hence } i_2 = \frac{\begin{vmatrix} 42 + 8.4s & 336/s \\ -42 & 0 \end{vmatrix}}{\Delta} = \frac{168}{s(s+2)(s+12)}$$

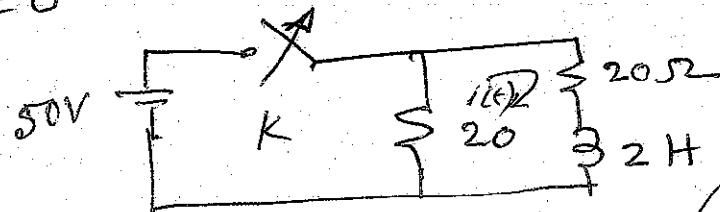Q. Find the Current Equation when the switch K is opened at $t = 0$



(2 mark)

Soln: Switch K opened at $t = 0$, KVL

$$20i' + 20i + 2 \frac{di}{dt} = 0$$

divide by 2

$$(s + 20)i' = 0$$


$$i' = C_1 e^{-20t}$$

$$\text{at } t = 0, i = 2.5$$

$$2.5 = C_1$$

$$\therefore i(t) = \underline{\underline{2.5 e^{-20t}}}$$

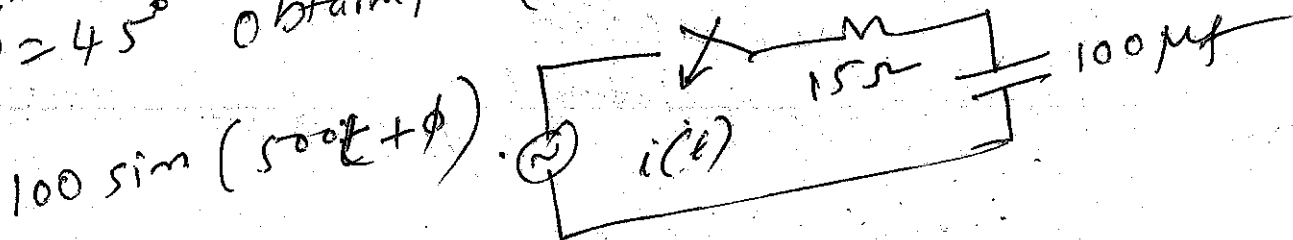Q2B) The circuit shown in figure c) consists of series RC elements with $R = 15 \Omega$ and $C = 100 \mu F$. A sinusoidal voltage $V = 100 \sin(500t + \phi)$ Volt is applied to the circuit at time corresponding to $\phi = 45^\circ$ obtain the current transient $i(t)$



KVL

$$15i + \frac{1}{100 \times 10^{-6}} \int i dt = 100 \sin(500t + \phi)$$

$$\text{diff: } 15 \frac{di}{dt} + \frac{i}{100 \times 10^{-6}} = (100)(500) \cos(500t + \phi)$$

Partial fraction

$$i_1 = \frac{15}{s} - \frac{14}{s+2} - \frac{1}{s+12}$$

$$i_2 = \frac{7}{s} - \frac{8.4}{s+2} + \frac{14}{s+12}$$

\therefore taking \mathcal{L}^{-1} transform

$$i_1 = \frac{15}{s} - \frac{14e^{-2t}}{s+2} - \frac{1}{s+12}$$


$$i_1 = (15 - 14e^{-2t} - e^{-12t}) \text{ A}$$

$$i_2 = (-8.4e^{-2t} + 1.4e^{-12t})$$

Ans

Z parameter

3A)

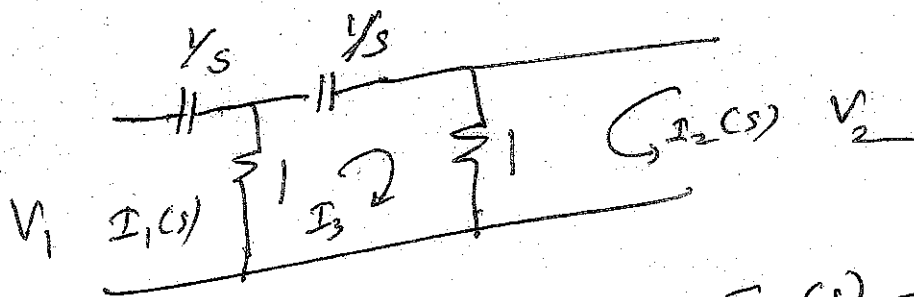

$$\text{Mesh 1 } V_1 = \left(1 + \frac{1}{s}\right) I_1(s) - I_3(s) \quad \text{--- (1)}$$

$$\text{Mesh 2 } V_2 = (I_2(s) + I_3(s)) \cdot 1 \quad \text{--- (2)}$$

$$\text{Mesh 3 } -I_1(s) + I_2(s) + I_3(s) \left(\frac{4s+1}{2s}\right) = 0 \quad \text{--- (3)}$$

$$\text{From (3) } I_3(s) = I_1(s) - I_2(s) \left(\frac{2s}{4s+1}\right) \quad \text{--- (4)}$$

(4) in (1)

$$V_1(s) = \frac{2s^2 + 5s + 1}{s(4s+1)} I_1(s) + \left(\frac{2s}{4s+1}\right) I_2(s) \quad \text{--- (5)}$$

$$(4) \text{ in (2) } V_2(s) = \left(\frac{2s}{4s+1}\right) I_1(s) + \left(\frac{2s+1}{4s+1}\right) I_2(s) \quad \text{--- (6)}$$

By Comparison $V_1 = Z_{11} I_1 + Z_{12} I_2$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

$$\therefore Z_{11} = \frac{2s^2 + 5s + 1}{s(4s+1)}$$

$$Z_{21} = \frac{2s}{4s+1}$$

$$Z_{12} = \frac{2s}{4s+1}$$

$$Z_{22} = \frac{2s+1}{4s+1}$$

Ch: Eqn: $(5 + 666.67) i = 3333.3 \cos(500t + \phi) \rightarrow (1)$

Complementary function $i_c = K_1 e^{-666.67t}$

Particular Current $i_p = A \cos(500t + 45) + B \sin(500t + 45)$

$i_p' = -500A \sin(500t + 45) + 500B \cos(500t + 45)$

Sub: i_p and i_p' in Eqn: (1)

$$-500A \sin(500t + 45) + 500B \cos(500t + 45) + 666.67A \cos(500t + 45) + 666.67B \sin(500t + 45) = 3333.3 \cos(500t + \phi)$$

$$500B + 666.67A = 3333.3$$

$$666.67B - 500A = 0$$

Solving $A = 3.2, B = 2.4$

$$\therefore i_p = 3.2 \cos(500t + 45) + 2.4 \sin(500t + 45)$$

$$i_p = 4 \sin(500t + 98.13)$$

$$\therefore i = i_c + i_p = K_1 e^{-666.67t} + 4 \sin(500t + 98.13)$$

at $t = 0, 15i = 100 \sin 45$

$$i = \frac{100}{15} \sin 45 = \underline{\underline{4.71}}$$

at $t = 0, 4.71 = K_1 + 4 \sin 98.13$


$$\therefore K_1 = 0.75$$

$$\therefore i(t) = 0.75 e^{-666.67t} + 4 \sin(500t + 98.13^\circ)$$



3B. $y(t) = t^2 x(t-1) \Rightarrow M, C, US, L, TV \& NIMV$
 with justification $\rightarrow 0.5 \times 6 = 3m$

3C. (i) $x(t) = e^{jt}$ is periodic
 with $\omega_0 = 1$, $T = \frac{2\pi}{\omega_0} = 2\pi$... 1m } (2m)
 (ii) $x(t) = \cos(3\pi t)$ is Nonperiodic

4A. $x(t) = u(t+1) - u(t-1)$

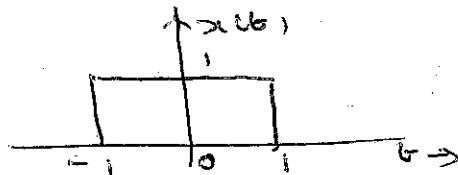

$h(t) = u(t-1) - 2u(t) + u(t+1)$

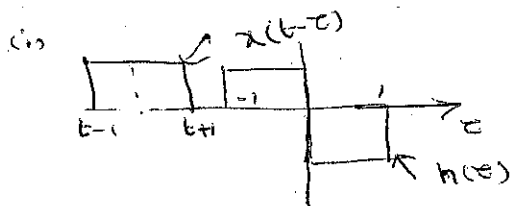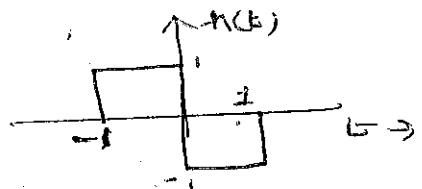

for $t+1 < -1$ i.e. $t < -2$
 $y(t) = 0$

1M

(i) for $t+1 > -1$ & $t+1 < 0$ i.e. $-2 \leq t \leq -1$,

$$y(t) = \int_{-1}^{t+1} d\tau = \underline{t+2}$$

(ii) for $t+1 > 0$ & $t-1 < -1$ i.e. $-1 \leq t < 0$

$$y(t) = \int_{-1}^0 d\tau - \int_0^{t+1} d\tau = \underline{-t}$$

1.5m

(iii) for $t-1 > -1$ & $t-1 < 0$ i.e. $0 \leq t \leq 1$


$$y(t) = \int_{t-1}^0 d\tau - \int_0^1 d\tau = \underline{-t}$$

1.5m

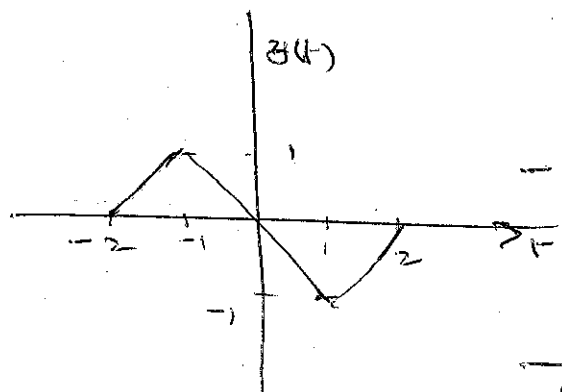(iv) for $t-1 > 0$ & $t-1 < 1$

i.e. $1 \leq t \leq 2$ $y(t) = -\int_{t-1}^1 d\tau = \underline{t-2}$

$$\begin{aligned} y(t) &= 0 & t \leq -2 \\ &= t+2 & -2 \leq t < -1 \\ &= -t & -1 \leq t < 1 \\ &= t-2 & 1 \leq t \leq 2 \\ &= 0 & t \geq 2 \end{aligned}$$



1m

5m

4B. (i) $x(t) = \delta(t+1) + \delta(t-1)$


$S(t) \xrightarrow{FT} 1$

$\delta(t-t_0) \xrightarrow{FT} e^{-j\omega t_0}$

$X(j\omega) = e^{-j\omega} + e^{-j\omega}$

$= 2\cos(\omega)$

(1M)

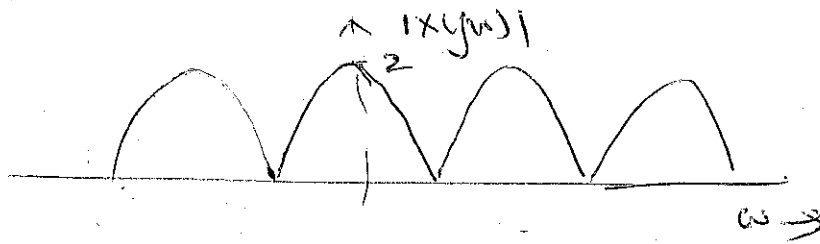

(0.5M)


(ii)

$x(t) = e^{-2t} u(t)$

$X(j\omega) = \int_0^{\infty} e^{-2t} e^{-j\omega t} dt = \frac{1}{2+j\omega}$

$X(j\omega) = \frac{1}{\sqrt{2^2 + \omega^2}} \angle -\tan^{-1} \omega/2$

(1M)

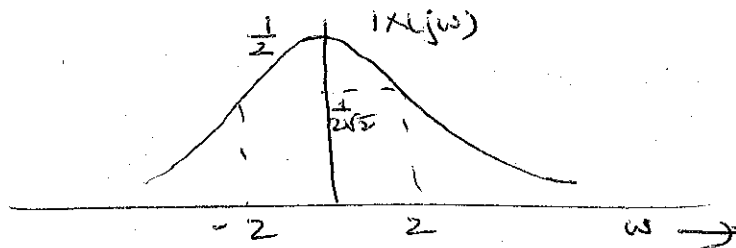

(0.5M)

(3M)

4C.

$x(t) = 1 + \cos(\pi t) + \cos(2\pi t) + \sin(5\pi t)$

Periodic signal \rightarrow Power signal

Use Parseval's theorem. $P = \sum_{k=-\infty}^{\infty} |a_k|^2$

(1M)

$x(t) = 1 + \frac{e^{j\pi t} + e^{-j\pi t}}{2} + \frac{e^{j2\pi t} + e^{-j2\pi t}}{2} + \frac{e^{j5\pi t} - e^{-j5\pi t}}{2j}$

$a_0 = 1, a_1 = a_{-1} = a_2 = a_{-2} = \frac{1}{2}, a_5 = \frac{1}{2j}, a_{-5} = -\frac{1}{2j}$

$P = 1^2 + \frac{1}{2^2} + \frac{1}{2^2} + \frac{1}{2^2} + \frac{1}{2^2} + \frac{1}{2^2} + \frac{1}{2^2}$

$= 2.5W$

(1M)

$E = \infty$

(2M)

5A. $\frac{d^2 y(t)}{dt^2} + 5 \frac{dy(t)}{dt} + 4y(t) = \frac{dx(t)}{dt} + x(t)$

FT $Y(j\omega) [(j\omega)^2 + 5j\omega + 4] = X(j\omega) [j\omega + 1]$ — (0.5M)

(ii) $\frac{Y(j\omega)}{X(j\omega)} = H(j\omega) = \frac{j\omega + 1}{(j\omega)^2 + 5j\omega + 4}$
 $= \frac{j\omega + 1}{(j\omega + 4)(j\omega + 1)} = \frac{1}{j\omega + 4}$ — (1M)

(iii) $h(t) = \mathcal{F}^{-1} \left\{ \frac{1}{j\omega + 4} \right\} = e^{-4t} u(t)$ — (1M)

(iv) for $x(t) = e^{-t} u(t)$

$y(t) = h(t) * x(t)$
 $Y(j\omega) = H(j\omega) \cdot X(j\omega)$ — (1M)

$= \frac{1}{(j\omega + 4)} \cdot \frac{1}{(j\omega + 1)}$

$= \frac{A}{j\omega + 4} + \frac{B}{j\omega + 1}$

$= \frac{1/3}{j\omega + 1} - \frac{1/3}{j\omega + 4}$

$A = \frac{1}{j\omega + 4} \Big|_{j\omega = -4} = \frac{1}{-3}$

$B = \frac{1}{j\omega + 1} \Big|_{j\omega = -1} = \frac{1}{-3}$

$y(t) = \frac{1}{3} \int e^{-t} - e^{-4t} u(t)$ — (1M)

5M

5B:

W.K.T $e^{-t} u(t) \xleftrightarrow{\text{FT}} \frac{1}{j\omega + 1}$ — (1M)

$t e^{-t} u(t) \longleftrightarrow \frac{1}{(j\omega + 1)^2}$ — (1M)

$\frac{d}{dt} [t e^{-t} u(t)] = \frac{j\omega}{(1 + j\omega)^2}$ — (1M)

$x(t) = \frac{d}{dt} [t e^{-t} u(t)]$
 $= (1 - t) e^{-t} u(t)$

2M

5c.

Property

$$x(t) \xrightarrow{\text{FT}} X(j\omega)$$

$$X(j\omega) \xrightarrow{\text{FT}} 2\pi f(-\omega)$$

$$e^{2t} x(t) \xrightarrow{\text{FT}} \frac{1}{2-j\omega}$$

$$- \textcircled{1M}$$

$$\frac{1}{2-j\omega}$$

$$\xrightarrow{\text{FT}}$$

$$2\pi e^{-2\omega} u(\omega)$$

$$- \textcircled{1M}$$

$$\underline{\underline{2M}}$$

_____ 0

_____ 0