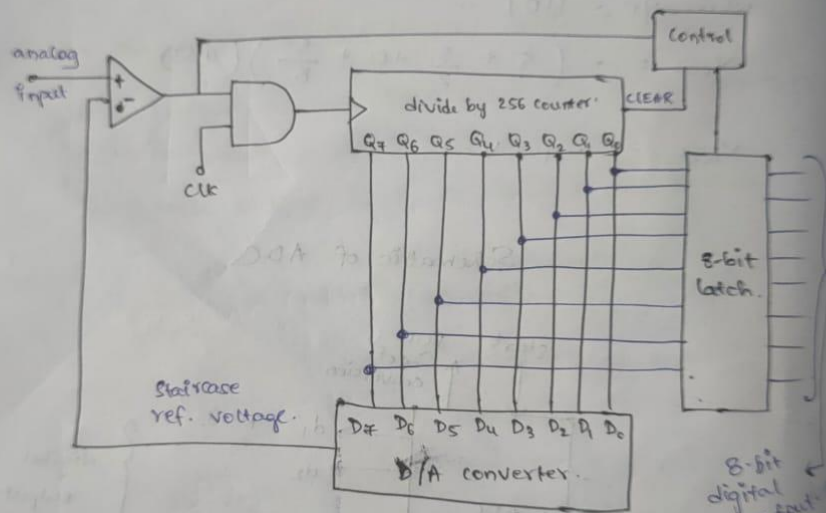


A) Direct type ADC → Compare a given analog signal with the internally generated equivalent signal.


B) Integrating type ADC

↓  
Perform conversion in an indirect manner by  
1<sup>st</sup> changing the analog input signal to a linear  
function of time or freq, & then to a digital code.

A1) Counter type ADC





28/5/22

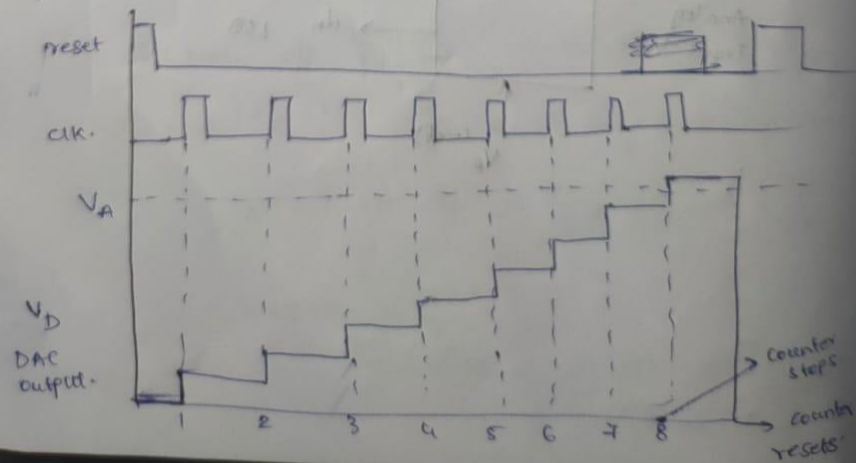


analog signal with the  
ted equivalent signal.

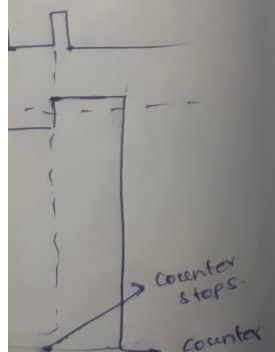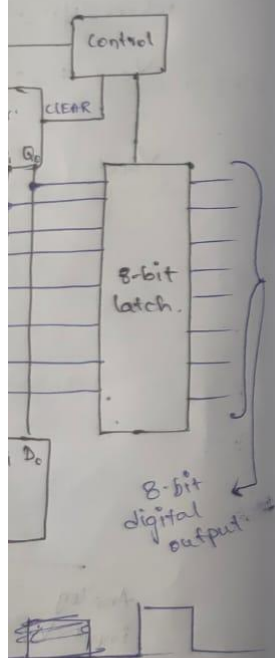direct manner by  
al to a linear  
a digital code.




## A2) Successive Approximation ADC

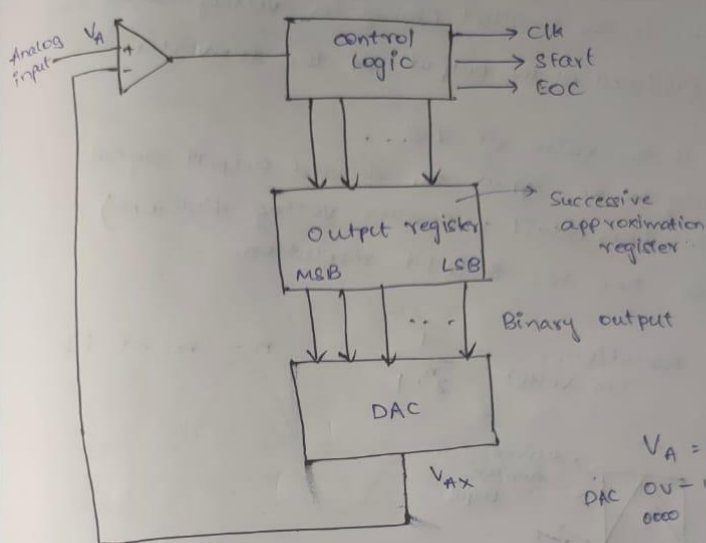

$V_A = 11.4V$

DAC	OV = 15V
0000	1111
1000	→ 2V
1100	→ 12
↓	
1000	
1010	→ 10
↓	
1011	→ 11

## B1) Dual slope ADC

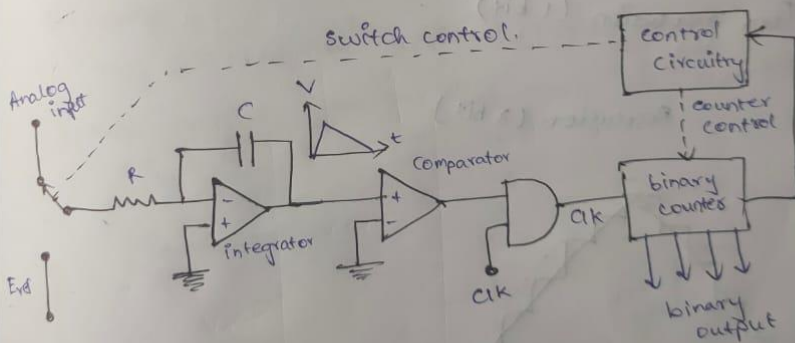

Range - low to medium frequencies

## Performance Specifications


Resolution: is the smallest change in voltage which may be produced at the output of the converter.

It is the value of LSB.

How closely can we approximate the desired output signal (high res. = finer detail = smaller voltage divisions).


A common DAC has 8-12 bit resolution.
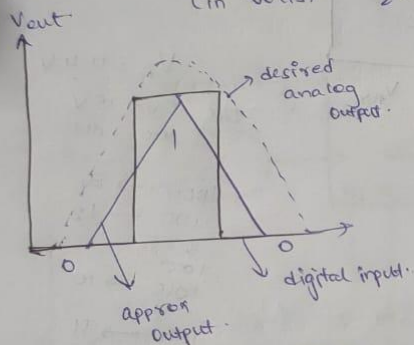
$$\text{Resolution (in volts)} = \frac{1}{2^n - 1} \quad n - \text{no. of bits}$$



Poor resolution (1 bit)


Resolution (3 bit)

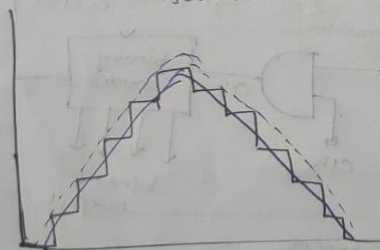

settling time:



time, req for i/p signal voltage to settle to the expected o/p voltage within  $\pm 1/2$  LSB.

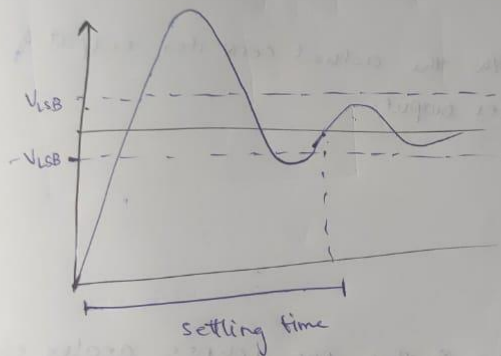Any change in input state will not be reflected in the o/p state



linearity:

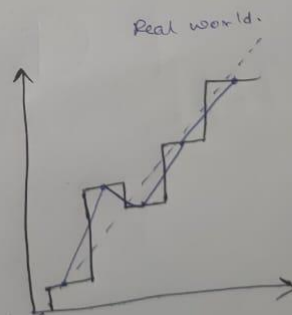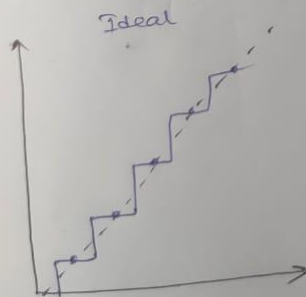The diff b/w the desired analog output and the actual output over the full range of expected values.



Speed :

Accuracy

The max deviation b/w the actual converter output & the ideal converter output.

Monotonicity.

A monotonic DAC is the one whose analog o/p increases for an increase in digital input.

