

I n d e x

S. No.	Name of the Experiment	Page No.	Date of Experiment	Date of Submission	Remarks
1.	Photo Devices & Error Analysis		15.11.2021		Nandalal
2.	Verification of series & parallel resonance		18.11.2021		
3.	Measurement of inductance by Maxwell's Bridge		22.11.2021		
4.	Torque & force transducers		25.11.2021		
5.	Measurement of self & mutual inductance.		29.11.2021		w-41
6.	Measurement of capacitance by De-Sauty Bridge.		29.11.2021		
7.	Verification of Network theorems.		02.12.2021		
8.	Viscosity measurement		06.12.2021		Nandalal
9.	Linear & Angular Displacement		09.12.2021		
10.	Temperature Transducer		09.12.2021		See 11/12/21

Date _____

Expt. No. 05

Page No. 02

PHOTO DEVICES AND ERROR ANALYSIS OF SINGLE PHASE ENERGY METER

OBJECTIVE

To study the characteristics of LDR, photodiode and phototransistor.

OBSERVATION

1. Measurement of resistance of LDR for change in source displacement and intensity.

Distance (cm)	Output Resistance (Ω)	
	Up readings	Down Readings
5	3.75	3.7
7	4.8	4.9
9	6.11	6.05

Intensity (LUX)	Output Resistance (Ω)	
	Up readings	Down Readings
595	13.85	13.82
750	9.82	9.67
930	6.71	6.66

2. Measurement of voltage in Photodiode for change in source displacement and intensity.

Distance (cm)	Output Voltage (V)	
	Up Readings	Down Readings
5 (20)	0.970	0.964
7 (18)	0.637	0.618
9 (16)	0.436	0.437

Teacher's Signature _____

Date _____

Expt. No. _____

Page No. 03


Intensity (LUX)	Output Voltage (V)	
	Up Readings	Down Readings
750	0.334	0.331
900	0.457	0.464
1200	0.884	0.846

3. Measurement of voltage in Phototransistor for change in source displacement and intensity.

Distance (cm)	Output Voltage (V)	
	Up Readings	Down Readings
5 (20)	4.98	4.97
7 (18)	4.38	4.17
9 (16)	2.89	2.99

Intensity (LUX)	Output Voltage (V)	
	Up Readings	Down Readings
500	0.669	0.659
750	1.254	1.251
1000	2.381	2.366

Teacher's Signature _____

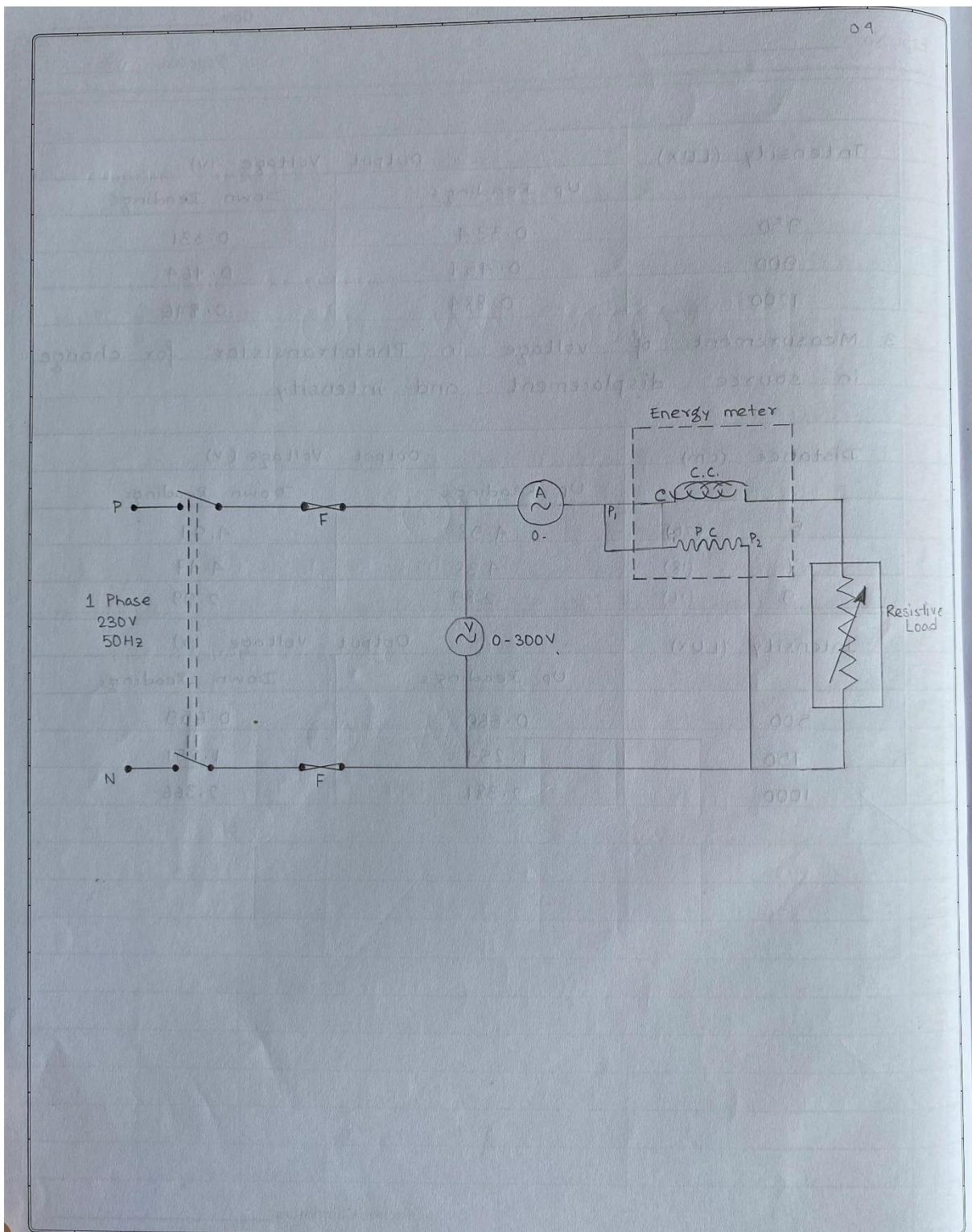

ERROR ANALYSIS OF SINGLE PHASE ENERGY METER

OBJECTIVE

To study the characteristics of single phase energy meter at unity power factor.

TABULAR COLUMN

1. Energy Meter constant, $K = 600 \text{ rev/kWh}$

2. Recorded Energy (RE) for 10 revolutions = $\frac{10 \times 3600 \times 1000}{K}$
 $= 6 \times 10^4 \text{ watt-sec}$


Trial No.	Load Current I (A)	Supply Voltage V (V)	Time for 10 revolutions 't' (secs)	True Energy = $(VI\cos\phi)t$ (watt-secs)	Percentage error = $\frac{RE - TE}{RE} \times 100$
1.	1.1	120	505	66660	-11.1
2.	1.6	120	330	63360	-5.6
3.	2.15	120	235	60630	-1.05
4.	2.7	120	185	59940	+0.1
5.	3.2	120	164	62976	-4.96


CONCLUSIONS

Given meter has an average error of -4.522%.

Nandkumar
18/1/2021

Teacher's Signature _____

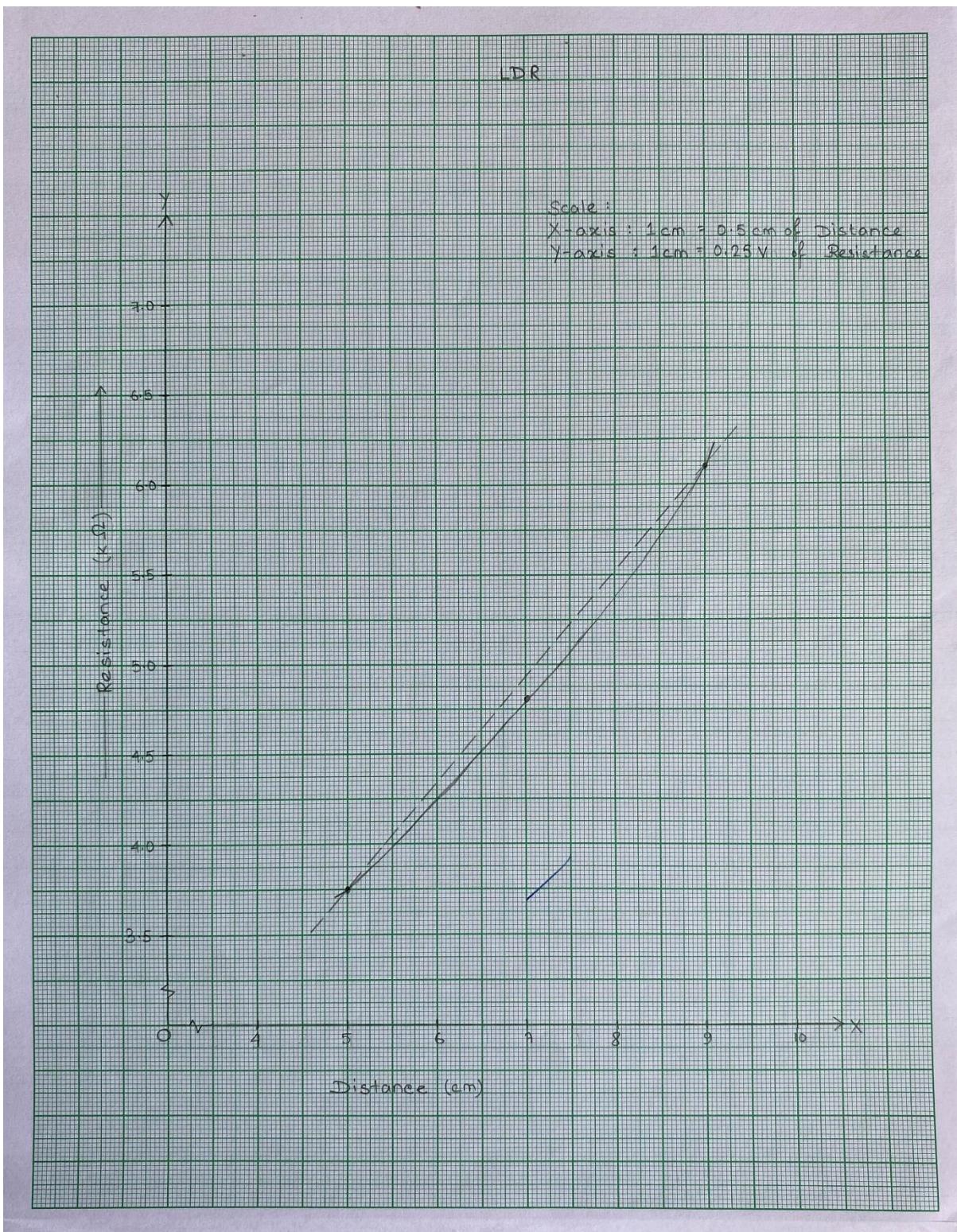


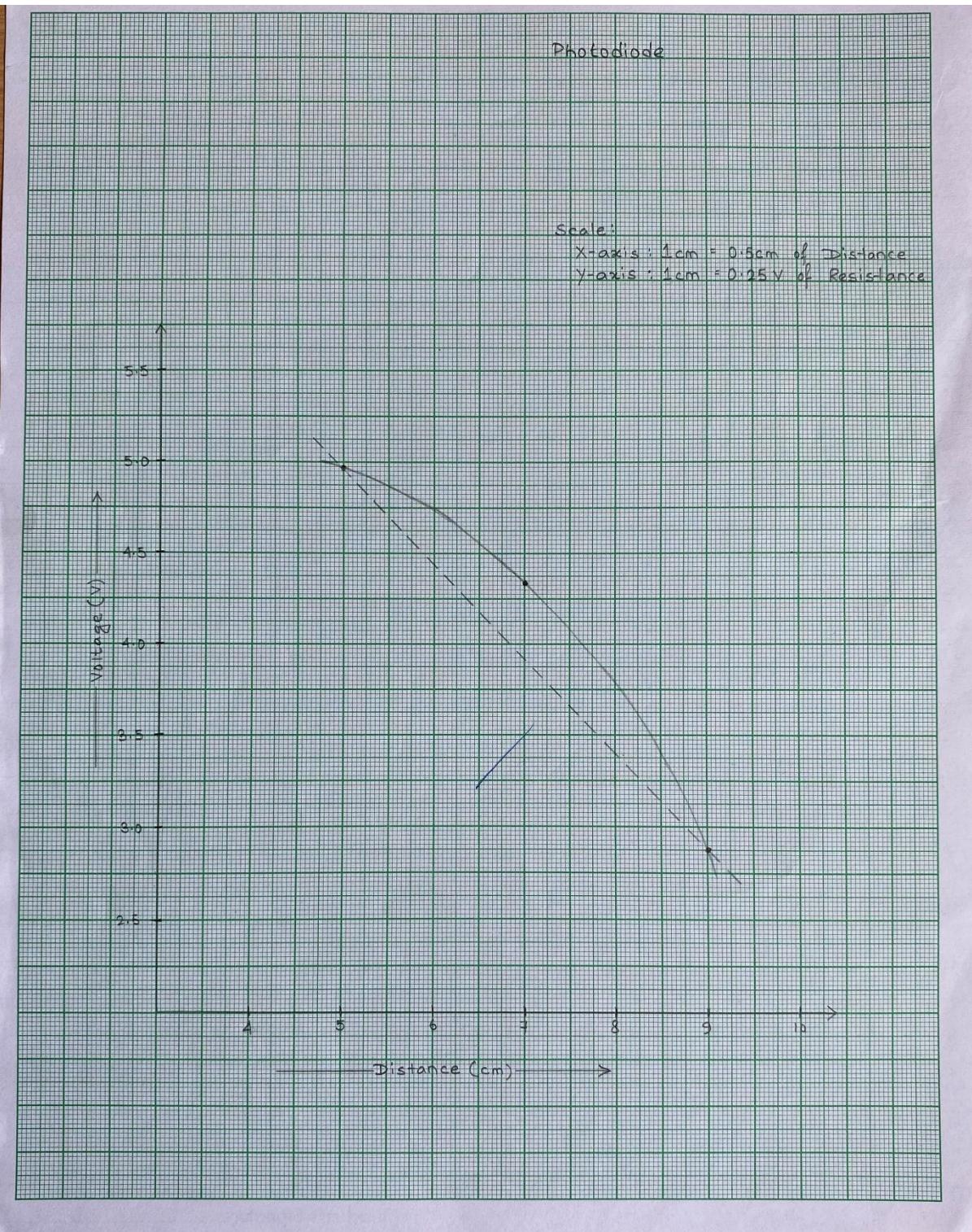

Phototransistor

Scale:

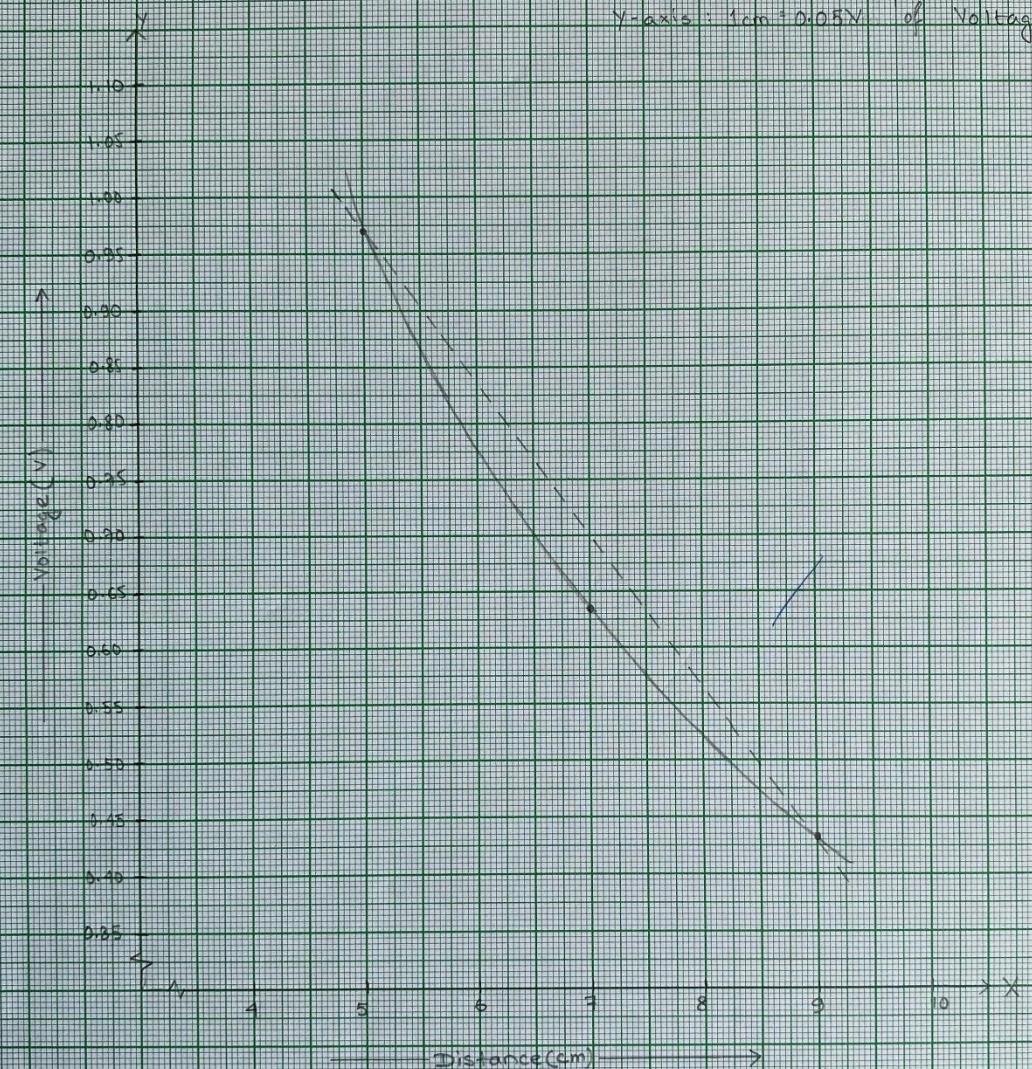X-axis : 1 cm = 0.5 cm of Distance
Y-axis : 1 cm = 0.05 V of Voltage



Date _____

Expt. No. 01

Page No. 09

VERIFICATION OF SERIES AND PARALLEL RESONANCE

OBJECTIVE

To observe series and parallel resonance for the given RLC circuit and obtain the frequency response.

FORMULA TO BE USED

$$\text{Resonant frequency (theoretically)}, F_r = \frac{1}{2\pi\sqrt{LC}} \text{ KHz}$$

TABULAR COLUMN

Series Resonance


Frequency (Hz)	Current (mA)	$X_L = 2\pi f L$ (Ω)	$X_C = 1/2\pi f C$ (Ω)	$Z = R + j(X_L - X_C) $ (Ω)
200	0.22	25.13	795.77	797.10
300	0.35	37.67	530.52	502.90
400	0.48	50.26	397.89	361.47
500	0.62	62.83	398.318.31	274.35
600	0.76	75.39	265.26	214.59
700	0.90	87.96	227.36	171.56
800	1.02	100.53	198.94	140.30
900	1.11	113.10	176.84	118.59
1000	1.17	125.663	159.235	105.47
1100	1.19	138.16	144.7596	100.208
1200	1.17	150.72 125.663	132.6963 159.235	101.64
1300	1.13	163.36	122.43	108.05
1400	1.07	175.92	113.68	117.79

Teacher's Signature _____


CIRCUIT DIAGRAM FOR ANALYSIS OF SINGLE PHASE

OBJECTIVE

(i) Series Resonance

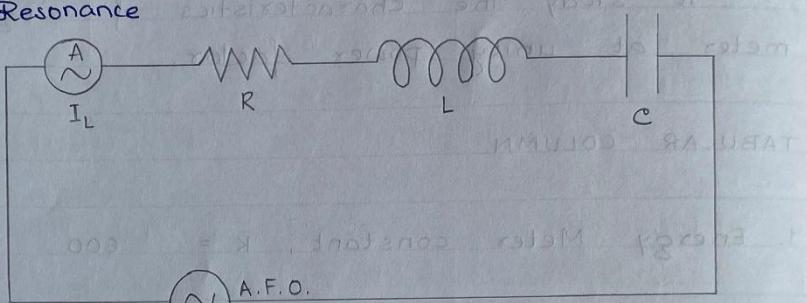

(ii) Parallel Resonance

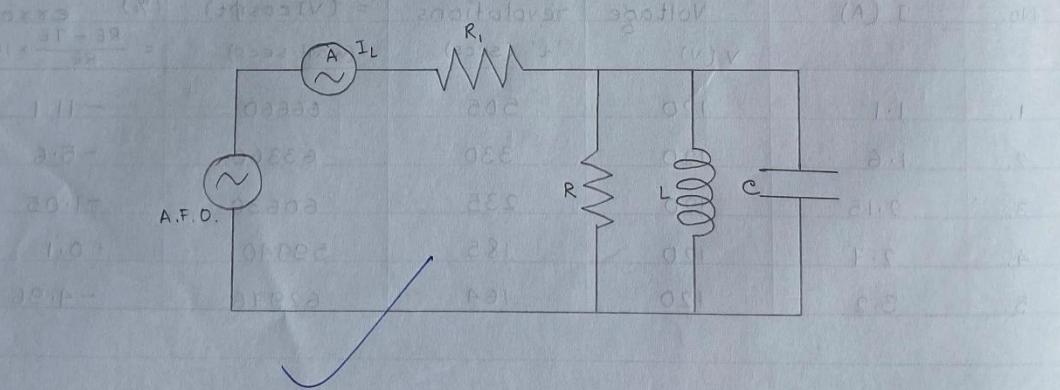

$$L_p = 0.02530 \text{ H}$$

$$C = 1 \text{ HF}$$

Date _____

Expt. No. _____

Page No. 08

1500	1.01	188.50	106.10	129.57
2000	0.74	251.33	79.58	198.74
2500	0.56	314.16	63.66	269.72
3000	0.44	376.98	53.05	339.02
4000	0.29	502.4	39.80	473.28
4500	0.24	565.2	35.38	539.17
5000	0.20	628	31.84	604.48

$$L = 20 \text{ mH} ; R = 100 \Omega ; C = 1 \text{ HF}$$

Parallel Resonance

$$L = 20 \text{ mH}$$

$$C = 1 \text{ HF}$$

$$R_s = 100 \Omega ; R_p = 300 \Omega$$

Frequency (Hz)	Current (mA)	$X_L = 2\pi f L$ (Ω)	$X_C = \frac{1}{2\pi f C}$ (Ω)	$P = \frac{1}{R} + \frac{1}{4} \left(\frac{1}{X_L} - \frac{1}{X_C} \right)$ (V)	$Z = \frac{1}{ P }$
200	0.96	25.12	796.17	0.038	26.32
300	0.91	37.68	530.78	0.025	40
400	0.85	50.24	398.08	0.0178	56.2
500	0.77	62.8	318.47	0.0134	74.6
600	0.68	75.38	265.39	0.0101	99.0
700	0.60	87.92	227.47	0.0078	128.2
800	0.51	100.48	199.04	0.0060	166.7
900	0.44	113.04	176.92	0.0046	217.4
1000	0.39	125.6	159.235	0.0037	270.3
1100	0.38	138.16	144.759	0.0033	303.0
1200	0.40	150.72	132.696	0.0034	294.1
1300	0.43	163.28	122.48	0.0038	263.2

Teacher's Signature _____

Date _____


Expt. No. _____

Page No. 09

1400	0.48	175.84	113.73	0.0045	222.2
1500	0.53	188.4	106.15	0.0052	192.3
2000	0.72	251.2	79.61	0.0091	109.9
2500	0.84	314	63.69	0.0130	76.92
3000	0.90	376.8	53.07	0.0160	62.5
3500	0.94	502.4	39.80	0.0260	38.46
4000	0.96	565.2	35.38	0.0270	37.04
5000	0.99	628	31.84	0.0300	33.3


CONCLUSION

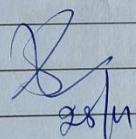
1. Series resonance occurs at 1100 Hz.
2. Parallel resonance occurs at 1100 Hz.



28/11/2020

Teacher's Signature _____

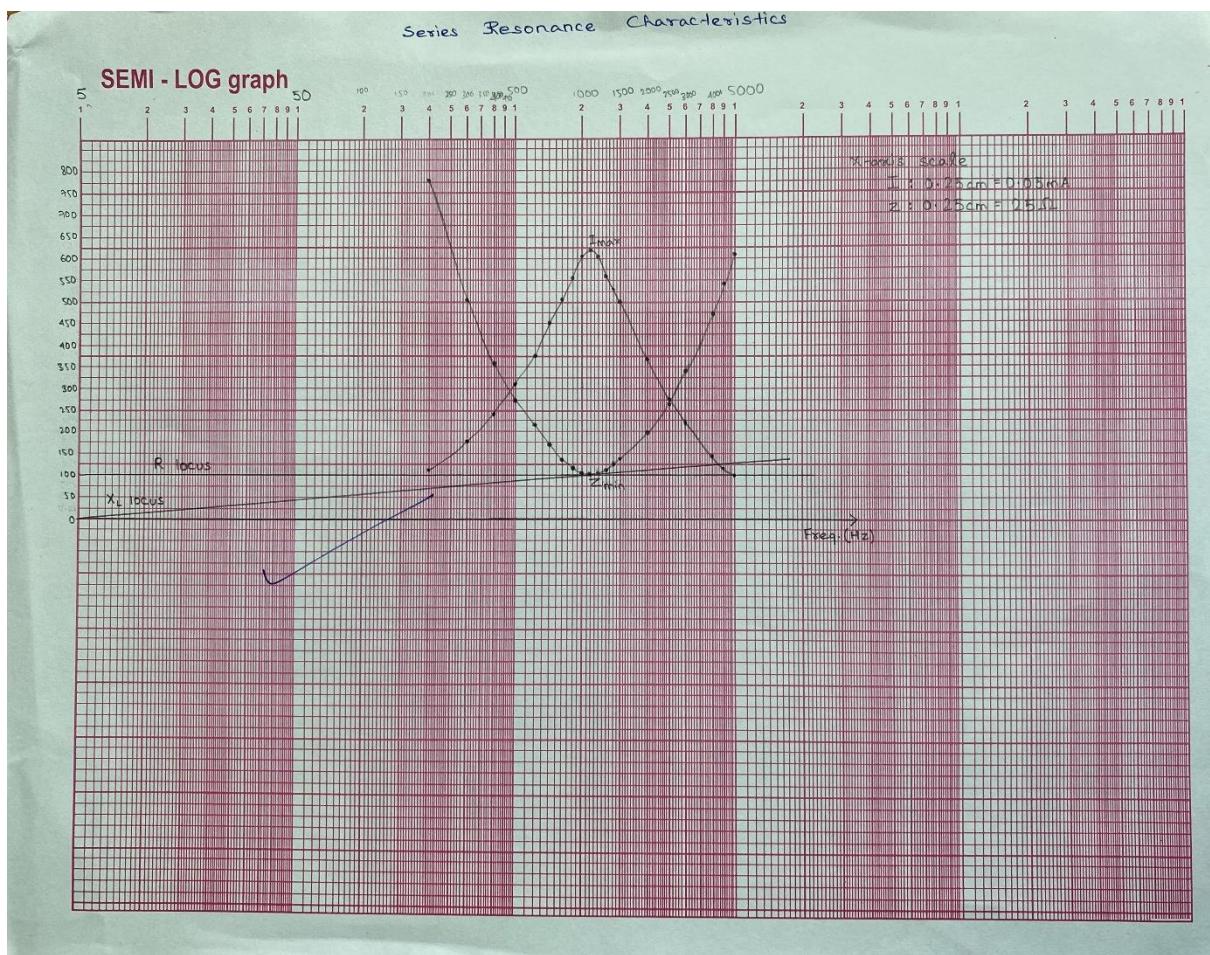

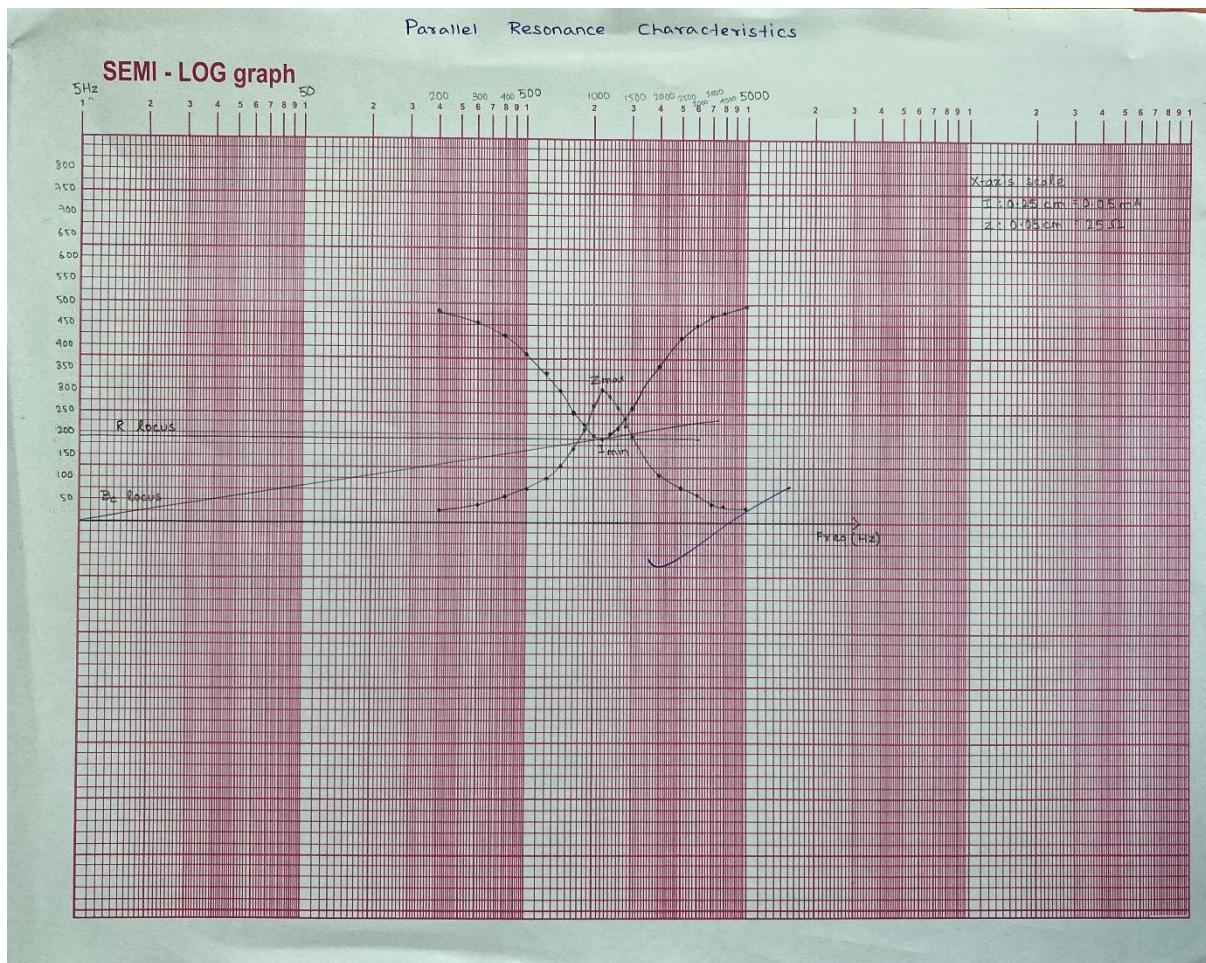

MEASUREMENT OF INDUCTANCE BY MAXWELL'S BRIDGE

OBJECTIVE

To measure the (a) inductance of the given inductor using Maxwell's bridge

TABULAR COLUMN

Frequency of supply from Oscillator, 'f' = Hz


$\frac{R_2}{R_1}$	R_2 (Ω)	R_3 (Ω)	R_4 ($k\Omega$)	C_1 (F)	$R_x = \frac{R_2 \times R_3}{R_4}$ (Ω)	$L_x = R_2 R_3 C_1$ (H)	$Q = \frac{WL_x}{R_x}$ = $WC_1 R_4$	Time constant $\tau = \frac{L_x}{R_x}$ (s)	Power factor of coil $\cos\phi = \frac{R_x}{\sqrt{R_x^2 + (WL_x)^2}}$
1.	200	200	7.6 k Ω	0.64 F	5.26 Ω	24 mH	6.84	4.56×10^{-3}	0.1446
2.	200	400	16 k Ω	0.34 F	5.00 Ω	24 mH	7.2	4.8×10^{-3}	0.1376

RESULTS

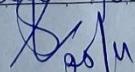- (1) DC resistance of the given coil = 5.13 Ω
- (2) Average Quality factor of the coil = 7.02
- (3) τ of given coil = 4.68×10^{-3} s
- (4) Power factor of the given coil = 0.1411


CONCLUSION :

Using Maxwell's bridge, the inductance of the given inductor was measured. And hence DC resistance, average Quality factor, time constant and power factor of the given coil were found.



Teacher's Signature _____

Circuit Diagram of Maxwell's bridge :

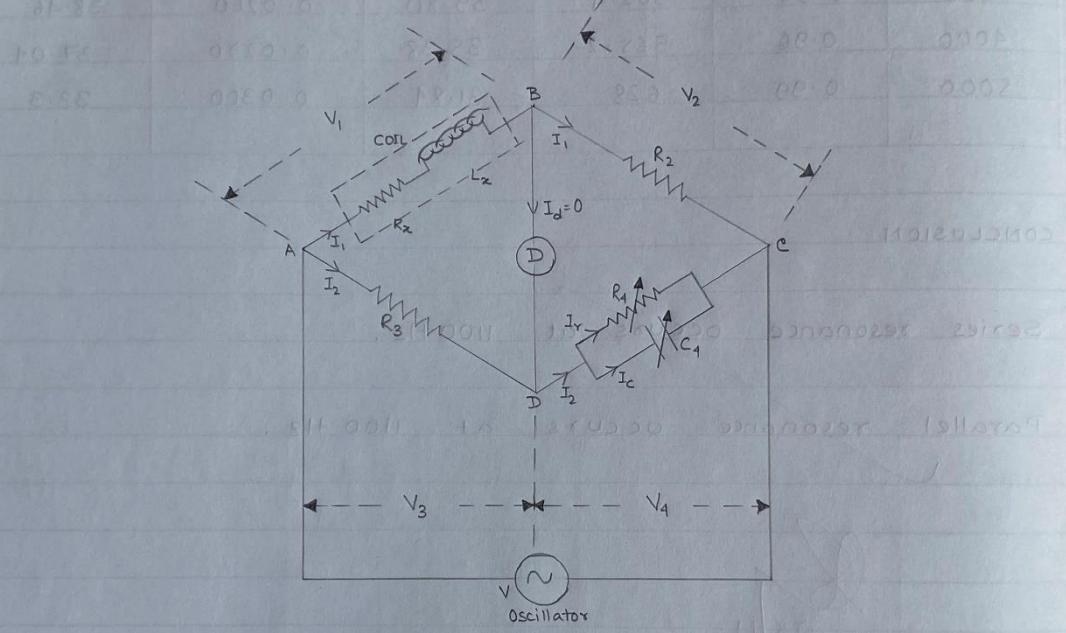

TORQUE AND FORCE TRANSDUCERS**A. TORQUE TRANSDUCERS****OBJECTIVE**

To study the characteristics of the developed torque due to load applied to the beam and the bridge output in millivolts.

FORMULA TO BE USED : (for radial distance = 1 meter)

Theoretical Torque = mass (m) * acceleration due to gravity (g)


* radial distance (x)

$$= 1 \text{ kg} * 9.81 \text{ m/s}^2 * 1 \text{ m} = 9.81 \text{ Nm}$$

TABULAR COLUMN

	Theoretical Torque (Nm)	Bridge Output Voltage (mV)	
		Loading	Unloading
1.	$(100g \times 1 \times 9.81)$	0.981	0
2.	$(200g \times 1 \times 9.81)$	1.962	0.1
3.	$(300g \times 1 \times 9.81)$	2.943	0.3
4.	$(400g \times 1 \times 9.81)$	3.924	0.5
5.	$(500g \times 1 \times 9.81)$	4.905	0.7
6.	$(600g \times 1 \times 9.81)$	5.886	0.8
7.	$(700g \times 1 \times 9.81)$	6.867	1.00
8.	$(800g \times 1 \times 9.81)$	7.848	1.1
9.	$(900g \times 1 \times 9.81)$	8.829	1.3
10.	$(1000g \times 1 \times 9.81)$	9.81	1.4

Teacher's Signature

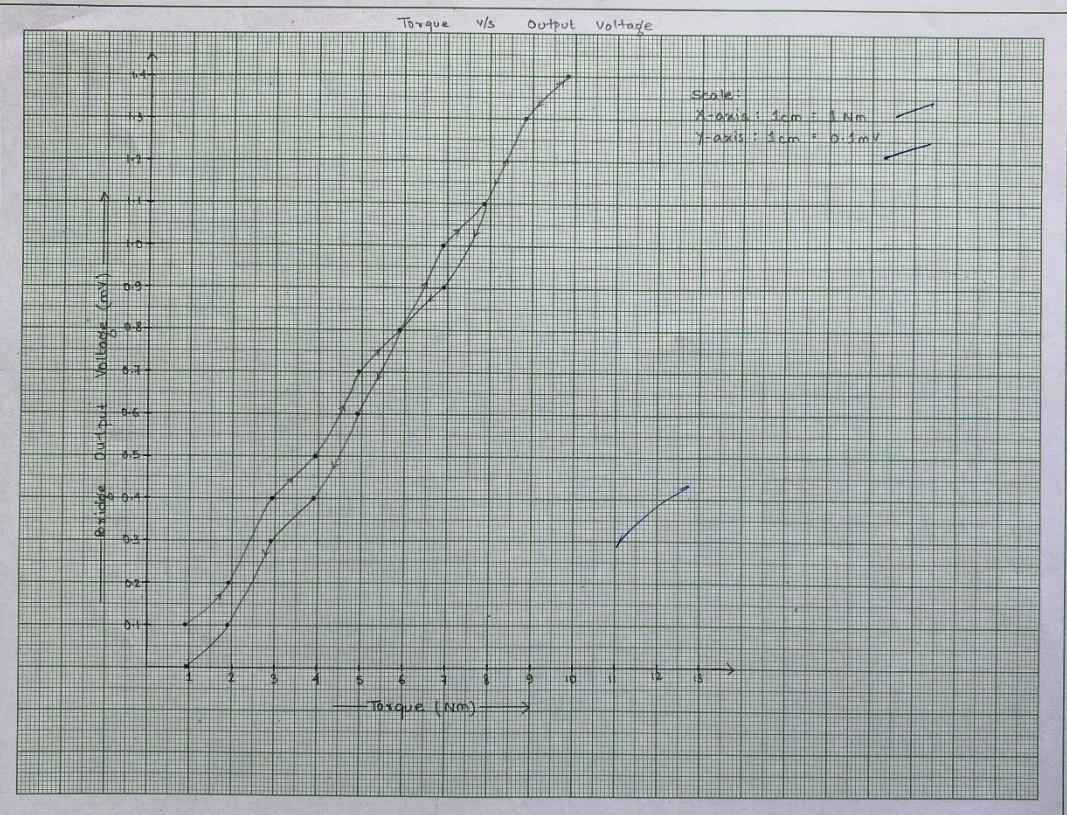

Date _____

Expt. No. _____

Page No. 13

OBJECTIVE

To study the characteristics of the developing torque and the signal conditioned sensor output voltage (for radial distance = 1 meter).

FORMULA TO BE USED

$$\% e = \frac{\text{Actual torque} - \text{Theoretical torque}}{\text{Actual torque}} \times 100$$


TABULAR COLUMN

Theoretical Torque (Nm)	Signal conditioning voltage (V)	Actual Torque (Nm)	% Error
1. 0.981	0.3	0.92	-6.6%
2. 1.962	0.8	1.82	-7.8%
3. 2.943	1.3	2.78	-5.86%
4. 3.924	1.8	3.78	-3.81%
5. 4.905	2.4	4.80	-2.08%
6. 5.886	2.7	5.80	-1.04%
7. 6.867	3.4	6.85	-0.24%
8. 7.848	3.9	7.79	-0.75%
9. 8.829	4.4	8.80	-0.32%
10. 9.81	4.98	9.81	0%

CONCLUSION

Characteristics of the developed torque due to load applied to beam and bridge output in mV were observed using graphs.

Teacher's Signature _____

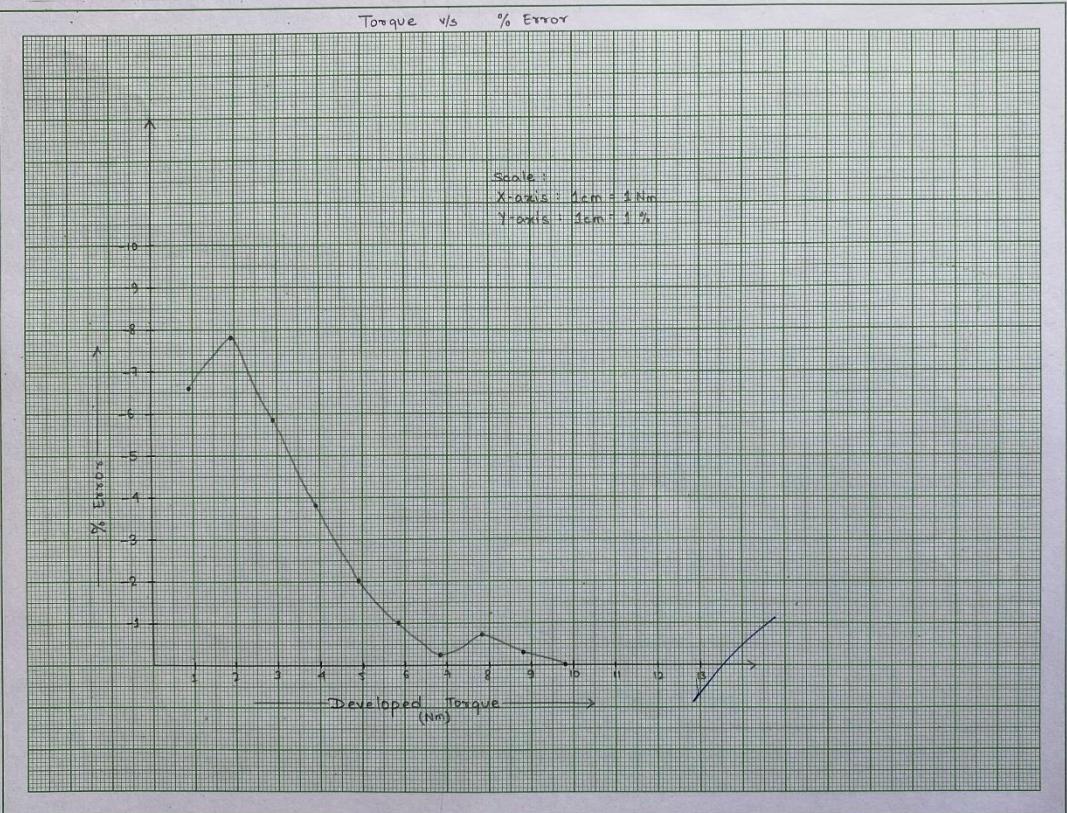

MEASUREMENT OF SELF AND MUTUAL INDUCTANCE

OBJECTIVE

To measure the self and mutual inductances of the given inductive coils.

TABULATION & CALCULATIONS

(i) To find DC resistances of the two coils

COIL - 1			COIL - 2		
V ₁ Volts	I ₁ Amp	$r_1 = \frac{V_1}{I_1} \Omega$	V ₂ Volts	I ₂ Amp	$r_2 = \frac{V_2}{I_2} \Omega$
1	0.12	8.3	1	0.12	8.3
2	0.25	8	2	0.25	8.0
3	0.37	8.1	3	0.38	7.9

$$R_1 = \text{Avg of } r_1 = 8.1 \Omega ; R_2 = \text{avg of } r_2 = 8.00 \Omega$$

✓

(ii) To find self inductances of the two coils

COIL - 1				
V ₁ Volts	I ₁ Amp	$Z_1 = \frac{V_1}{I_1} (\Omega)$	$X_{L1} = \sqrt{Z_1^2 - R_1^2}$ (Ω)	$L_1 = \frac{X_{L1}}{2\pi f} (H)$
10	0.92	10.86	7.23	0.023
20	1.46	13.69	11.03	0.035
30	1.94	15.30	12.9	0.041


$$\text{Avg. self inductance} = 0.033 H$$

✓


Teacher's Signature _____

Circuit Diagram:

(i) To find DC resistances of the coil

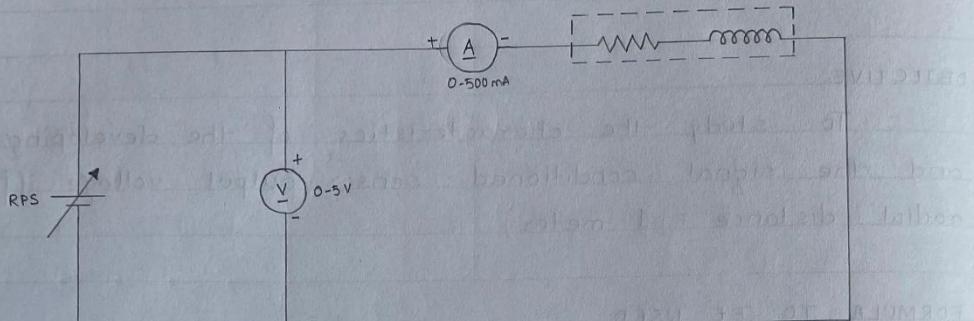


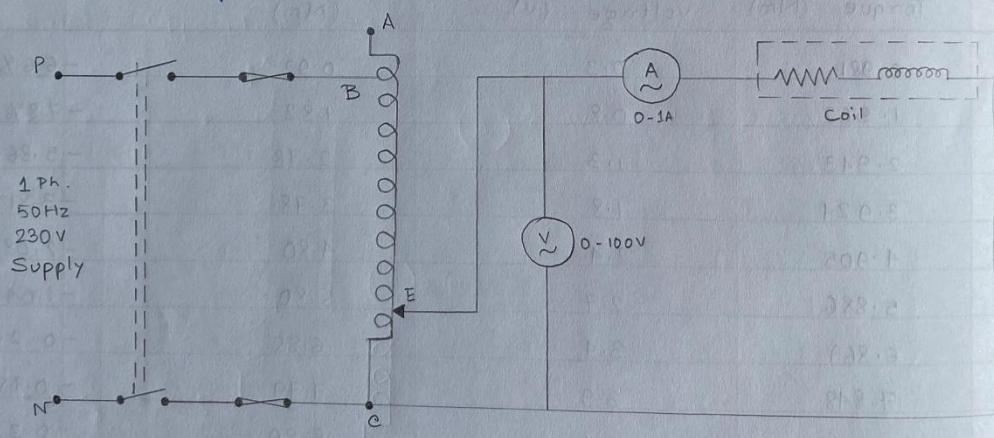(ii) To find self-inductances of the coils




(iii) To find mutual inductance between the two coils. 16

(a) Series Addition:

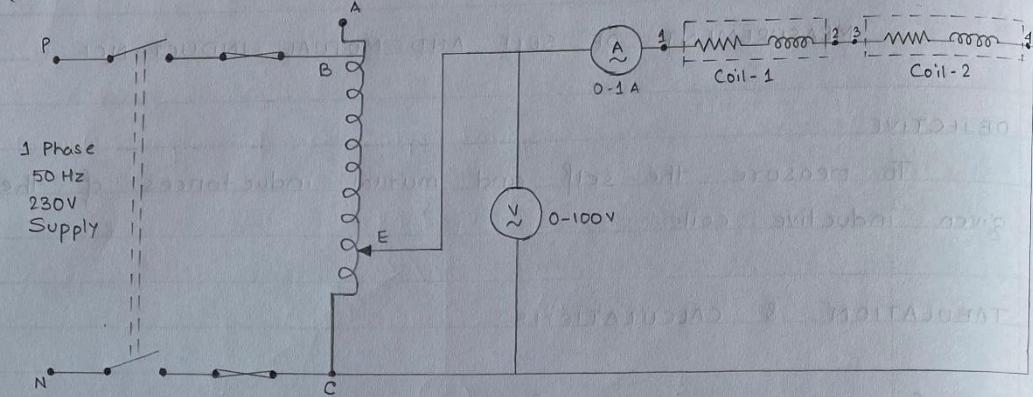

(b) Series Opposition

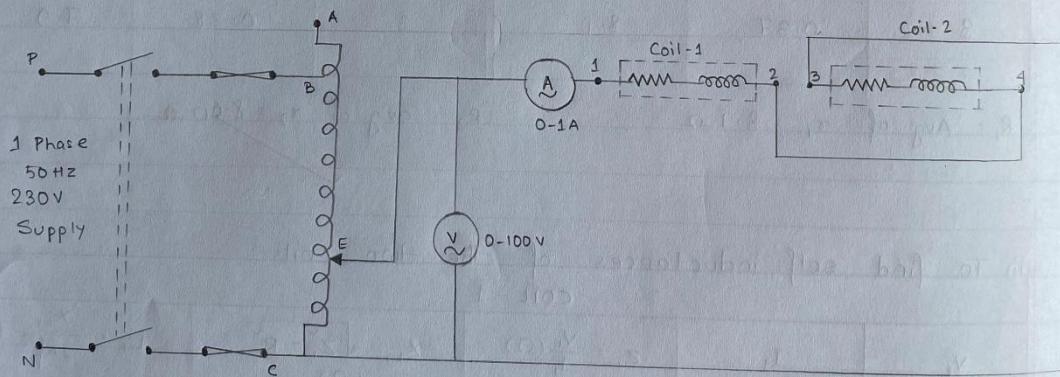

CALCULATIONS

$$1. \quad X_{L_1} + X_{L_2} - 2\omega M = \sqrt{(Z'_2)^2 - (R_1 + R_2)^2} \quad = m_1 = 29.73 \text{ A} \quad (1)$$

$$II. \quad X_{L_1} + X_{L_2} - 2\omega M = \sqrt{(Z'_2)^2 - (R_1 + R_2)^2} \quad = m_2 = 9.15 \text{ A} \quad (II)$$

From (I) & (II) : $4\omega M = m_1 - m_2$

$$M = \frac{m_1 - m_2}{4\omega} = \frac{m_1 - m_2}{8\pi f}$$

$$M = 0.016 \text{ H}$$

Date _____

Expt. No. _____

Page No. 17

COIL - 2

V_2 Volts	I_2 Amp	$Z_2 = \frac{V_2}{I_2}$ (Ω)	$X_{L2} = \sqrt{Z_2^2 - R_2^2}$ (Ω)	$L_2 = \frac{X_{L2}}{2\pi f}$ (H)
10	0.52	10.86	7.34	0.023
20	1.48	13.51	10.82	0.034
30	1.94	15.46	13.23	0.042

Avg. self inductance = 0.033 H

(iii) To find mutual inductance between the two coils

Series Addition			Series Opposition		
V'_1 Volts	I'_1 Amps	$Z'_1 = \frac{V'_1}{I'_1}$ (Ω)	V'_2 Volts	I'_2 Amps	$Z'_2 = \frac{V'_2}{I'_2}$ (Ω)
10	0.35	20.57	10	0.66	15.15
20	0.51	39.21	20	1.02	19.60
30	0.72	41.66	30	1.44	20.83

RESULTS

- Self inductance of coil 1 = 0.033 H
- Self inductance of coil 2 = 0.033 H
- Mutual inductance between 2 coils = 0.016

CONCLUSIONS

self inductance of both coils are 0.033 H.
 Mutual inductance of coils is 0.016 H.

W-1
on 10/10/21

Teacher's Signature _____

MEASUREMENT OF CAPACITANCE BY DE-SAUTY BRIDGE

OBJECTIVE

To measure the capacitance of the given capacitor using De Sauty's bridge.

TABULAR COLUMN

Frequency of supply from Oscillator, 'f' = Hz


$\frac{R_2}{R_1 + R_2}$	R ₁ (Ω)	R ₂ (Ω)	R ₃ (Ω)	R ₄ (Ω)	C ₂ (MF)	$R_x = \left(\frac{R_2 \times R_1}{R_4} \right) - R_1$ (Ω)	$C_x = \left(\frac{R_4}{R_3} \right) \times C_2$ (MF)	Dissipation Factor $D = \omega C_x R_x$
1.	400	200	600	300	3	0	2	0
2.	400	400	400	400	2.15	0	2	0
3.	200	100	200	100	40	0	1.5	0
4.	200	200	200	200	2.1	0	1.5	0

RESULTS

- DC resistance of the unknown capacitor = Ω ?
- Capacitance of the unknown capacitor = MF
- Dissipation factor of the given coil =


CONCLUSION

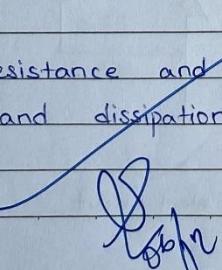DC resistance and capacitance of the unknown resistor capacitor and dissipation factor of the given coil were found.



Teacher's Signature _____

Circuit Diagram of De Sauty's Bridge:

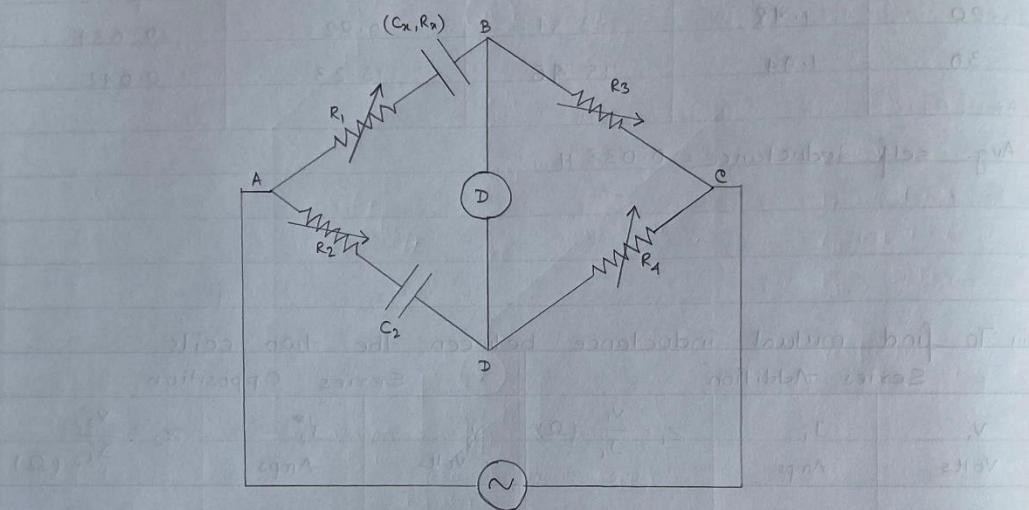

VERIFICATION OF NETWORK THEOREMS

OBJECTIVE

To verify (a) Thevenin's theorem, (b) Maximum power transfer theorem, (c) Superposition theorem & (d) Reciprocity as applied to electric circuits.


(b) Maximum Power Transfer Theorem

For the circuit shown in Fig. 1(b), replace R_L with decade resistance box and vary the value of resistance measuring corresponding voltage and current across it.

$V_{th} =$

$R_{th} =$

$\frac{V}{R_L}$	V (Volts)	I_L' in (mA)	$R_L = \frac{V}{I_L'} (\Omega)$	$P = (I_L'^2 R_L)$ (mW)
1.	0.078	0.7	100	49
2.	0.15	0.7	200	98
3.	0.21	0.66	300	130
4.	0.38	0.59	500	174.05
5.	0.56	0.51	1000	260
6.	0.72	0.43	1500	277.35
7.	0.85	0.37	2000	273.8
8.	0.89	0.36	2200	285.12
9.	0.95	0.33	2500	272.25
10.	1.03	0.30	3000	270

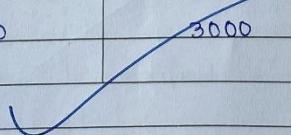


$R_1 =$ _____

$R_L =$ _____

Teacher's Signature _____

(a) Verification of Thevenin's theorem

(i) To find Load current in the circuit

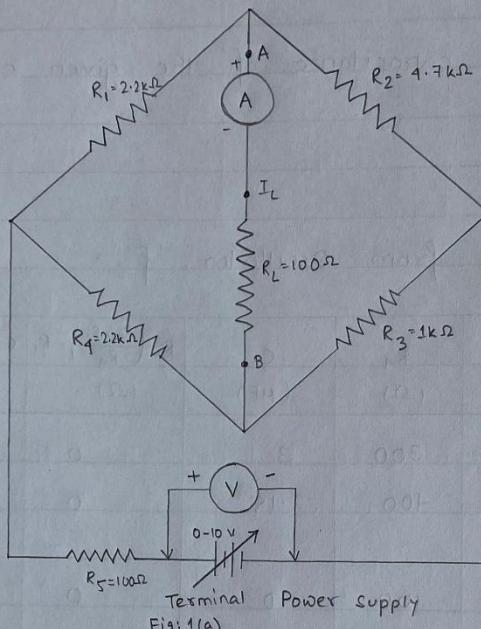

$$V = 5 \text{ V}$$


$$I_L = 0.73 \text{ mA}$$

$$V_{Th} = 1.75 \text{ V}$$

$$R_{Th} = 2.17 \text{ k}\Omega$$


$$\text{Verification } I_L = 0.73 \text{ mA } \checkmark$$

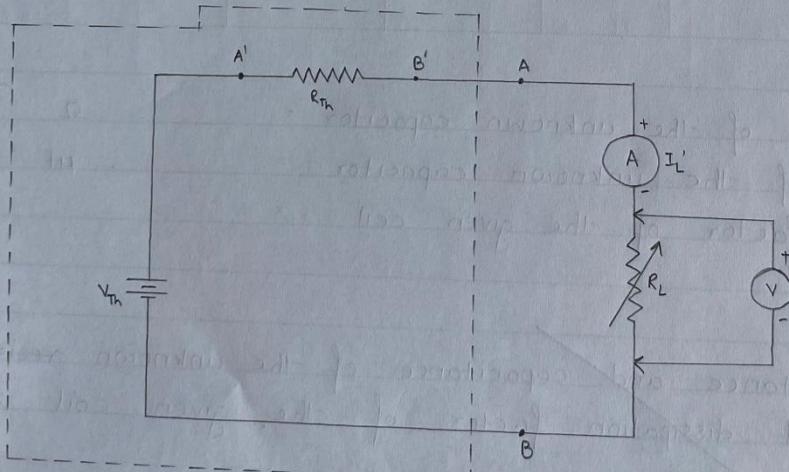(ii) To find load current from Thevenin's equivalent circuit




(c) Superposition theorem

(i) With both energy sources acting

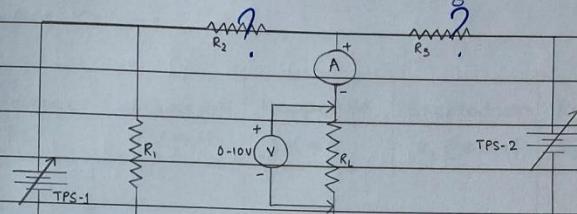

(ii) With only one source acting:

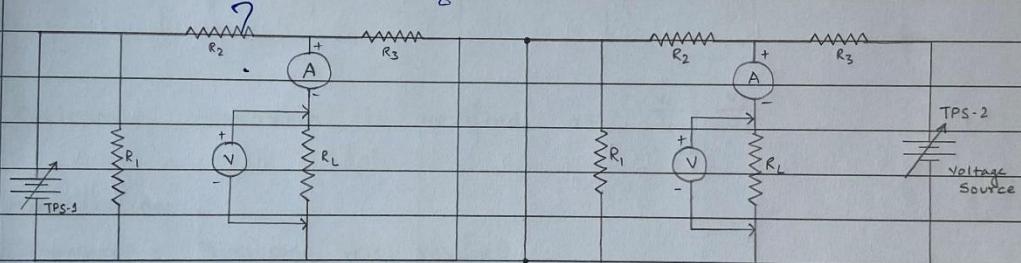

Tabular Column

SUPPLY Voltage		Both sources acting		Source 1 acting		Source 2 acting		V ₁ + V ₂	I ₁ + I ₂
TPS-1	TPS-2	V (Volts)	I (mA)	V ₁ (Volts)	I ₁ (mA)	V ₂ (Volts)	I ₂ (mA)	(Volts)	(Amps)
8	3	0.389	3.9	0.105	1.02	0.283	2.86	0.388	3.88
9	4	0.497	5.04	0.120	1.17	0.377	3.81	0.497	4.98

Superposition theorem is verified as $V = V_1 + V_2$ & $I = I_1 + I_2$

Teacher's Signature _____

(d) Reciprocity theorem

Tabular Column

Supply Voltage (TPS)	Excitation V_1 (Volts)	Response I_1 (mA)	Excitation V_2 (Volts)	Response I_2 (mA)	$\frac{V_1}{I_1}$ (Ω)	$\frac{V_2}{I_2}$ (Ω)
5	5	0.42 mA	5	0.42	11.90	11.90
7	7	0.60 mA	7	0.6	11.66	11.66

Reciprocity theorem is verified as $\frac{V_1}{I_1} = \frac{V_2}{I_2}$

CONCLUSION

- (a) Thevenin's Theorem was verified
- (b) Maximum Power Transfer Theorem was verified using a graph.
- (c) Superposition theorem was verified as $V = V_1 + V_2$ & $I = I_1 + I_2$
- (d) Reciprocity theorem was verified as $\frac{V_1}{I_1} = \frac{V_2}{I_2}$




ob/12

Sudipta Basak.

Maximum Power Transfer Theorem ✓

SEMI - LOG graph

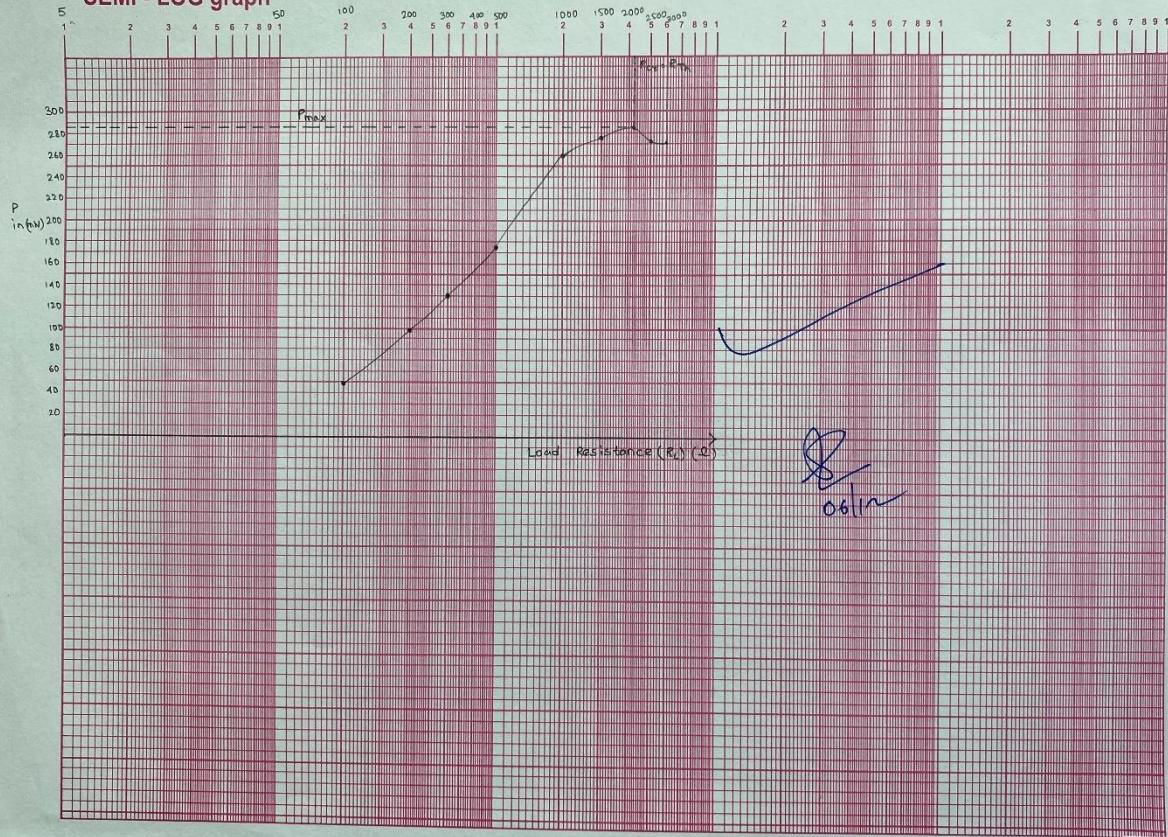

Date _____

Expt. No. 09

Page No. 24

VISCOSEITY MEASUREMENT

OBJECTIVE

To measure the Kinematic viscosity of the oil sample.

FORMULA TO BE USED

$$\text{For } t < 100\text{s} \quad v = 0.00226 f - 1.95/t$$

$$\text{For } t > 100\text{s} \quad v = 0.00220 t - 1.35/t$$

TABULAR COLUMN

$\frac{T^{\circ}\text{C}}{N^{\circ}}$	Temperature (°C)	Time 't' (sec)	Kinematic viscosity (Stokes)
1.	30	87	0.174
2.	40	80	0.156
3.	50	69	0.128
4.	60	58	0.097
5.	70	51	0.077

Volume of oil in flask at the end of the reading = 60ml

CONCLUSION

The kinematic viscosity of the oil sample was found.

Teacher's Signature _____

Date _____

Expt. No. 08Page No. 25

LINEAR AND ANGULAR DISPLACEMENT TRANSDUCER

OBJECTIVE

To analyze the characteristics of Capacitive transducer, Resistive transducer for variation in displacement.

TABULAR COLUMN:

Measurement of linear displacement using potentiometer

Distance (mm)	Output Voltage (V)		Resistance ($k\Omega$)
	Up readings ($k\Omega$)	Down readings ($k\Omega$)	
0	9.95	9.98	
10	8.93	9.0	
20	8.80	7.99	
30	7.07	7.04	
40	6.07	6.04	
50	5.03	5.14	
60	4.08	4.08	
70	3.120	3.057	
80	2.133	2.043	
90	1.199	1.199	

Teacher's Signature J. D. S.

Date _____

Expt. No. _____

Page No. 26

Measurement of angular displacement using capacitive transducer		
Angle	Output capacitance (nF)	
	Up readings	Down readings
20	1.290	1.293
40	1.260	1.272
60	1.248	1.251
80	1.220	1.221
100	1.199	1.199

Measurement of linear displacement using ultrasonic transducer

Distance (mm)	Output voltage (V)	
	Up readings	Down Readings
100	0.534	0.559
200	1.046	1.070
300	1.536	1.566
400	2.058	2.078
500	2.560	2.590
600	3.078	3.094
700	3.614	3.60
800	4.10	4.11
900	4.6	4.62
1000	5.02	5.02


CONCLUSION

Linear displacement using potentiometer, ultrasonic transducer and angular displacement using capacitive transducer were found.

Teacher's Signature Jebu

Ultrasonic Transducers

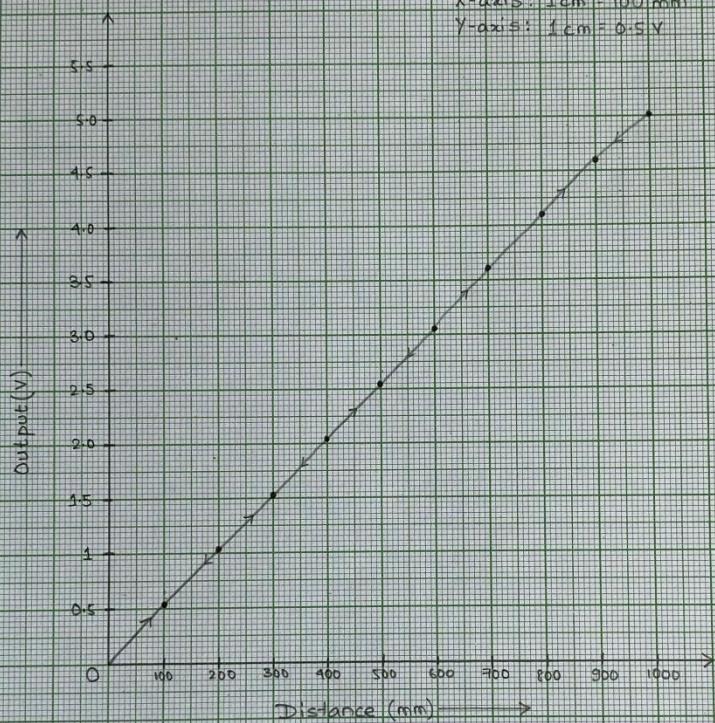
Scale :
X-axis: 1 cm = 100 mm
Y-axis: 1 cm = 0.5 V




Ans

Capacitive Transducer

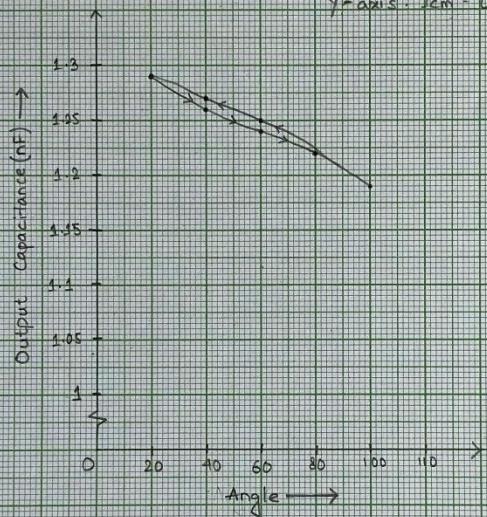Scale:
X-axis: 1cm = 20°
Y-axis: 1cm = 0.05 nF



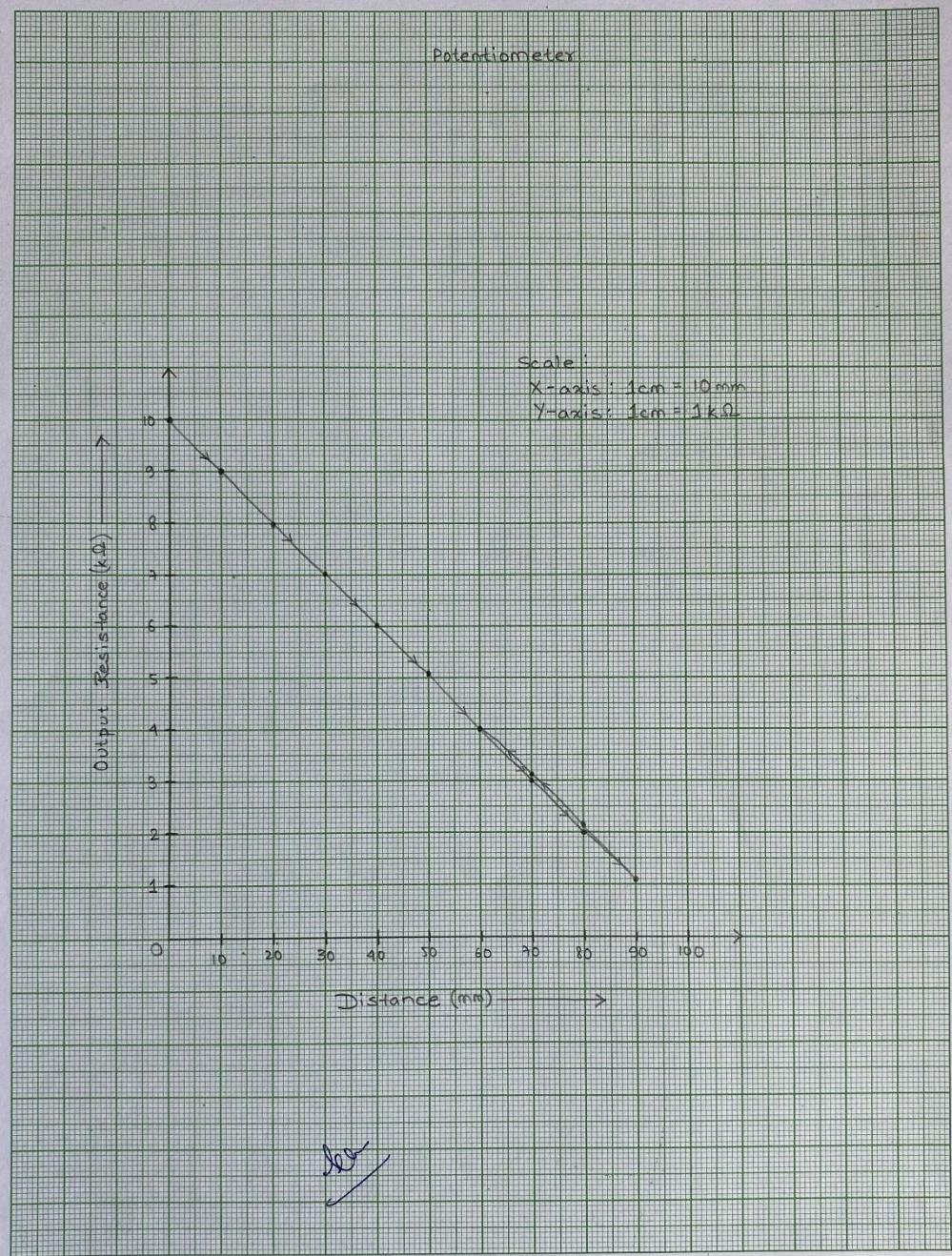

Date _____

Expt. No. _____

Page No. 29

TEMPERATURE TRANSDUCERS

OBJECTIVE

To study the characteristics of Resistance Temperature Detector (RTD) for variation in temperature.

OBSERVATIONS

Resistance in RTD for change in temperature:

$$R_{ref} = 103 \Omega$$

Trial No.	Temperature (°C)	Theoretical Output (Ω)	Output Resistance		Measured Voltage (mV)
			UP (Ω)	DOWN (Ω)	
1.	35	103	113.2	113.7	0.01
2.	40	105.1	116.3	116.5	7.8
3.	45	107.02	117.5	117.8	15.9
4.	50	109.04	119.2	119.2	37.5
5.	55	111.05	120.2	120.5	52
6.	60	113.06	122.4	122.4	67.2

CONCLUSION

Studied the characteristics of RTD

Teacher's Signature _____

Ram

