



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

*(A constituent institution of MAHE, Manipal)*



# Basic Electrical Technology

[ELE 105 I]

## 4. Three Phase AC Circuits

---

***L2 I – Generation & Representation of three phase supply***


# Topics Covered

---



- ➡ *Generation of Three Phase Supply*
- ➡ *Representation of Three Phase Excitation*
- ➡ *Relationship between Phase and Line Voltages*
- ➡ *3 Phase Supply & Loads*


# Generation of Three Phase

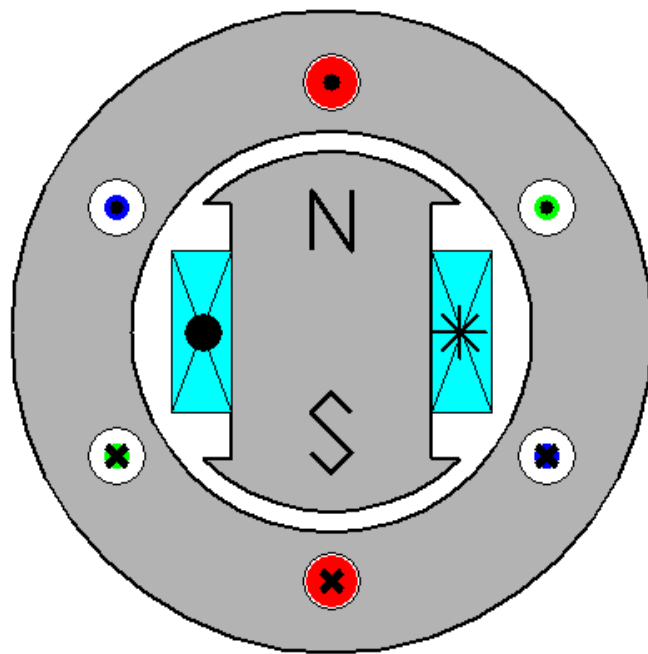

Phase A

Phase B

Phase C

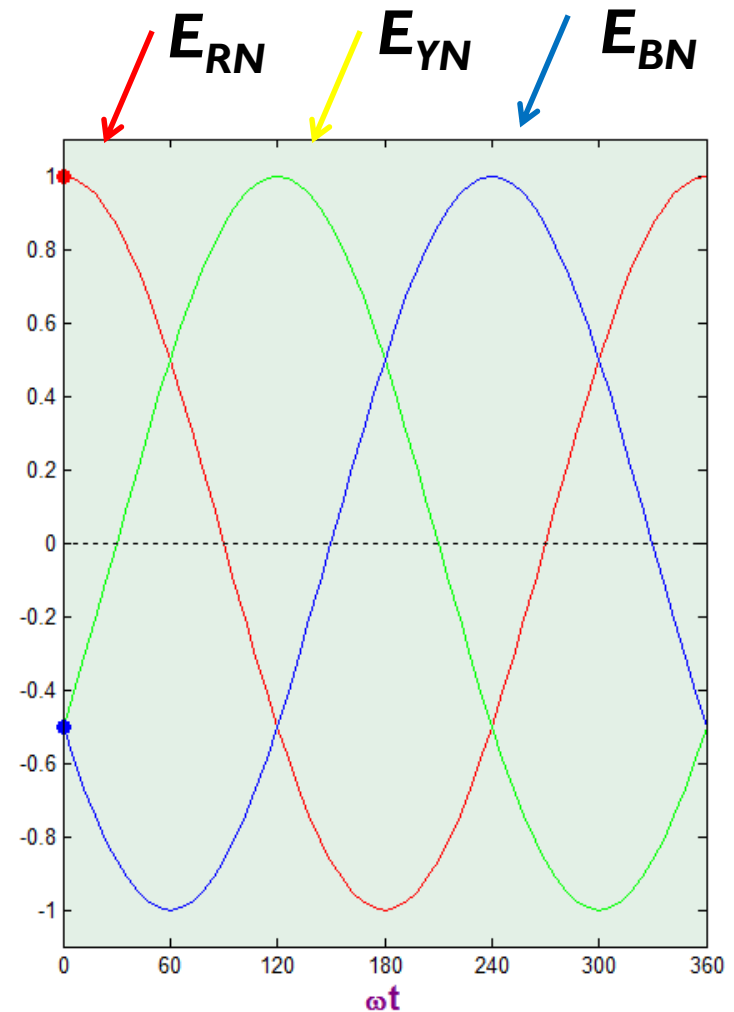

Courtesy : [www.ece.umn.edu](http://www.ece.umn.edu)

# 3 Phase Excitation (Phase Voltages)





## Phase Voltages,

$$\hat{V}_{RN} = V_m \sin(\omega t)$$

$$\hat{V}_{YN} = V_m \sin(\omega t - 120^\circ)$$
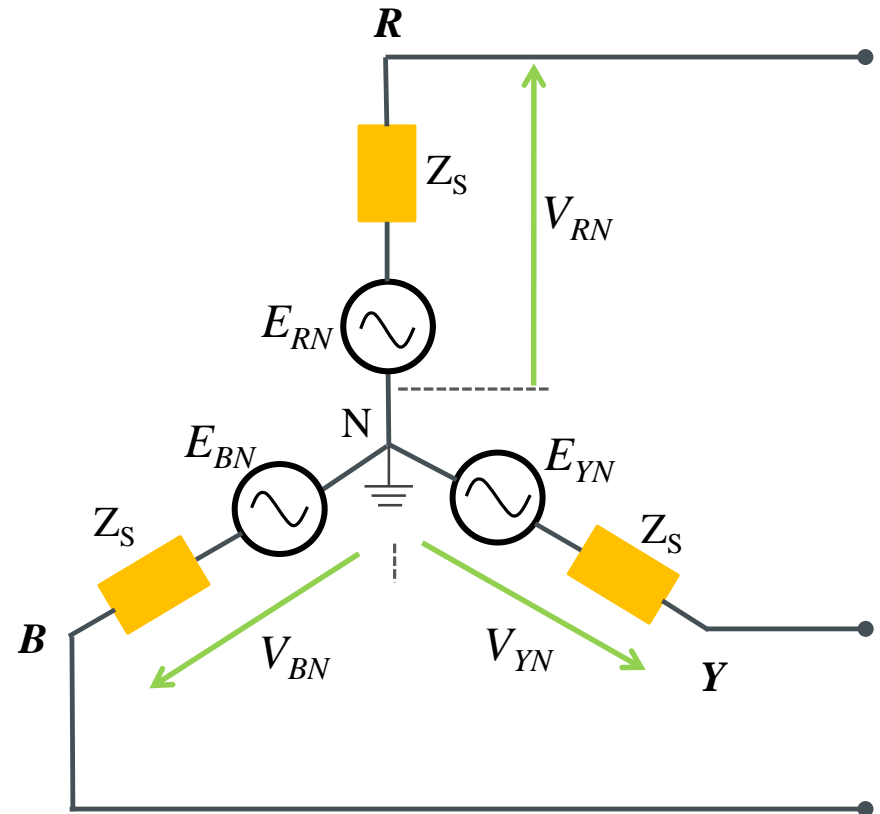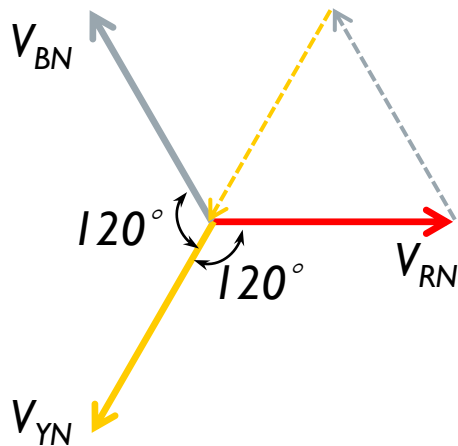
$$\hat{V}_{BN} = V_m \sin(\omega t - 240^\circ)$$




**Three Phase Source**



Summing up the phase voltages,

$$\hat{V}_{RN} + \hat{V}_{YN} + \hat{V}_{BN} = 0$$
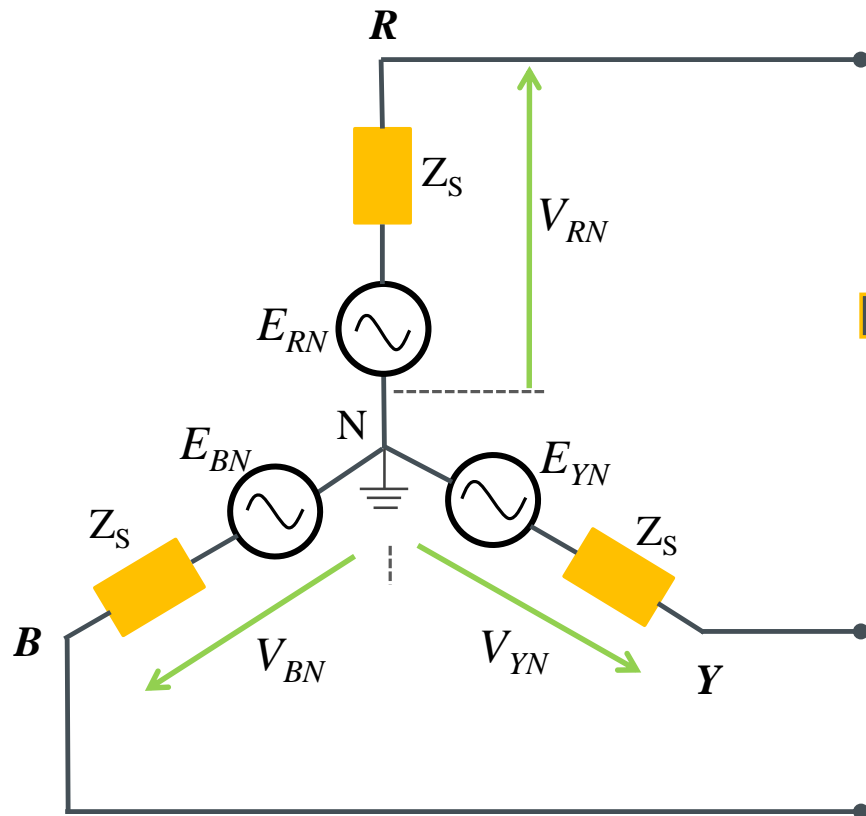
# 3 Phase Excitation (Phase Voltages).. ---




**Three Phase Source**

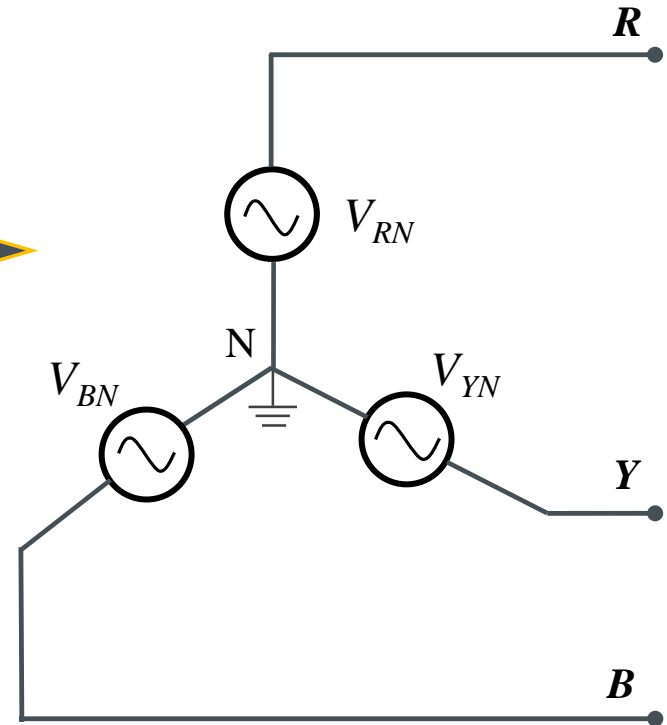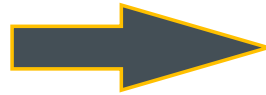


**Three Phase Source**

# 3 Phase Excitation (Line Voltages)

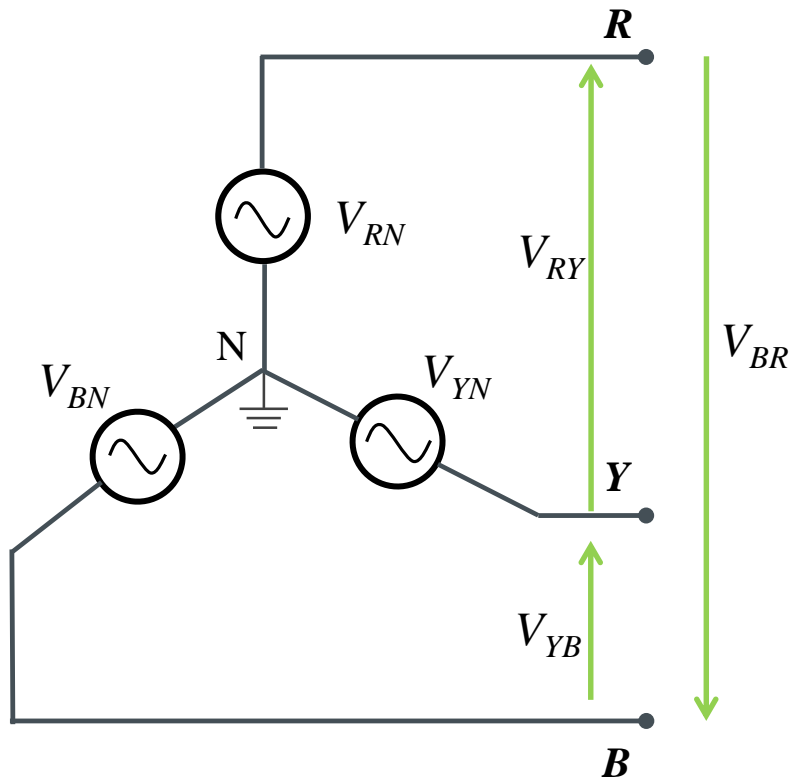

**Three Phase Source**

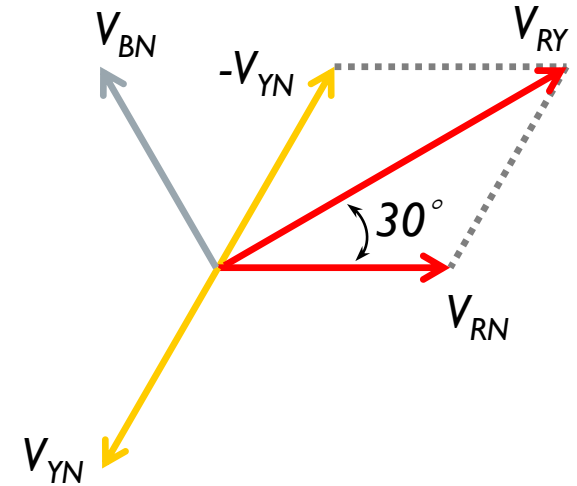

**Line Voltages,**

$$\begin{aligned}\hat{V}_{RY} &= \hat{V}_{RN} - \hat{V}_{YN} \\ &= V_m \sin(\omega t) - V_m \sin(\omega t - 120^\circ) \\ &= \sqrt{3} \times V_m \sin(\omega t + 30^\circ)\end{aligned}$$



# 3 Phase Excitation (Line Voltages)...



**Similarly,**


$$\begin{aligned}\hat{V}_{YB} &= \hat{V}_{YN} - \hat{V}_{BN} \\ &= V_m \sin(\omega t - 120) - V_m \sin(\omega t - 240^\circ) \\ &= \sqrt{3} \times V_m \sin(\omega t - 90) \\ &= V_{RY} \sin(\omega t - 120)\end{aligned}$$

$$\begin{aligned}\hat{V}_{BR} &= \hat{V}_{BN} - \hat{V}_{RN} \\ &= V_{RY} \sin(\omega t + 120)\end{aligned}$$

*Summing up the Line voltages,*

$$\hat{V}_{RY} + \hat{V}_{YB} + \hat{V}_{BR} = 0$$

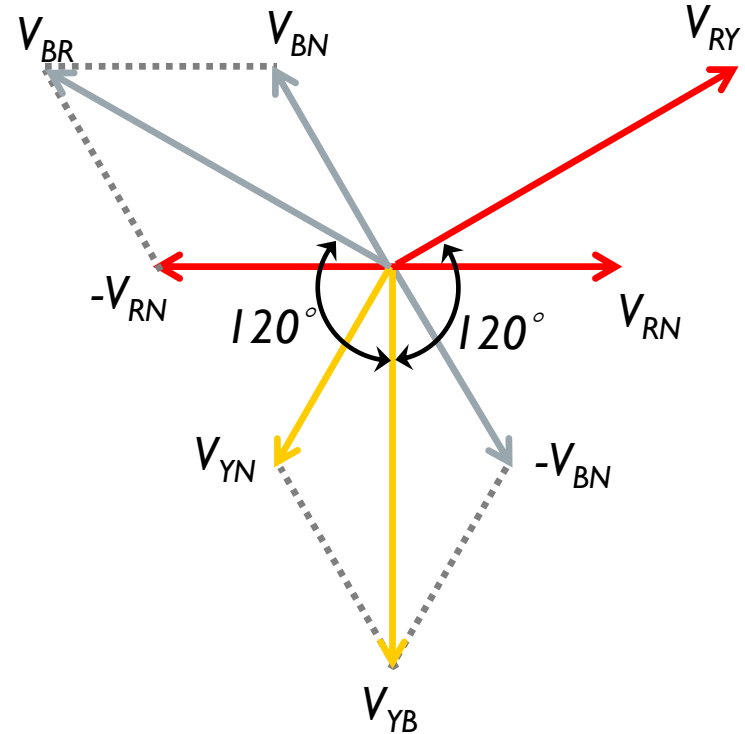**In a Three Phase balanced Supply, the summation of Phase voltages and summation of Line Voltages is zero.**





# Relation b/w Phase & Line Voltages



## Phase Voltages

$$\hat{V}_{RN} = V_m \sin(\omega t)$$

$$\hat{V}_{YN} = V_m \sin(\omega t - 120^\circ)$$


$$\hat{V}_{BN} = V_m \sin(\omega t - 240^\circ)$$

## Line Voltages

$$\hat{V}_{RY} = \sqrt{3} \times V_m \sin(\omega t + 30^\circ)$$

$$\hat{V}_{YB} = \sqrt{3} \times V_m \sin(\omega t - 90^\circ)$$
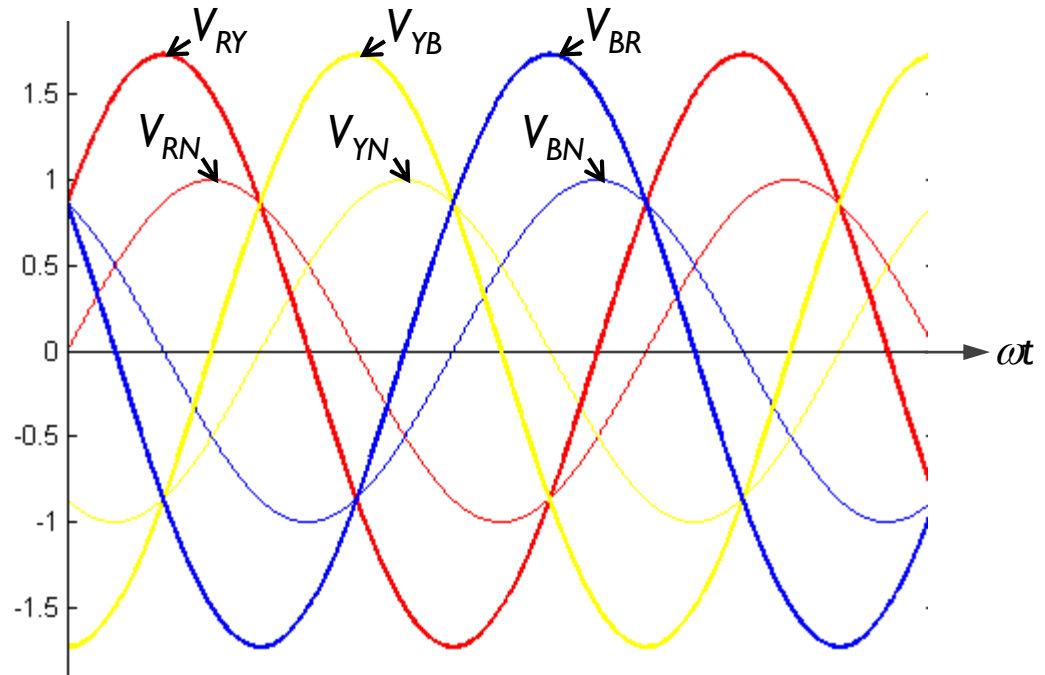
$$\hat{V}_{BR} = \sqrt{3} \times V_m \sin(\omega t + 150^\circ)$$




$$|V_{Line}| = \sqrt{3} |V_{Phase}|$$


# Phase Sequence



## 1. RYB

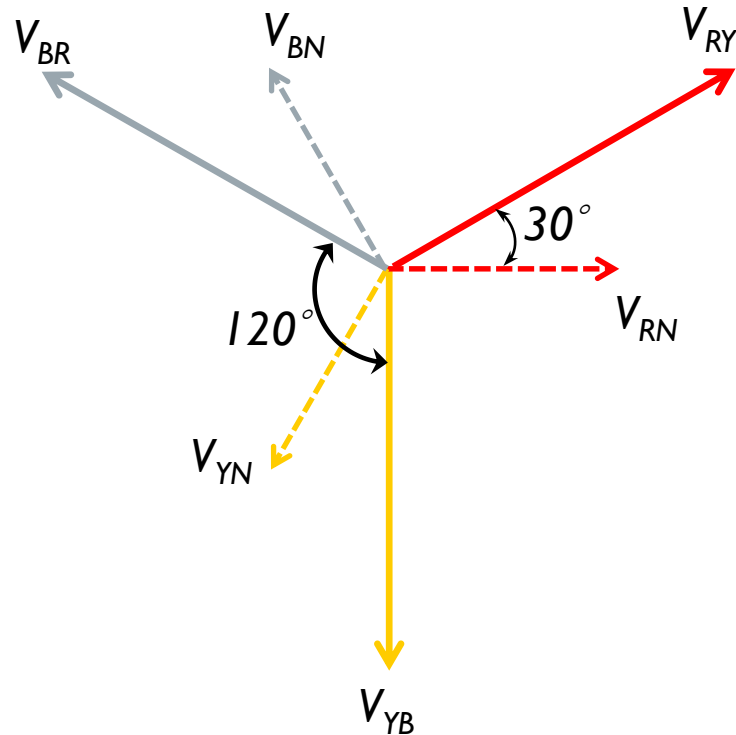

## 2. RBY

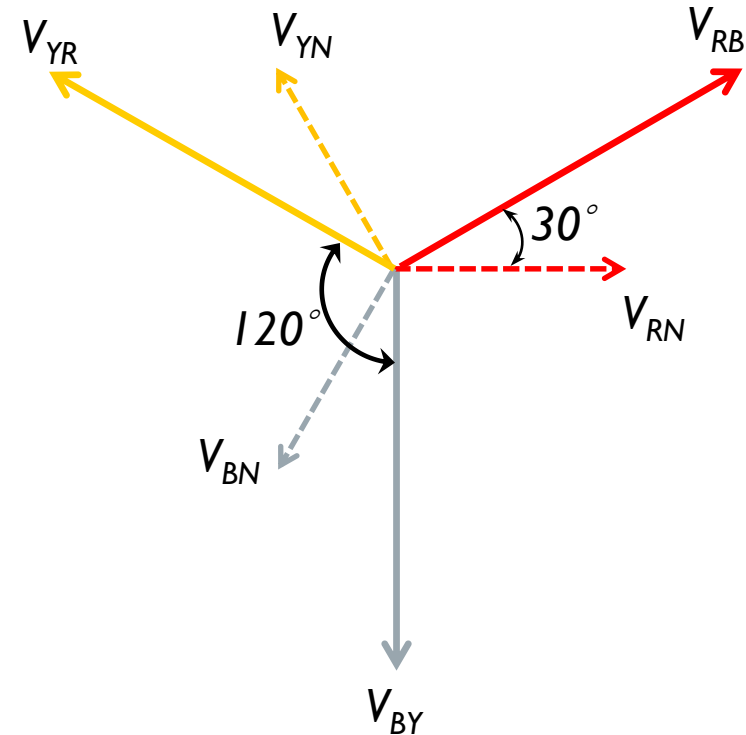

Phase Sequence is the order in which three phases attain their peak or maximum values

# Exercise- I



Given the phase voltage  $V_{RN}$  of a 3 phase balanced RYB system as 240V, express the phase and line voltages mathematically. Also sketch the phasor diagram.

## Solution:

### Phase Voltages:

$$\hat{V}_{RN} = 240 \times \sqrt{2} \times \sin(\omega t)$$

$$\hat{V}_{YN} = 240 \times \sqrt{2} \times \sin(\omega t - 120^\circ)$$


$$\hat{V}_{BN} = 240 \times \sqrt{2} \times \sin(\omega t - 240^\circ)$$

### Line Voltages:

$$\hat{V}_{RY} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t + 30^\circ)$$

$$\hat{V}_{YB} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t - 90^\circ)$$

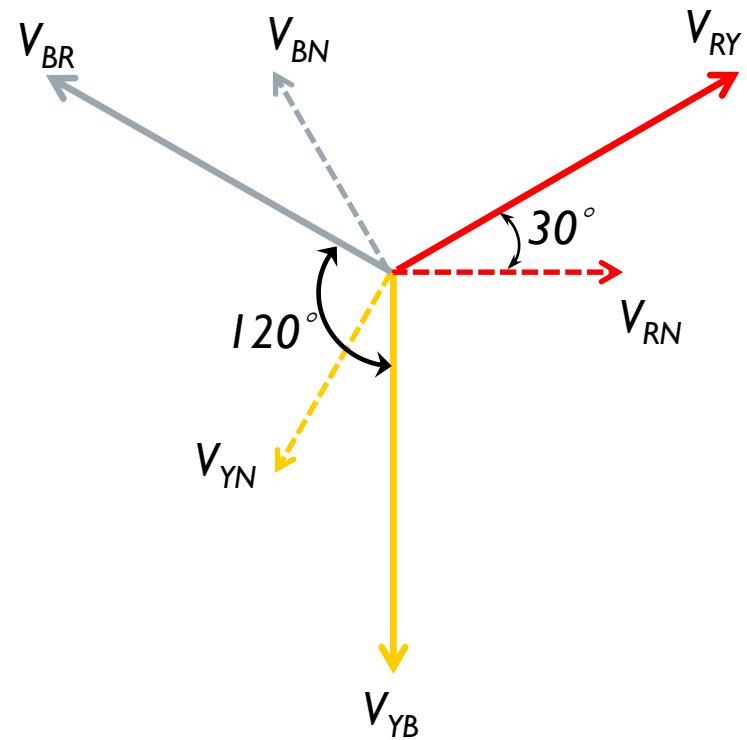
$$\hat{V}_{BR} = \sqrt{3} \times 240 \times \sqrt{2} \times \sin(\omega t + 150^\circ)$$




# 3 Phase 3 Wire & 4 Wire Supply



## 3 Phase 3 Wire Supply

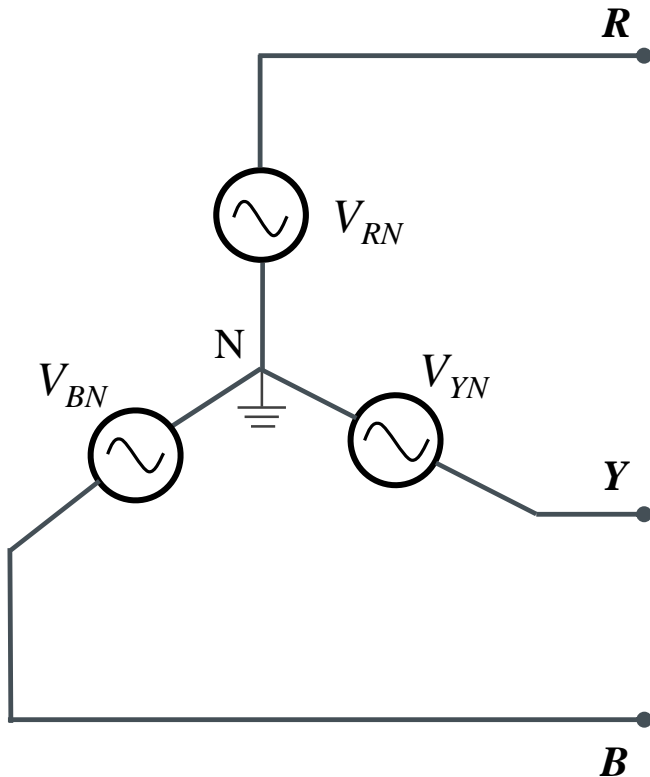


## 3 Phase 4 Wire Supply

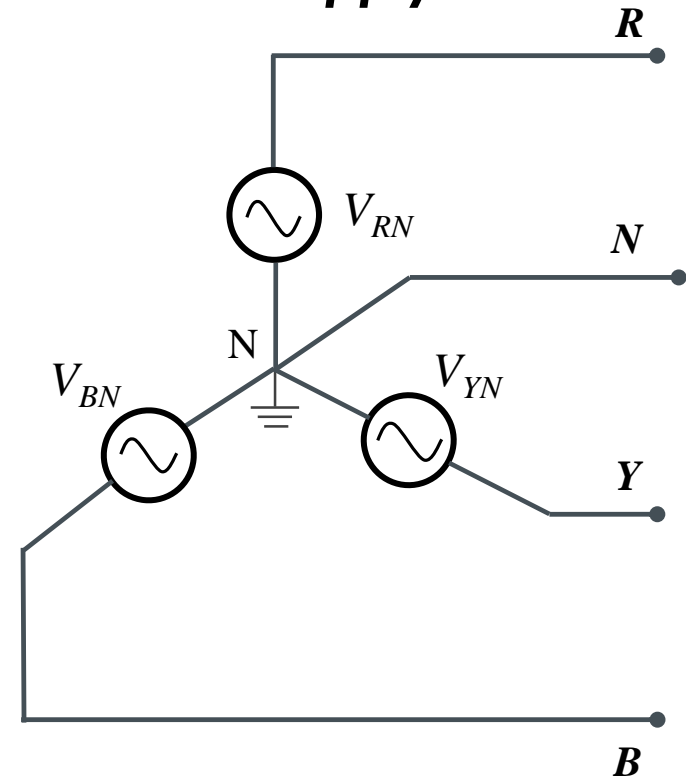

# 3 Phase Load

- Star Connected Load
- Delta Connected Load

# Star Connected Load

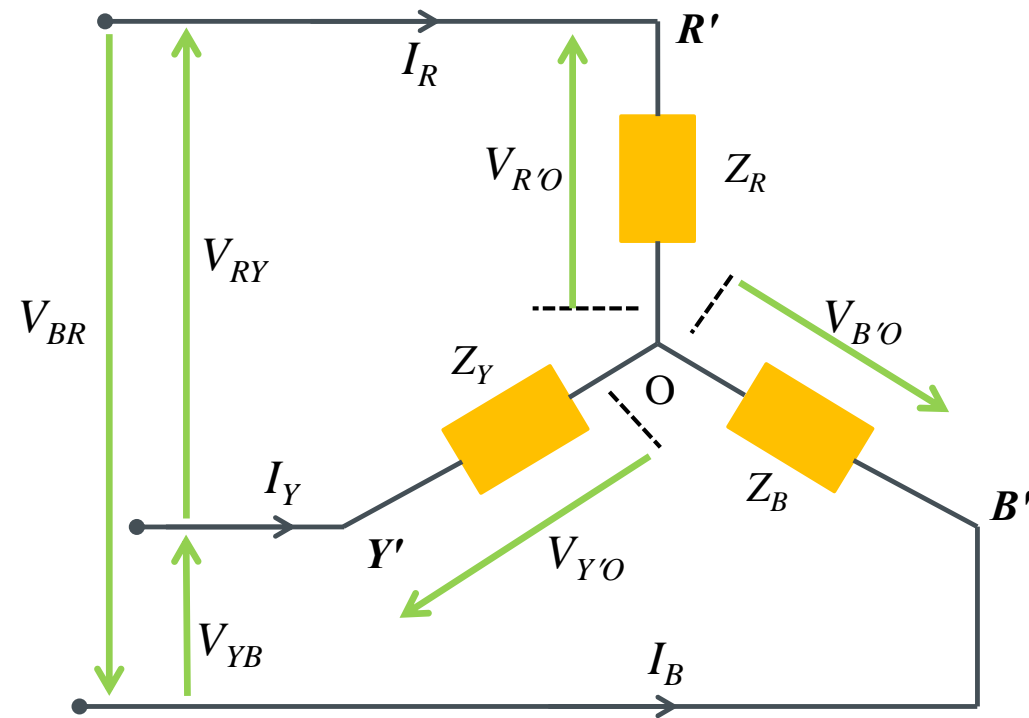


Phase Voltages:  $V_{R'O}, V_{Y'O}, V_{B'O}$

Line Voltages:

$$\hat{V}_{RY} = \hat{V}_{R'O} - \hat{V}_{Y'O}$$


$$\hat{V}_{YB} = \hat{V}_{Y'O} - \hat{V}_{B'O}$$
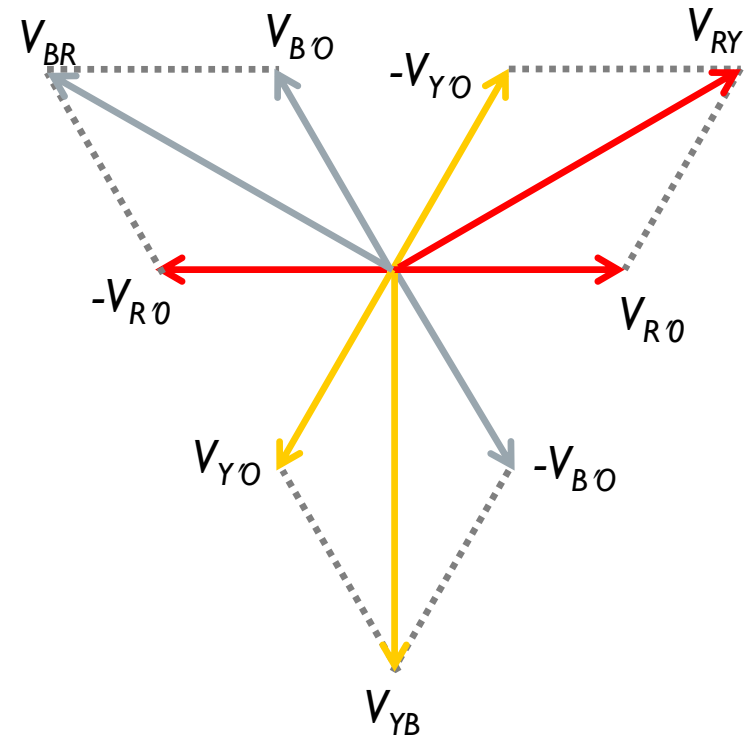
$$\hat{V}_{BR} = \hat{V}_{B'O} - \hat{V}_{R'O}$$


Line Currents = Phase Currents

**For Balanced load,**  
Line Voltage =  $\sqrt{3}$  X Phase Voltage

# Delta Connected Load

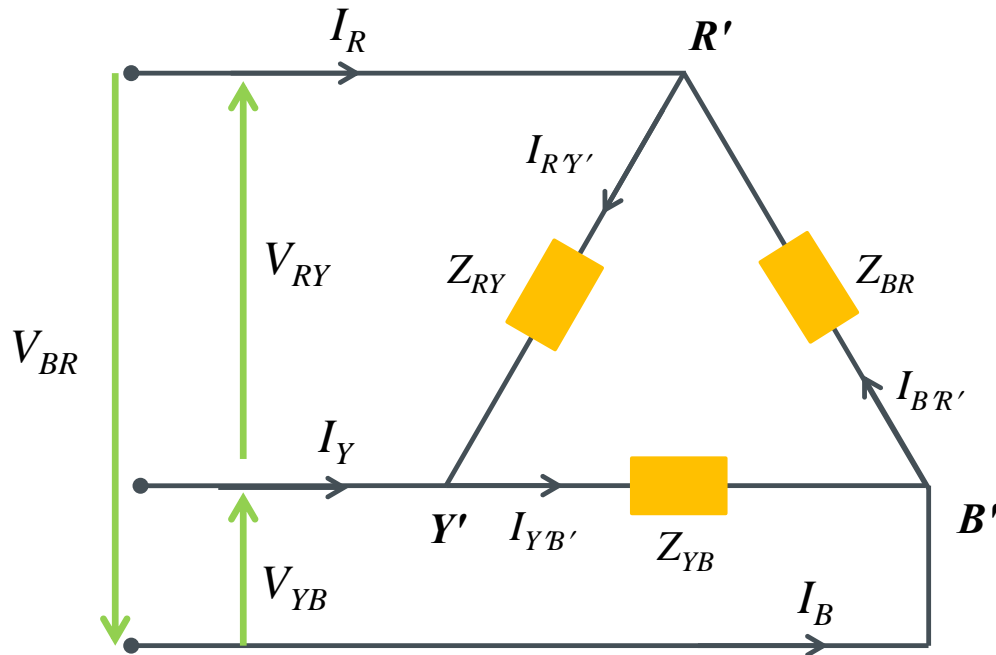


Phase Currents:  $I_{RY'}, I_{YB'}, I_{BR'}$

Line Currents:  $\hat{I}_R = \hat{I}_{R'Y'} - \hat{I}_{B'R'}$

$\hat{I}_Y = \hat{I}_{Y'B'} - \hat{I}_{R'Y'}$

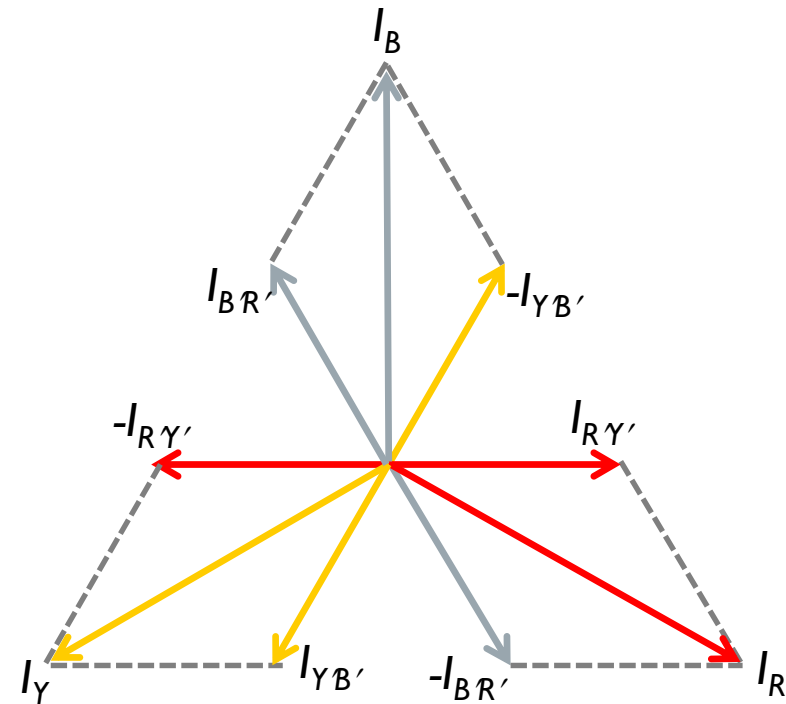
$\hat{I}_B = \hat{I}_{B'R'} - \hat{I}_{Y'B'}$



Phase Voltages = Line Voltages


**For Balanced load,**  
Line Current =  $\sqrt{3}$  X Phase Current

# 3 Phase 4 Wire System

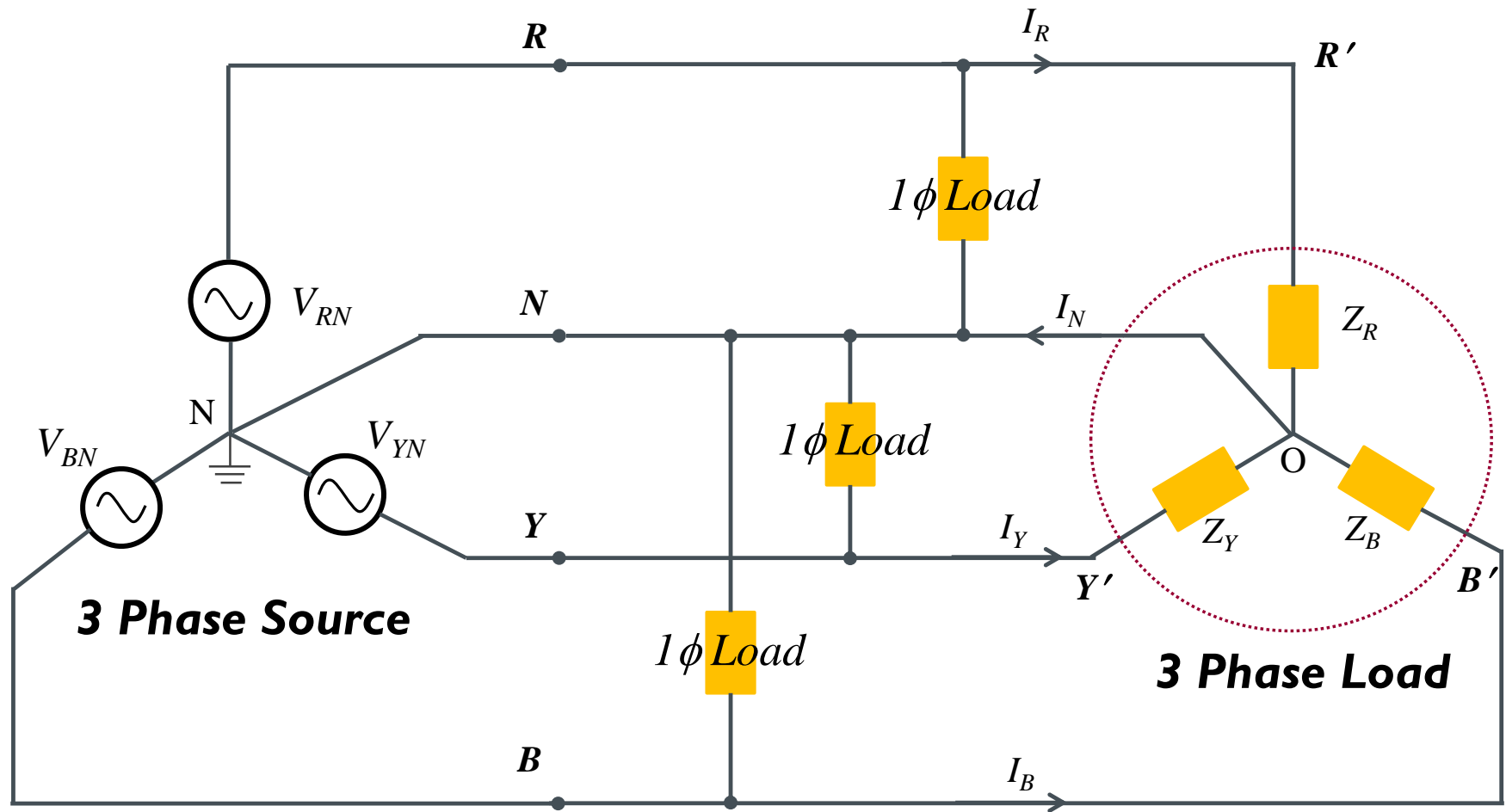



# 3 Phase 3 wire System

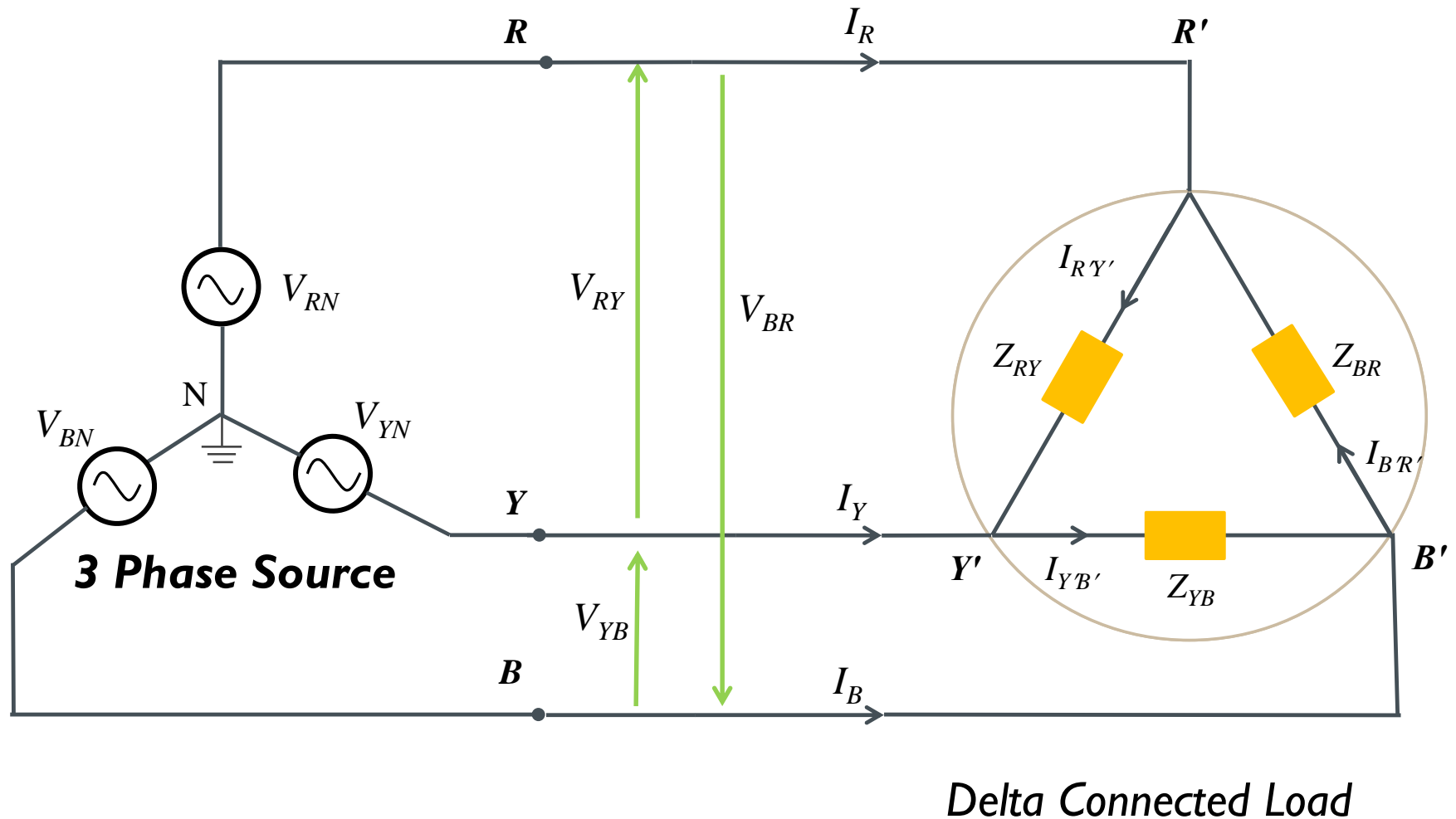

# Summary

*In a three phase balanced supply,*

- ✓ *Summation of phase voltages = zero*
- ✓ *Summation of Line voltages = zero*
- ✓ *Line voltage is  $\sqrt{3}$  x Phase Voltage*
- ✓ *In an RYB sequence,  $V_{RY}$  leads  $V_{RN}$  by  $30^\circ$*
- ✓ *Power transmission is generally through 3 phase 3 wire network and distribution is through 3 phase 4 wire network.*
- ✓ *For Balanced Star connected load, the line voltage =  $\sqrt{3}$  x phase voltage.*
- ✓ *For Balanced Delta connected load, the line current =  $\sqrt{3}$  x phase current*