



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

*(A constituent institution of MAHE, Manipal)*



# Basic Electrical Technology

## RC Transient

---

# Charging of a Capacitor through a Resistor

Applying KVL,

$$V - Ri - v_c = 0$$

where,  $i = C \frac{dv_c}{dt}$


Initial Conditions,

$$\text{At } t = 0 \text{ sec, } V_c = 0 \text{ V}$$

Final current & voltage equation,

$$v_c = V \left( 1 - e^{-\frac{1}{RC}t} \right)$$

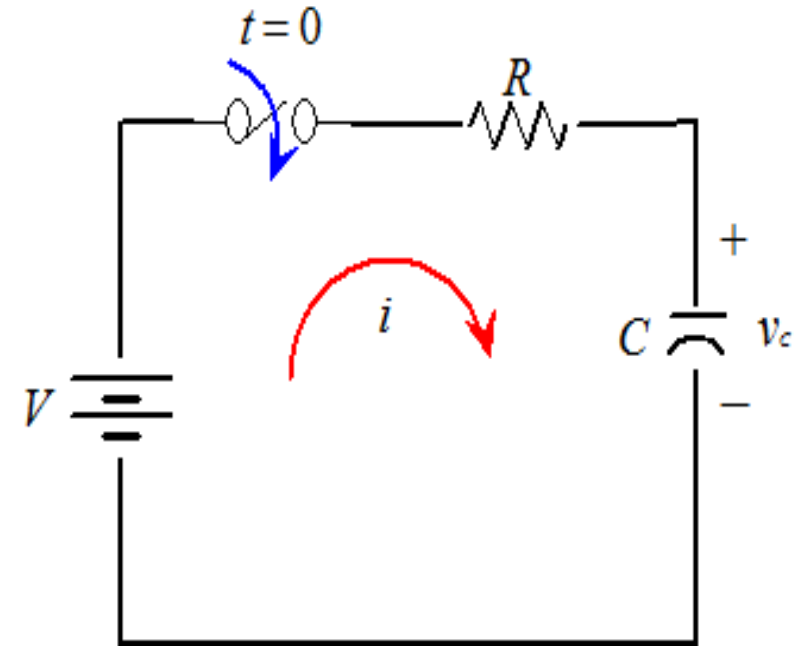
$$i_c = \left( \frac{V}{R} \right) e^{-\left( \frac{1}{RC} \right) t}$$



# Growth of current in an inductive circuit

**Time Constant ( $\tau$ ):** Time taken by the voltage of the capacitor to reach its final steady state value, had the initial rate of rise been maintained constant

$$\tau = RC$$

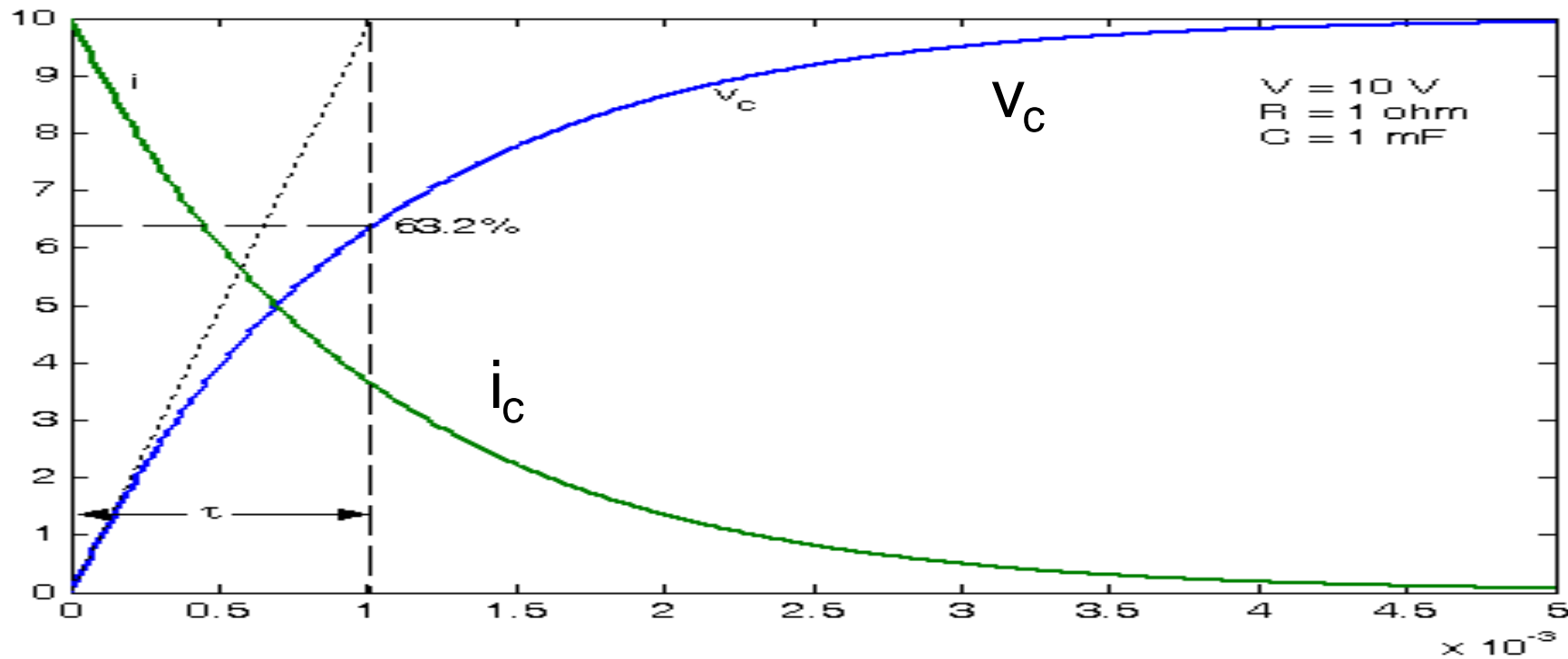

# Discharging of a Capacitor through a Resistor

➤ Capacitor is initially charged to a voltage  $V$

➤ At  $t = 0$ , switch is moved from position  $a$  to  $b$

Applying KVL,


$$v_c + Ri = 0$$

$$\text{Where, } i = C \frac{dv_c}{dt}$$


Using initial conditions and then solving

$$v_c = V e^{-\left(\frac{1}{RC}\right)t}$$
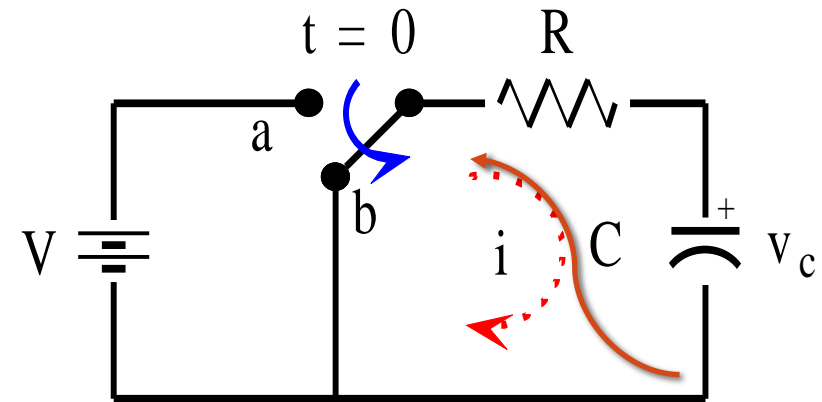
$$i_c = -I e^{-\left(\frac{1}{RC}\right)t}$$


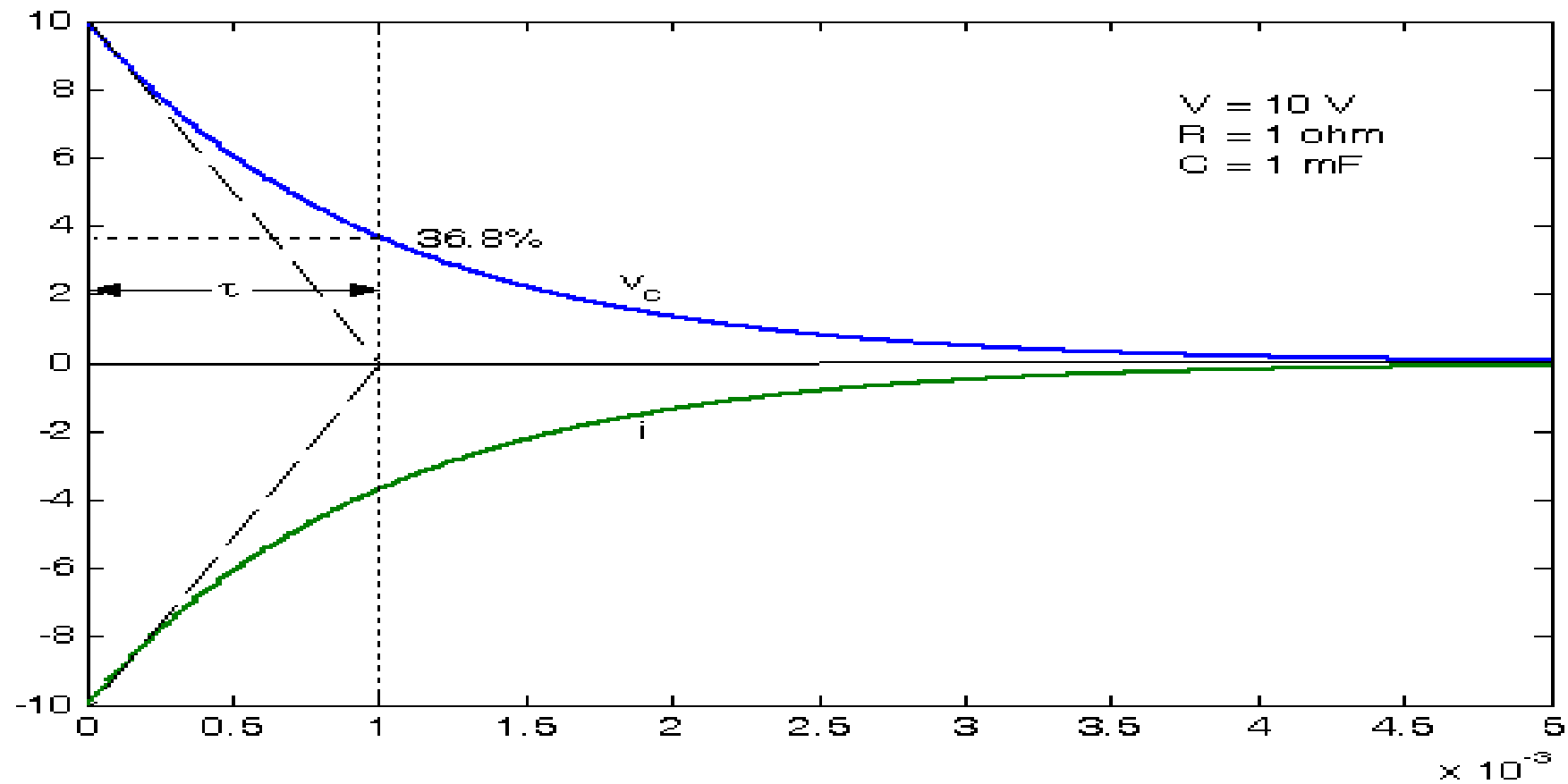
# Discharging of a Capacitor through a Resistor



# Illustration 1

An  $8\ \mu\text{F}$  capacitor is connected in series with a  $0.5\ \text{M}\Omega$  resistor, across a  $200\ \text{V}$  dc supply through a switch. At  $t=0$  sec, the switch is turned on. Calculate

- i. Time constant of the circuit
- ii. Initial charging current.
- iii. Time taken for the potential difference across the capacitor to grow to  $160\ \text{V}$ .
- iv. Current & potential difference across the capacitor  $4.0$  seconds after the switch is turned on.
- v. Derive the expressions used


**Ans:**

**(i) 4 seconds, (ii)  $400\ \mu\text{A}$  , (iii) 6.44 seconds**

**(iv)  $126.424\ \text{V}$  & (v)  $147.15\ \mu\text{A}$**
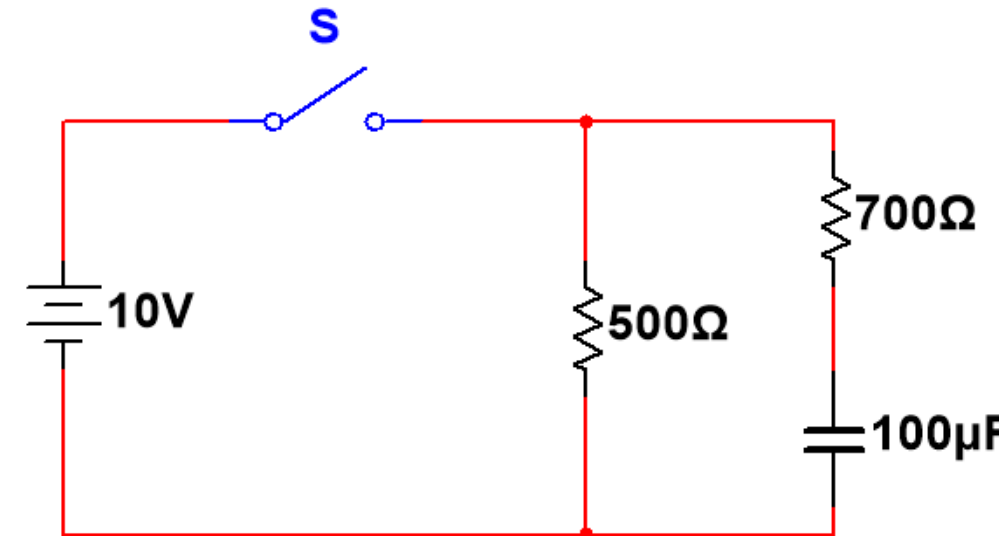
# Illustration 2

For the circuit shown in the figure below, the switch 'S' is closed at  $t = 0$  sec. Determine how long will it take, after the switch is closed, for the total current drawn from the supply to reach 25mA.




**Ans:  $t = 73.5$  ms**
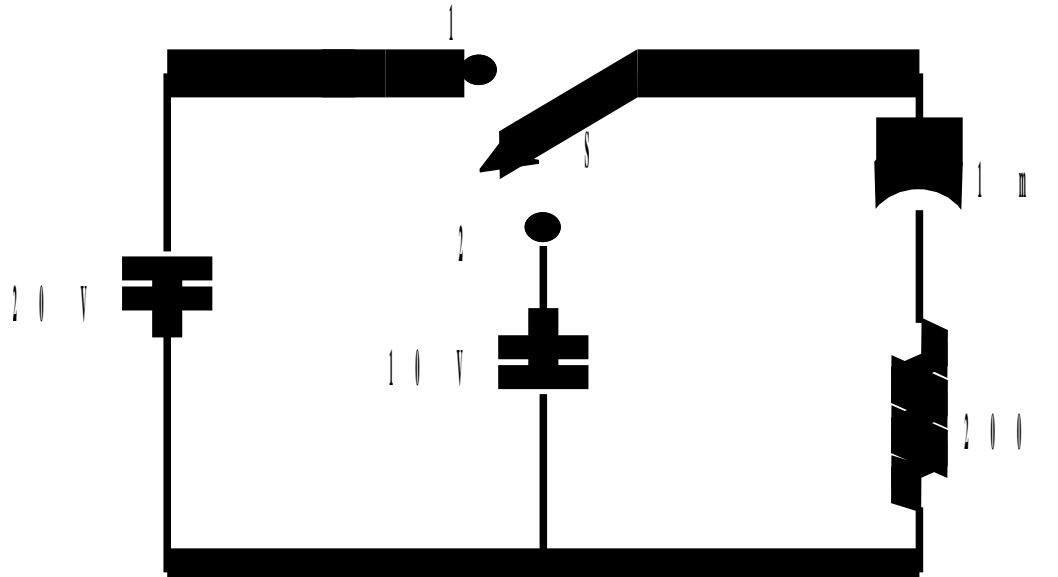
# Illustration 3

In the network shown below, the switch is closed to position 1 at  $t = 0$  & is moved to position 2 at  $t = 0.4$  sec. Determine the voltage across the capacitor  $v_c(t)$  & sketch it for  $0 \leq t \leq 1$  sec

Also find the value of 't' for which  $v_c(t) = 0$





# Solution

$$v_c = 20(1 - e^{-t/0.2})$$

At  $t = 0.4 \text{ sec}$ ,  $v_c = 17.29 \text{ V}$

After 0.4 second, the switch is in position 2

$$v_c = -10 + 27.29e^{-(t-0.4)/0.2}$$

At  $t = 1 \text{ sec}$ ,  $v_c = -8.64 \text{ V}$

**Ans: At  $t = 0.6 \text{ sec}$ ,  $v_c = 0 \text{ V}$**

