



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

*(A constituent institution of MAHE, Manipal)*




# Basic Electrical Technology


## Mesh Current Analysis

---
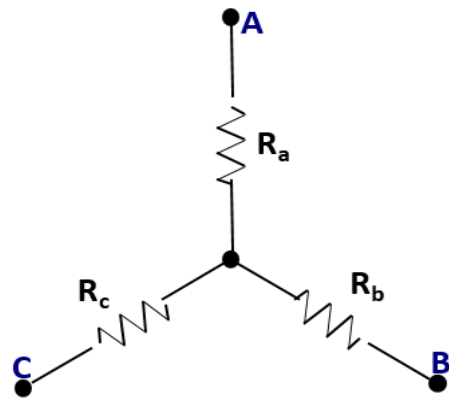
# Recap: Star-Delta & Source Transformations




Star Connection

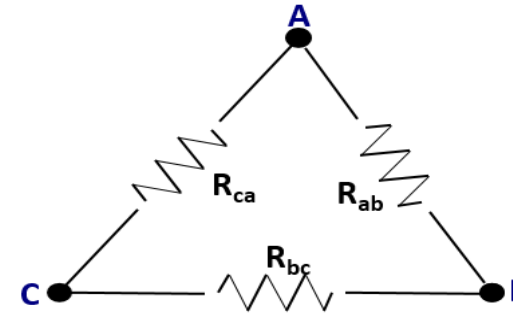


Delta Connection

Practical Voltage source

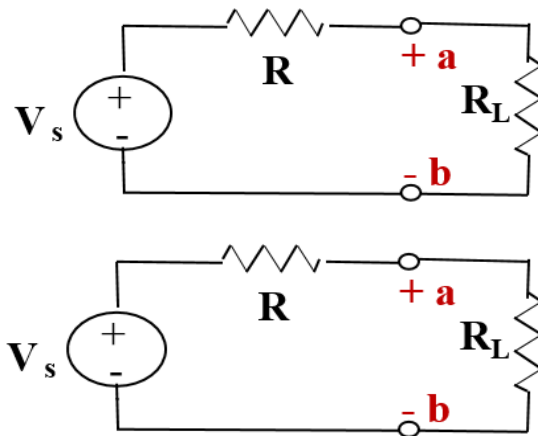

$$V_s = R \times I_s$$

Practical Current source

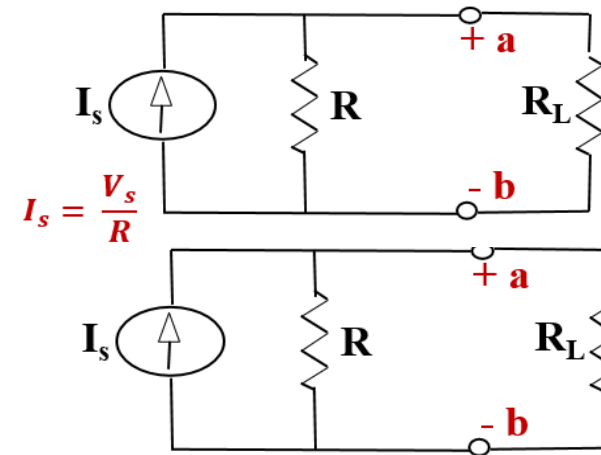



# Objective

---

Application of KVL for the analysis of DC circuits

# Introduction

## Kirchhoff's Voltage Law (KVL)


- States that in a closed circuit, the algebraic sum of all source voltages must be equal to the algebraic sum of all the voltage drops.

## Loop

- Any closed path in an electric circuit
- Inside loops: a-b-g-a, b-c-g-b & a-c-b-a
- Outside loops: a-c-g-a & a-b-c-g-a
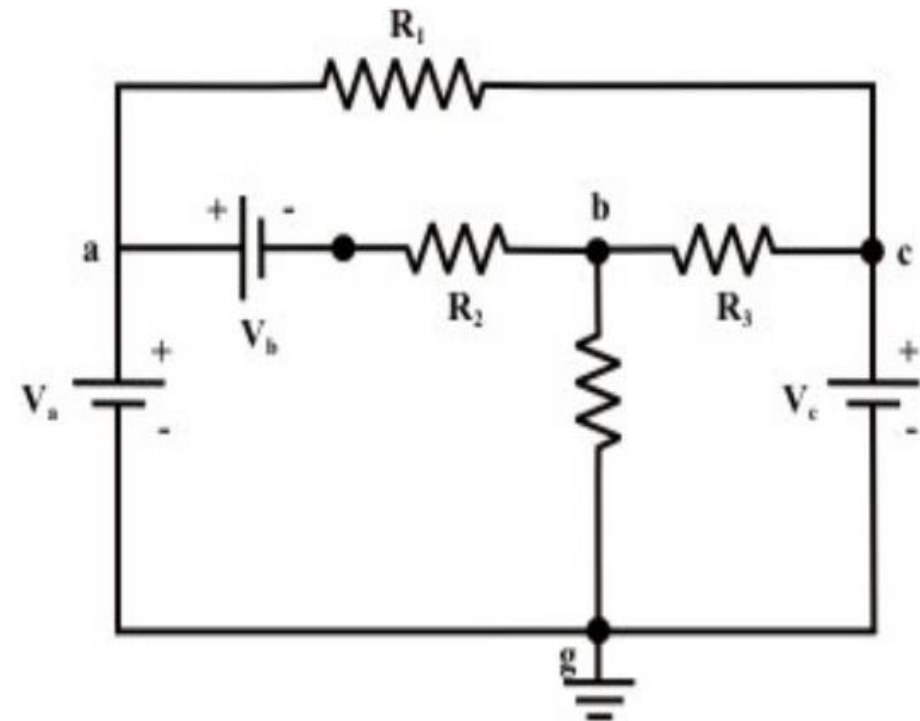
## Mesh

- Special case of loop that does not have any other loops within it.
- a-b-g-a, b-c-g-b & a-c-b-a




# Mesh Current Analysis Method

---

1. Transform all the practical current sources to voltage sources
2. Mark currents in all the meshes (or independent loops) in clockwise direction
3. Write KVL equations for these independent meshes
  - a) Sign convention: Voltage drop ---> as negative
  - b) Voltage rise ---> as positive
4. Solve for the currents
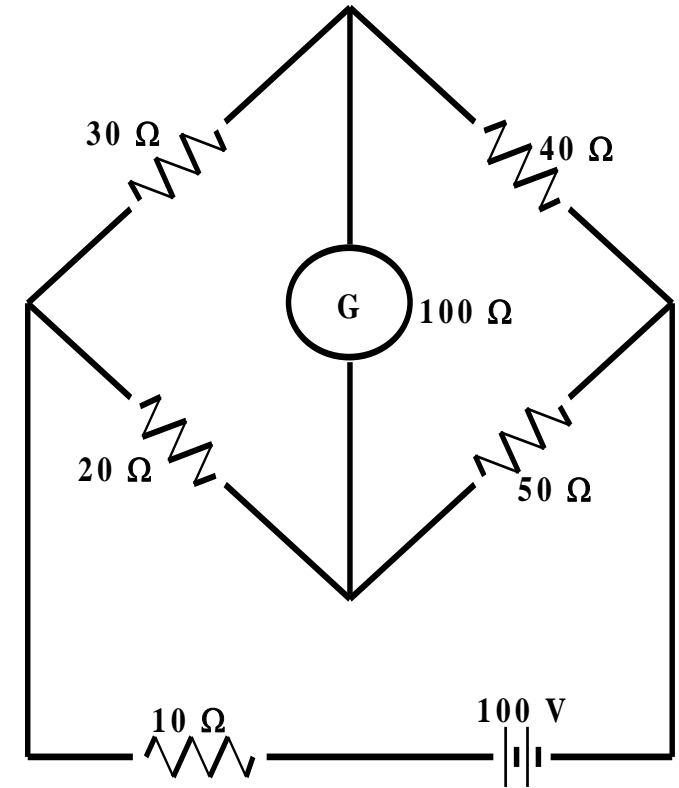
# Illustration 1


Determine the current through the galvanometer “G”



**Answer : 84 mA**


# Illustration 1 contd...

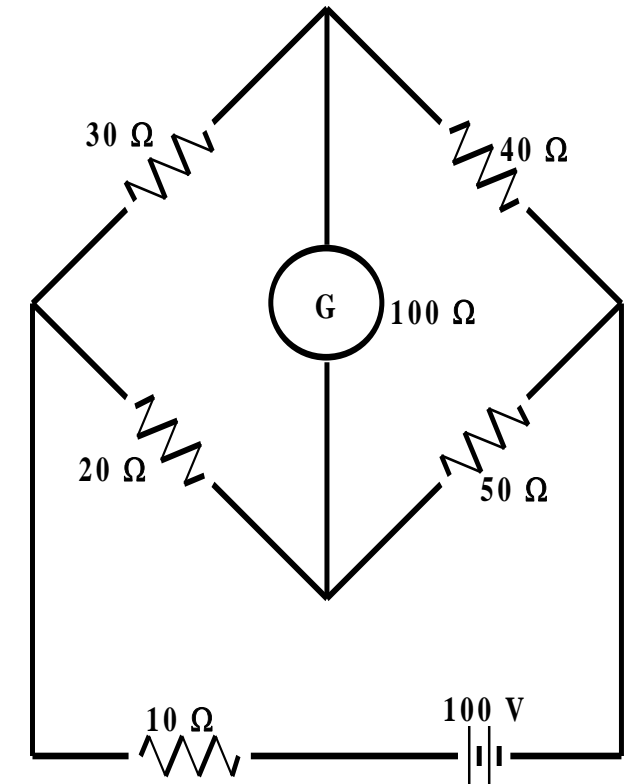**How to write the network equations by inspection?**


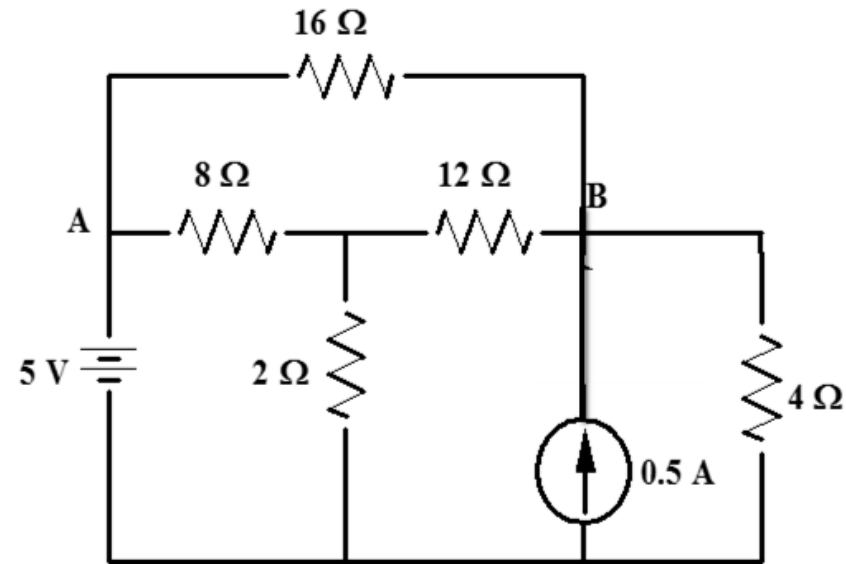
# Illustration 2

Determine the current and its direction through the  $2\ \Omega$  resistor. Also, determine the potential difference between A & B




**Answer :**  $I_{2\Omega} = 0.575\text{ A}$  (downwards)  
 $V_A - V_B = +2.7\text{ V}$


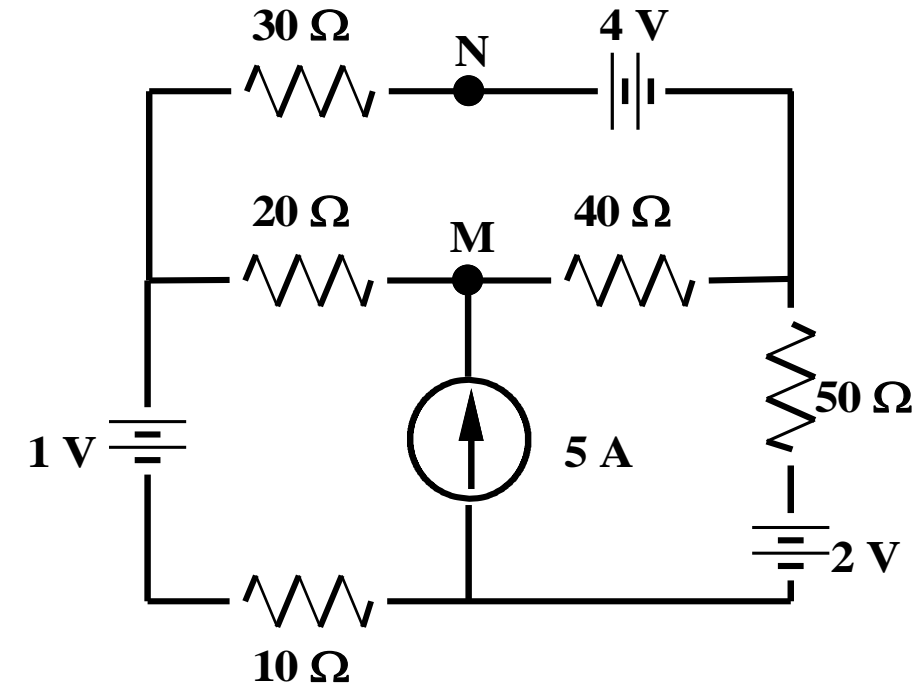
# Illustration 3

Find the power supplied by the 5 A current source. Also, determine the voltage between the points M & N.



**Answer:**  $P_{5A} = 556.5 \text{ W}$

$V_M - V_N = 55.8 \text{ V}$

# Summary

---

- Mesh currents are determined
- Other operating conditions can be determined using the mesh currents
- Concept of super-mesh: If there is a current source between two meshes