

12.

The actual circuit gains are found by conversion of the PB and reset time into values appropriate to the circuit. The 80% PB means that if the input changes by 80% of its range, or,  $0.8(5) = 4.0$  volts then the output must change by 100% of its range, or, 12 volts. This means the circuit gain is,

$$G_P = 12/4 = 3$$

The 0.03 min reset time means that the integral gain is given by,

$$K_I = 1/T_I = 1/0.03 = 33.33 \text{ \%}/(\text{\%-min})$$

We convert this to seconds so that it will be more appropriate to the circuit,

$$K_I = (1 \text{ min}/60 \text{ s})[33.33 \text{ \%}/(\text{\%-min})]$$

$$K_I = 0.5556 \text{ \%}/(\text{\%-s})$$

The interpretation of this number is that if the input changes by 1% of its range for 1 s, then the output must change by 0.556% of its range. Thus,

$$G_I = (0.005556)(12)/[(0.01)(5)]$$

$$G_I = 1.333 \text{ s}^{-1}$$

Using the circuit of Fig. 10.13 we make,

$$R_2/R_1 = 3 \quad 1/R_2C = 1.333$$

If we select  $C = 2 \mu\text{F}$  then  $R_2 = 375 \text{ k}\Omega$  and so we must have  $R_1 = R_2/3 = 125 \text{ k}\Omega$ . The inverter resistance can be any convenient value, say  $10 \text{ k}\Omega$ .

14

$\pm I/P \text{ range} - 2.5 - 8V$        $PB = 62\%$   
 $O/P \text{ range} - 0 - 7V$        $T_r = 0.08 \text{ min}$   
     $T_d = 0.09 \text{ min}$

$\therefore K_P = \frac{100}{62} = 1.613 \text{ \%}/\%$

$G_P = \frac{1.613 \times 7}{0.08 \times 5.5} = 2.053 = \frac{R_2}{R_1}$

$T_r = 0.08 \text{ min} = 0.08 \times 60 \text{ s} = 4.8 \text{ Sec}$

$K_I = \frac{1}{T_r} = \frac{1}{4.8 \text{ s}} = 0.2083 \text{ \%}/\text{\%-s}^{-1}$

$G_I = \frac{1}{R_2 C_I} = 0.2083 \times \frac{7}{5.5} = 0.265$

$T_D = 0.09 \text{ min} = 5.4 \text{ sec} \quad G_D = 5.4 \times \frac{7}{5.5} = 6.873 = R_D C_P$

$2\pi R_3 C_D = 0.1 \times 0.8 \text{ min} = 0.08 \text{ min} = 4.8 \text{ s}$