

# Basic Electrical Technology

[ELE 105 I]

---

*SINGLE PHASE AC CIRCUITS*

# Recap

---



- Average value of an alternating waveform
- RMS value of an alternating waveform
- Representing AC
- R, L, C circuit response with AC supply
- Power associated with a pure R, L, C

# Topics covered...

---

- RL, RC, RLC circuit response with AC supply
- Power associated with a series RL, RC circuits
- Loads in parallel

# RL circuit analysis

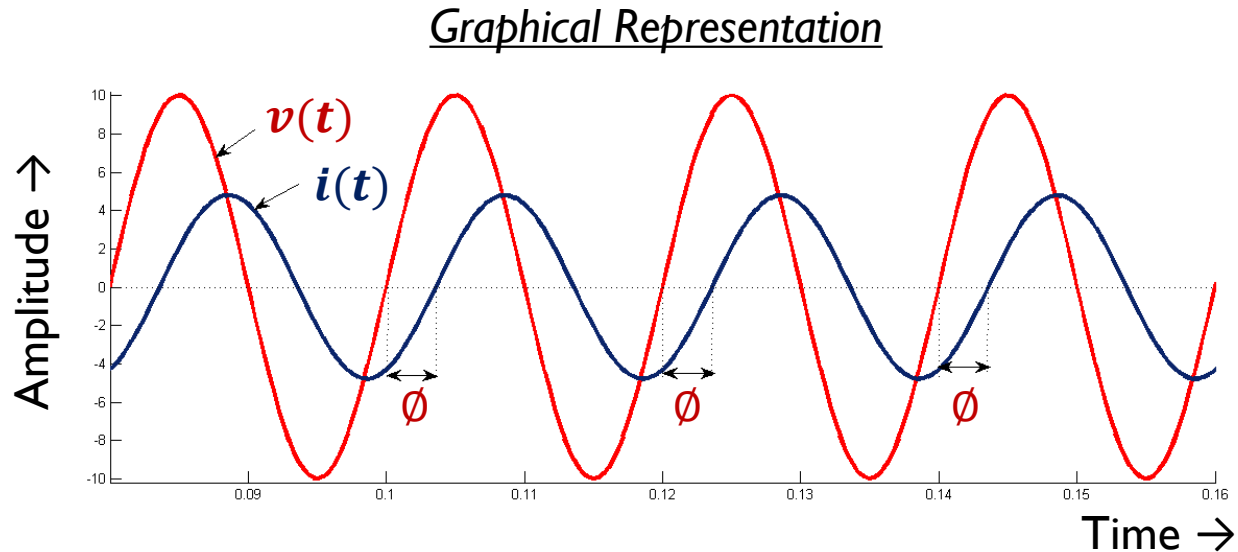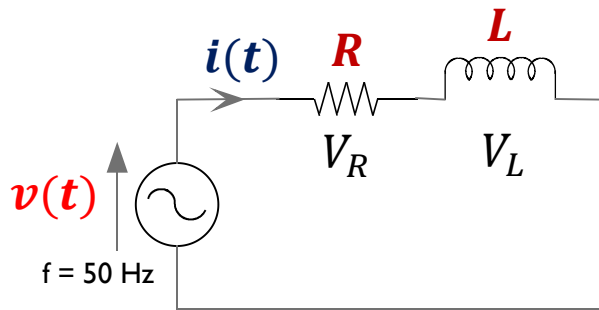


Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_L = j\bar{I}X_L$$

$$\bar{V} = \bar{V}_R + \bar{V}_L = |V|\angle\phi$$

Phasor Representation

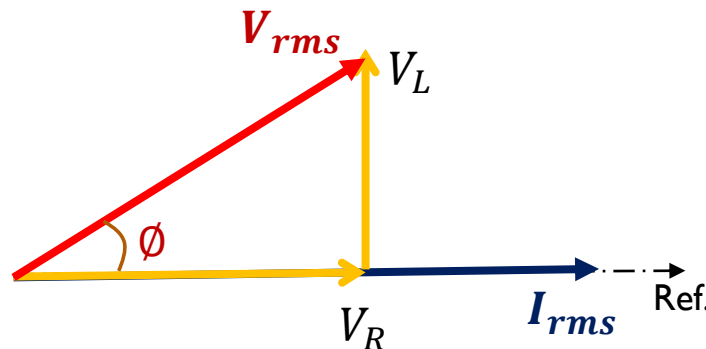

Impedance

$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R + jX_L)}{\bar{I}} = R + jX_L = |Z|\angle\phi$$

$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_L = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_L^2} \quad \phi = \tan^{-1} \frac{X_L}{R}$$


Mathematical Representation

$$i(t) = I_m \sin(\omega t)$$

$$v(t) = V_m \sin(\omega t + \phi)$$

$\phi$  – Phase Angle

# Power associated - RL circuit

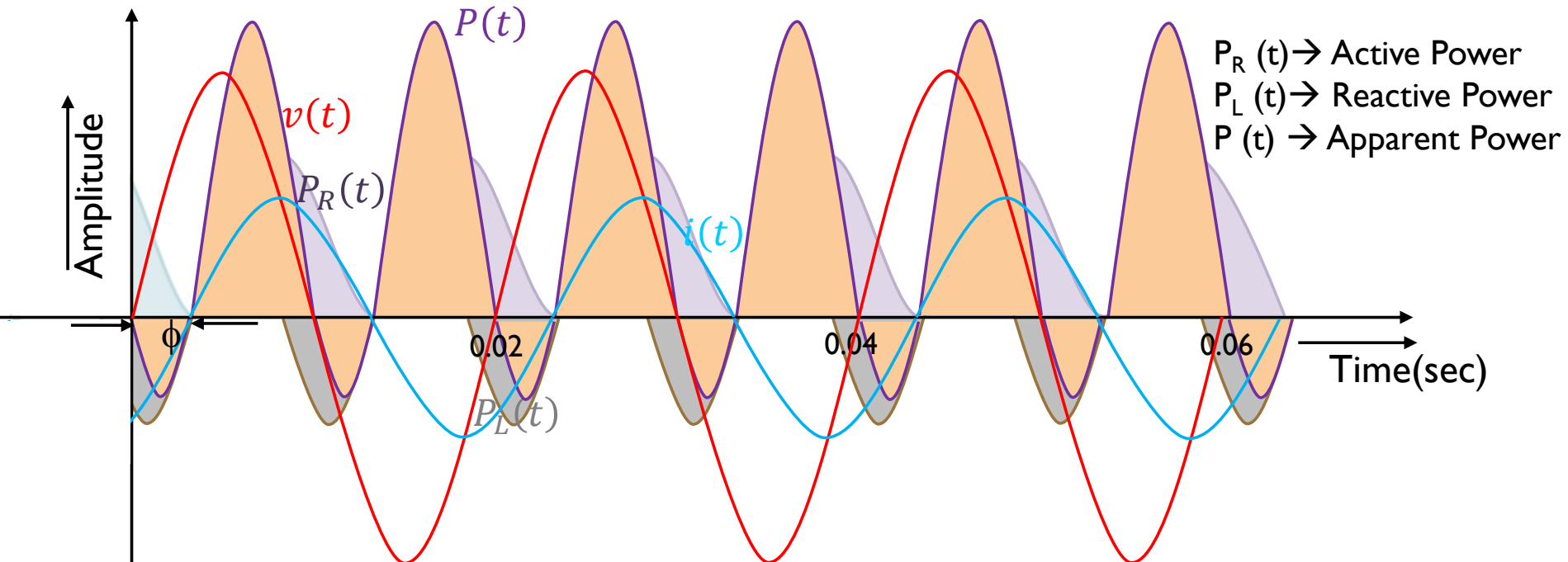

Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t + \phi)$$


$$= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t + \phi)]$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

$\cos \phi$  is called the **Power Factor**

# RC circuit analysis

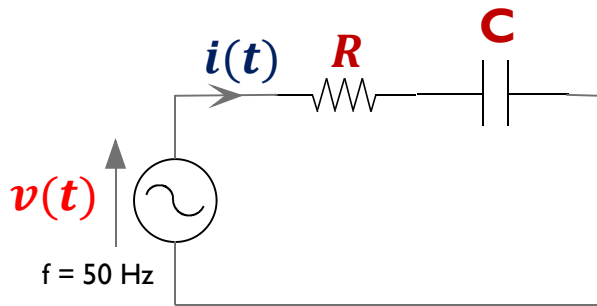

Let  $\bar{I}$  be along the reference

$$\bar{V}_R = \bar{I}R$$

$$\bar{V}_C = -j\bar{I}X_C$$

$$\bar{V} = \bar{V}_R + \bar{V}_C = |V|\angle -\phi$$


## Mathematical Representation

$$i(t) = I_m \sin(\omega t)$$


$$v(t) = V_m \sin(\omega t - \phi)$$

$\phi$  – Phase Angle

## Graphical Representation

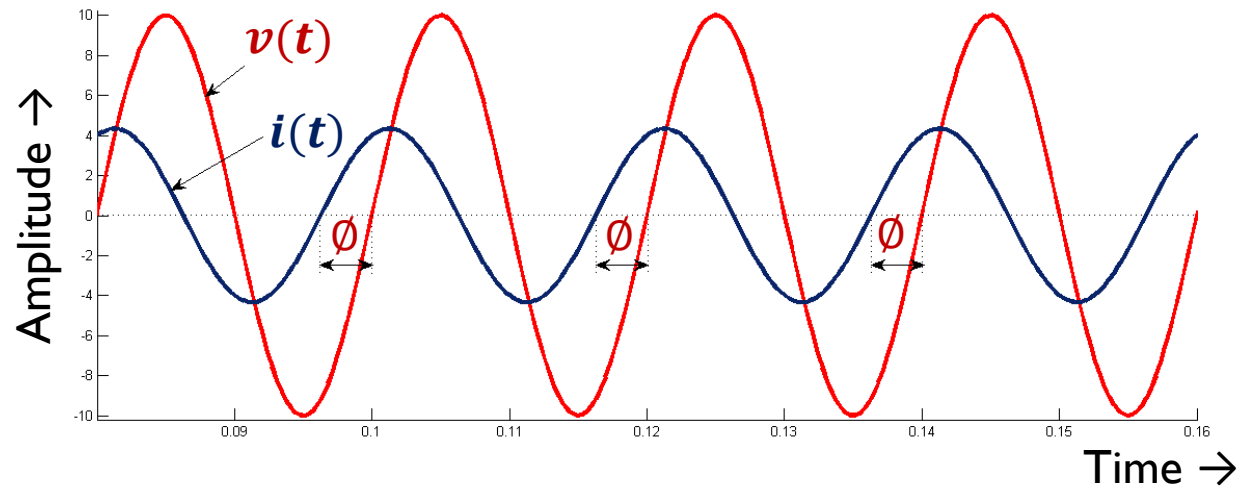

## Phasor Representation

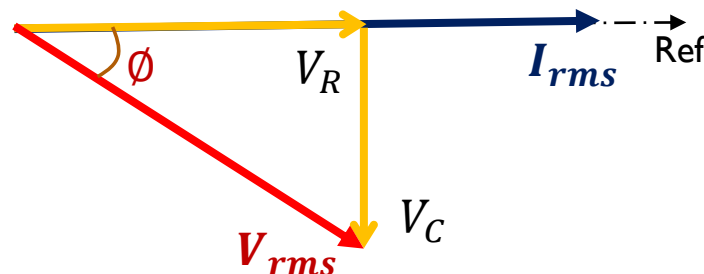

## Impedance


$$\frac{\bar{V}}{\bar{I}} = \frac{\bar{I}(R - jX_C)}{\bar{I}} = R - jX_C = |Z|\angle -\phi$$

$Z$  – Impedance of the circuit

$$\therefore R = |Z| \cos \phi \quad X_C = |Z| \sin \phi$$

$$|Z| = \sqrt{R^2 + X_C^2} \quad \phi = \tan^{-1} \frac{X_C}{R}$$

# Power associated - RC circuit

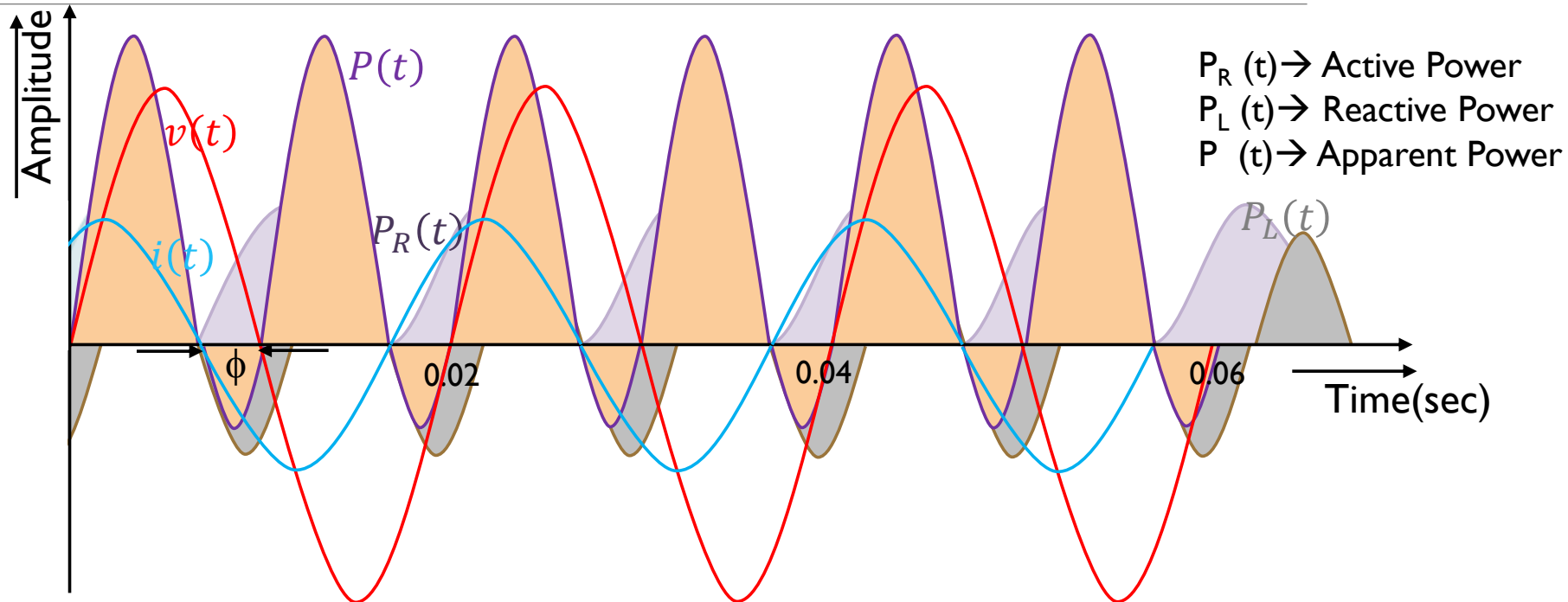

Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$


$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$= V_{rms} I_{rms} [\cos \phi - \cos(2\omega t - \phi)]$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt = \frac{V_m I_m}{2} \cos \phi$$

$$\boxed{P_{avg} = V_{rms} I_{rms} \cos \phi}$$

# RLC circuit

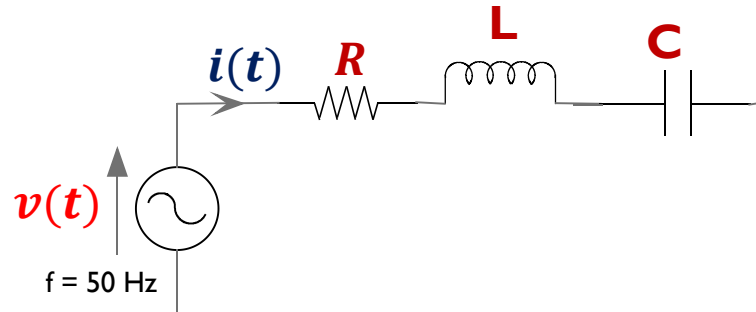

Let  $i(t)$  be the reference

**Impedance,  $Z = R + j(X_L \sim X_C)$**



|                        |               |  |
|------------------------|---------------|--|
| $\text{if } X_L = X_C$ | $\Rightarrow$ | <i>Resistive circuit<br/>(Resonance condition)</i> |
| $\text{if } X_L > X_C$ | $\Rightarrow$ | <i>RL series circuit</i>                           |
| $\text{if } X_L < X_C$ | $\Rightarrow$ | <i>RC series circuit</i>                           |


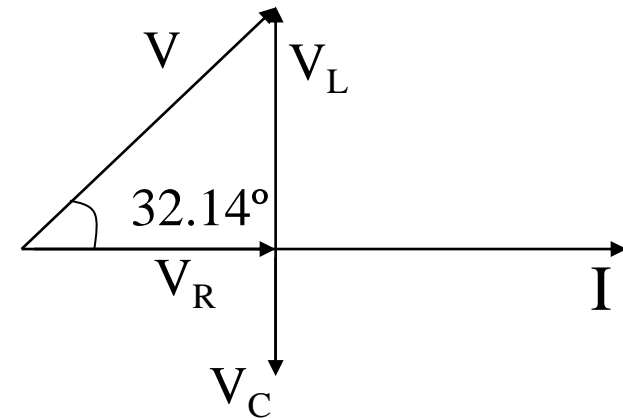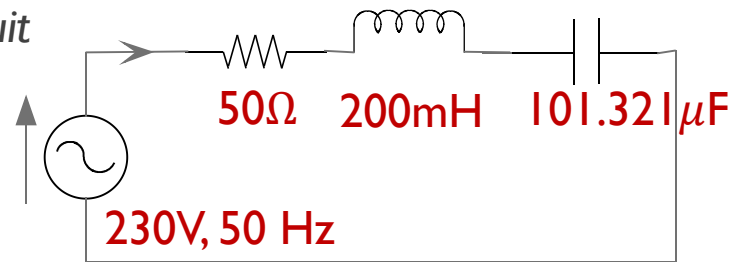
# Illustration I

A resistance of  $50\Omega$  is connected in series with an inductance of  $200\text{mH}$  and capacitance of  $101.321\mu\text{F}$  across a  $230\text{V}, 50\text{ Hz}$ , single phase AC supply. Obtain,

- Impedance of the circuit
- Current drawn
- Power factor
- Power consumed
- Phasor diagram



$$X_L = 2 \times \pi \times 50 \times 0.2 = 62.8315\Omega$$

$$X_C = \frac{1}{2 \times \pi \times 50 \times 101.321\mu} = 31.4159\Omega$$

$$PF = \cos(32.14) = \mathbf{0.846 \text{ lag}}$$


$$Z = R + jX_L - jX_C = \mathbf{50 + j31.4156\Omega = 59.050\angle 32.14^\circ \Omega}$$

$$I = \frac{230\angle 0}{59.05\angle 32.14} = \mathbf{3.898\angle -32.14^\circ A}$$

$$\begin{aligned} P &= |V_{rms}| |I_{rms}| \cos\phi \\ &= 230 \times 3.898 \times 0.846 = \mathbf{759.15W} \end{aligned}$$
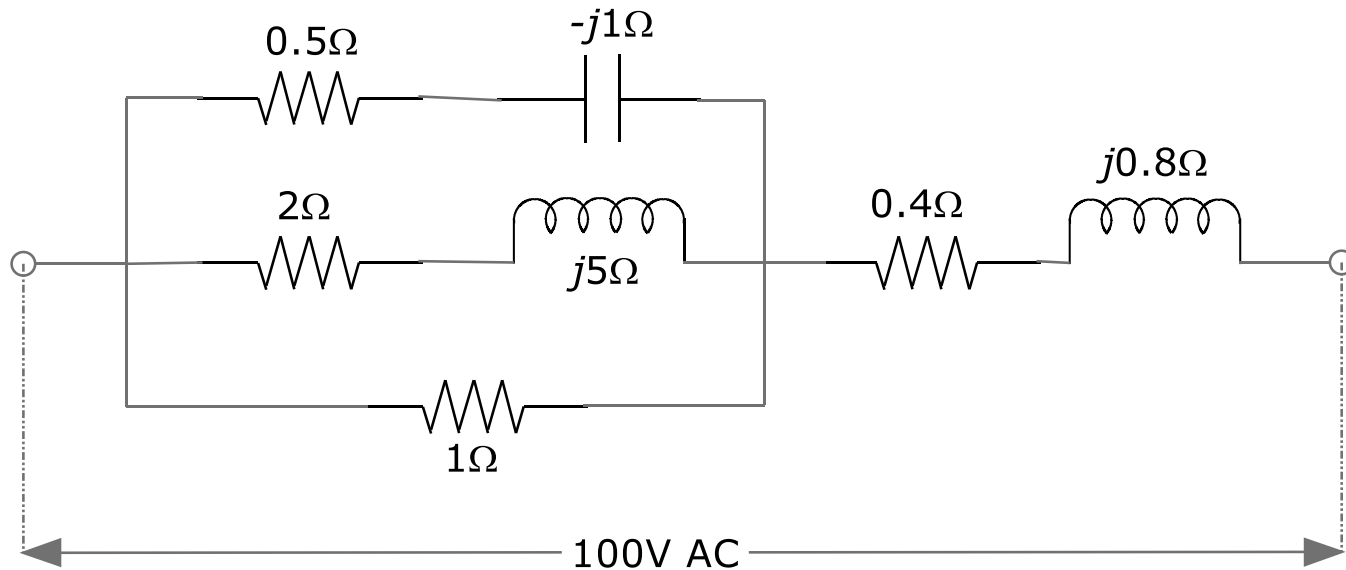
# Illustration 2

Determine the impedance of the circuit shown and the power consumed in each branch



$$Z_1 = 0.5 - j1\Omega$$

$$Z_3 = 1\Omega$$

$$Z_2 = 2 + j5\Omega$$

$$Z_4 = 0.4 + j0.8\Omega$$

$$\bar{I} = \frac{100\angle 0}{1.12\angle 29.5} = 89.285\angle -29.5\text{ A} = \bar{I}_4$$

$$Z_{eq} = (Z_1 || Z_2 || Z_3) + Z_4 = 1.12\angle 29.5^\circ\Omega$$


$$\bar{V}_2 = \bar{I}_4 \times Z_4 = 79.85\angle 33.934\text{ V}$$

$$\bar{V} = \bar{V}_1 + \bar{V}_2$$


$$\bar{V}_1 = 55.91\angle -52.868\text{ V}$$

$$\bar{I}_1 = \frac{\bar{V}_1}{Z_1} = 50.00\angle 10.565\text{ A} \quad \bar{I}_2 = 10.38\angle -121.068\text{ A} \quad \bar{I}_3 = 55.91\angle -52.868\text{ A}$$

$$P_1 = |I_1|^2 \times R_1 = 1.25\text{ kW} \quad P_2 = 0.215\text{ kW} \quad P_3 = 3.125\text{ kW} \quad P_4 = 3.188\text{ kW}$$

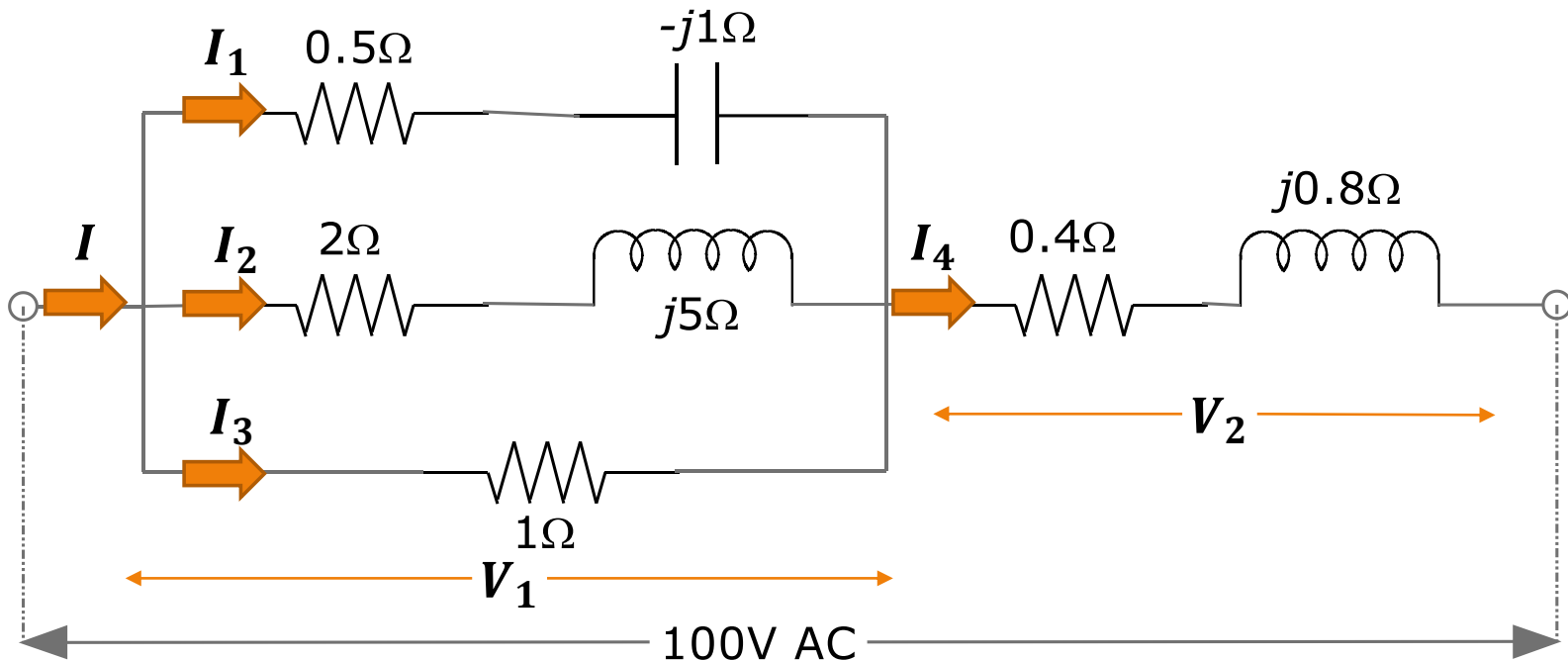

# Impedance in parallel

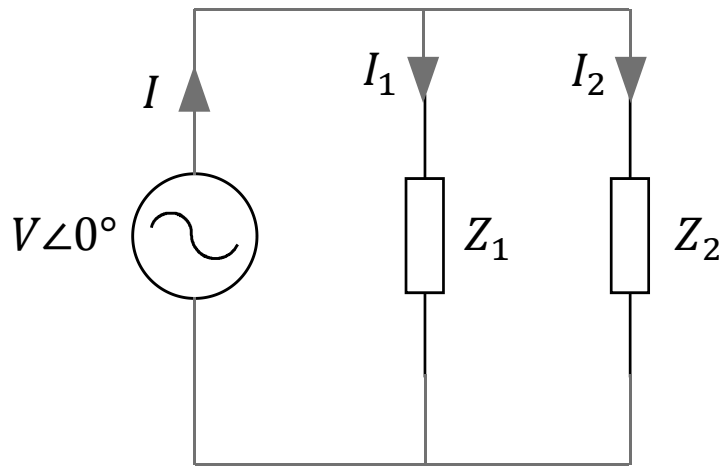

$$\text{Let } Z_1 = R_1 + jX_1 \quad Z_2 = R_2 + jX_2$$

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} \quad I_1 = I * \frac{Z_2}{Z_1 + Z_2} \quad I_2 = I * \frac{Z_1}{Z_1 + Z_2}$$

$$Y_{eq} = Y_1 + Y_2 \quad \textcolor{red}{Y: \textit{Admittance}}$$

$$Y_1 = \frac{1}{Z_1} = \frac{1}{R_1 + jX_1} = \frac{1}{(R_1 + jX_1)} * \frac{(R_1 - jX_1)}{(R_1 - jX_1)} = \frac{R_1}{(R_1^2 + X_1^2)} - j \frac{X_1}{(R_1^2 + X_1^2)} = G_1 - jB_1$$

$$Y_2 = \frac{1}{Z_2} = \frac{1}{R_2 + jX_2} = \frac{1}{(R_2 + jX_2)} * \frac{(R_2 - jX_2)}{(R_2 - jX_2)} = \frac{R_2}{(R_2^2 + X_2^2)} - j \frac{X_2}{(R_2^2 + X_2^2)} = G_2 - jB_2$$

$\textcolor{red}{G: \textit{Conductance}} \quad \textcolor{red}{B: \textit{Susceptance}}$

$$\textcolor{red}{Y_{eq} = (G_1 + G_2) - j(B_1 + B_2) = G_{eq} - jB_{eq}}$$


# Impedance in parallel

For 'N' impedances connected in parallel,

$$\frac{1}{Z_{eq}} = \frac{1}{Z_1} + \frac{1}{Z_2} + \frac{1}{Z_3} + \dots + \frac{1}{Z_N}$$

$$Y_{eq} = Y_1 + Y_2 + Y_3 + \dots + Y_N$$
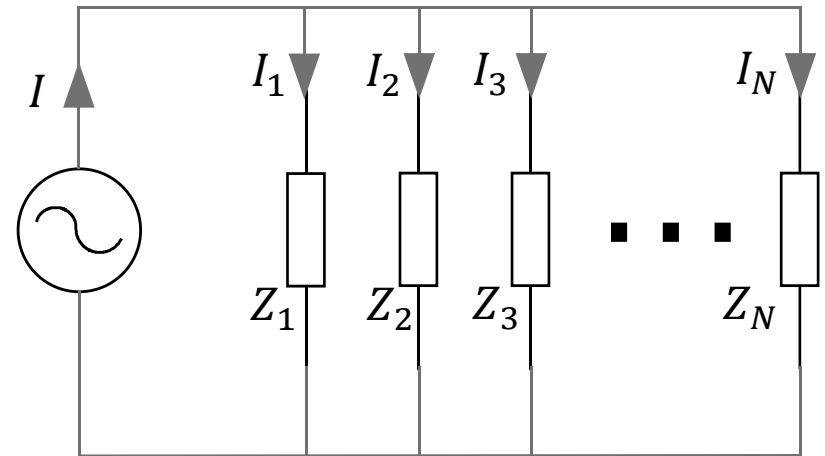
$$\mathbf{Y}_{eq} = \mathbf{G}_{eq} \pm j\mathbf{B}_{eq}$$



$$I_1 = VY_1; I_2 = VY_2; I_3 = VY_3; \dots \dots I_N = VY_N$$

$$I = I_1 + I_2 + I_3 + \dots + I_N = VY_{eq}$$