

Basic Electrical Technology

[ELE 105 I]

SINGLE PHASE AC CIRCUITS

Topics covered...

- Average value of an alternating waveform
- RMS value of an alternating waveform
- Representing AC
- R, L, C circuit response with AC supply
- Power associated with a pure R, L, C

Average value of Sinusoidal Alternating Current

Definition: “It is that steady current which transfers the same amount of charge to any circuit during the given interval of time, as is transferred by the alternating current to the same circuit during the same time”


For a periodic function $f(t)$ with period T ,

$$F_{avg} = \frac{1}{T} \int_0^T f(t) dt$$

For sinusoidal signal,

$$I_{avg} = \frac{1}{T/2} \int_0^{T/2} I_m \sin \omega t dt$$

$$I_{avg} = \frac{2I_m}{\pi}$$

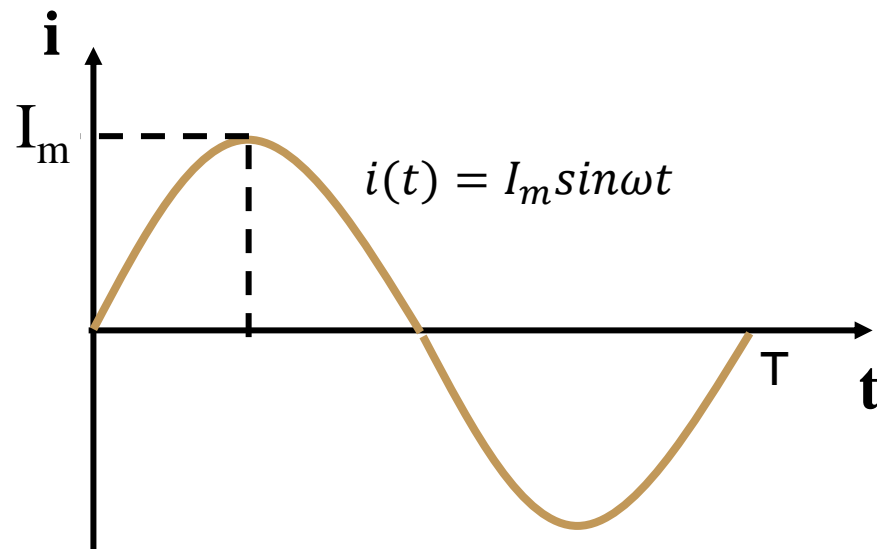

RMS value of Sinusoidal Alternating Current


Definition: “It is that value of direct current which when flowing through a circuit produces the same amount of heat for a given interval of time as that of the alternating current flowing through the same circuit during the same time”

For a periodic function $f(t)$
with period T ,

$$F_{rms} = \sqrt{\frac{1}{T} \int_0^T f^2(t) dt}$$

$$I_{rms} = \sqrt{\frac{1}{T} \int_0^T I_m^2 \sin^2 \omega t dt}$$

$$I_{RMS} = \frac{I_m}{\sqrt{2}}$$

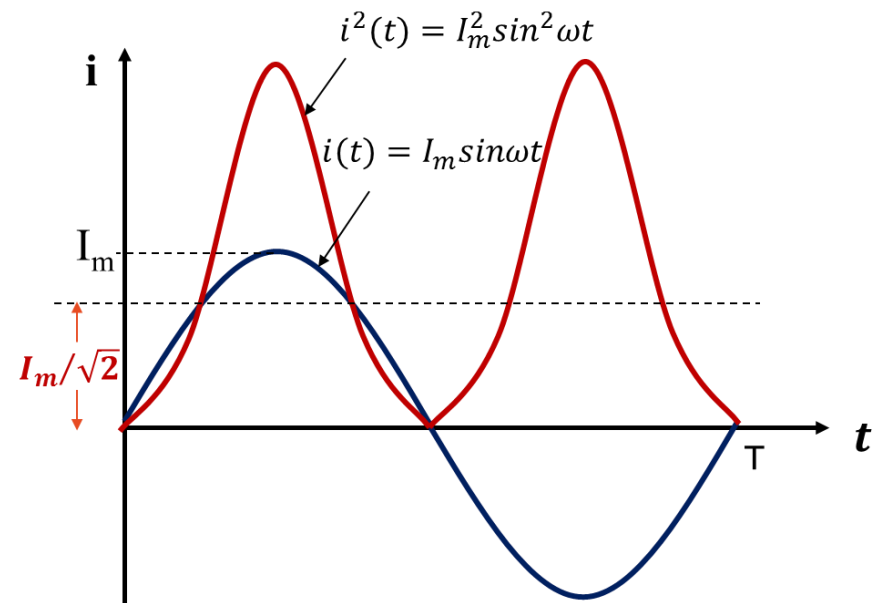

Form Factor & Peak Factor

$$\text{Form Factor} = \frac{\text{RMS Value}}{\text{Average Value}} = \mathbf{1.11} \text{ for sinusoidal}$$

$$\text{Peak Factor} = \frac{\text{Maximum Value}}{\text{RMS Value}} = \mathbf{\sqrt{2}} \text{ for sinusoidal}$$


Exercise I

If an alternating voltage has the equation $v(t) = 141.4 \sin 377t$, calculate


- a. Maximum voltage value
- b. RMS value of the voltage
- c. Frequency
- d. The instantaneous voltage when $t = 3\text{ms}$

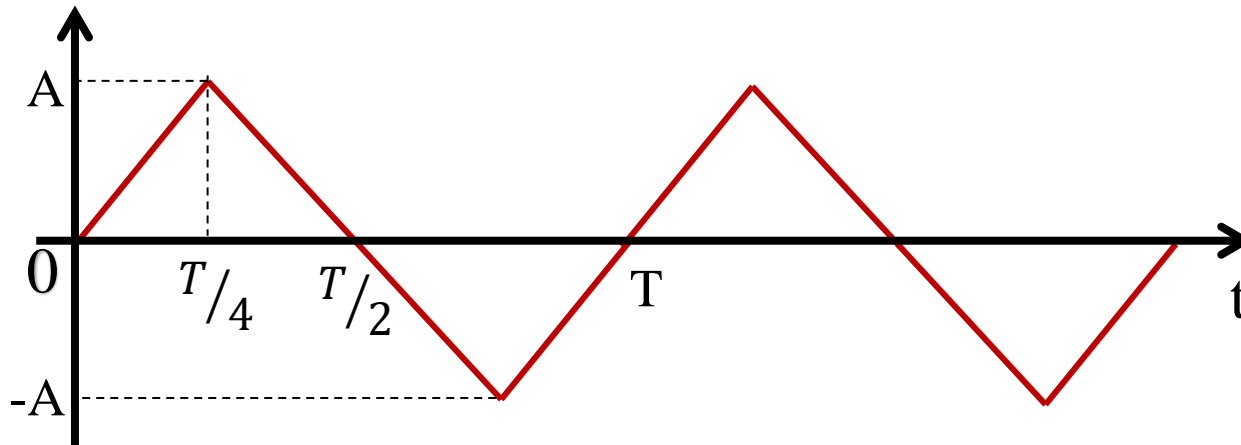Exercise 2

Find the Average value and RMS value of the given non-sinusoidal waveform



Solution:

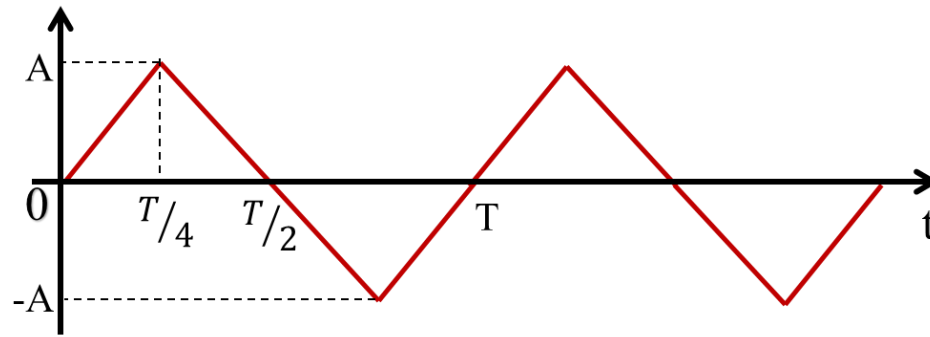

Average Value

$$I_{avg} = \frac{1}{T/4} \int_0^{T/4} f(t) \cdot dt$$

$$I_{avg} = \frac{4}{T} \int_0^{T/4} \frac{4At}{T} \cdot dt$$

$$I_{avg} = \frac{4}{T} \times \frac{4A}{T} \times \left[\frac{t^2}{2} \right]_0^{T/4}$$

$$I_{avg} = \frac{8A}{T^2} \times \left[\frac{T^2}{16} \right]$$

$$I_{avg} = \frac{A}{2}$$

RMS Value

$$I_{rms}^2 = \frac{1}{T/4} \int_0^{T/4} f^2(t) \cdot dt$$

$$I_{rms}^2 = \frac{4}{T} \int_0^{T/4} \frac{16A^2 t^2}{T^2} \cdot dt$$


$$I_{rms}^2 = \frac{4}{T} \times \frac{16A^2}{T^2} \times \left[\frac{t^3}{3} \right]_0^{T/4}$$

$$I_{rms}^2 = \frac{4}{T} \times \frac{16A^2}{T^2} \times \frac{1}{3} \times \left[\frac{T^3}{4^3} \right]$$


$$I_{rms} = \frac{A}{\sqrt{3}}$$

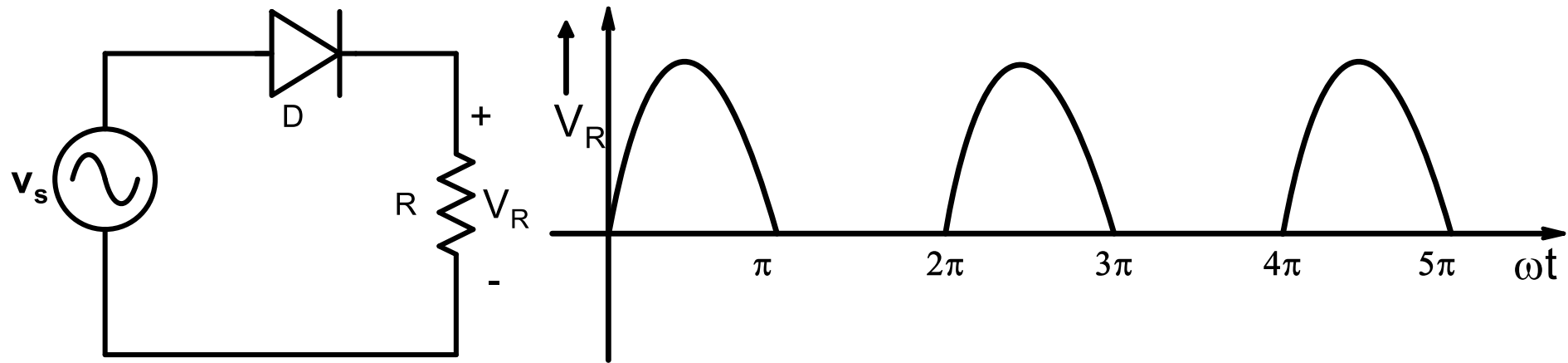Exercise 3

For the circuit shown below, sketch the voltage across the resistance, & then find the Average value and RMS value of the same.



Solution:

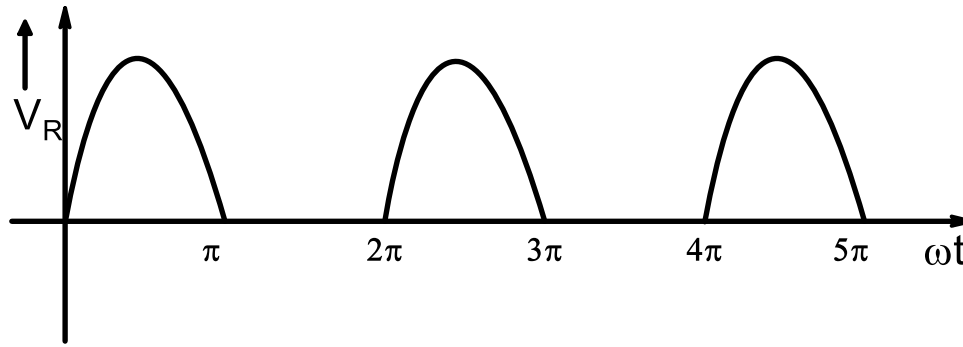

Average Value

$$V_{avg} = \frac{1}{2\pi} \left[\int_0^{\pi} V_m \sin \omega t \cdot d\omega t + \int_{\pi}^{2\pi} 0 \cdot d\omega t \right]$$

$$V_{avg} = \frac{V_m}{2\pi} (-\cos \omega t) \Big|_0^{\pi}$$

$$V_{avg} = \frac{-V_m}{2\pi} (-1 - 1)$$

$$V_{avg} = \frac{V_m}{\pi}$$

RMS Value

$$V_{rms}^2 = \frac{1}{2\pi} \left[\int_0^{\pi} V_m^2 \sin^2 \omega t \cdot d\omega t + \int_{\pi}^{2\pi} 0 \cdot d\omega t \right]$$

$$V_{rms}^2 = \frac{V_m^2}{2\pi} \left[\int_0^{\pi} \frac{1 - \cos 2\omega t}{2} \cdot d\omega t \right]$$

$$V_{rms}^2 = \frac{V_m^2}{4\pi} [\omega t \Big|_0^{\pi} - \sin 2\omega t \Big|_0^{\pi}]$$

$$V_{rms}^2 = \frac{V_m^2}{4\pi} [\pi]$$

$$V_{rms} = \frac{V_m}{2}$$

Representing AC

- Consider three sinusoidal signals $x(t)$, $y(t)$ & $z(t)$ with same frequency


Mathematical Representation

$$x(t) = X_m \sin(\omega t)$$


$$y(t) = Y_m \sin(\omega t - \phi)$$

$$z(t) = Z_m \sin(\omega t + \theta)$$

Graphical Representation

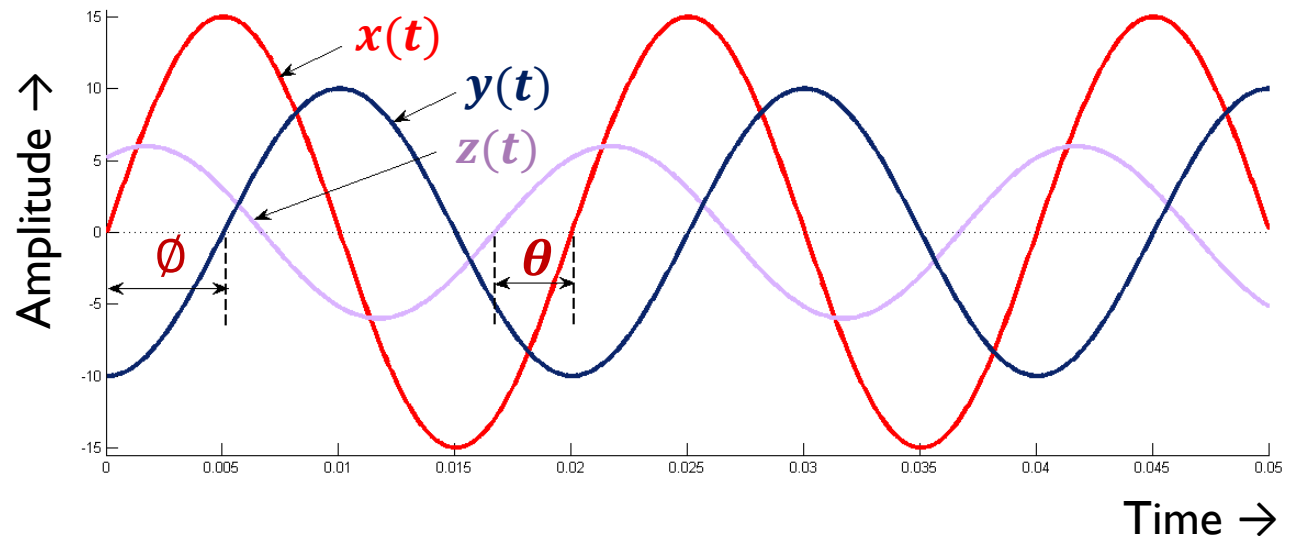


Phasor Representation

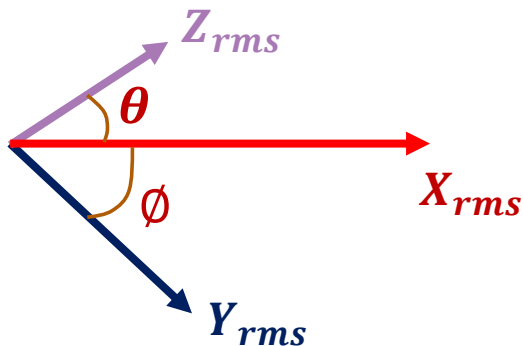

- Representing the relationship between sinusoidal signals with same frequency in graphical or mathematical form is tedious
- Phasor representation is often used


R circuit response with AC supply

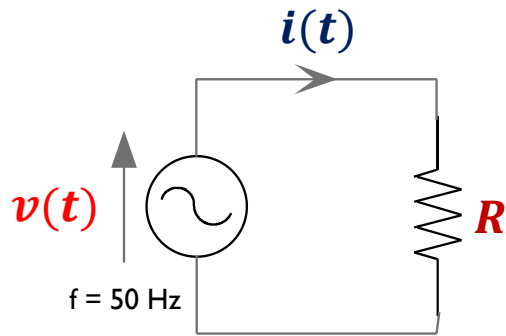

$$i(t) = \frac{v(t)}{R}$$

'Current through the resistor is in phase with the voltage across it'

Graphical Representation

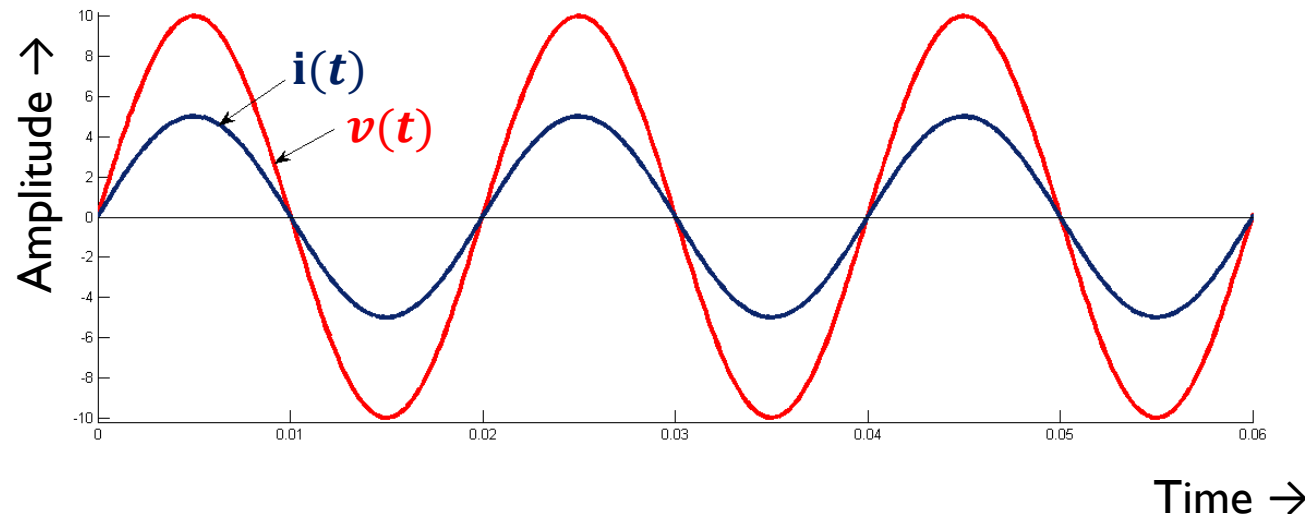

Mathematical Representation


$$v(t) = V_m \sin(\omega t)$$

$$i(t) = I_m \sin(\omega t)$$

Phasor Representation



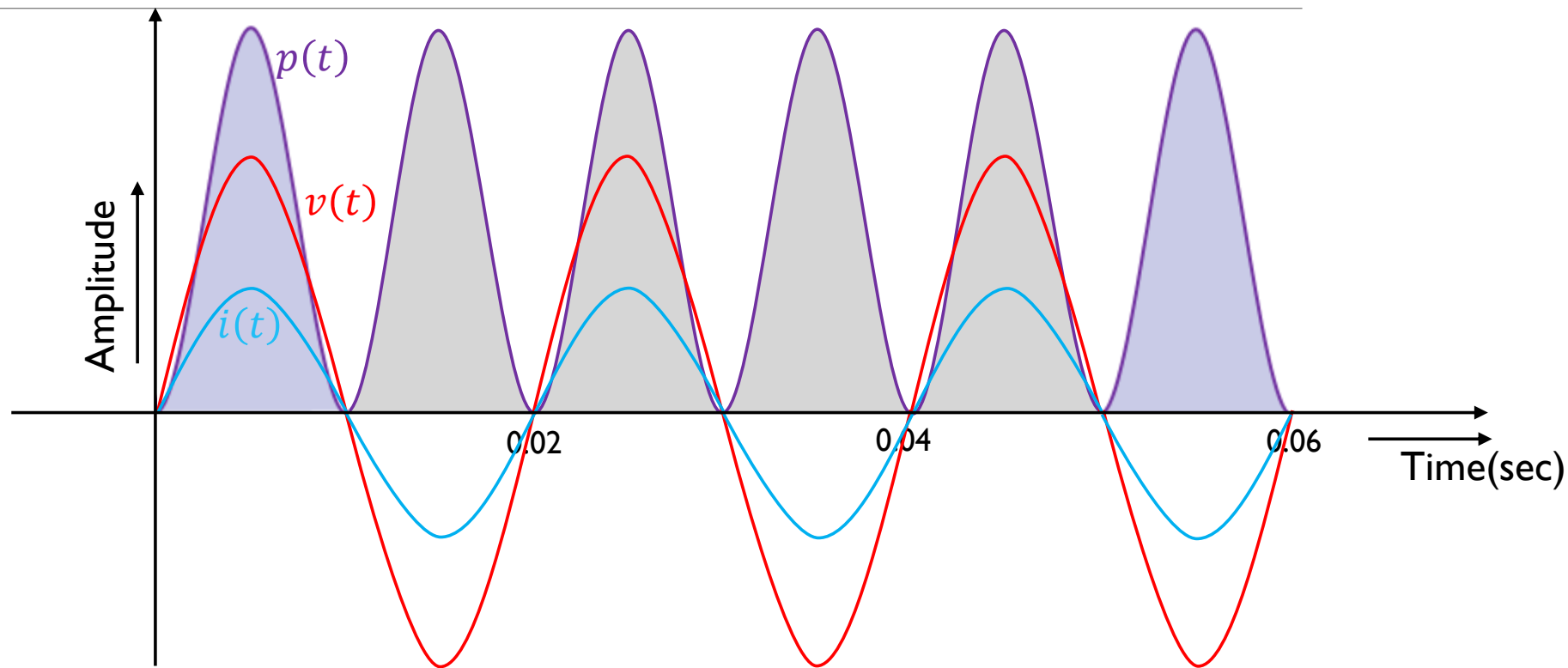Power Associated - Pure Resistive Circuit




Instantaneous power,

$$p(t) = v(t) \cdot i(t) = V_m I_m \sin^2 \omega t$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt$$

$$P_{avg} = \frac{V_m I_m}{2} = V_{rms} I_{rms} = \frac{V_{rms}^2}{R} = I_{rms}^2 R$$

L circuit response with AC supply

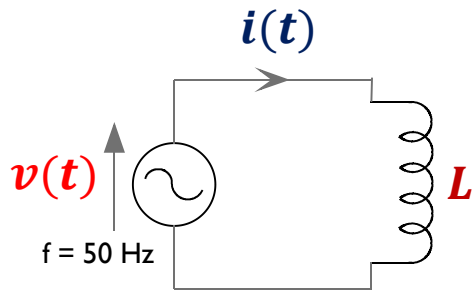

$$i(t) = \frac{1}{L} \int v(t) dt$$


'Current through the inductor lags the voltage across it by 90° '

$$\bar{V} = V \angle 0^\circ \quad \bar{I} = I \angle -90^\circ$$

$$\frac{\bar{V}}{\bar{I}} = \frac{V \angle 0^\circ}{I \angle -90^\circ} = jX_L \quad \text{where } \frac{V}{I} = X_L$$

X_L is called **Inductive Reactance**

Graphical Representation

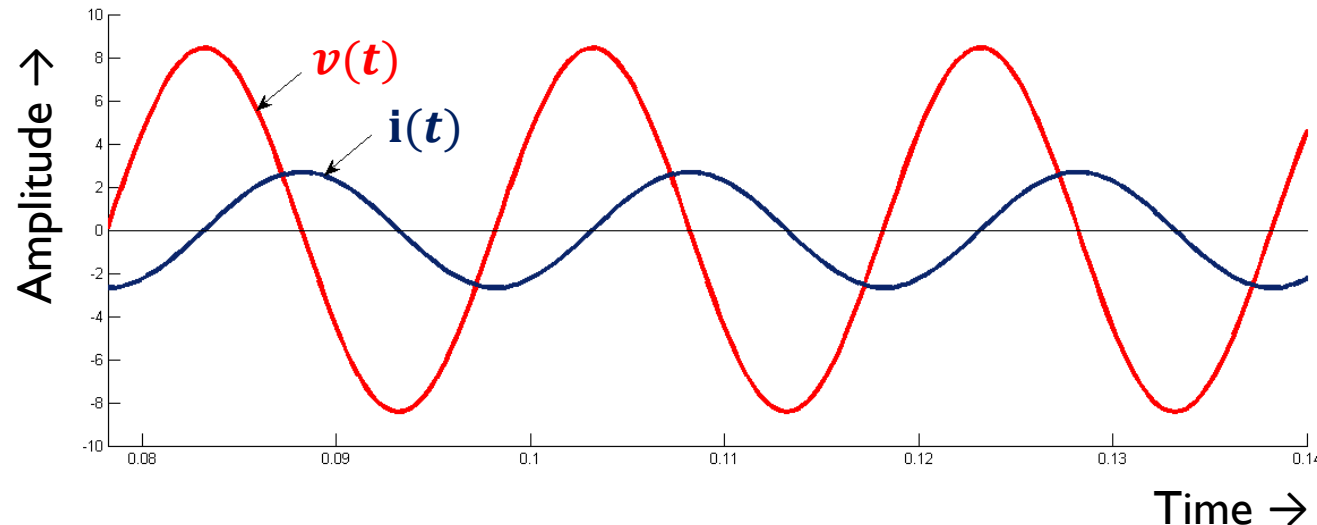

Mathematical Representation


$$v(t) = V_m \sin(\omega t)$$

$$i(t) = I_m \sin(\omega t - 90^\circ)$$

Phasor Representation



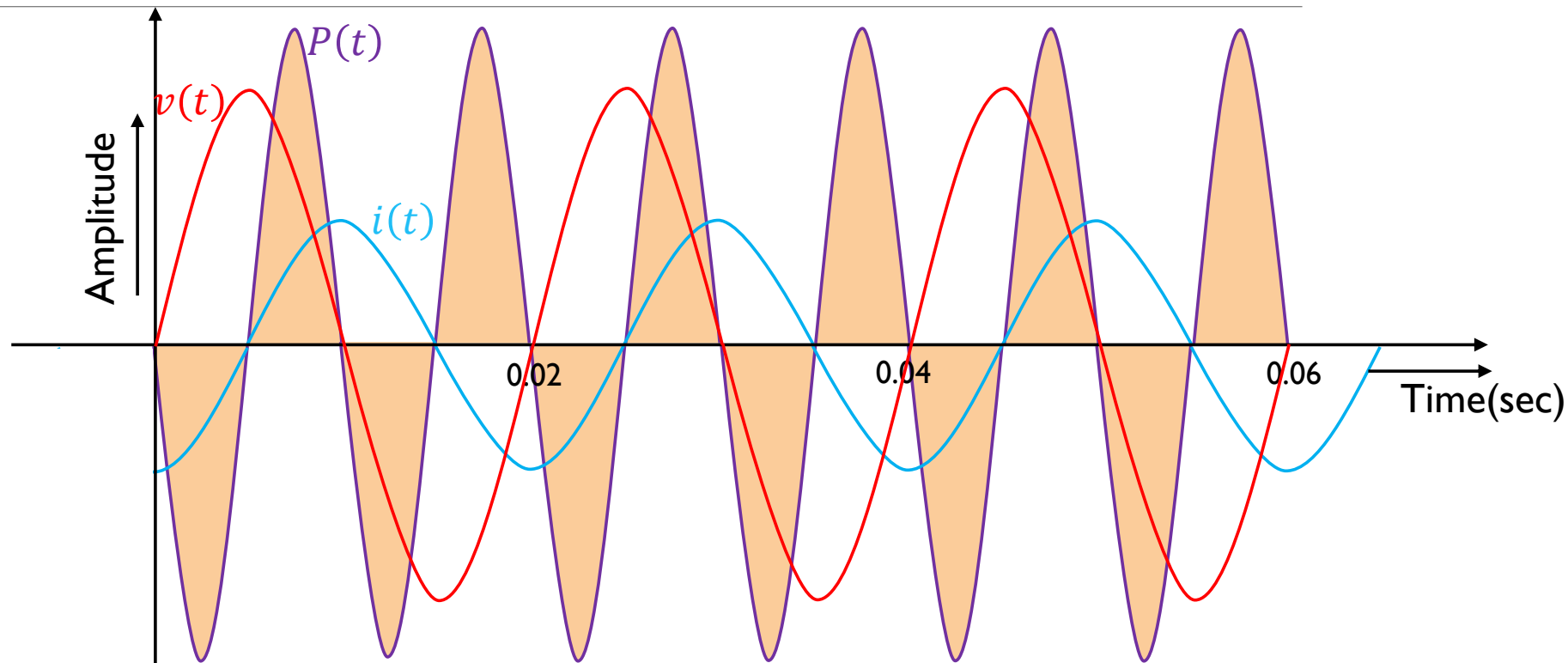Power Associated – Pure Inductive Circuit




Instantaneous power,

$$\begin{aligned} p(t) &= v(t) \cdot i(t) \\ &= V_m I_m \sin \omega t \cdot \sin(\omega t - 90^\circ) \\ &= -\frac{V_m I_m}{2} \sin 2\omega t \end{aligned}$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt$$

$$\boxed{P_{avg} = 0}$$

C circuit response with AC supply

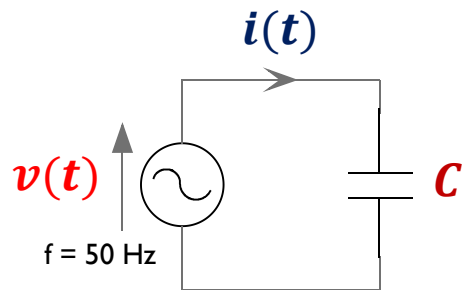

$$i(t) = C \frac{dv(t)}{dt}$$

'Current through the capacitor leads the voltage across it by 90° '


$$\bar{V} = V \angle 0^\circ$$

$$\bar{I} = I \angle 90^\circ$$

$$\frac{\bar{V}}{\bar{I}} = \frac{V \angle 0^\circ}{I \angle 90^\circ} = -jX_C \quad \text{where } \frac{V}{I} = X_C$$

X_C is called **Capacitive Reactance**

Graphical Representation

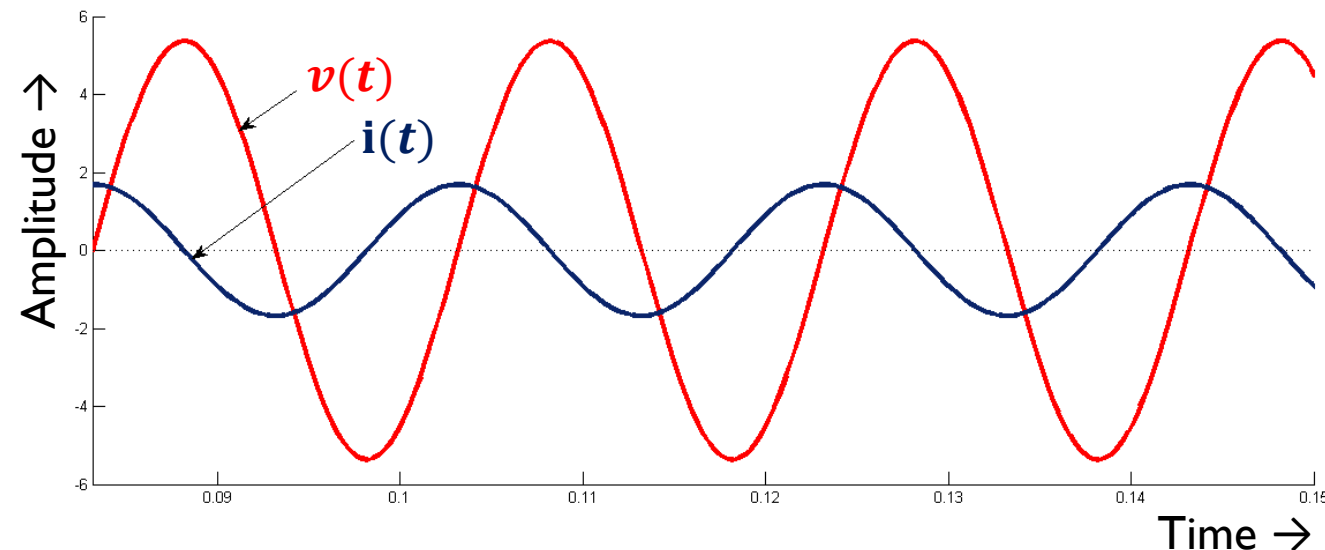

Mathematical Representation


$$v(t) = V_m \sin(\omega t)$$

$$i(t) = I_m \sin(\omega t + 90^\circ)$$

Phasor Representation



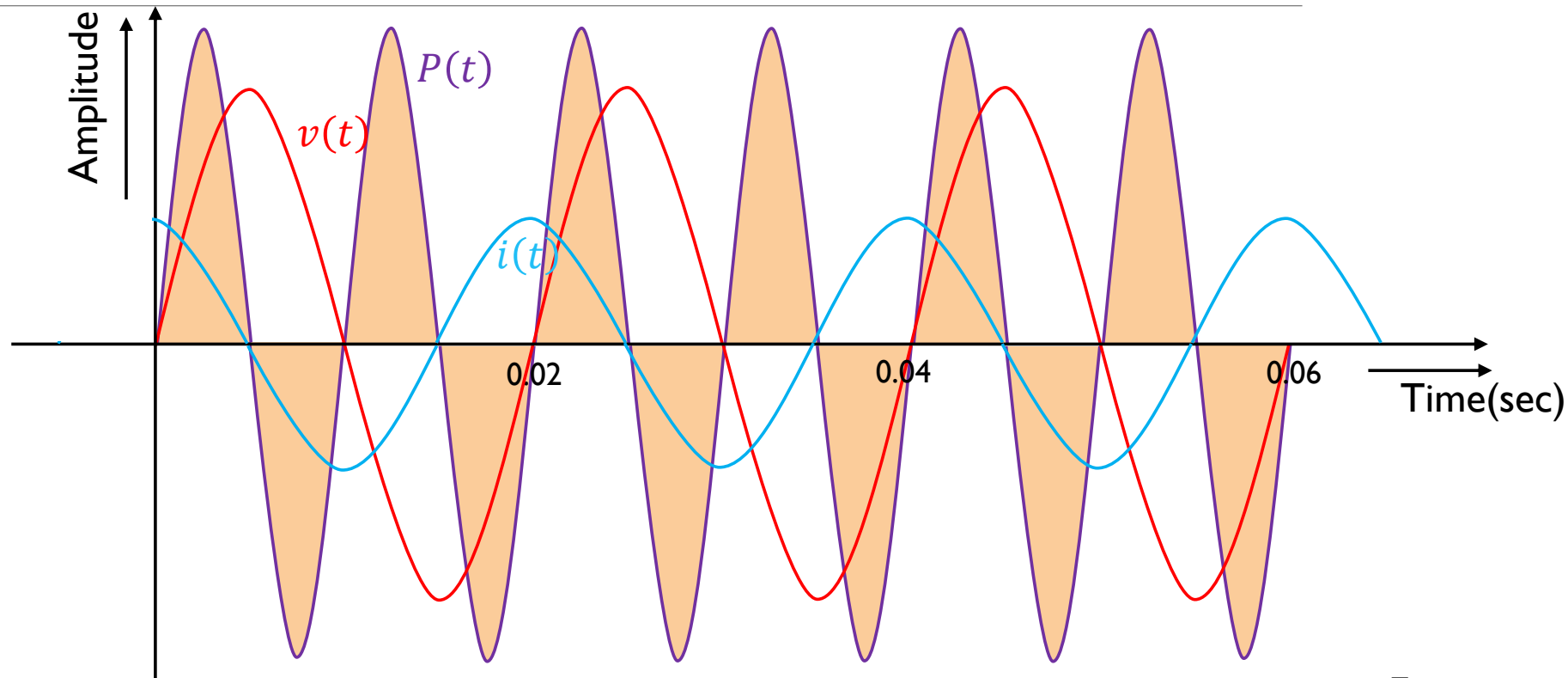Power Associated – Pure capacitive Circuit



Instantaneous power,

$$p(t) = v(t) \cdot i(t)$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t + 90^\circ)$$

$$= \frac{V_m I_m}{2} \sin 2\omega t$$

$$\text{Average Power, } P = \frac{1}{T} \int_0^T p(t) dt$$

$$\boxed{P_{avg} = 0}$$


Practice Quiz Questions

Link:

https://forms.microsoft.com/Pages/ResponsePage.aspx?id=Qr2-Kf_xPUyWiAZ-NGDcHxdWYFLgt7pFmZiZBmJljiIUMDA0OU84WIVHRTINVINHOOVVPOUI3ODBITyQIQCN0PWcu

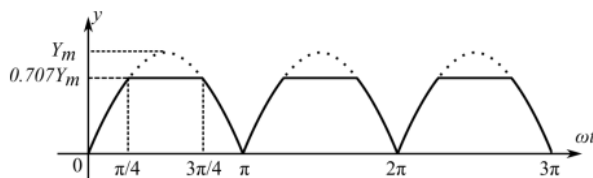
Q1

Find the average and RMS value of the waveform



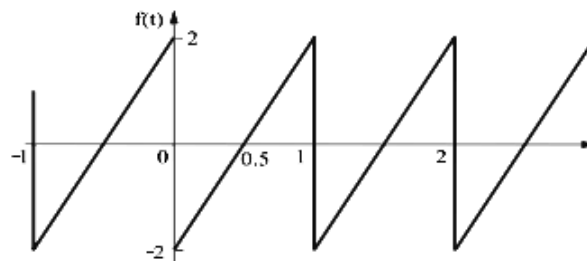
Q2

Find the average and RMS value of the waveform



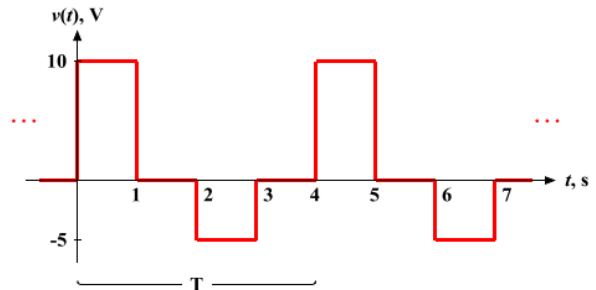Q3

Find the average and RMS value of the waveform



Deadline: 17 December 2020, 9AM