



$$h_{12} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

$$I_3 = 2I_2 \Rightarrow 2(2I_2) = 4I_2$$

$$\therefore I_3 = 4I_2 \quad \text{--- (3)}$$

$$V_1 = 4I_2 \Rightarrow V_1 = -V_2$$

$$V_2 = -4I_2$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0} = -1 = h_{12}$$

$$\begin{bmatrix} -2 \\ -1.5 \end{bmatrix} \begin{bmatrix} -1 \\ -1/4 \end{bmatrix} \quad \text{--- (14)}$$

$$\Rightarrow \frac{I_2}{V_2} = -\frac{1}{4} V = h_{22}$$

$$\text{--- (14)}$$

$$V_1 = 10(I_1 - I_3) + 5I_1$$

$$V_1 = 15I_1 - 10I_3 \quad \text{--- (1)}$$

$$V_2 = 5I_1 + 10I_3 \quad \text{--- (2)}$$

$$I_3 = I_1 \cdot \frac{10}{(10+20+10)} = I_1/4$$

$$V_2 = 5I_1 + 10(I_1/4)$$

$$V_2 = 7.5I_1$$


$$\left. \frac{V_2}{I_1} \right|_{I_2=0} = 7.5$$

4 Find V_1

5 Determine

Using N


Return

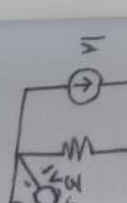

6 Find V_1

Using N


Return

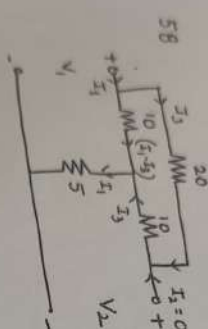

Solving (1) and (2)

$$V_1 = 15I_1 - 10(I_1/4) = 12.5I_1$$

$$\left. \frac{V_1}{I_1} \right|_{I_2=0} = 12.5 \Omega$$

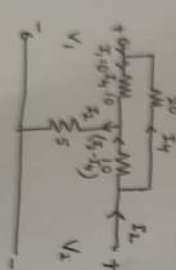

$$V_1 = 10(I_1/4) + 5I_2$$

$$V_1 = 7.5I_2$$

$$\left. \frac{V_1}{I_2} \right|_{I_1=0} = 7.5 \Omega$$

$$V_1 = 10I_4 + 5I_2 \quad \text{--- (1)}$$

$$V_2 = 10(I_2 - I_4) + 5I_2$$

$$V_2 = 15I_2 - 10I_4 \quad \text{--- (2)}$$

$$I_4 = I_2 \cdot \frac{10}{40} = (I_2/4) \quad \text{--- (3)}$$

$$V_2 = 15I_2 - 10(I_2/4)$$

$$V_2 = 12.5I_2$$

$$\left. \frac{V_2}{I_2} \right|_{I_1=0} = 12.5 \Omega$$

$$Z = \begin{bmatrix} 12.5 & 7.5 \\ 7.5 & 12.5 \end{bmatrix}$$

$$\Delta Z = 100 \quad Y = [Z]^{-1}$$

$Y_{11} = 0.0125 \text{ } \Omega$	$Y_{22} = 0.0125 \text{ } \Omega$
$Y_{12} = -0.0075 \text{ } \Omega$	$Y_{21} = -0.0075 \text{ } \Omega$


$$\textcircled{D} \times 4 = 4H$$

(2M)

$$\frac{5}{3} x(t-3)$$


$$2x(t-4)$$
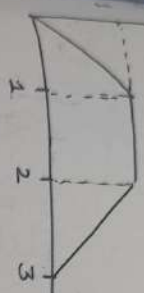
$$x(t) = x(t) - x(t-1) - x(t-2) + x(t-3)$$



(1M)

$$y(t) = 2x(t) - 4u(t-2) + 2u(t-4)$$

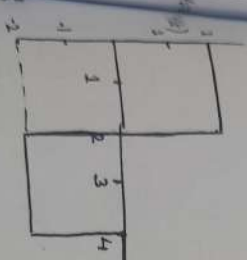

(1M)

$$= \frac{5}{7}$$

$$= \frac{1.5}{s+1} - \frac{2.5}{s+1} [(s+1)-1] \cdot \frac{e^{-2s}}{s}$$

$$= \frac{1.5}{s+1} - 2.5 \left[1 - \frac{1}{s+1} \right] \cdot \left(\frac{e^{-2s}}{s} \right)$$

$$= \frac{1.5}{s+1} - 2.5 \frac{e^{-2s}}{s} + \frac{2.5}{s+1} \cdot \frac{e^{-2s}}{s}$$


$$h(s) = \frac{1.5}{s+1} - 2.5 \frac{e^{-2s}}{s} + \frac{2.5}{s+1} \cdot \frac{e^{-2s}}{s}$$

$$v(t) = 1.5e^{-t} - 2.5u(t-2) + 2.5e^{-t}u(t-2) \quad (24)$$

$$v(t) = 5u(t) - \frac{5}{3}\delta(t) + \frac{5}{3}h_1$$

$$-2\lambda(t-3) + 2\lambda(t-4)$$

$$(24)$$

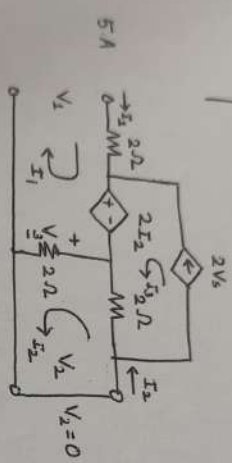

$$V_1 = h_{11}I_1 + h_{12}V_2$$

$$I_2 = h_{21}I_1 + h_{22}V_2$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$I_3 = 2V_3$$

$$= 2[2(I_1 + I_2)]$$

$$I_3 = 4I_1 + 4I_2 \quad (25)$$

$$4I_1 + 2I_2 = V_1 - 2I_2$$

$$4I_1 + 4I_2 = V_1 \quad (1)$$

$$4I_2 + 2I_1 - 2I_3 = 0$$

$$4I_2 + 2I_1 - 2[4I_1 + 4I_2] = 0$$

$$4I_2 - 8I_2 + 2I_1 - 8I_1 = 0$$

$$-4I_2 - 6I_1 = 0 \Rightarrow \frac{I_2}{I_1} = \frac{6}{-4}$$

$$\frac{I_2}{I_1} = \frac{6}{-4} = \boxed{-1.5 = h_{21}}$$

$$4I_1 + 4(-1.5I_1) = V_1$$

$$4I_1 - 6I_1 = V_1$$

$$-2I_1 = V_1$$

$$\Rightarrow \frac{V_1}{I_1} = -2 = \boxed{h_{11}}$$

$$I = 9V$$

$$I = \frac{V_1}{Z}$$

$$\frac{1}{Z} = \frac{1}{R_1 + j\omega L_1}$$

$$\frac{1}{Z} = \frac{1}{R_1 + j\omega L_1}$$


$$Y_1 = \left(\frac{1}{10 + j5} \right) \times \frac{10 + j5}{10 + j5} = \frac{10 + j5}{135} + \frac{10}{j5} \left(\frac{5}{135} \right)$$

$$Y_2 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{(R_1 + j\omega L_1)(R_1 - j\omega L_1)} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$

$$Y = Y_1 + Y_2 = \frac{10}{135} + \frac{R_1}{R_1^2 + 100} + j \left[\frac{5}{135} - \frac{10}{R_1^2 + 100} \right]$$

for Resonance Susceptance = 0
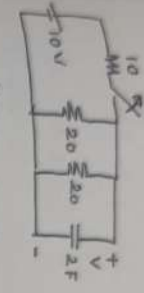
$$\frac{5}{135} = \frac{10}{R_1^2 + 100} \Rightarrow R_1 = 12.247 \Omega$$



At $t = 0^-$

$$V_C(0^-) = \frac{10}{1+10} \times 10 = 5V$$

$$V_C(0^+) = V = 5V$$


At $t = \infty$ (when switch open)

$$V_m = 0$$

$$V_C(t) = V_m - [V_m - V_0] e^{-t/\tau}$$

$$= 0 - [0 - 5] e^{-t/10\mu s}$$

$$V(t) = 5 e^{-0.05t}$$

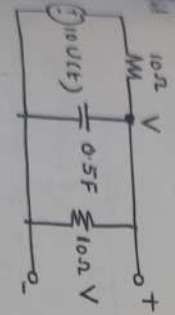

diffy eqn (A)

$$0 = C \frac{d^2 V}{dt^2} + \frac{2}{10} \frac{dV}{dt}$$

$$= 0.5 \frac{d^2 V(t)}{dt^2} = -\frac{2}{10} \frac{dV(t)}{dt} \Rightarrow \frac{d^2 V(t)}{dt^2} = -0.8 \frac{dV(t)}{dt}$$

At $t = 0^-$ $V_C(0^-) = 0 = V_C(0^+) = V(0^+)$

$$\therefore V(0^+) = 0$$


At $t = 0^+$

$$1 = C \frac{dV}{dt} + \frac{2}{10} V$$

$$1 = 0.5 \frac{dV(t)}{dt} + \frac{V(t)}{10}$$

$$\Rightarrow \frac{dV(t)}{dt} = 2V/sec$$


The transformed network

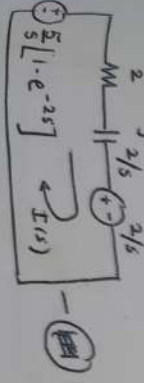


$$I(s) = \frac{5}{s} \left[\frac{1 - e^{-2s}}{2} - \frac{2}{s} \right] = \frac{3}{s} - \frac{5}{s} e^{-2s}$$

$$= \frac{3 - 5e^{-2s}}{2(s+1)} = \left(\frac{1.5}{s+1} \right) - \left(\frac{2.5}{s+1} \right) e^{-2s}$$

2B.

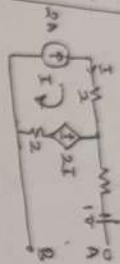


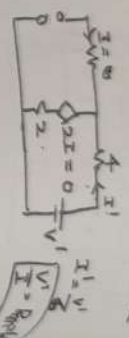Ckt $\Rightarrow I = 2A$
 $V_{oc} = V_{AB} = 8I + 2I + 1 = 9V$




$V_{oc} = 9V, R_{th} = 6\Omega$


2C.

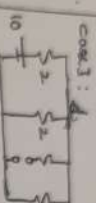

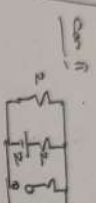Cosk I:
 $10 \parallel 2 \Rightarrow 10 \parallel 2 = 1.82$
 $I = \frac{10}{3}$
 $I_{10\Omega} = \frac{10}{3} \times \frac{2}{2+2} = \frac{10}{6}$



$I_{2V} = \frac{1}{3}A$

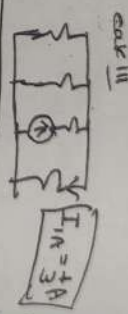


$I_{1A} = \frac{1}{3}A$

$I_{10\Omega} = \frac{10}{3} + \frac{1}{3} + \frac{1}{3} = 2.32A$


3A

$t < 0$

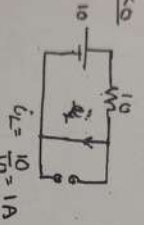

$i_L = \frac{10}{10} = 1A$

$t = 0^+$

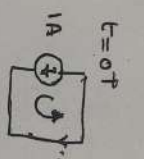

$i_L(0^+) = i_L(0^-) = 1A$
 $v_L(0^+) = v_L(0^-) = 0V$
 $i_L(t)|_{0^+} = -1A$

$t > 0$



$\frac{d^2 i}{dt^2} + \frac{1}{L} \int i dt = 0$
 $\frac{d^2 i}{dt^2} + 2i = 0$

$S^2 + 2 = 0$

$S = \pm j\sqrt{2}$

$i(t) = A \cos 2t + B \sin 2t$

$i(0) = -1, \therefore A = -1$

$\frac{di}{dt} = 0, \therefore -2A \sin 2t + 2B \cos 2t = 0$


$\Rightarrow B = 0$

$i(t) = -\cos 2t$


$t > 0$

3B

$Y = Y_1 + Y_2$
 For R & C

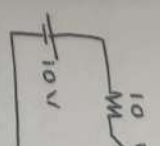

At $t = \infty$






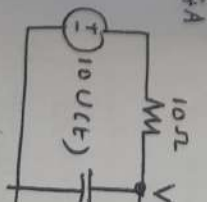


4B

Diffy equation
 $0 = C \cdot \frac{d^2}{dt^2}$
 $= 0.5 \cdot \frac{d^2}{dt^2}$

The trans f



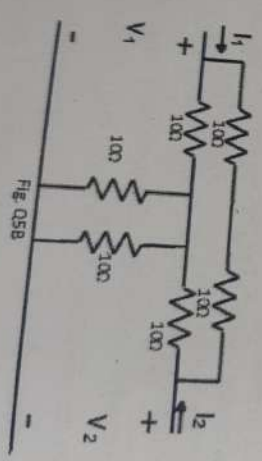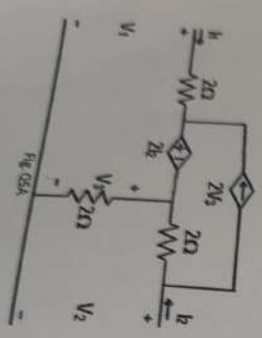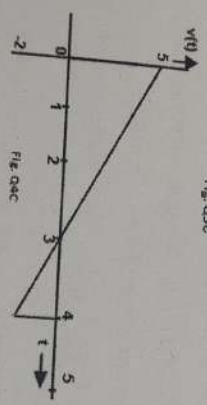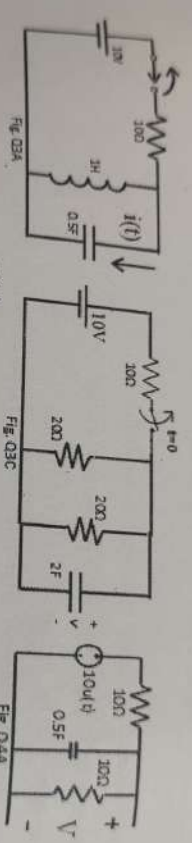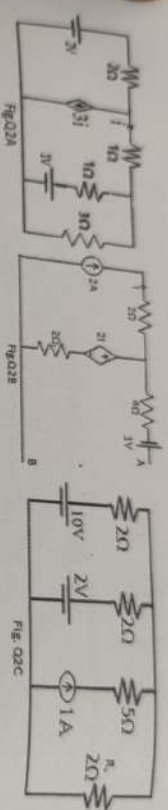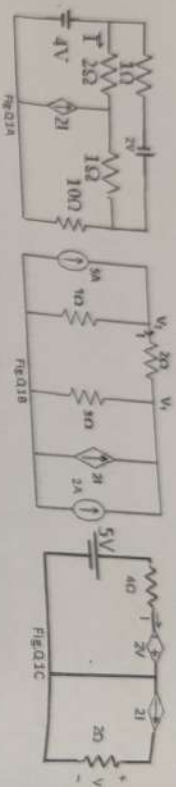

Reg. No.

--	--	--	--	--	--	--	--	--	--

Instructions to Candidates:

- ❖ Answer ALL the questions.
- ❖ Missing data may be suitable assumed.

- 1A. Find the mesh currents in the circuit shown in Fig.Q1A. 5
- 1B. Obtain node voltages V_1 and V_2 for the circuit shown in Fig.Q1B 3
- 1C. Determine V in the circuit shown in Fig.Q1C. 2
- 2A. Using Norton's theorem determine current in 3Ω resistor of Fig.Q2A. 5
- 2B. Obtain Thevenin's equivalent for the circuit shown in Fig.Q2B with respect to AB. 3
- 2C. Using superposition theorem determine the current in R_L . 2
- 3A. In the network shown Fig. Q3A, the switch is opened at $t=0$, a steady state having previously been attained. Obtain expression for current in complementary and particular solution form. 5
- 3B. An impedance of $(10-j5)\Omega$ is connected in parallel with a coil with inductive reactance $j10\Omega$ and variable coil resistance of R_L . Find the value of R_L for which the circuit is in resonant. 3
- 3C. For the circuit shown in Fig.Q3C find V , if switch is opened at $t=0$ assuming that a steady state having previously been attained. 2
- 4A. For the network shown in Fig. Q4A, find V , dV/dt & d^2V/dt^2 at $t=0^+$. 5
- 4B. Obtain expression for current in the circuit shown in Fig.Q4B. 3
- 4C. Express the waveform shown in Fig. Q4C using basic signals. 2
- 5A. For the circuit shown in Fig.Q5A, find h parameters 4
- 5B. For the network shown in Fig.Q5B find Y parameters. 4
- 5C. Sketch the signals (i) $x(t) = r(t) - r(t-1) - r(t-2) + r(t-3)$ 2
(ii) $y(t) = 2u(t) - 4u(t-2) + 2u(t-4)$