



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)





Basic Electrical Technology

Circuit Elements

What is an Electric Circuit?

Definition:

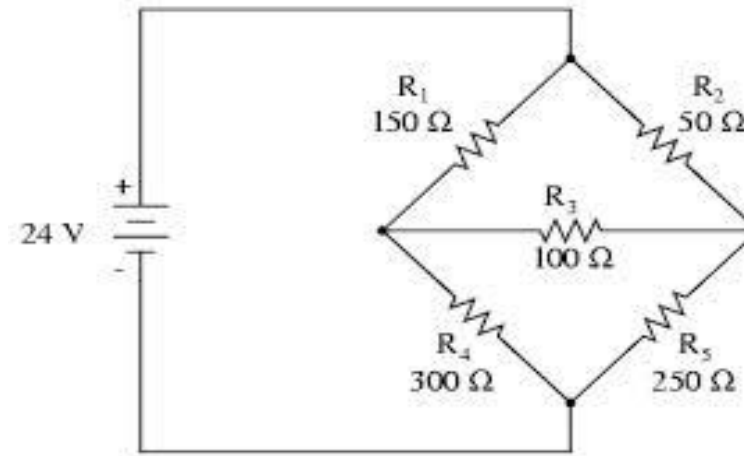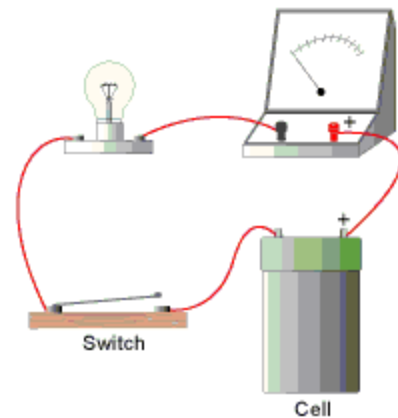“An interconnection of simple electrical devices with at least one closed path in which current may flow”



Circuit Elements



Active & Passive

- Active Elements: *Voltage & Current Sources*
- Passive Elements: *Resistor, Inductor, Capacitor*

Linear & Non-linear Elements



- Linear: *Resistor, Inductor, Capacitor*
- Nonlinear: *Diode, LDR (Light Dependent Resistor), Thermistor, transistor*

Unilateral & Bilateral Elements

- Unilateral (Current Flow in one direction): *Diode, Transistor*
- Bilateral: *Resistor, Inductor, Capacitor**

Lumped & Distributed

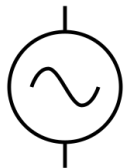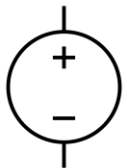- Lumped elements are simplified version of distributed elements
- Discuss only **lumped linear bilateral** circuit elements





Active Elements - Sources

Voltage Source:

➤ Ideal:

- Maintains constant voltage irrespective of connected load
- Internal resistance $R_s = 0$



Ideal Voltage Source (DC)

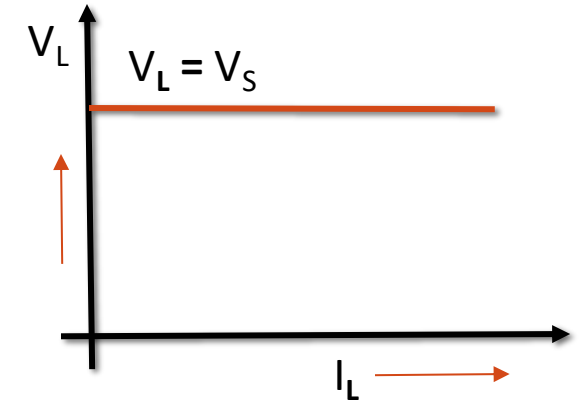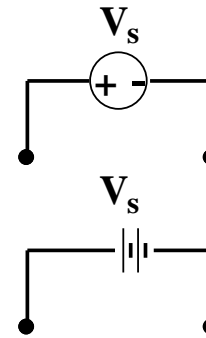

➤ Practical:

- Terminal voltage changes based on the connected load
- Internal resistance $R_s \neq 0$

Practical Voltage Source

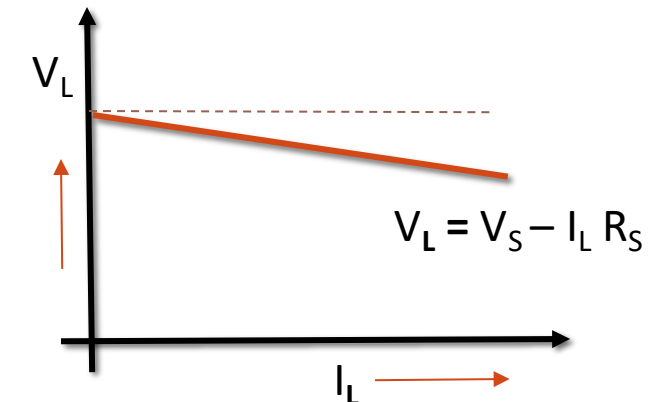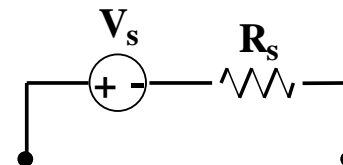



Active Elements - Sources

Current Source:

➤ Ideal:

- Maintains constant current irrespective of the load connected
- Internal resistance $R_s = \infty$



Ideal Current Source (DC)

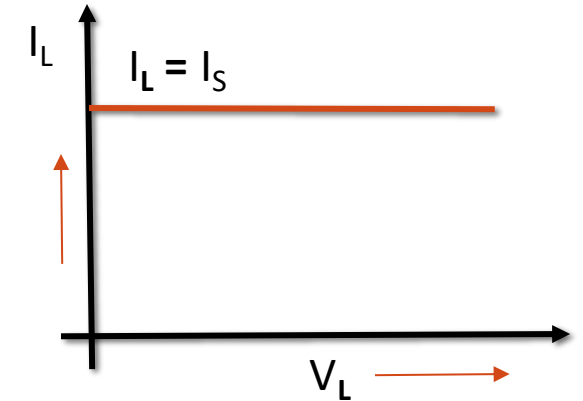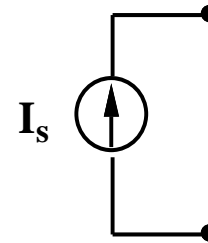

➤ Practical:

- Output current changes based on the connected load
- Internal resistance $R_s < \infty$

Practical Current Source

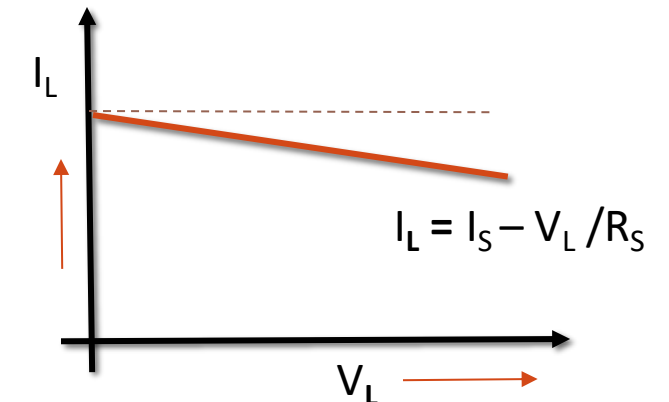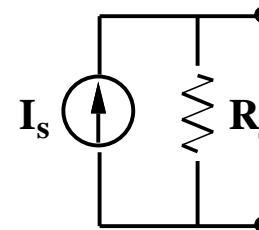

Resistor

Energy Consuming Element

Resistor

➤ **Passive electric device** that **dissipates energy**

➤ **Resistance:** property which opposes flow of current

- Symbol: R
- Unit: Ohms (Ω)
- Power Consumed = $I^2 R$

➤ **Conductance**

- Reciprocal of resistance
- Symbol: G
- Unit – Siemens (S)




Resistors in Series

Current (I) is same

$$V = V_1 + V_2 + V_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

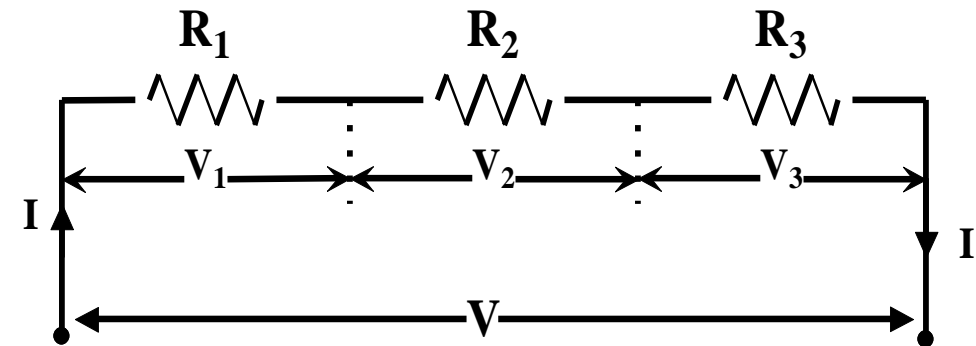


Resistors in Parallel

Voltage (V) is same

$$I = I_1 + I_2 + I_3$$
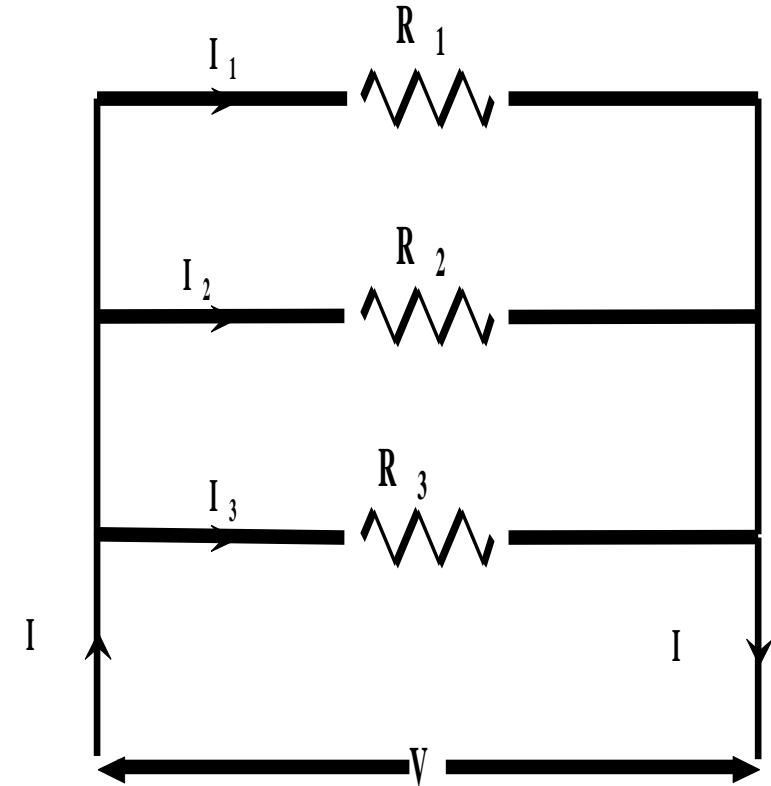
$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$




Delivering and Absorbing Power by a Source

Power is absorbed or dissipated by a circuit element if

- Current flows from the +ve terminal to -ve terminal.
- In a battery, it is said to be charging.
- In a resistance, it is absorbing/dissipating power.

In the circuit shown,

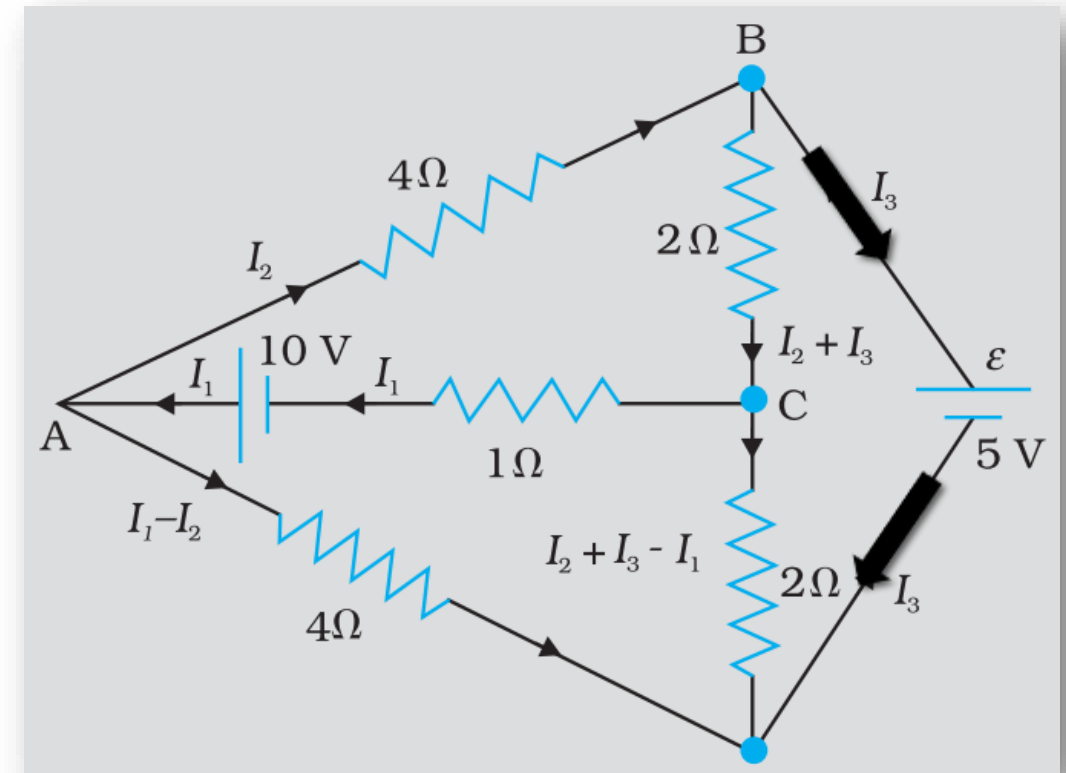- Current I_3 , is flowing from the +ve plate of the 5 V battery to the -ve plate. Therefore, **charging**
- Current I_1 , is flowing from the -ve terminal to +ve terminal of 10 V. Therefore, generating power.





Inductor

Energy Storing Element

Inductor

- **Passive** electric device that **stores energy in its magnetic field** when current flows through it
- A coil of wire wound on a core
 - Eg.: Air core Inductor, iron core inductor
- **Inductance**: property which opposes rate of change of current
 - Symbol: L
 - Unit: Henry (H)
- The voltage across inductor is proportional to the rate of change of current through it

$$v_L = L \frac{di}{dt}$$



Inductive Circuit

For a coil uniformly wound on a **non-magnetic core** of uniform cross section, self-inductance is given by

$$L = \frac{\mu_0 AN^2}{l}$$

Where,

l = length of the magnetic circuit in meters

A = cross sectional area in square meters


μ_o = Permeability of air = $4\pi \times 10^{-7}$

N = *No. of turns in the coil*

Equivalent Inductance


Inductors in series

$$L_{eq} = L_1 + L_2 + \dots + L_n$$

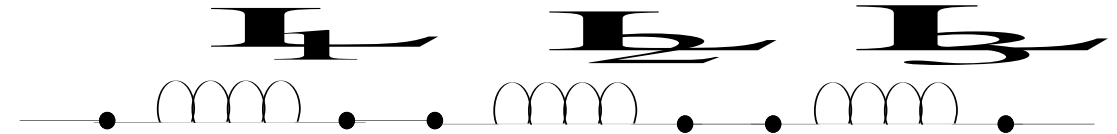

Inductors in Parallel
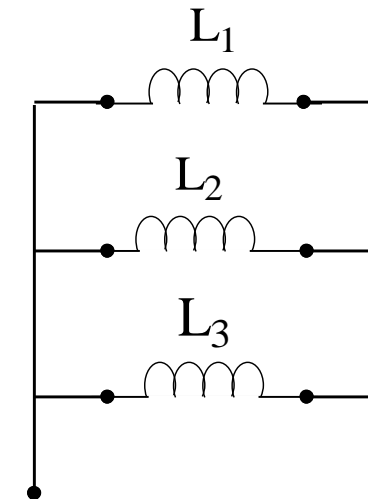
$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \dots + \frac{1}{L_n}$$



Energy Stored in an Inductor

➤ Instantaneous power,

$$p = v_L \cdot i = L i \frac{di}{dt}$$

➤ Energy absorbed in ' dt ' time is

$$dw = L i di$$

➤ Energy absorbed by the magnetic field when current increases from **0** to **I** amperes, is

$$W = \int_0^I L i di = \frac{1}{2} L I^2$$

Capacitor

Energy Storing Element

Capacitors

➤ **Passive electric device** that **stores energy in the electric field** between a pair of closely spaced conductors

➤ **Capacitance:** Property which opposes the rate of change of voltage

○ Symbol: **C**


○ Unit: Farad (F)

➤ The capacitive current is proportional to the rate of change of voltage across it

$$i_c = C \frac{dv_c}{dt}$$

➤ Charge stored in a capacitor whose plates are maintained at constant voltage:

$$Q = CV$$

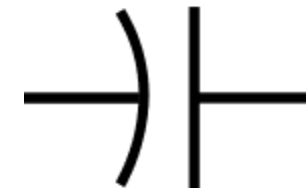

Terminologies

- Electric field strength,

$$E = \frac{V}{d} \text{ volts/m}$$

- Electric flux density,

$$D = \frac{Q}{A} \text{ C/m}^2$$


- Permittivity of free space,

$$\epsilon_0 = 8.854 \times 10^{-12} \text{ F/m}$$

- Relative permittivity, ϵ_r

- Capacitance of parallel plate capacitor

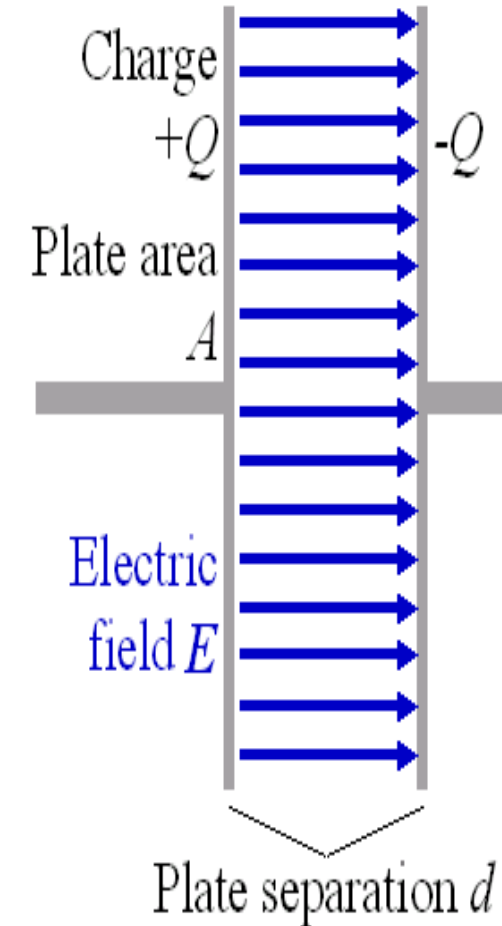
$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$



Equivalent Capacitance


Capacitors in Series
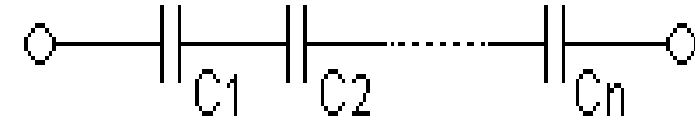
$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots + \frac{1}{C_n}$$



Capacitors in Parallel

$$C_{eq} = C_1 + C_2 + \dots + C_n$$

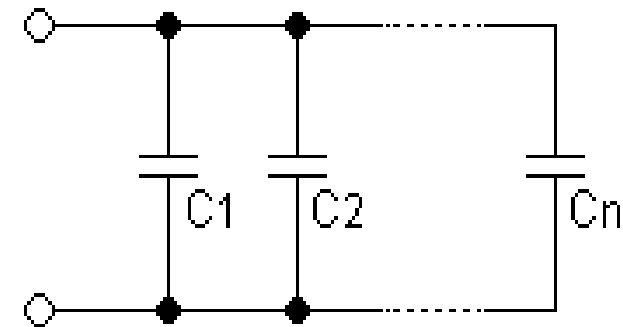

Energy stored in a Capacitor

➤ Instantaneous power

$$p = v_c \times i = C v_c \frac{dv_c}{dt}$$

➤ Energy supplied during ' dt ' time is:

$$dw = C v_c dv_c$$

➤ Energy stored in the electric field when potential rises from **0** to **V** volts is,

$$W = \int_0^V C v_c dv_c = \frac{1}{2} CV^2 \text{ Joules}$$



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

(A constituent institution of MAHE, Manipal)




Quiz Time

Quick Quiz 1

1. An inductor and a resistor opposes _____ & _____ respectively

- A) flow of current, rate of change of current
- B) rate of change of current, flow of current
- C) rate of change of current, rate of change of current
- D) flow of current, flow of current

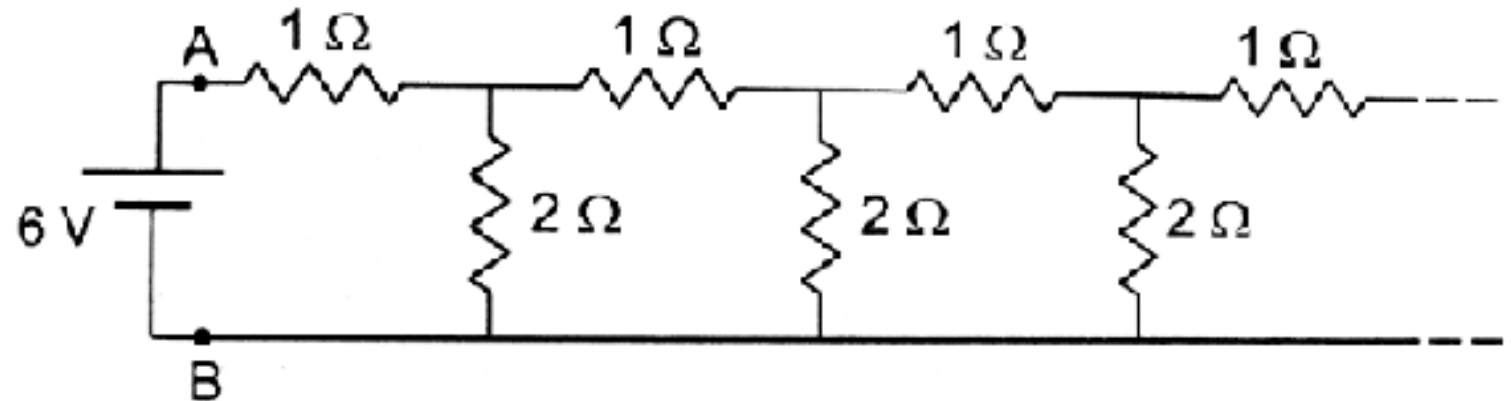
2. What is the equivalent resistance across the terminals A & B in the network shown?



Quick Quiz 1

3.

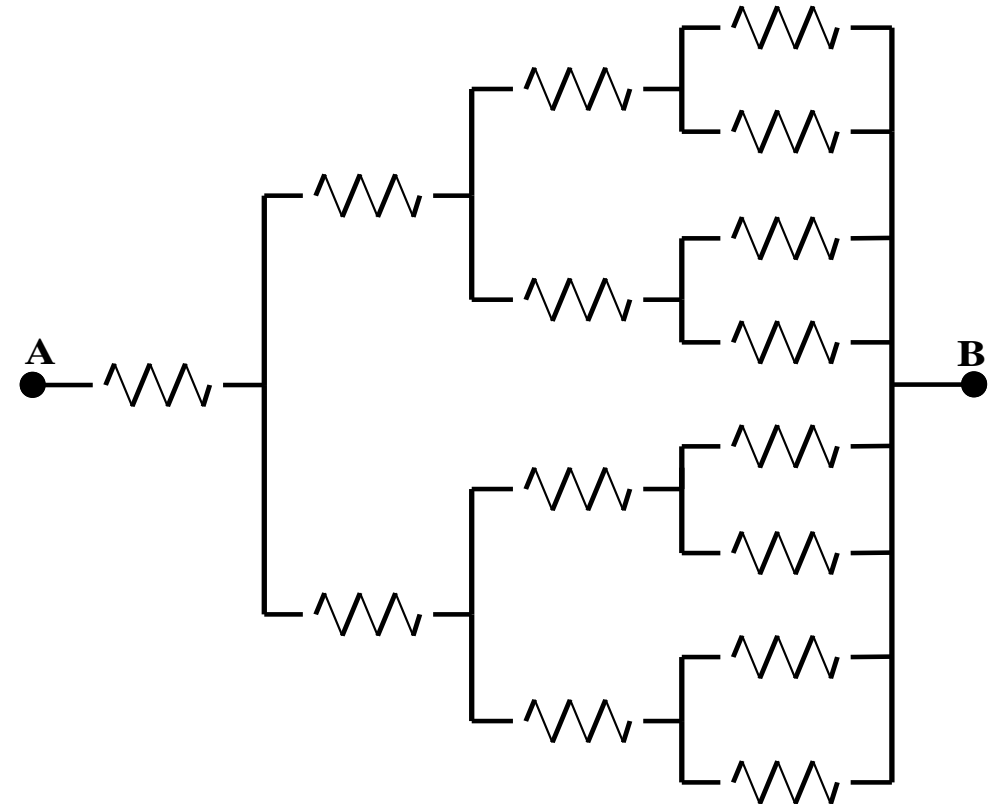- a) 15 resistors are connected as shown in the diagram. Each of the resistors has resistance $1\ \Omega$. Find the equivalent resistance of the network between A & B.
- b) What will be the equivalent resistance of this network if the resistors arranged in the sequence extends to infinity?



Quick Quiz 1

4. Two incandescent bulbs have the following ratings:

Bulb-1: 120 V, 60 W;

Bulb-2: 240 V, 480 W

Both are connected in series with a voltage source.

- i. Which bulb will glow brighter and why?
- ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?

Assume that the incandescent bulbs are purely resistive.

Quick Quiz 1

5. Two incandescent bulbs have the following ratings:

Bulb-1: 120 V, 60 W;

Bulb-2: 240 V, 480 W

Now both are connected in parallel with a voltage source.


- i. Which bulb will glow brighter and why?
- ii. What is the maximum voltage that can be applied so that none of the bulbs fuse?

Assume that the incandescent bulbs are purely resistive.

Quick Quiz 1


6. The source voltage is ____

- A) 10 V
- B) 20 V
- C) 30 V
- D) 40 V

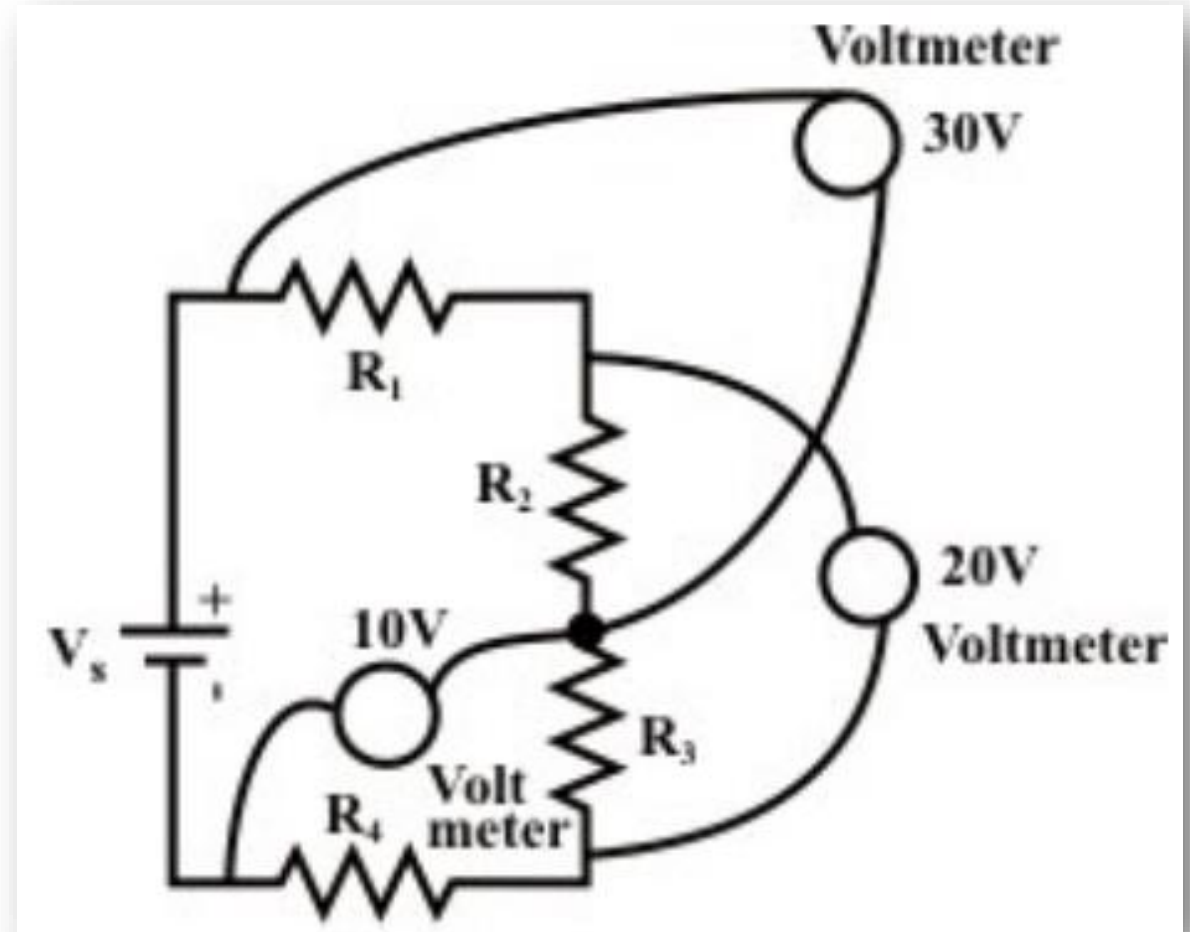

Homework 1

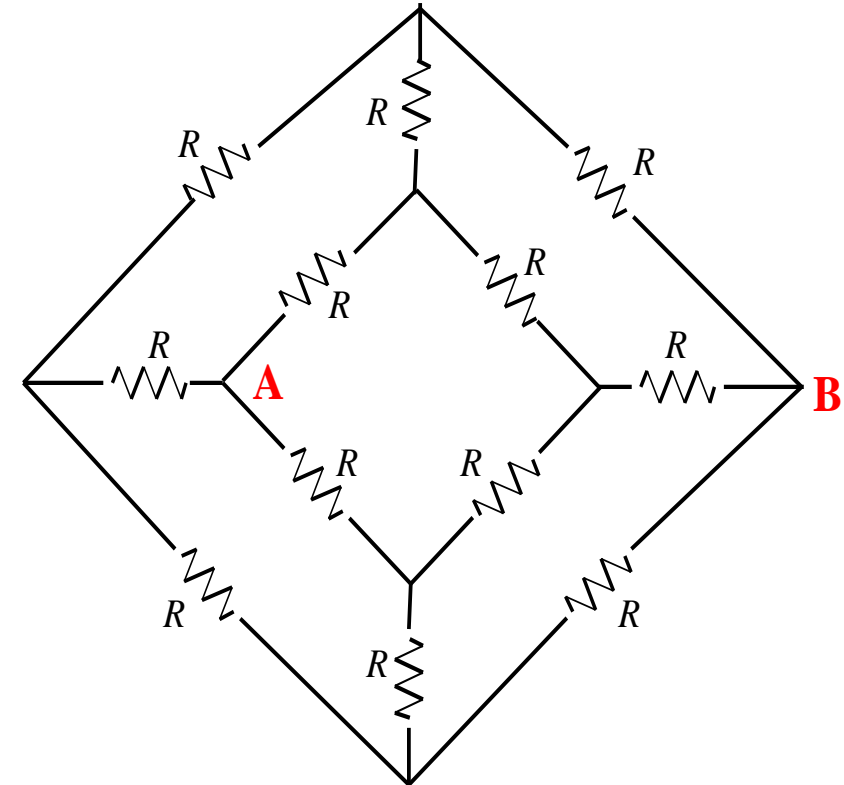Reduce the network to its equivalent resistance between terminals A and B





Answers to Quiz Questions

Answers

1. B)

2. $2\ \Omega$

3.

a) $1.875\ \Omega$

b) $2\ \Omega$

4. i) Bulb-1 since it consumes more power, ii) $180\ \text{V}$

5. i) Bulb-2 since it consumes more power, ii) $120\ \text{V}$

6. $40\ \text{V}$

Homework 1: $5R/6$