

14102
OP-Amp fundamentally:

$\text{I}_{\text{IP}} = \text{I}_{\text{O}} = 0$

$\text{I}_{\text{IP}} = \text{I}_{\text{O}} = 0$

2^o input 1 output device.


Amplifier fundamentally:

$\text{O}_{\text{IP}} = \text{gain} \times \text{I}_{\text{IP}} \Rightarrow \text{Linear Amp.}$

① Voltage amplifier $\Rightarrow \text{I}_{\text{IP}} = \text{Voltage}$

$\text{I}_{\text{IP}} = \text{Voltage}$

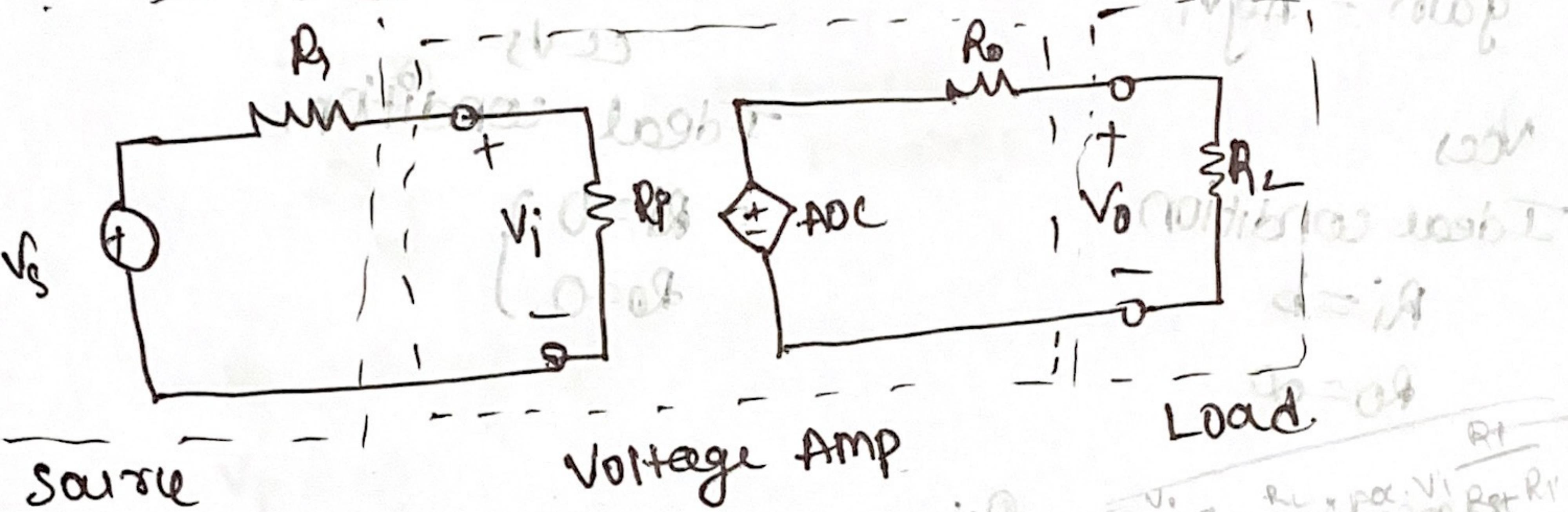$\text{gain} = V_o / V_s (\text{dimension less})$



$$V_o / V_s = ??$$

$$V_o = \frac{R_2}{R_1 + R_2} \times A_{\text{OC}} V_i$$

$$V_i = \frac{R_1}{R_1 + R_2} \times V_s$$


$$\frac{V_o}{V_s} = \frac{R_2}{R_1 + R_2} \times A_{\text{OC}} \frac{R_1}{R_1 + R_2} = \frac{R_2}{R_1} \times A_{\text{OC}}$$

$$\Rightarrow \frac{V_o}{V_s} = A_{\text{OC}}$$

② Current Amplifier:

$\text{I}_{\text{IP}} = \text{current}$

$\text{O}_{\text{IP}} = \text{current}$

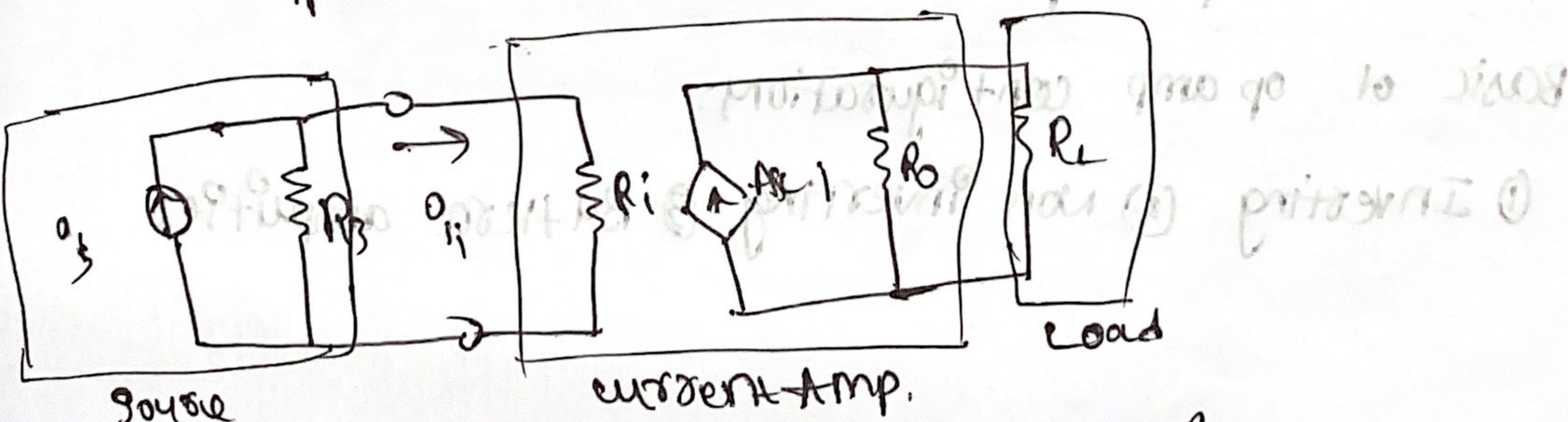

ASC \rightarrow short Ckt current gain.

$$\frac{V_o}{V_s} = \frac{R_f}{R_f + R_i} \times A_{sc} \times \frac{R_o}{R_o + R_L}$$

$$I_1 = \frac{R_s}{R_s + R_i} \times I_s$$

$$\frac{V_o}{V_s} = \frac{R_o}{R_o + R_s} \times A_{sc} \quad R_i = 0, R_o = \infty$$

③ Transconductance Amp: ④ Transistor amp:

V_{ip} = voltage

I_{op} = current

gain = A_{gv}

V_{ccs}

Ideal condition,

$R_i = b$

$R_o = 0$

I_{ip} = current

V_{op} = voltage

gain = A_{gv}



cc vs

Ideal condition.

$R_i = 0$

$R_o = 0$

Operational Amplifier:

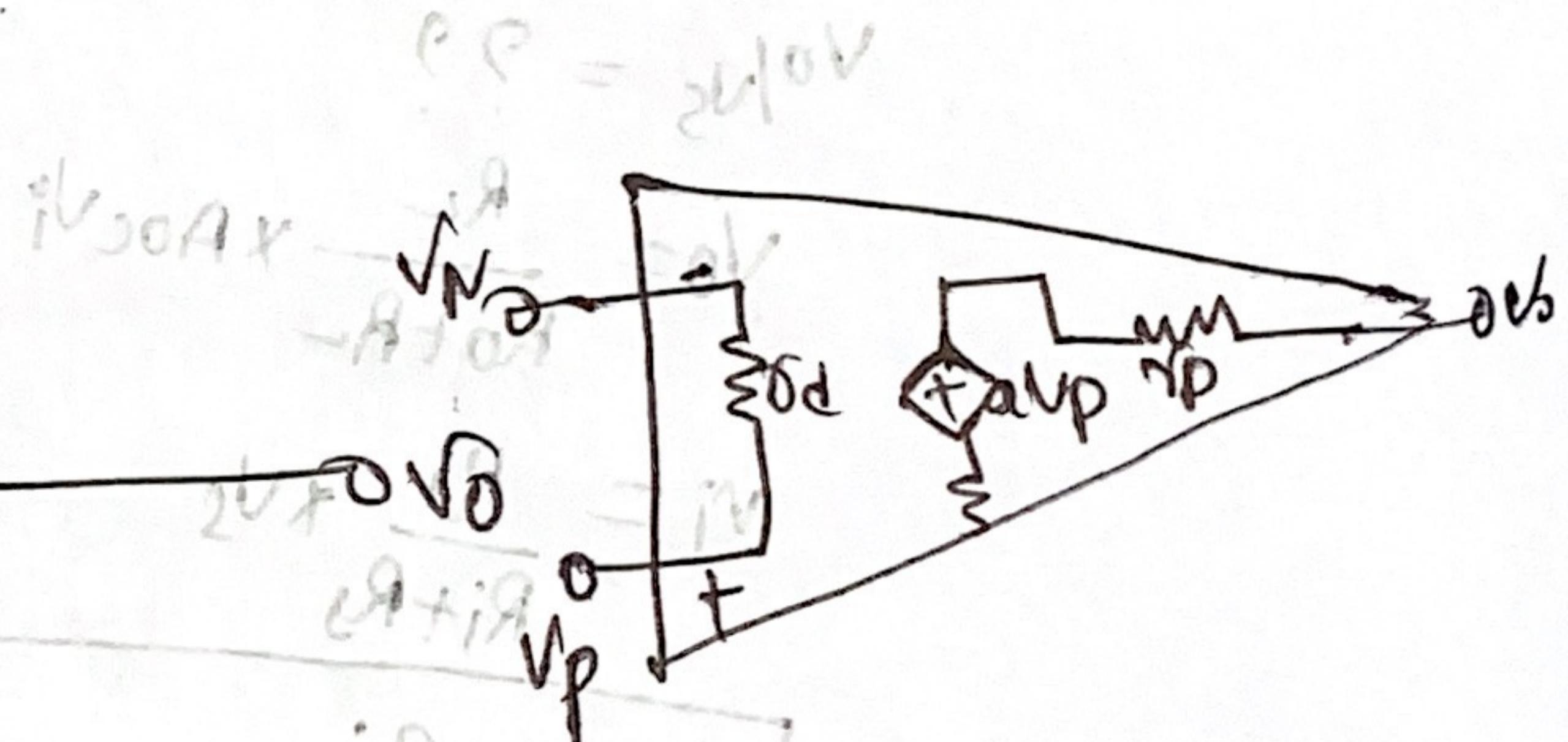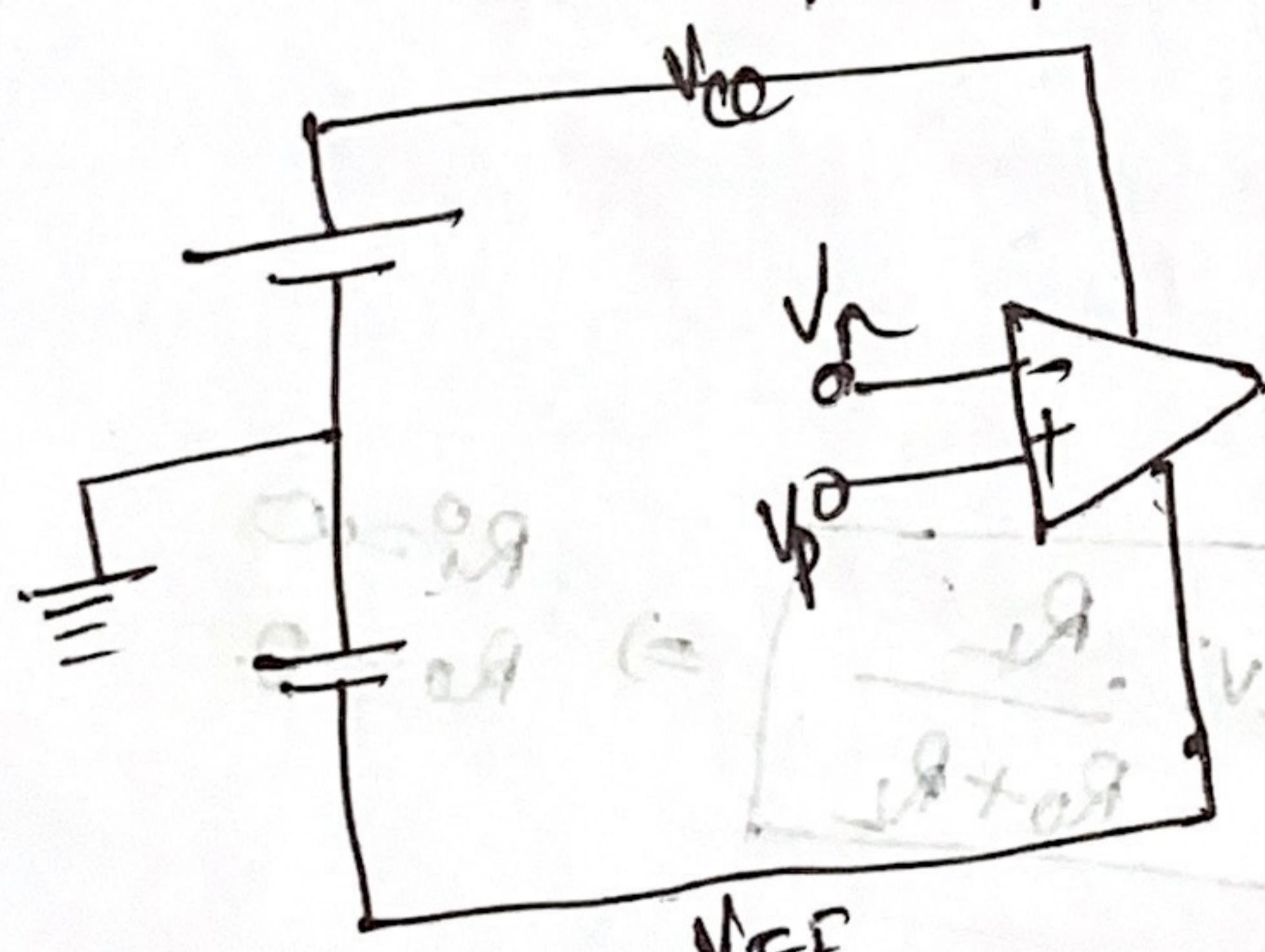

$R_o = V_{op}$ resistance } often
 $R_d = V_{ip}$ resistance } loop
 $a = \text{voltage gain.}$ parameter

$$V_o = aV_D = a[V_p - V_N]$$


→ Ideal op-amp.

Basic of op amp configurations:


- ① Inverting
- ② Non Inverting
- ③ Buffer or amplifier

Non-Inverting Amplifiers:

an op-amp + 2 external resistors

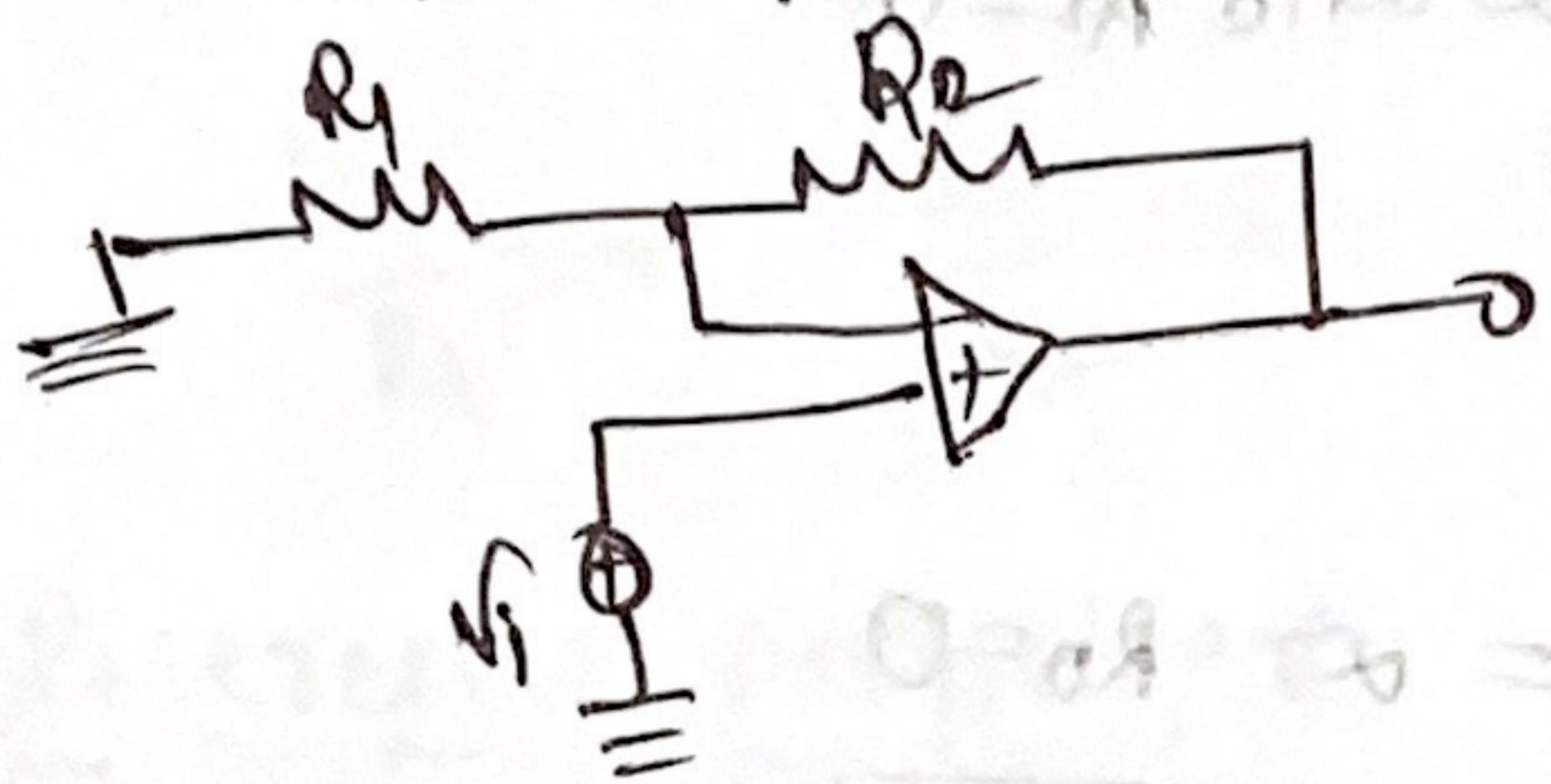

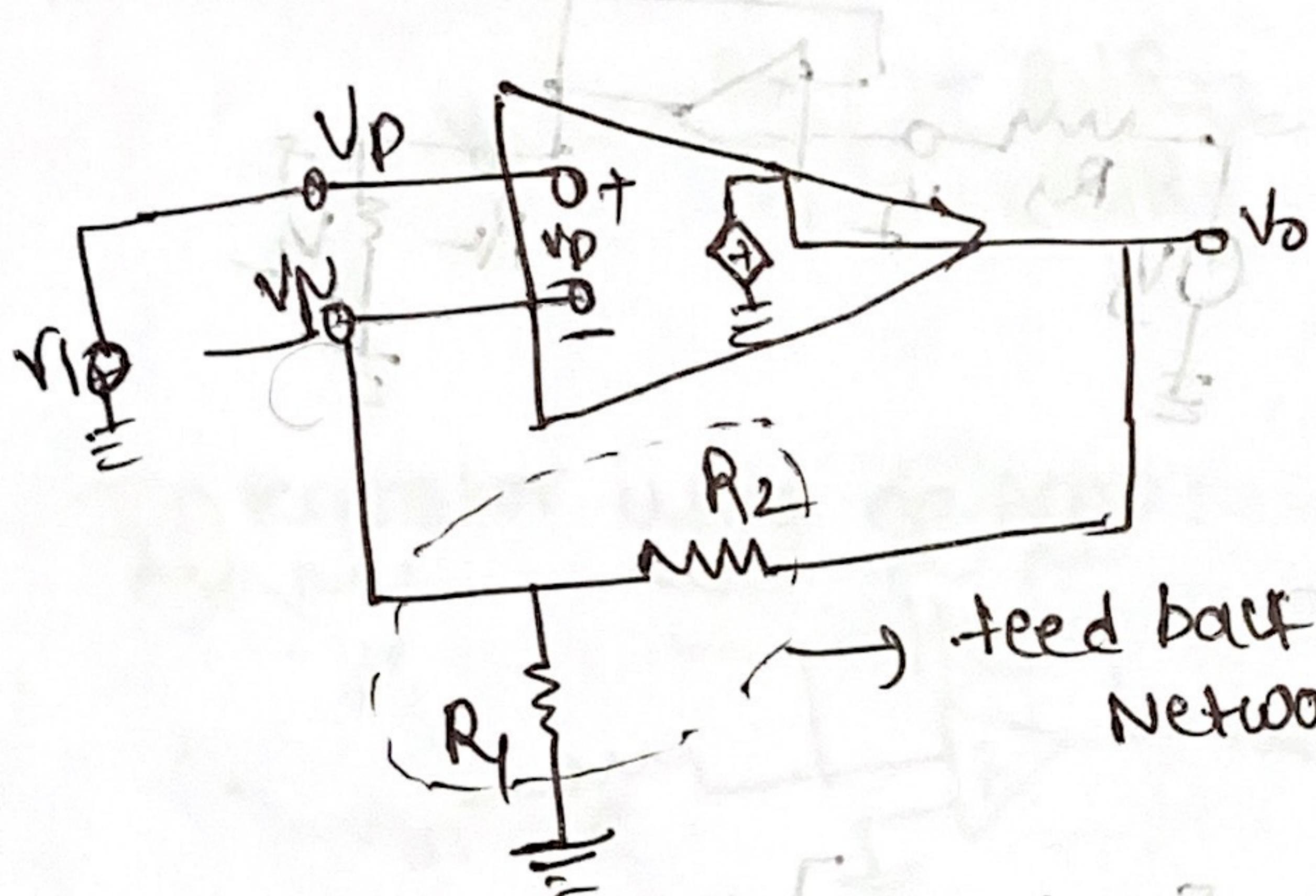$\text{Op-amp} \rightarrow \text{a} = \infty$ (non-inverting amplifier)



feed back
Network.

$$V_o = a(V_p - V_N)$$

$$V_p = V_i$$

$$V_N = \frac{R_1}{R_1 + R_2} V_o \Rightarrow V_N = \frac{1}{1 + R_1/R_2} V_o$$

$$\Rightarrow V_o = a \left(V_i - \frac{V_o}{1 + R_1/R_2} \right) = \frac{aV_i}{1 + R_1/R_2}$$

$$\frac{V_o}{V_i} = A = \left(1 + \frac{R_2}{R_1} \right) \left[1 + \left(\frac{R_2}{R_1} \right) \frac{1}{a} \right]$$

(voltage gain)

$A = \text{voltage gain for closed loop}$

$a = \text{voltage gain for open loop}$

$$A^{\text{ideal}} = K_A A = 1 + \frac{R_2}{R_1} \quad \text{Letting } a \rightarrow \infty$$


assuming $a \rightarrow \infty$ (ideal op-amp, no load effect, no other factors)

negligible input pd


negligible output pd

$$\frac{aV}{V_i} = \frac{aV}{V_i} + \frac{aV}{V_i} + \frac{aV}{V_i}$$

16/02/22

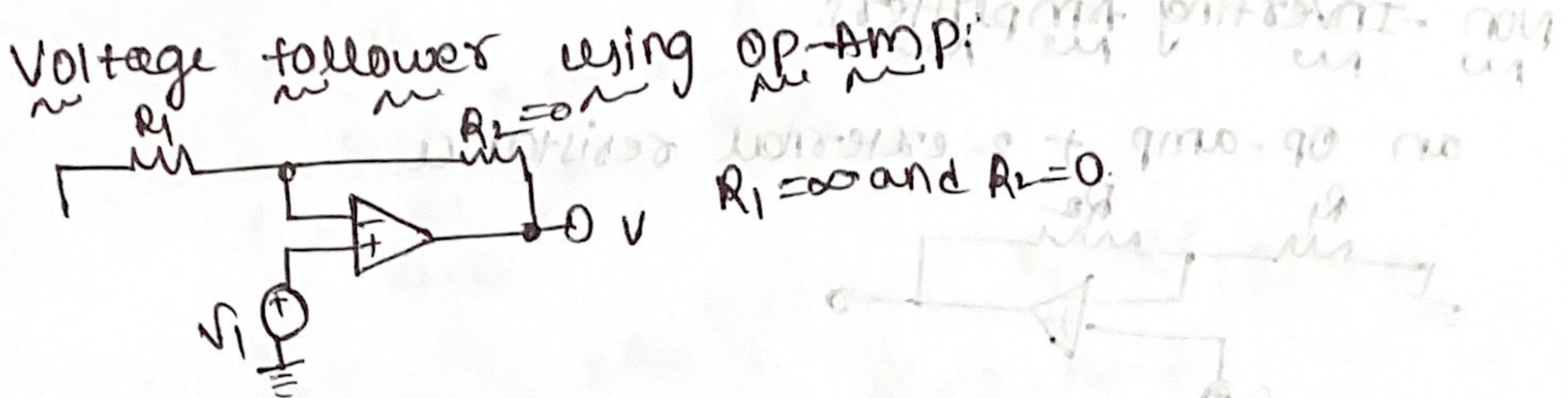

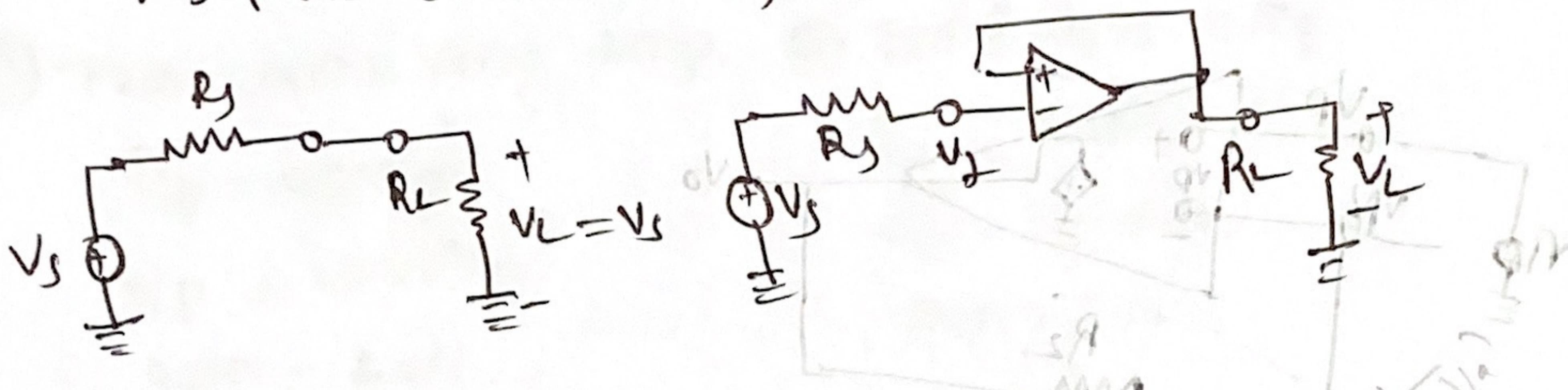resistance transformer; $R_i = \infty$ $R_o = 0$.



Inverting Amplifier

$$V_p = 0$$


$$V_N = [R_2 / (R_1 + R_2)] V_1 + [R_1 / (R_1 + R_2)] V_o$$

$$V_N = \frac{1}{1 + R_1 / R_2} V_1 + \frac{1}{1 + R_2 / R_1} V_o$$

$$V_o = \alpha (V_p - V_N) = \alpha \left(-\frac{1}{1 + R_1 / R_2} V_1 - \frac{1}{1 + R_2 / R_1} V_o \right)$$

$$A = \frac{V_o}{V_1} = \left(-\frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2 / R_1) / \alpha}$$
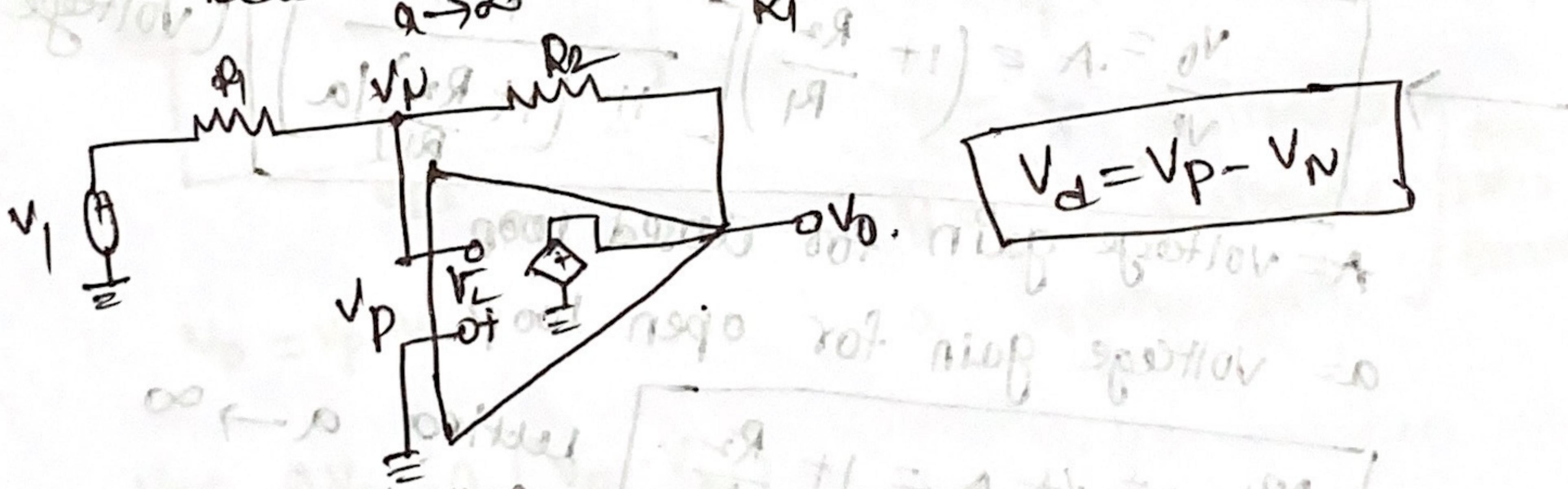
$$A_{\text{ideal}} = 19 \text{ mA} = -\frac{R_2}{R_1} \quad \alpha \rightarrow 0$$



→ Applications of Inverting AMP:
Summing Amplifiers:

we can do sum, sub, differentiation, integration by this amplifier.

$$i_1 + i_2 + i_3 = i_f$$

$$\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} = \frac{V_o}{R_f} \quad V_o = - \left(\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 \right)$$

Ex: Using standard 5% resistances, design a circuit

$$\text{such } V_o = -2(3V_1 + 4V_2 + 2V_3)$$

$$Q_f \text{ and } R_f = 20k\Omega$$

$$\frac{R_f}{R_1} = 6$$

$$\frac{R_f}{R_2} = 8$$

$$\frac{R_f}{R_3} = 4$$

$$R_1 = 3.33k\Omega$$

$$R_2 = 2.50k\Omega$$


$$R_3 = 5.00k\Omega$$

→ Difference Amplifier:

$$V_o = \frac{R_2}{R_1} \left(\frac{V_2 - V_1}{1 + R_3/R_4} \right) \quad V_2 - V_1 = V_o$$

Non Inverting
Inverting

Integrator using OP-AMP:

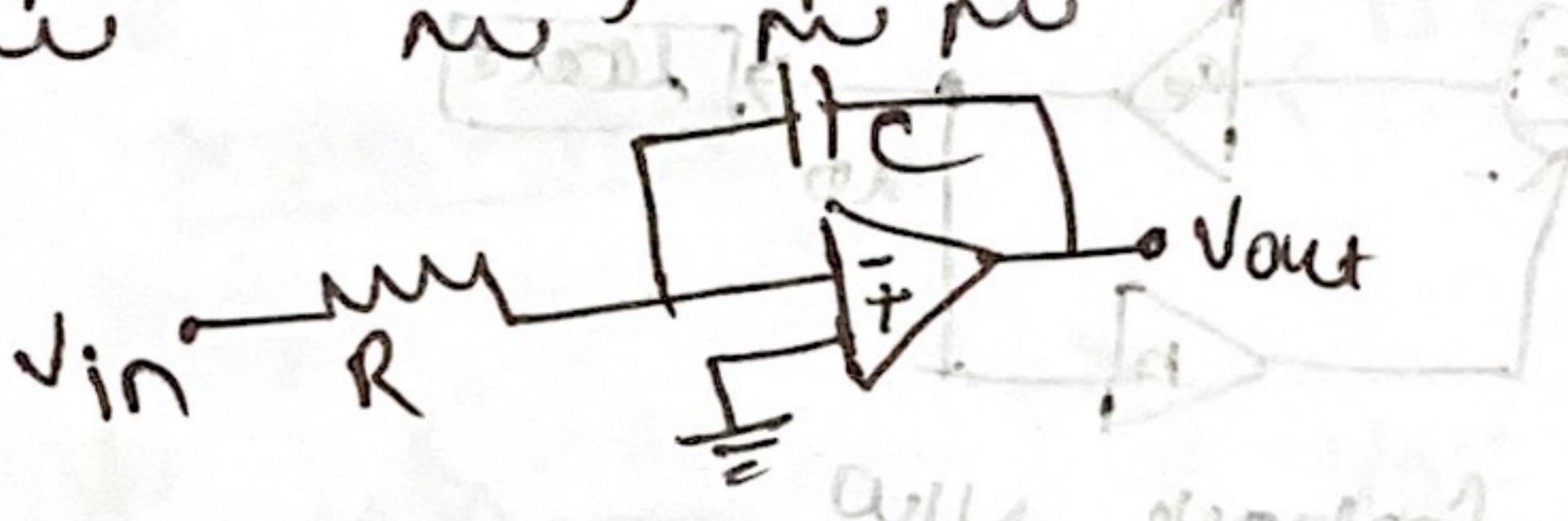

$$\frac{dV_{out}}{dt} = -\frac{1}{RCF} \cdot V_{in}(t)$$

$$\rightarrow V_{out} = -\frac{1}{RCF} \int V_{in}(t) dt$$

$$\frac{V_{in}-0}{R} = C F \frac{dV_{in}}{dt}$$

$$V_{in}/R = C F \frac{d(V_o - V_{out})}{dt}$$

$$\frac{V_{in}}{R} = -CF \frac{dV_{out}}{dt}$$

If initial op voltage is V_{out}

$$V_{out} = -\frac{1}{RCF} \int V_{in}(t) + V_{out}(0) dt$$

Differentiator using OP-AMP:

$$\rightarrow V_{out} = -R F C \frac{dV_{in}}{dt}$$

Ex: In a circuit let $V_1 = 1V$, $R_1 = 2k\Omega$, $R_2 = 18k\Omega$

find V_o if (a) $a = 10^2 V/V$ (b) $a = 10^4 V/V$ (c) $a = 10^6 V/V$.

$$A = \frac{V_o}{V_1} = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2/R_1)a} \quad V_o = \left(1 + \frac{R_2}{R_1} \right) \frac{1}{1 + (1 + R_2/R_1)a}$$

$$(a) V_o = 10 / (1 + 10 \cdot 10^2) = 9.091V.$$

$$(b) V_o = 9.990V$$

$$(c) V_o = 9.999V$$

Higher the gain a , the closer V_o is to $10.0V$.

21/02/20

Differentiator

closed gain finite

Open circuit


Integrator

open feed back

gain ∞

$$V_o(t) = \frac{1}{RC} \int_0^t V_i(\tau) d\tau + V_o(0) \quad (1.34)$$

Negative feed back:

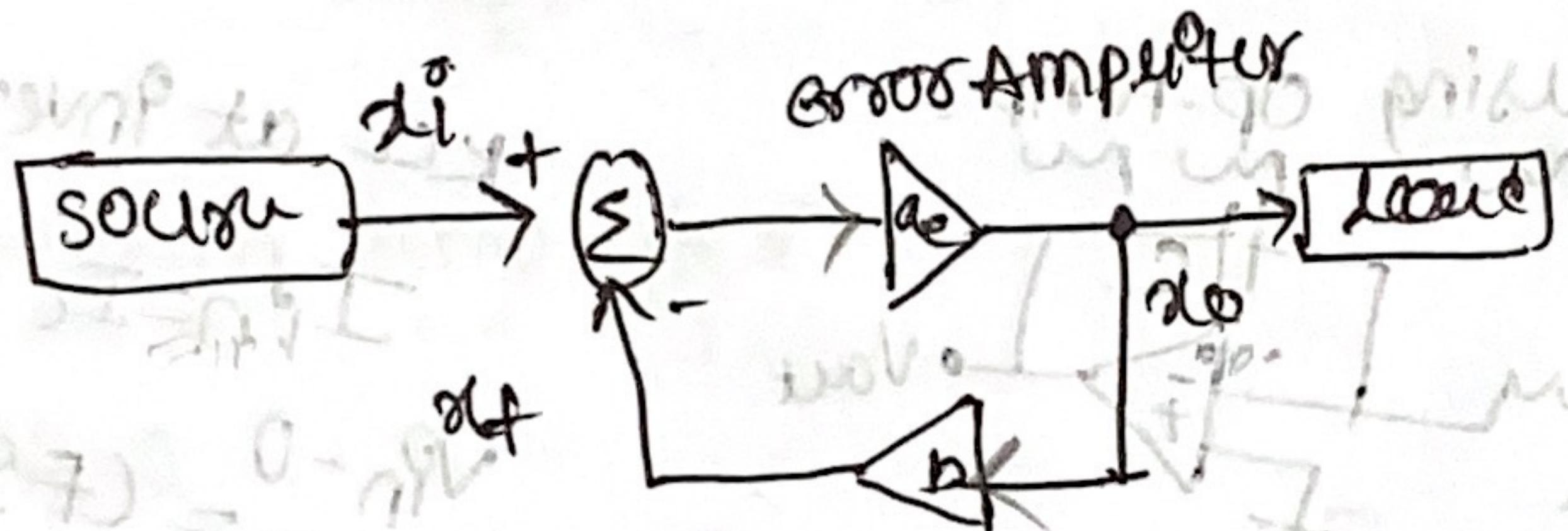

① Error Amplifiers:

$a_e = \text{open loop gain}$.

$a_e = 1/P$

$a_o = 1/P$

② Feedback network:

$a_f = 1/P$

gain ∞

$a_f = b a_o$

$b = \text{feedback factor}$

③ Summing network: Σ'

$a_e = -a_e a_f$ [∴ negative feedback]

$$a_o = a_e (d_i - b a_o)$$

$$A = \frac{a_o}{d_i} = \frac{a_e}{1 + a_e b}$$

closed loop gain

$a_e b > 0$ for feedback to be $-ve$.


$V_o = 0.01 \text{ mV}$ or $a_{ab} = 10^6 \text{ dB}$ at 100 Hz

Feed back in op-amp circuit:

$$a_o = a_e (1 + b \frac{V_o}{V_i}) \Rightarrow a_e \Rightarrow \text{open loop gain}$$

$b \rightarrow$ feed back factor.

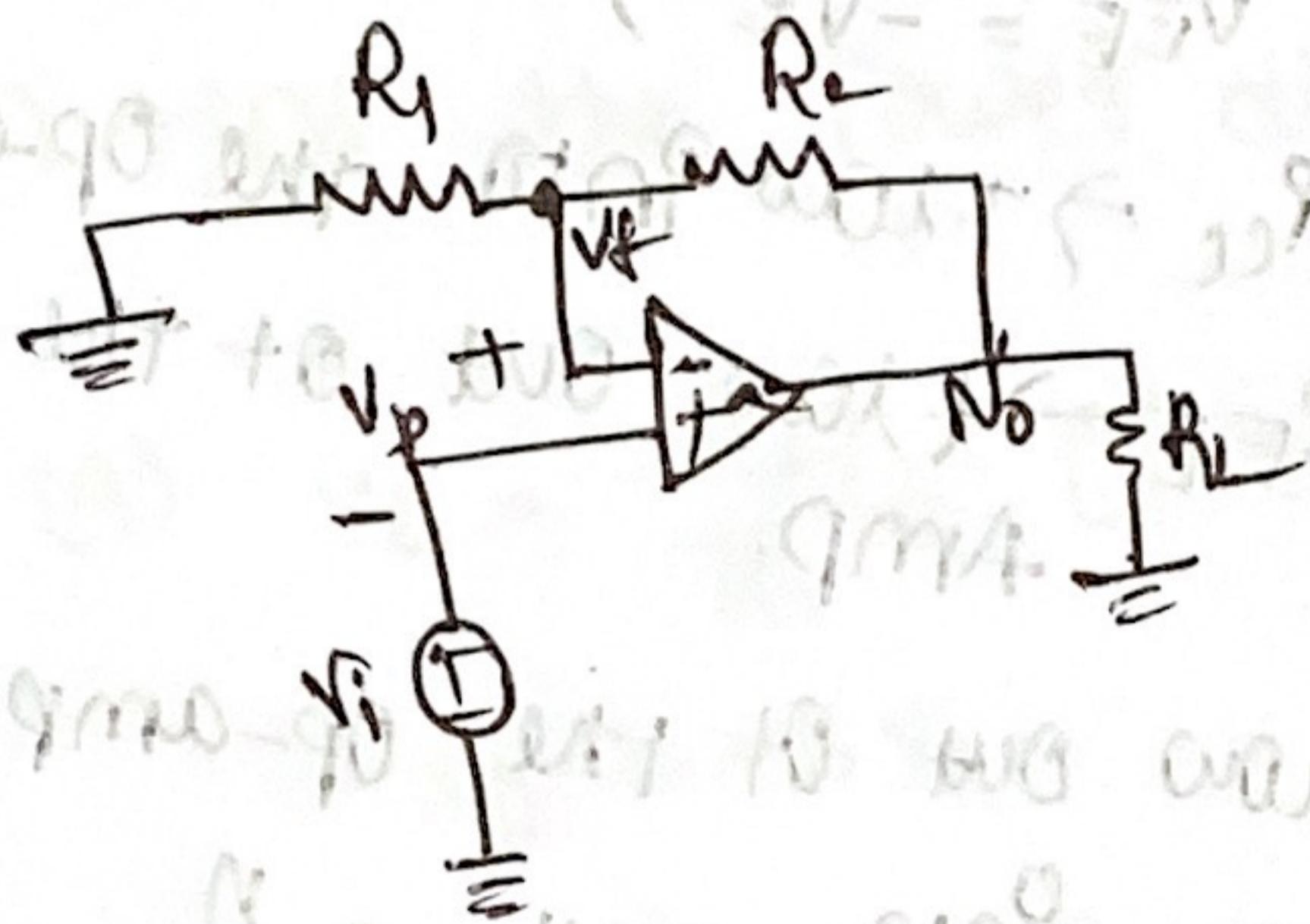① series-shunt and shunt-shunt topologies:




$$V_o = a V_D$$

$$= a(V_i - V_f)$$

$$V_o = a \left(V_i - \frac{R_1}{R_1 + R_2} V_o \right)$$

series-shunt

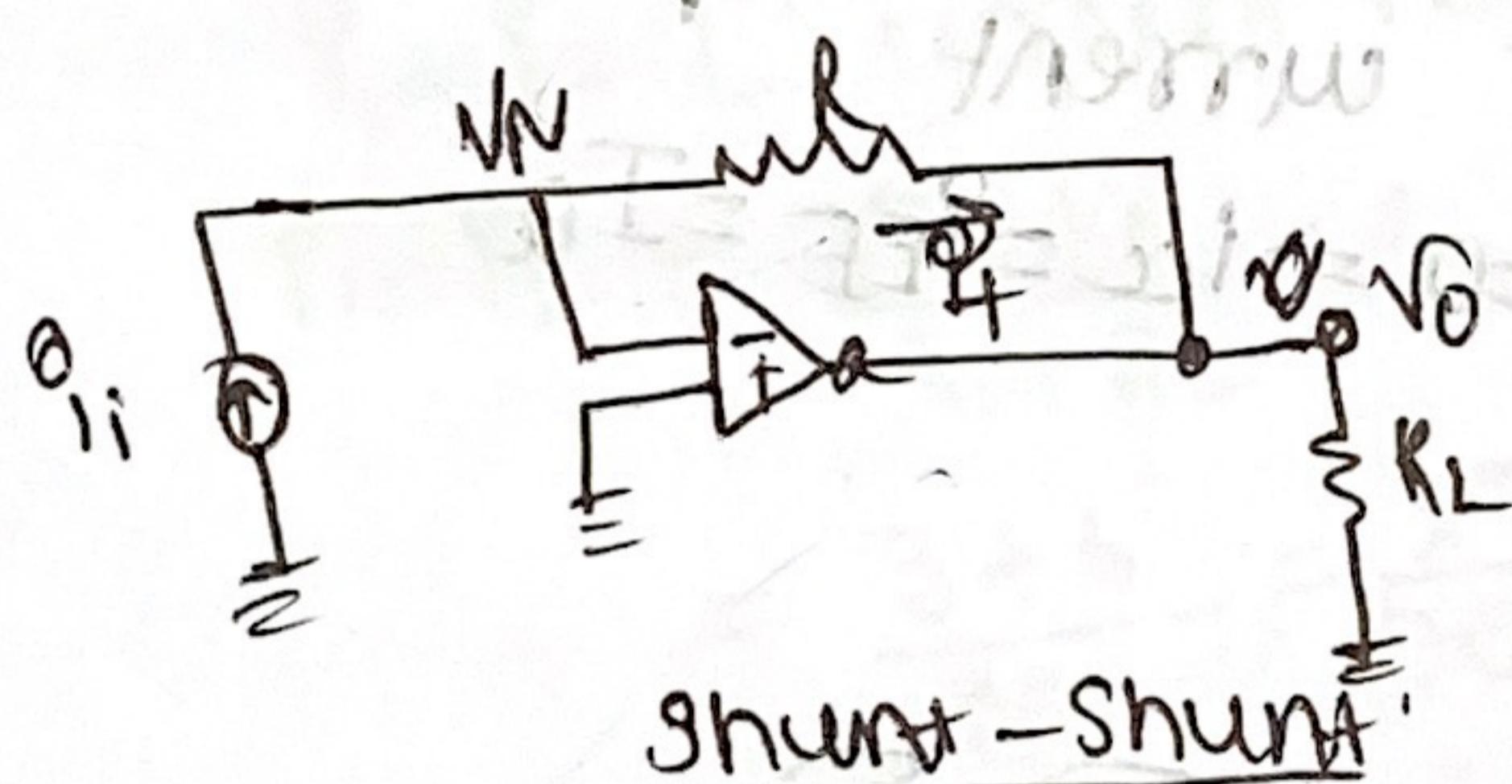

$$V_o = -a V_N$$

$$V_o = -a R \left[V_i - \left(-\frac{1}{R} \right) V_o \right]$$

shunt-shunt


② series-series and shunt-series topologies.

$$\text{series-series: } V_o = (R + R_L) i_o$$

$$V_o = a(V_i - V_f)$$

$$V_f = i_o R_L$$

shunt-series: current amplifier

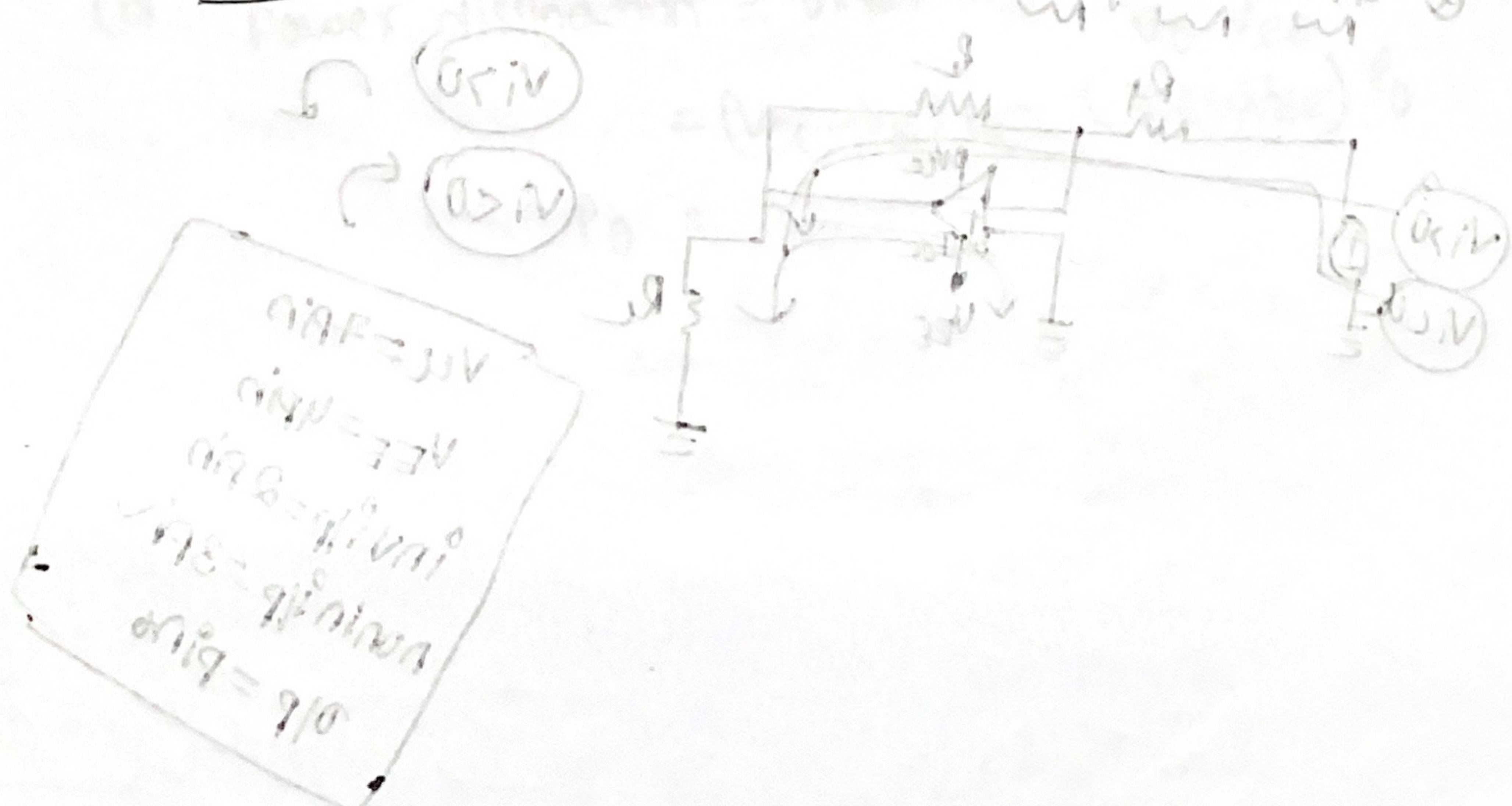

op-amp powering:

current flow & power dissipation:

i_{cc} \rightarrow DC current $V_{EE} = -V_E$

i_{EE} \rightarrow DC current $V_{DD} = 0V$

V_{CC} \rightarrow DC voltage

$i_{cc} \rightarrow$ Flow into the Op-amp

$i_{EE} \rightarrow$ flow out of the Op-Amp.


sourcing current $\rightarrow i_D$ flow out of the Op-amp

sinking current $\rightarrow i_I$ " i_{DD} into


$i_{cc} = i_{EE} + i_D$ \rightarrow Positive supply

$i_{EE} = i_{cc} + i_D$ $\rightarrow i_D = 0 \Rightarrow i_{cc} = i_{EE} = I_Q$ \rightarrow Current

① Non-inverting AMP:

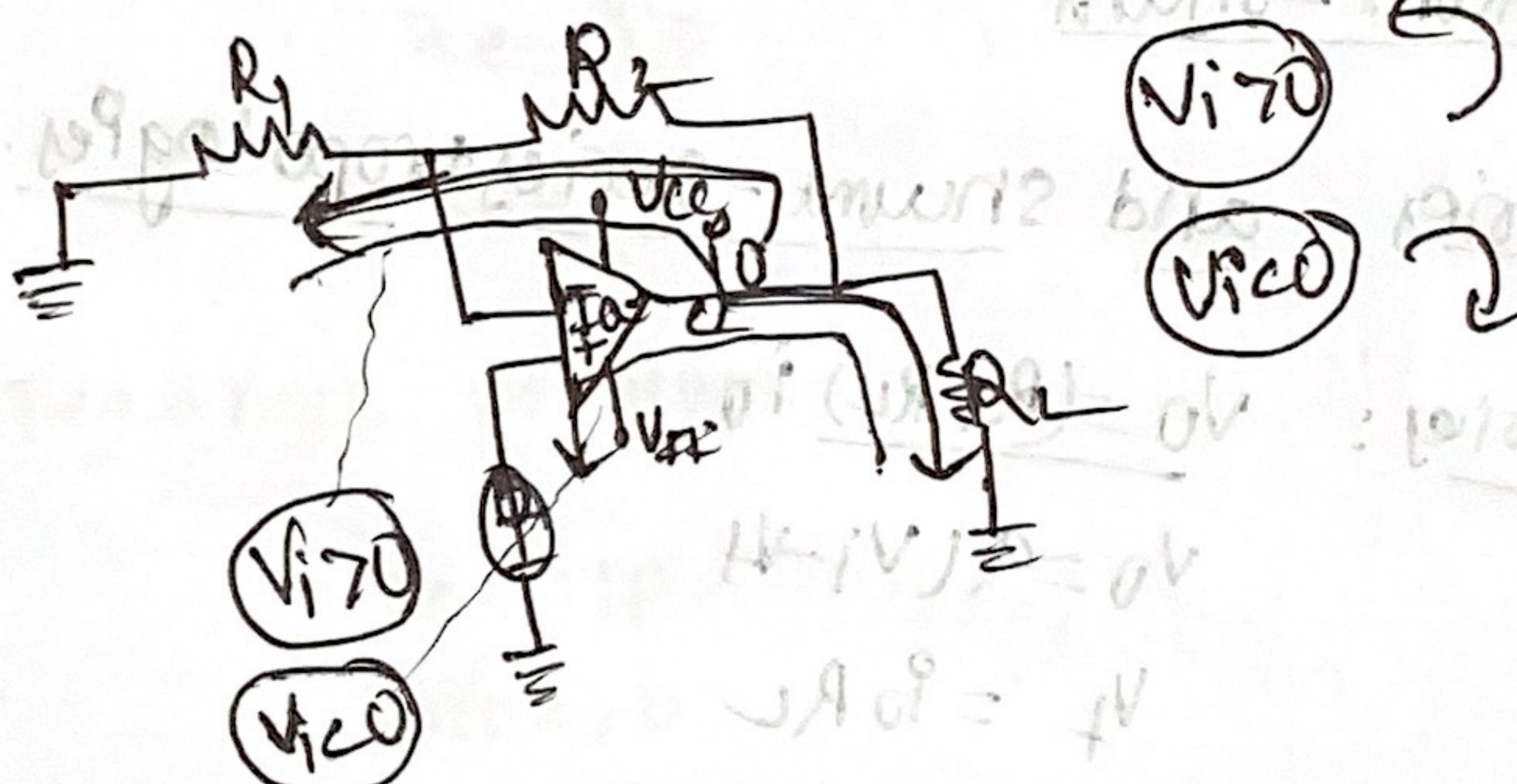

② Inverting AMP:

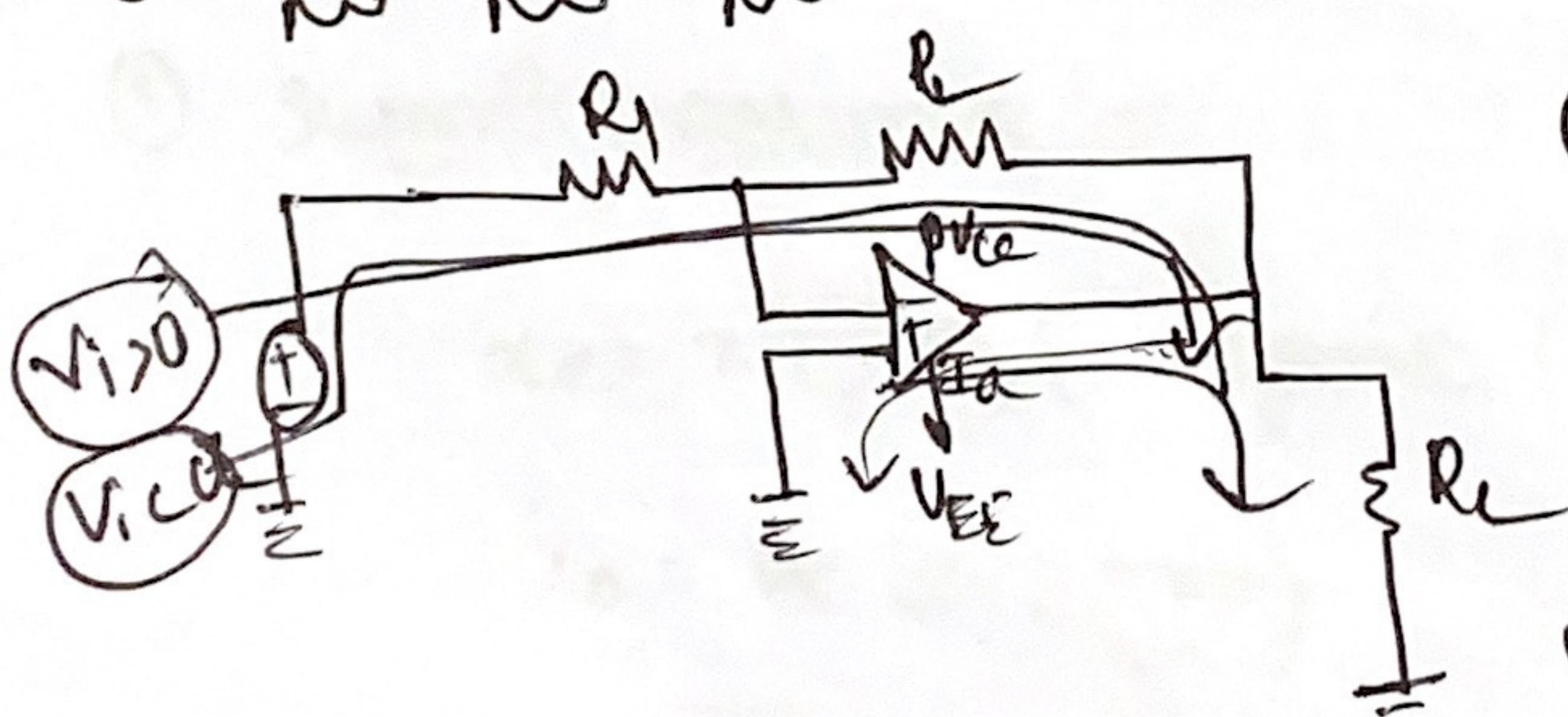

$V_{IL} = 7\text{Pin}$
 $V_{EE} = 4\text{Pin}$
 $\text{inv}^o \text{IP} = 2\text{Pin}$
 $\text{nonin}^o \text{IP} = 3\text{Pin}$
 $\text{DIP} = \text{Pin}_6$

- (a) An inverting amplifier with $R_1 = 10\text{k}\Omega$, $R_2 = 20\text{k}\Omega$ and $V_i = 3\text{V}$ drives a $2\text{k}\Omega$ load.
- (a) Assuming $\pm 15\text{V}$ supplies and $I_Q = 0.5\text{mA}$, find I_{CC} , I_{EE} & i_o .

(b) Find the power dissipation inside the OP-Amp. (use i_o above i_{Qout}).

Ans)

$$(a) V_o = -\frac{R_2}{R_1} V_i \quad [\text{Inverting Amp}]$$

$$V_o = -6\text{V}$$

$$i_L^o = \frac{V_o}{R_L} = \frac{-6}{2000} = 0.003 = 3\text{mA}$$

$i_1 = i_2$ [i current flows in the same direction or i].

$$i_1 = i_2 = \frac{V_i - V_o}{R_1 + R_2}$$

$$= \frac{3 + 6}{30} = \frac{9}{30} = 0.3\text{mA}$$


$$i_o^o = i_{CC} + i_L^o \quad i_o^o = i_2 + i_L^o \\ = 0.3 + 3 \\ = 3.3\text{mA}$$

$$\text{Assume } i_{CC} = i_Q = 0.5\text{mA}$$

$$i_{EE} = i_{CC} + i_o = 3.8\text{mA}$$

$$(b) \text{Power dissipation} = V_x \cdot i^o \\ = (V_{CC} - V_{EE}) i_Q - (V_{CC} - V_{EE}) P_0$$

$$P_0 =$$

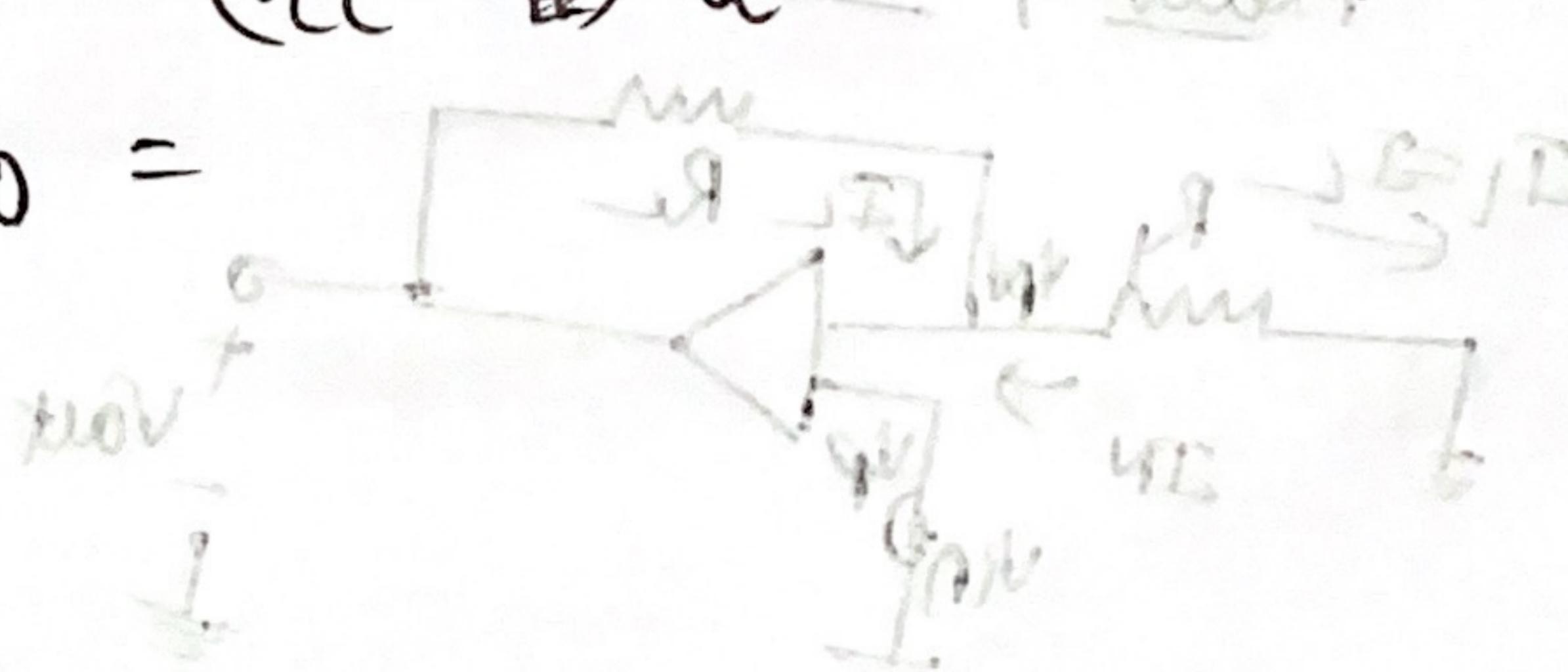


23/02/22


Circuits with Resistive Feed back:

Current to Voltage (I-V) converter:
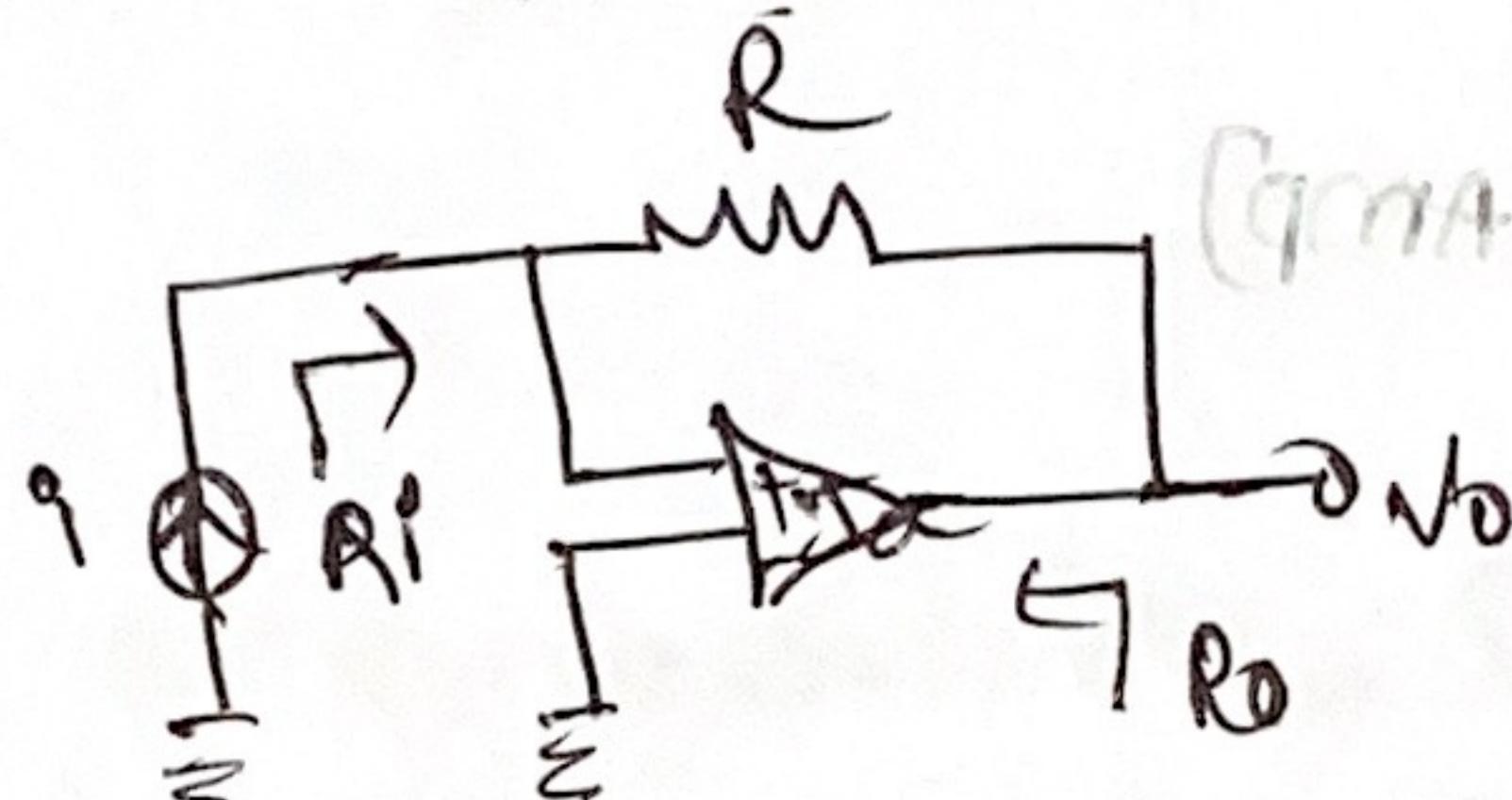
$$\text{Gain} = \frac{V_o}{I_p} = \frac{R_f}{R_i}$$




Ex:

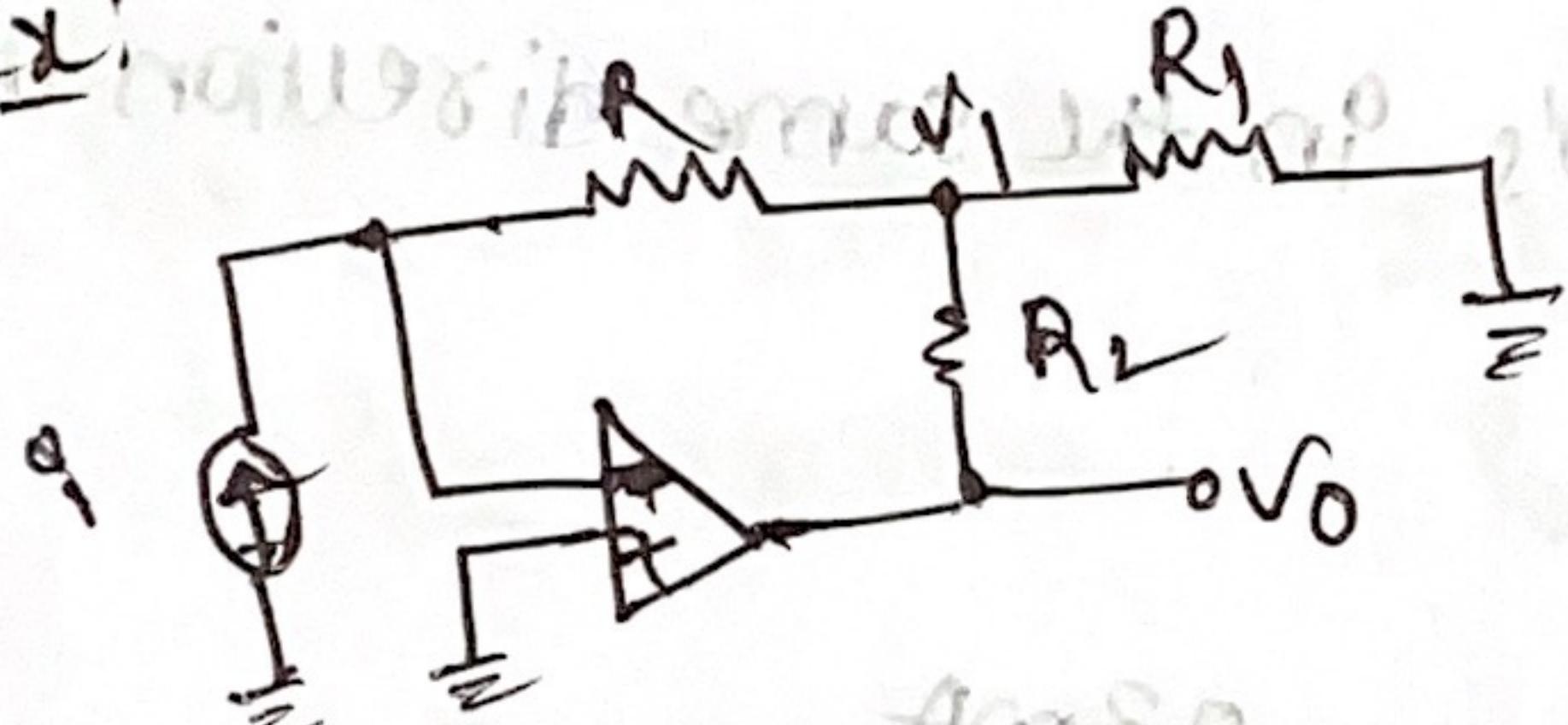


Design the circuit for a sensitivity 0.1 V/nA. $\rightarrow K_R = 100 M\Omega$

$$K = 1 + \frac{R_f}{R_i} + \frac{R_e}{R} = 100$$
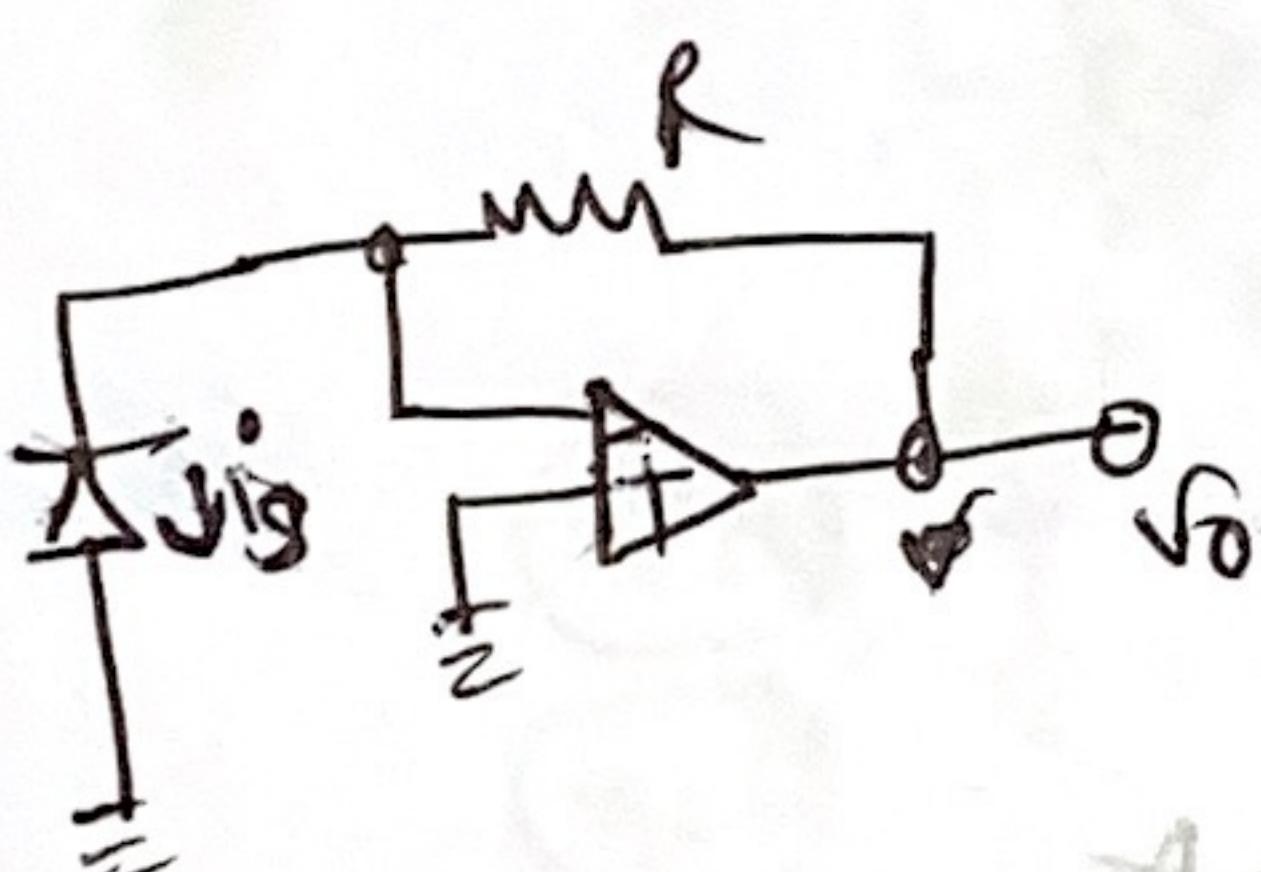
$$1 + R_2 = 100 \rightarrow R_2 = 99 K\Omega$$



Voltage to current converter:

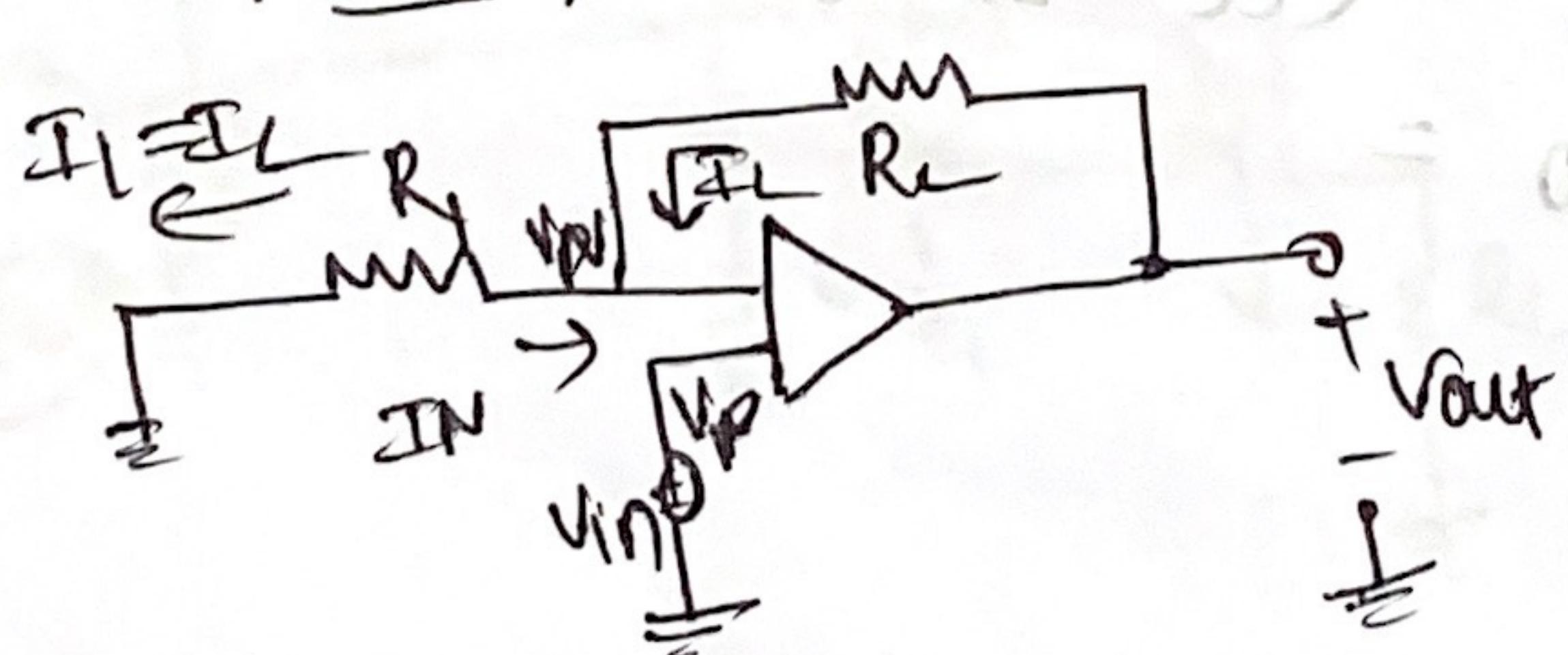

KCL at node V_N:

$$I_L = I_1 + I_{IN}$$

$$I_L = I_1$$

$$I_1 = \frac{V_{IN}}{R_1}$$


$$V_P = V_N = V_{IN}$$

$$I_{LOC} = V_{IN}$$

$$I_L = \frac{V_{IN}}{R_L}$$

Ex.

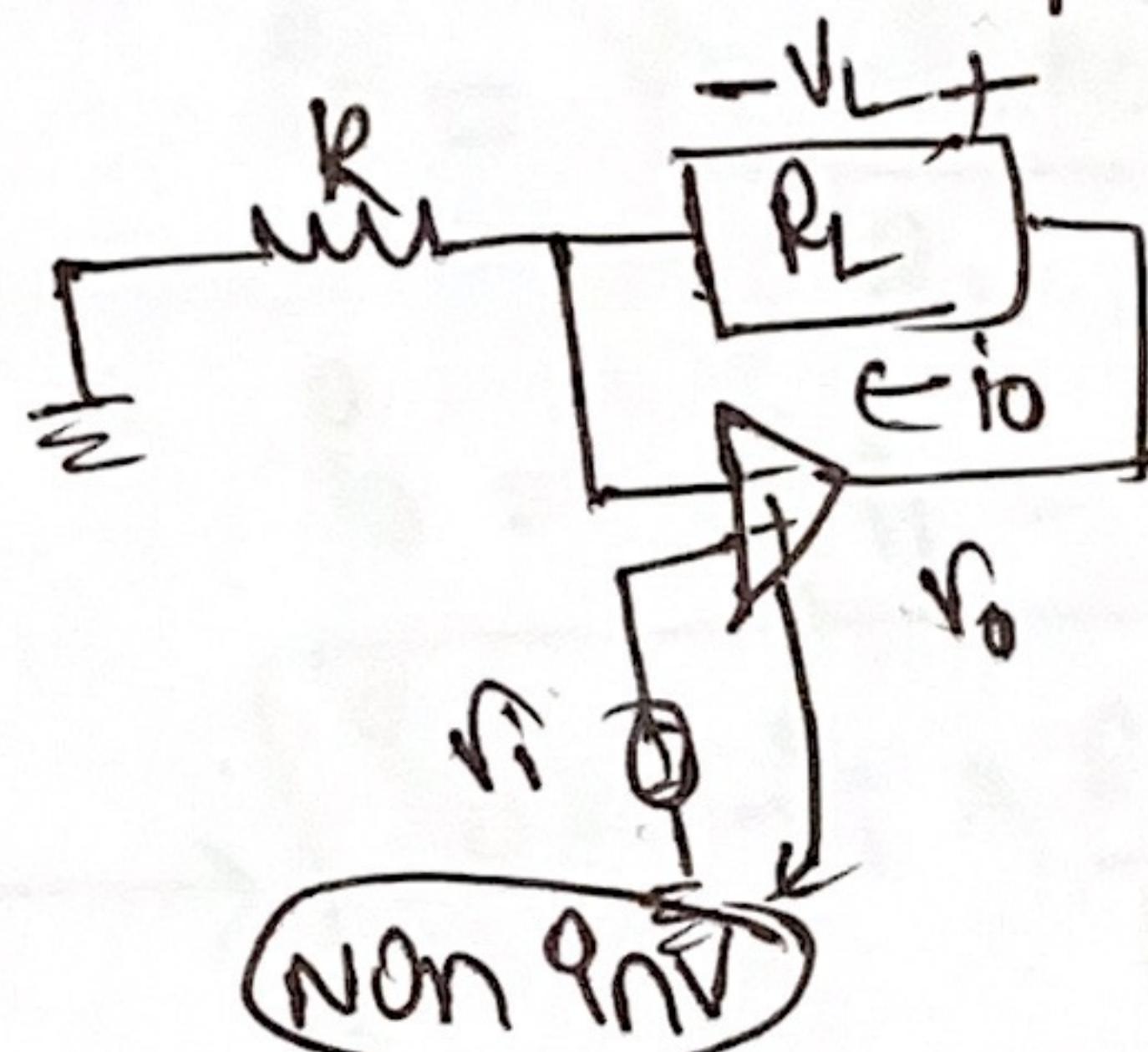In the circuit $V_i = 5V$, $R = 10k\Omega$, $\pm V_{sat} = \pm 13V$.
The resistive load R_L calculate I_o , voltage compliance
and maximum permissible value of R_L .



$$I_o = \frac{5}{10} = 0.5mA$$

Voltage compliance

$$(-13 - 5)V \leq V_L \leq (13 - 5)V$$

$$R_L \leq 810.5 = 10k\Omega$$

$$\left(\frac{13 + 5}{10} \right) \cdot 0.5mA = 0.9mA$$

Output current

$$V = 10 \\ 10$$

$$I_o = 0.5mA$$

Voltage compliance

$$-13V \leq V_L \leq 13V$$

$$R_L \leq 13/0.5 = 26k\Omega$$


$$\frac{13 + 5}{10} \cdot 0.5mA = 0.9mA$$

$$\left(\frac{13 + 5}{10} \right) \cdot 0.5mA = 0.9mA$$

Q10.17 7000GUN b601 → b96nworks ③

$$10V - 8V = 2V$$

$$2V = 4V$$

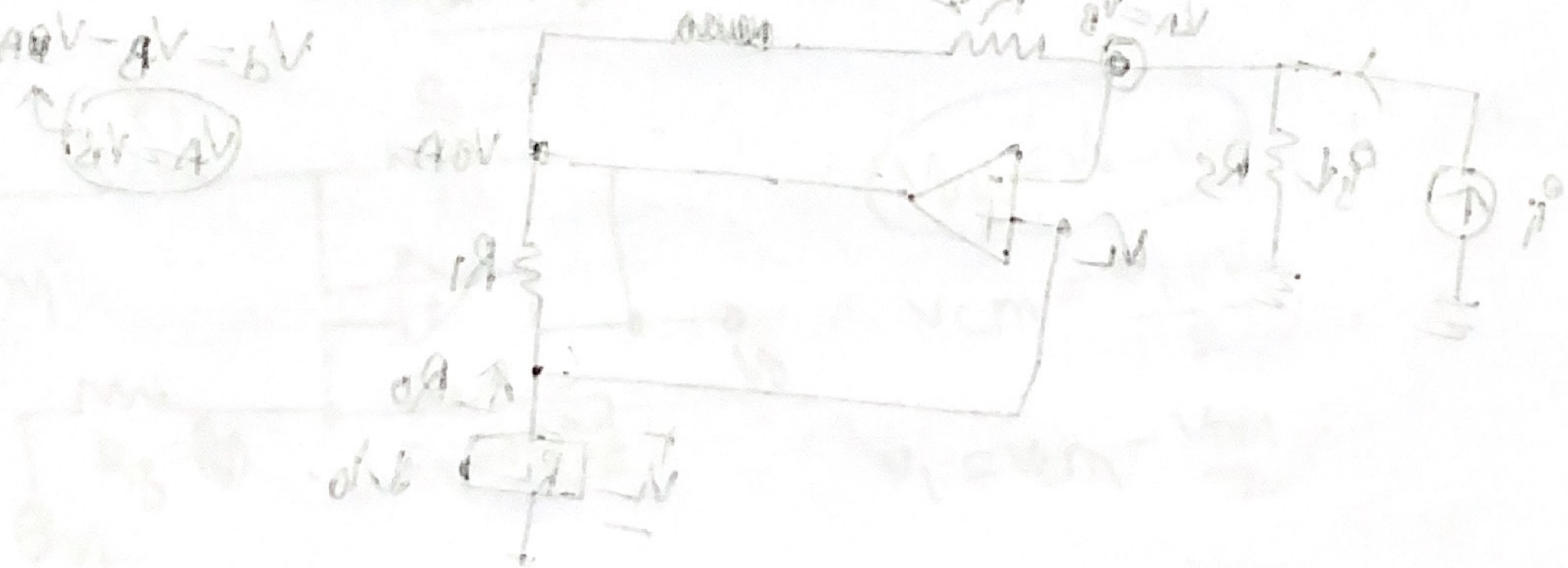

input bias current I_b

$$\frac{10V - 8V}{1A} = \frac{2V}{1A} = 0.2A$$

$$-8V - 10V = -18V$$


28/02/20

Current Amplifier

$$I_O = A_i I_i \quad \rightarrow \quad I_O = A_i i_i - \frac{V_L}{R_O}$$

$R_O = \infty$

① Floating Load type:

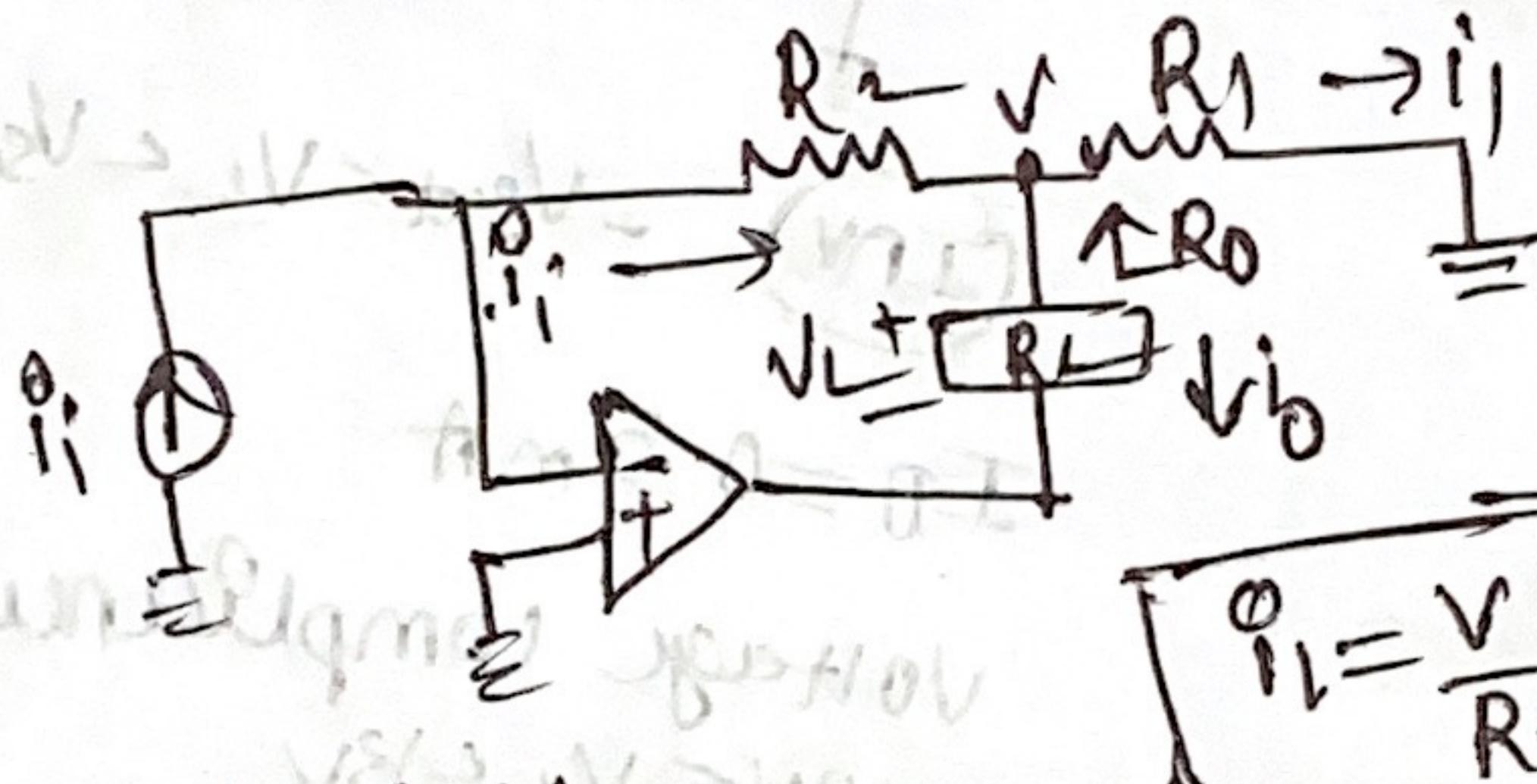

apply KCL

$$I_O = I_i + (-I_i)$$

$$I_O = I_i + \frac{R_2}{R_1} \times I_i$$

$$\rightarrow I_O = I_i \left(1 + \frac{R_2}{R_1}\right)$$

$$I_i = \frac{V}{R_1}$$


$$A_m = \frac{V_o}{V} = \frac{R_2}{R_1}$$

$$V_o = -I_i R_2$$

$$V_o = -I_i R_2 = -V_i \left(1 + \frac{R_2}{R_1}\right)$$

current gain

② Grounded-load Current Amp:

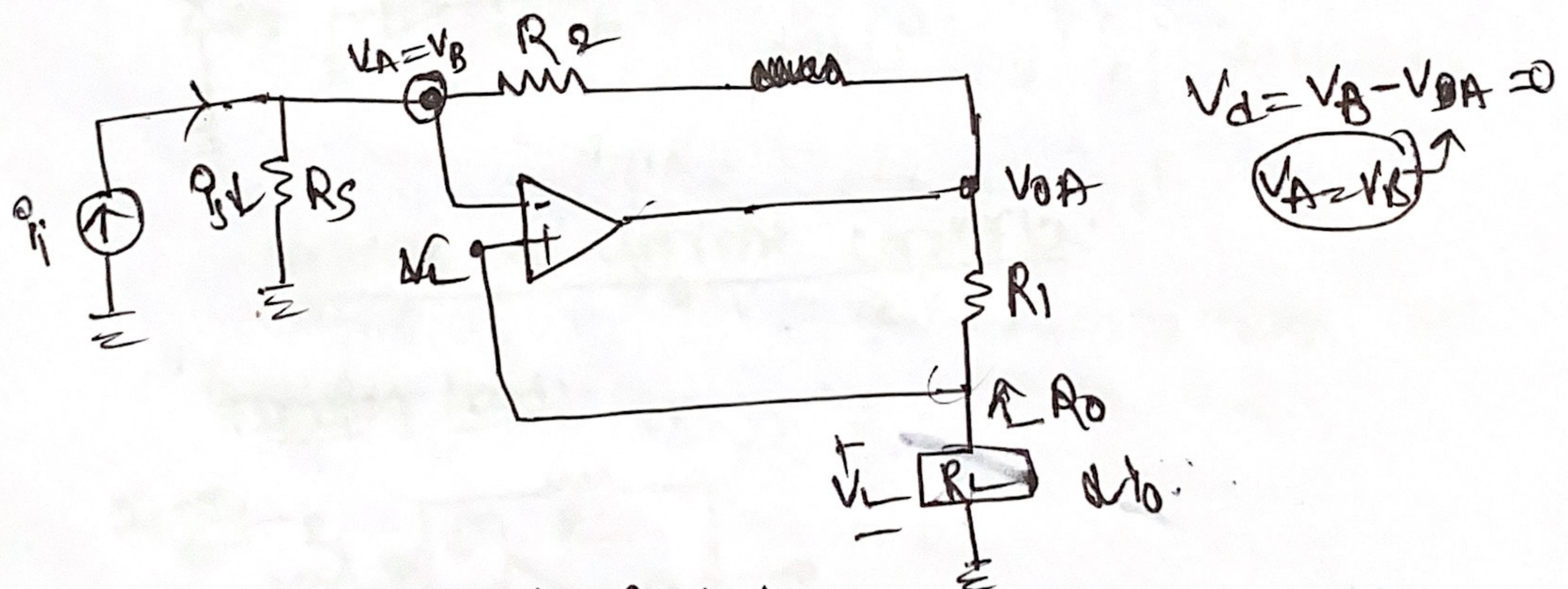

Apply KCL, Node Analysis

$$I_O = \frac{V_{OA} - V_L}{R_1}, \quad I_{D2} = \frac{V_L - V_{OA}}{R_2}$$

$$\Rightarrow V_{OA} = V_L - I_{D2} R_2$$

$$i_1 = i_{S1} + i_{S2}$$

$i_2 = i_1 - i_{S2}$ } current through Reg.

$$i_2 = i_1 - \frac{V_S}{R_S} I_{R_S}$$

$$i_0 = \frac{V_L - i_2 R_2 - V_L}{R_1} = \frac{-i_2 R_2}{R_1}$$

$$i_0 = -(i_1 - \frac{V_S}{R_S} I_{R_S}) \frac{R_2}{R_1} I_{R_1}$$

$$i_0 = -i_1 \frac{R_2}{R_1} + \frac{V_L R_2}{R_S R_1}$$

$$A = -\frac{R_2}{R_1} \quad \text{and} \quad R_O = -\frac{R_S R_1}{R_2} \Rightarrow \text{current mirror.}$$

Differential Amplifiers:


$$V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

$$\frac{A_H}{R_3} = \frac{R_2}{R_1} \Rightarrow \text{Bridge is balanced.}$$

Differential mode } opp component

Common mode

$$\underline{V_{CM} \quad V_{DM}}$$

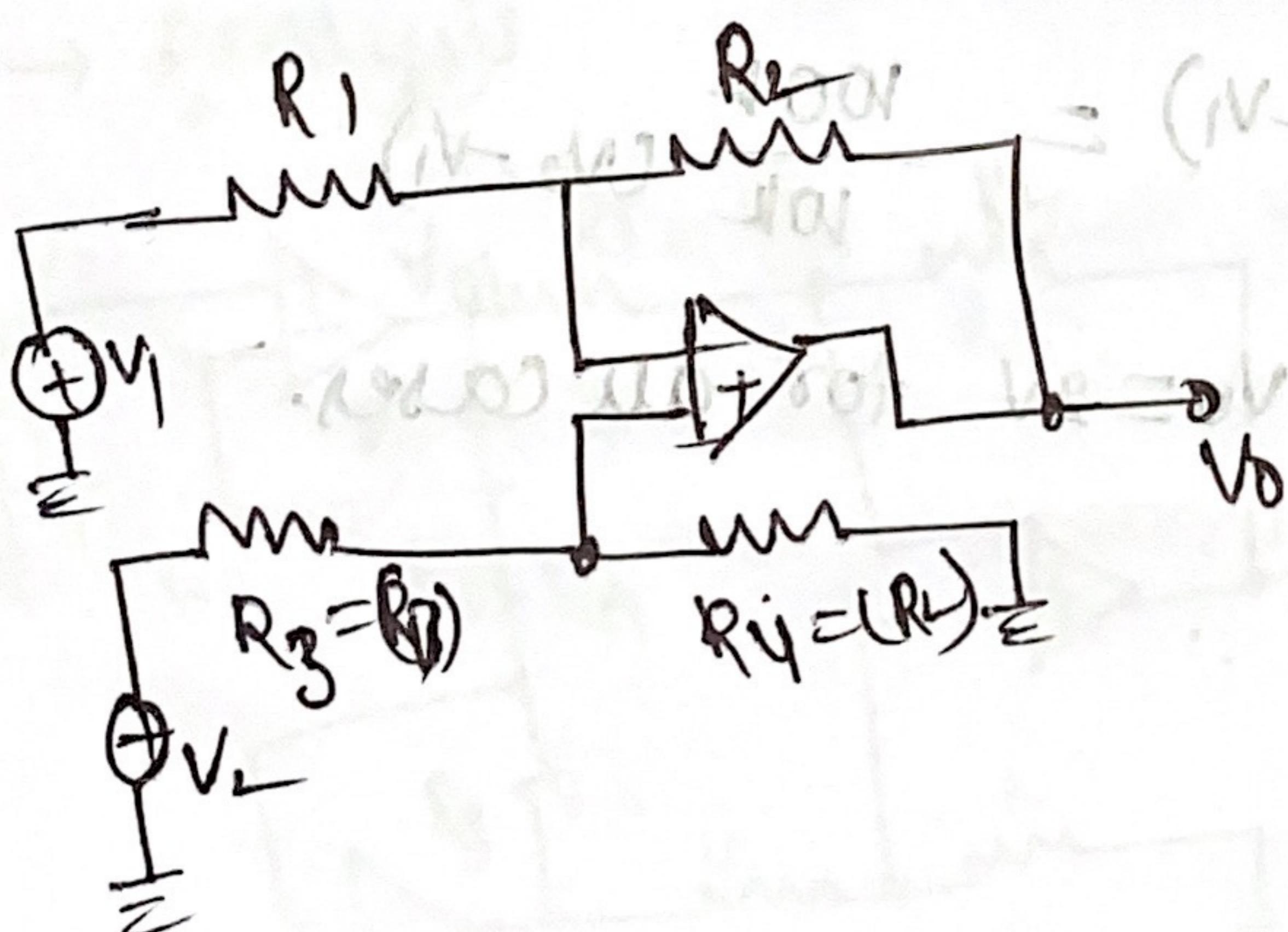

$$V_{DM} = V_2 - V_1$$

$$V_{CM} = \frac{V_1 + V_2}{2}$$

$$V_1 = V_{CM} - \frac{V_{DM}}{2}$$

$$V_2 = V_{CM} + \frac{V_{DM}}{2}$$

$$\left[\frac{V_1}{R_1} + \frac{V_2}{R_2} \right] = 0$$

$$\frac{V_1}{R_1} = \frac{V_2}{R_2}$$

$$= 1A = 5A$$

\Rightarrow Imbalance factor:

$$\rightarrow V_o = A_{dm} V_{dm} + A_{cm} V_{cm}$$

A_{dm} = differential mode gain

V_{cm} = common mode gain

$$V_o = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_o = \frac{R_2}{R_1} - V_{cm}$$

$$V_o = A_{dm} V_{DM}$$

$$A_{dm} = \frac{R_2}{R_1} \left(1 - \frac{R_1 + 2R_2}{(R_1 + R_2)} \times \frac{e}{2} \right)$$

$$A_{cm} = \frac{R_2}{R_1 + R_2} \times e$$

(Q) In the difference amplifier circuit, let $R_1 = R_3 = 10k\Omega$,

$$R_2 = R_4 = 100 k\Omega$$

(a) Assuming perfectly matched resistors find V_o for each of the following 91p voltage pairs, $(V_1, V_2) \in (-0.1V, +0.1V), (4.9V, 5.1V), (9.9V, 10.1V)$.

(b) Repeat (a) with mismatched resistors, $R_1 = 10k\Omega$

$$R_2 = 98k\Omega, R_3 = 9.9k\Omega, R_4 = 103k\Omega$$

A) (a) $V_o = \frac{R_2}{R_1} (V_2 - V_1) = \frac{100k}{10k} (V_2 - V_1)$

$$\Rightarrow V_o = 10(V_2 - V_1) \Rightarrow V_o = 2V \text{ for all cases.}$$

$$V_{cm} = 0, 15V, 10V$$

(b) $V_o = A_2 V_2 - A_1 V_1$


$$A_2 = \left[1 + R_2/R_1 \right] \left[1 + \frac{R_3}{R_4} \right]$$

$$A_1 = \frac{R_2}{R_1}$$

$$A_2 = A_1 =$$

$$V_o =$$

Difference Amplifier with variable gain:

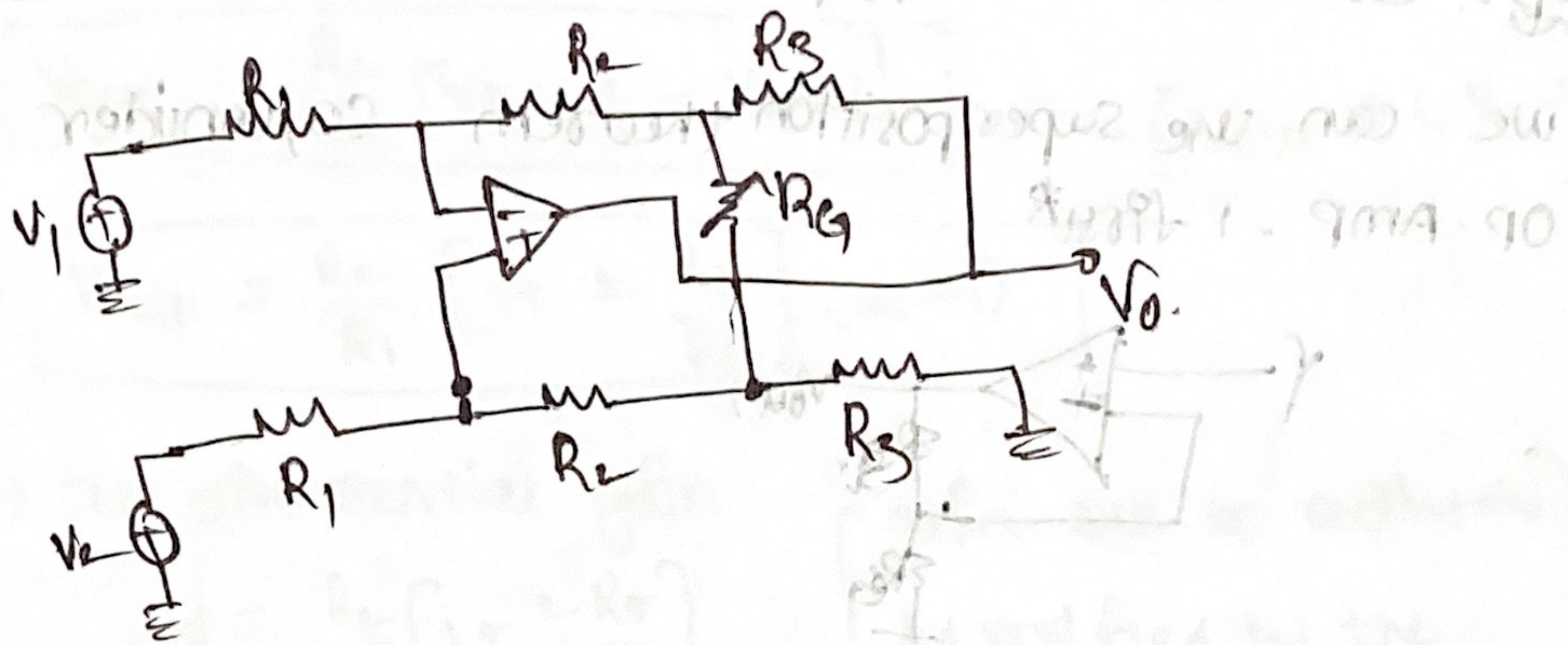

when,

$$\frac{R_2}{R_3} = \frac{R_2}{R_1}, V_0 = \frac{R_2}{R_1} (V_2 - V_1)$$

$$V_0 = \frac{2R_2}{(R_1 + R_2)} (V_2 - V_1).$$

gain varies inversely with R_g .

Instrumentation Amplifiers:

1- CMR.


2- High Resistance IP.

Low Resistance OP.

3- Stable gain.


4- extremely high common-mode ratio

Analysis

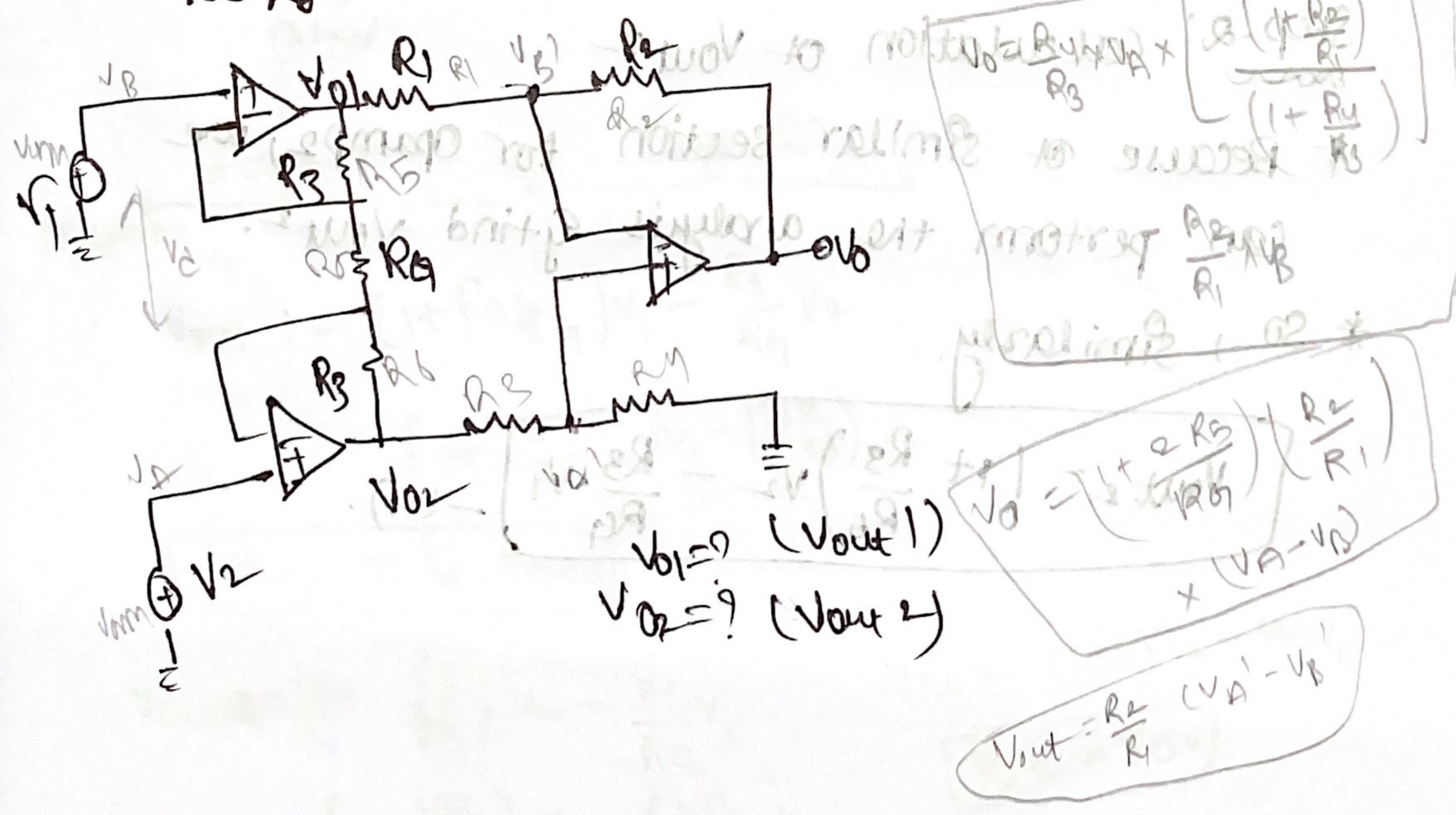

Step 1: calculation of V_{out}^1

we can use superposition theorem. So, consider OP-Amp - 1 first*

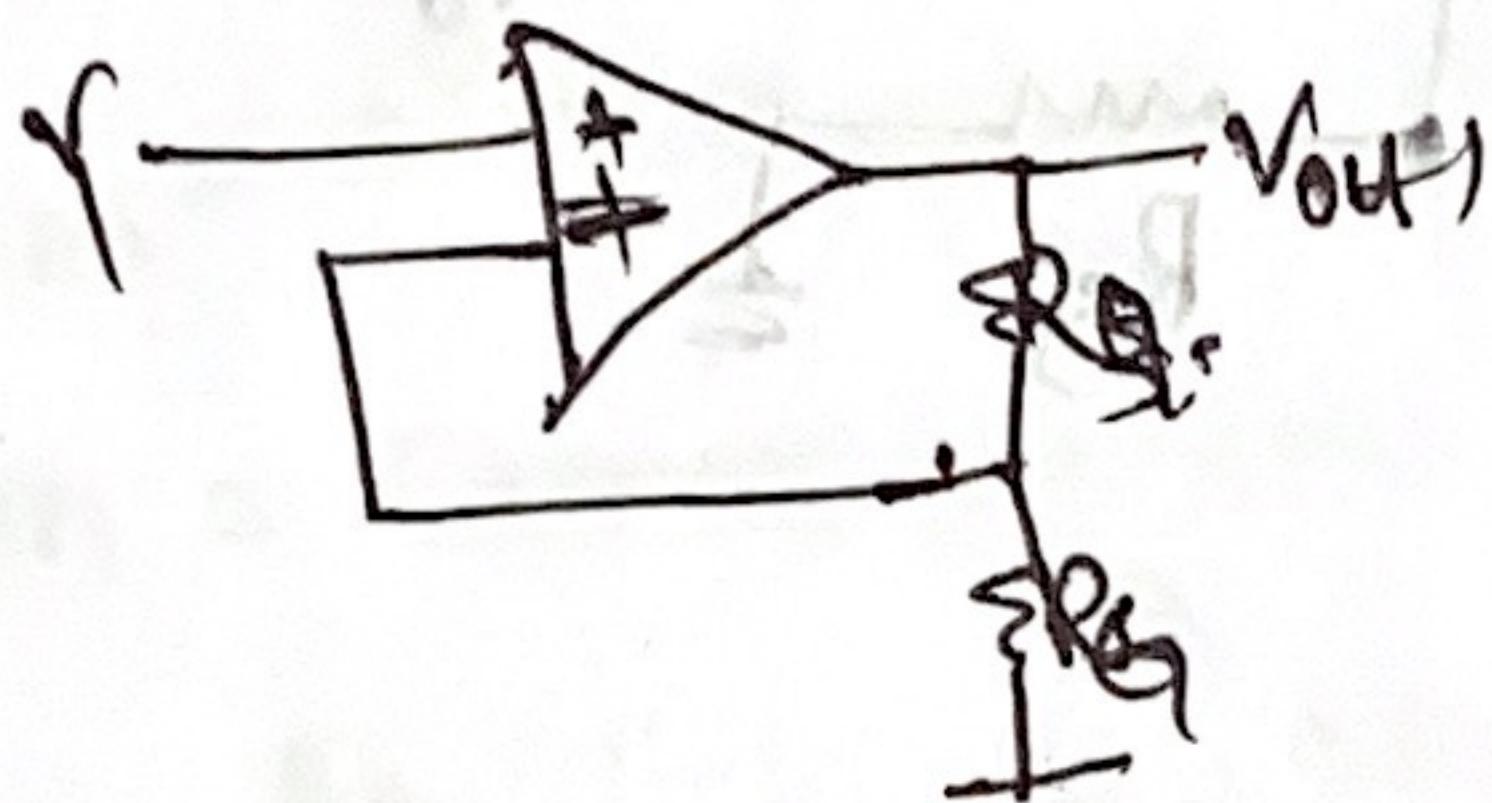

Case 1: V_1 source active, V_2 source deactivated

so circuit becomes non inverting amp.

$$V_{out} = \left(1 + \frac{R_3}{R_g}\right) V_1 \quad (1)$$

Case 2: V_2 source active, V_1 source deactivated

so circuit becomes inverting amp.

$$V_{out1} = -\frac{R_3}{R_g} V_2 \quad (2)$$

$$V_{out1} = V_{out1} + V_{out1}^n$$

$$V_{out1} = \left(1 + \frac{R_3}{R_g}\right) \left(V_1 - \frac{R_3}{R_g} V_2\right) \quad (3)$$

Step-2: calculation of V_{out}^2

* Because of similar section for Opamp2, we can perform the analysis & find V_{out}^2 .

* So, similarly.

$$V_{out2} = \left(1 + \frac{R_3}{R_g}\right) V_2 - \frac{R_3}{R_g} V_1 \quad (4)$$

Step-3: Since OP-amp-3 is a differential amplifier.

$$V_{out} = \frac{R_2}{R_1} [V_{out2} - V_{out1}]$$

(V_{out} of (V₂-V₁))

$$\rightarrow V_{out} = \frac{R_2}{R_1} \left[1 + 2 \frac{R_3}{R_G} \right] (V_2 - V_1) \quad (V_{10.8} = 100V)$$

→ In differential gain

$$A_d = \frac{R_2}{R_1} \left[1 + 2 \frac{R_3}{R_G} \right]$$

Gain of
2nd stage

Gain of
1st stage


gain can be affected

by varying by the
adjusting variable
resistance.

Q1)

for the given IA, determine the output voltage
for the circuit given below. $R_3 = 10k$, $R_G = 100k$,
 $R_1 = 10k$, $V_2 = 5V$, $V_1 = 4.995V$, $R_2 = 20k$

AN)

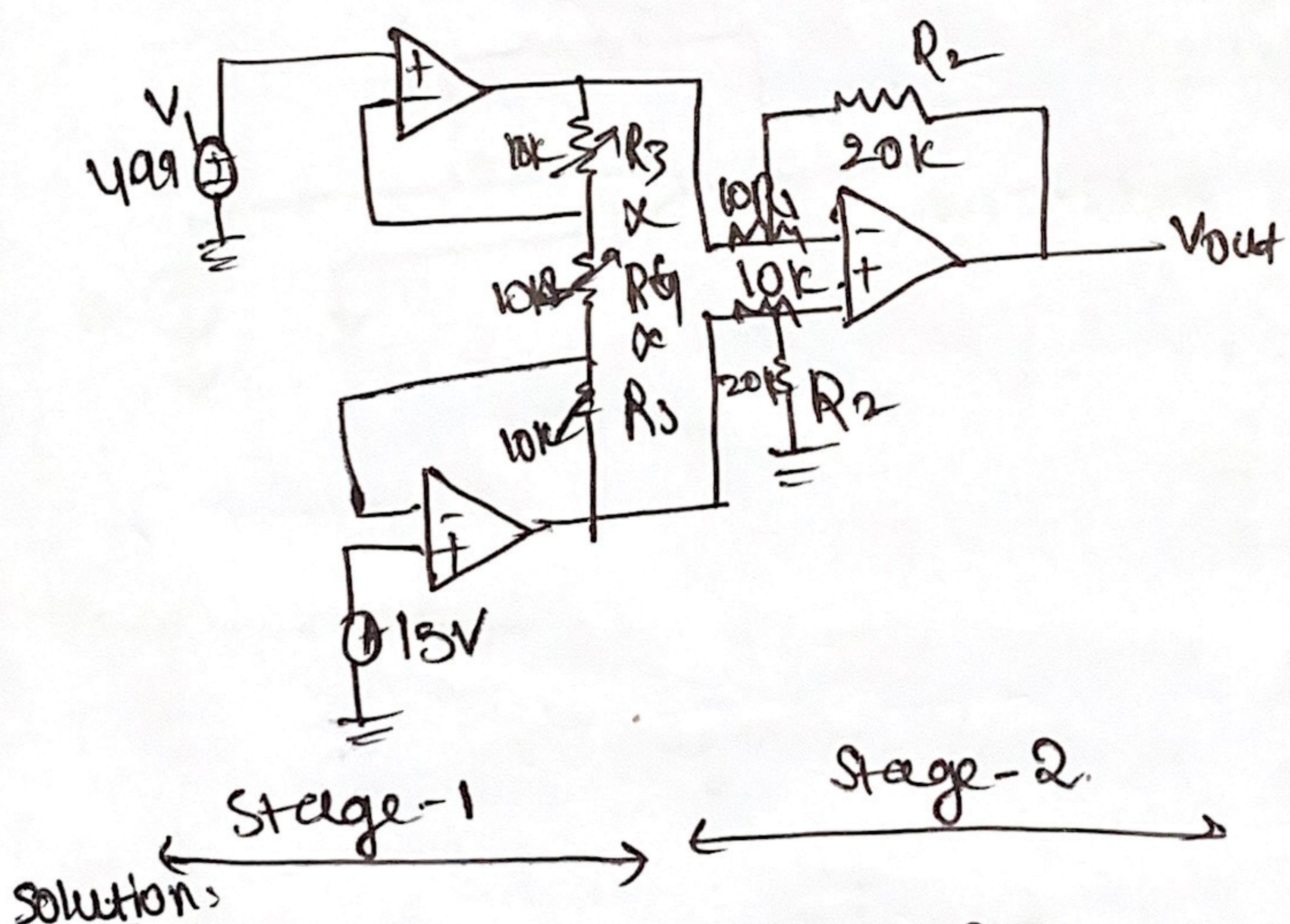

solution:

$$\begin{aligned} V_{out1} &= \left(1 + \frac{R_3}{R_G} \right) V_1 - \frac{R_3}{R_G} V_2 \\ &= \left(1 + \frac{10k}{100} \right) V_1 - \left(\frac{10k}{100} \right) V_2 \end{aligned}$$

$$V_{out1} = 4.995V$$

$$\begin{aligned} V_{out2} &= \left(1 + \frac{R_3}{R_G} \right) V_2 - \frac{R_3}{R_G} V_1 \\ &= \left(1 + \frac{10k}{100} \right) V_2 - \left(\frac{10k}{100} \right) V_1 \end{aligned}$$

$$V_{out2} = (100) V_2 - 100V_1$$

$$V_{out2} = 55V$$

$$V_{out} = \frac{R_2}{R_1} (V_{out2} - V_{out1})$$

$$= \frac{20k}{10k} (5.5 - 4.95)$$

$$\boxed{V_{out} = 2.01V}$$

Dual op-amp instrumentation AMP:


$$\text{when } \frac{R_4}{R_3} = \frac{R_2}{R_1} \quad V_{out} = \left(\frac{R_2}{R_1} + \frac{2R_2}{R_3} \right) (V_2 - V_1)$$

$$V_{out} = 2.01V$$

$$V_{out} = 2.01V$$

$$V_{out} = 2.01V$$

$$V_{out} = 2.01V$$

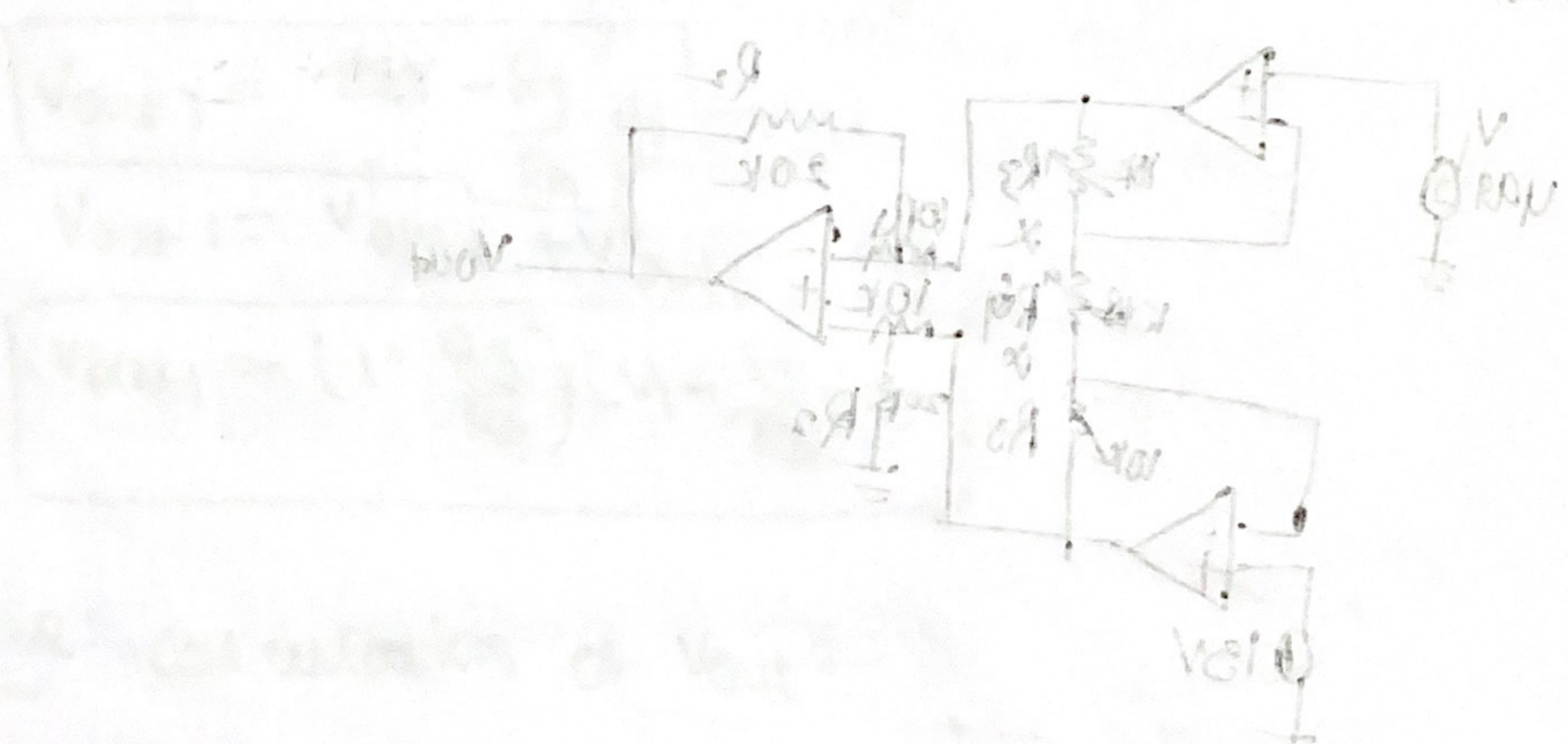

$$+V \frac{2}{\beta A} - V \left(\frac{1}{\beta A} + 1 \right) = 1 \text{ mV}$$

$$+V \left(\frac{1}{\beta A} \right) - V \left(\frac{1}{\beta A} + 1 \right) =$$

$$\boxed{V_{app} \cdot N \approx 1 \text{ mV}}$$


$$V_{app} = V_{app1} = 1 \text{ mV}$$

$$\boxed{V_{app} = 1 \text{ mV}}$$


$$N \frac{2}{\beta A} - V \left(\frac{2}{\beta A} + 1 \right) = 3 \text{ mV}$$

$$V \left(\frac{1}{\beta A} \right) - V \left(\frac{1}{\beta A} + 1 \right) =$$


Voltage to current converter

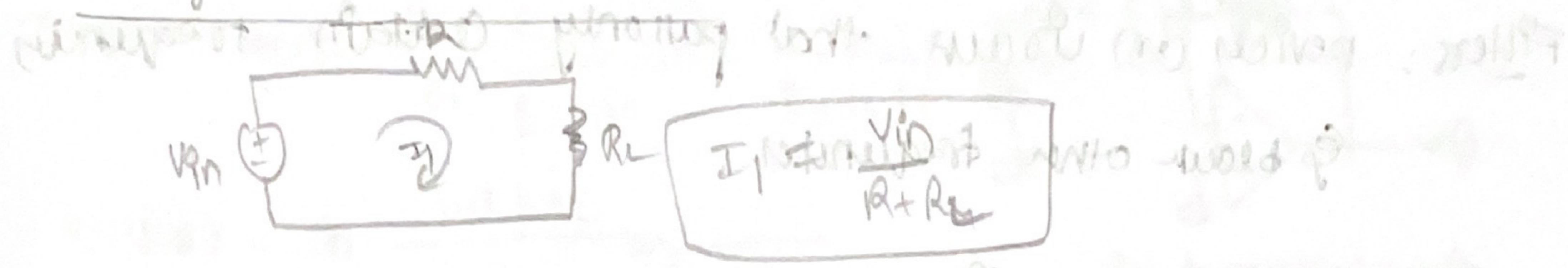


By opamp

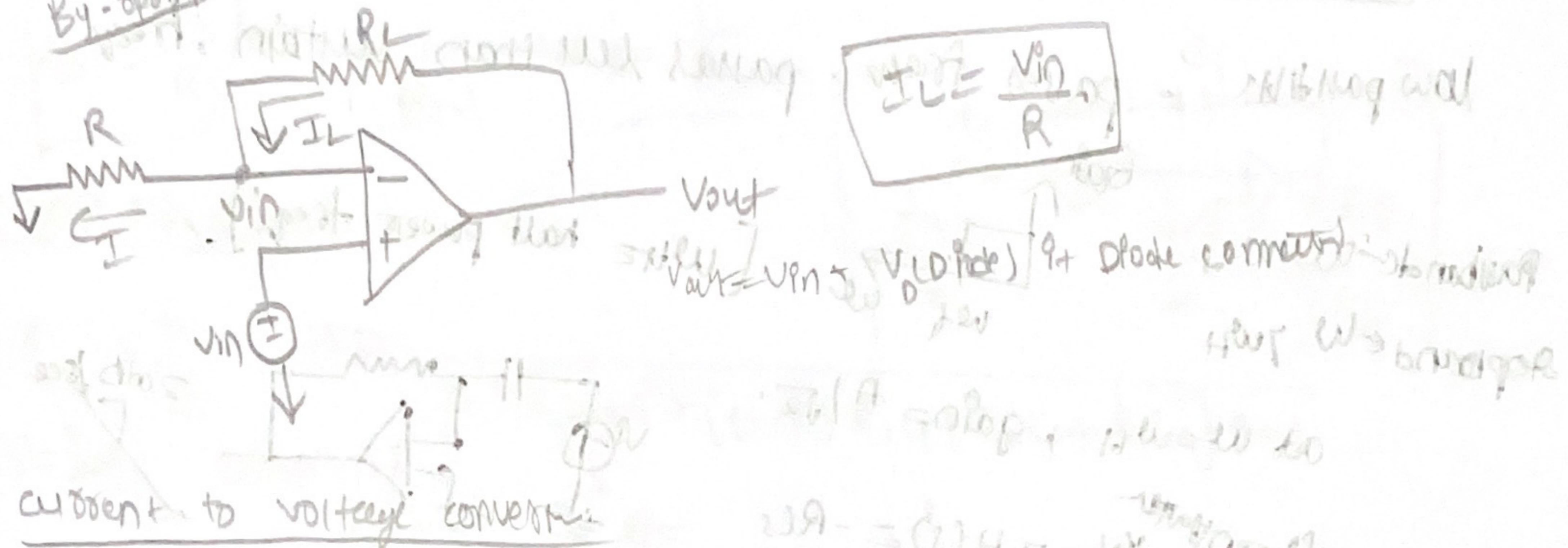

current to voltage converter

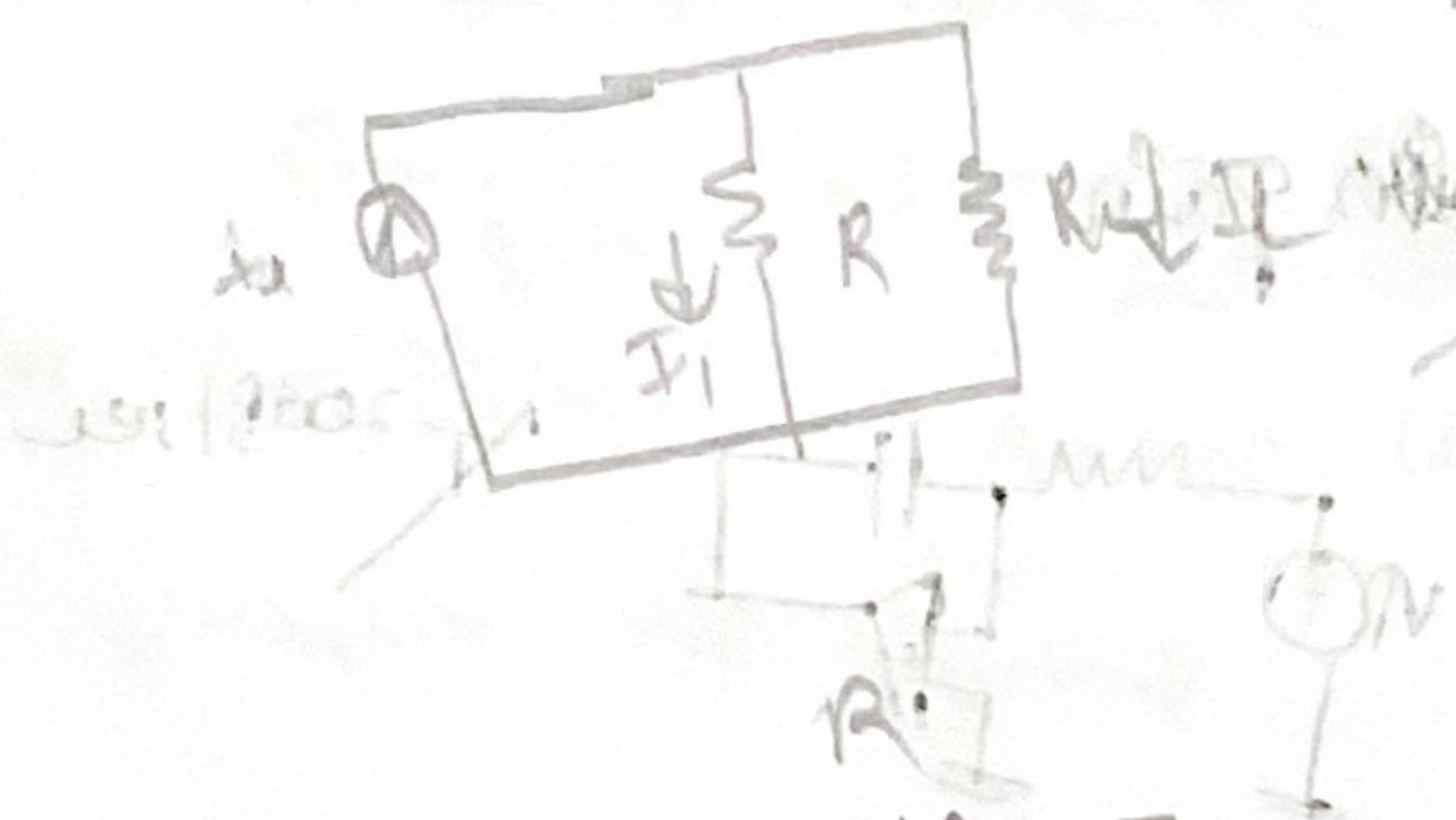

$$I_S = \frac{V_{out}}{R}$$

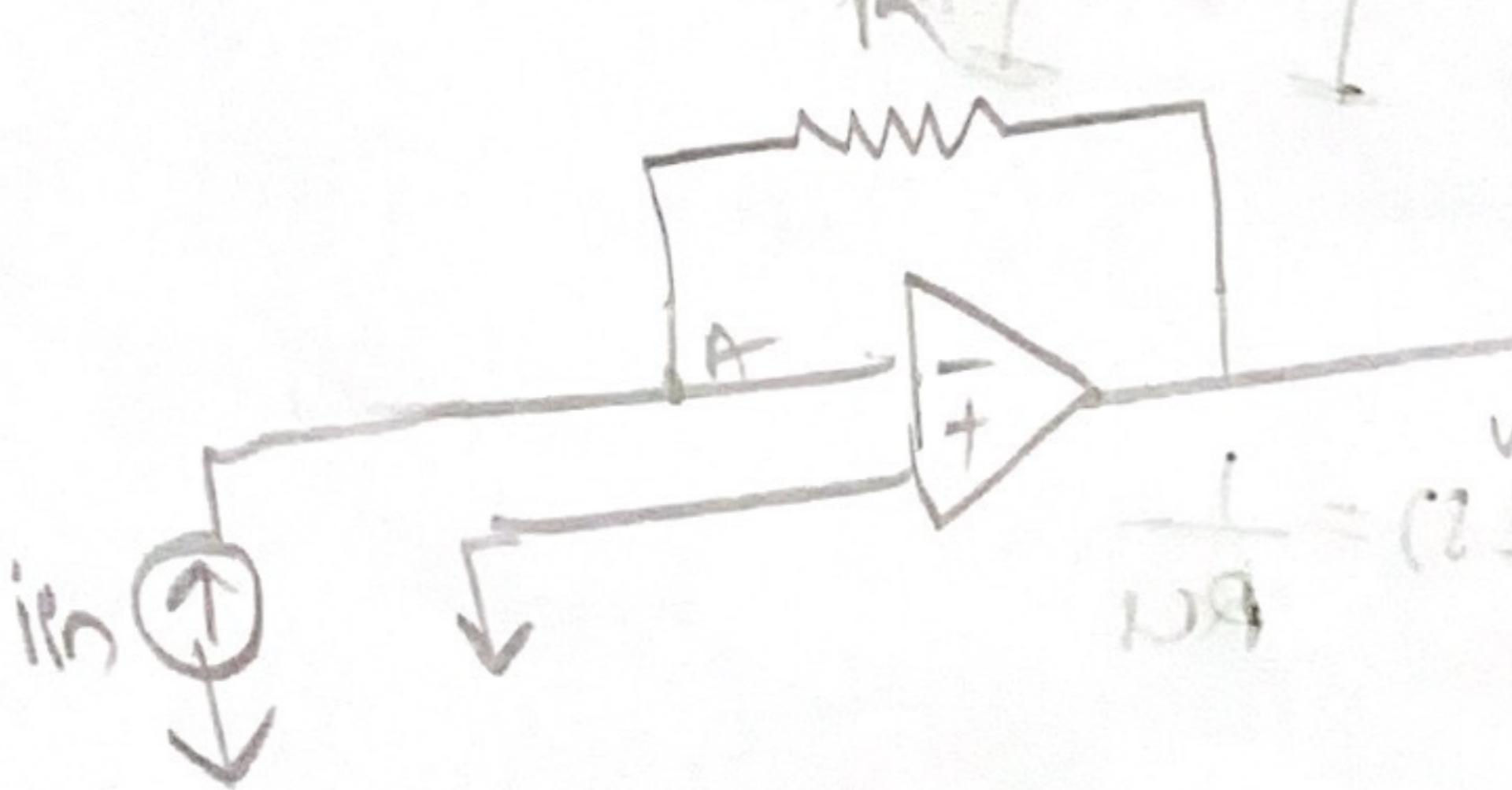

$$I_S = \frac{V_{out}}{R}$$


voltage drop after driving resistors please with out any watt

• UH circuit will be equal to the output current



$$\frac{1}{1+2.2} \frac{2.2}{1} = (UH)$$
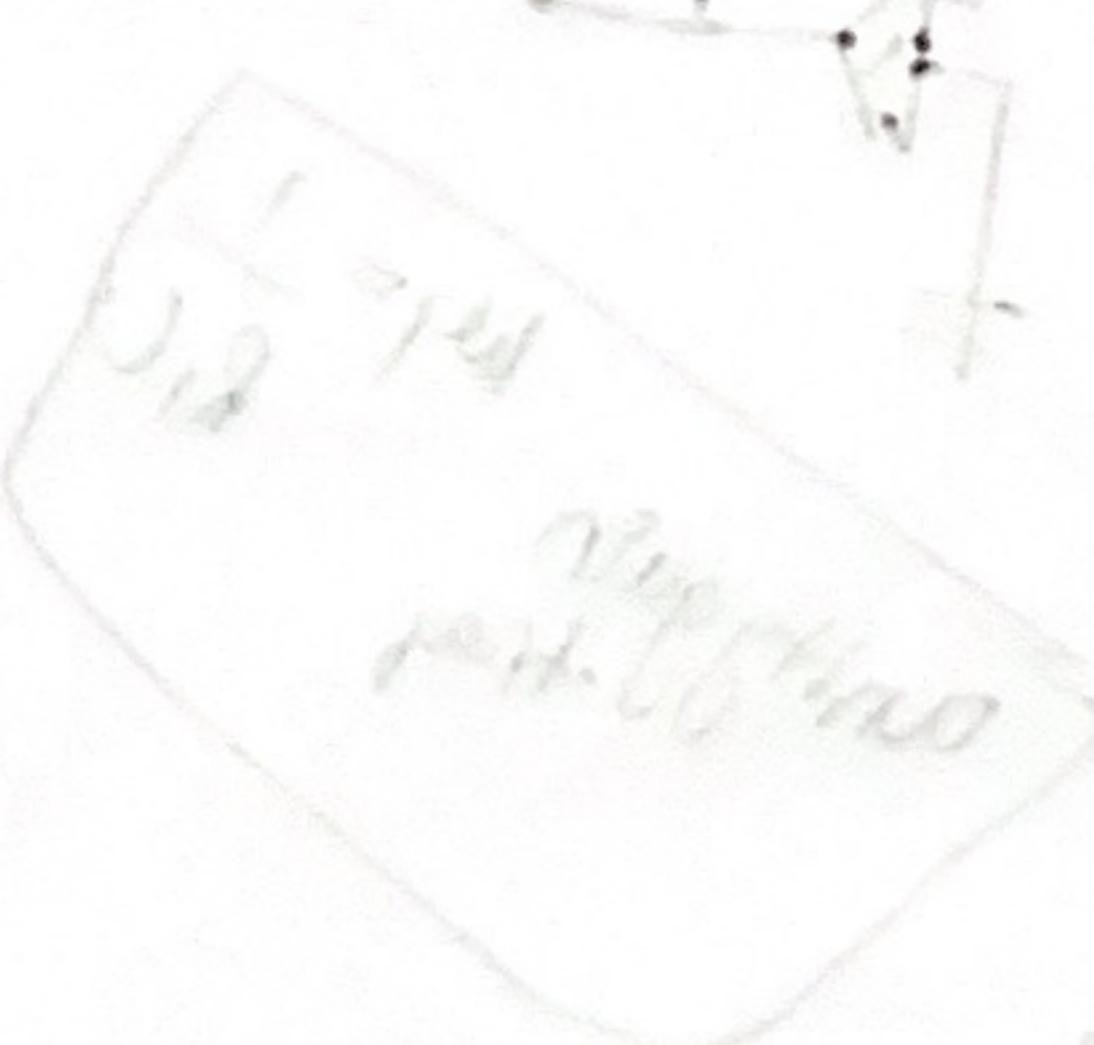
$$\text{circuit} \quad \text{off} = (UH) \cdot H$$



another term that gives voltage is given with the help

of $\frac{1}{1+2.2} \frac{2.2}{1} = (UH) \cdot H$ and resistance in series

$$\frac{1}{1+2.2} \frac{2.2}{1} = 0.22$$

$$\frac{3.2}{1+2.2} \frac{2.2}{1} = (UH)$$